

**HOMEWORK 4 (Section21)**  
**HOMEWORK 5 (Section22)**

**Due Date:** 02.01.2015, Friday. Turn it in to teaching assistant Serkan Öztürk.

1. A 10-hp, 120-V, 1000 rpm, shunt dc motor has a rated armature current of 70 A. The armature resistance of the motor is  $R_A = 0.12 \Omega$ , and the field resistance is  $R_F = 40 \Omega$ . The adjustable resistance in series with the field circuit ( $R_{adj}$ ) may be varied over a range from  $0 \Omega$  to  $200 \Omega$ , and it is currently set to  $100 \Omega$ . Armature reaction is ignored in this problem. The magnetization curve for his motor, taken at a speed of 1000 rpm, is presented in the below table and figure:

$E_A, V$	5	78	95	112	118	126
$I_F, A$	0.00	0.80	1.00	1.28	1.44	2.88

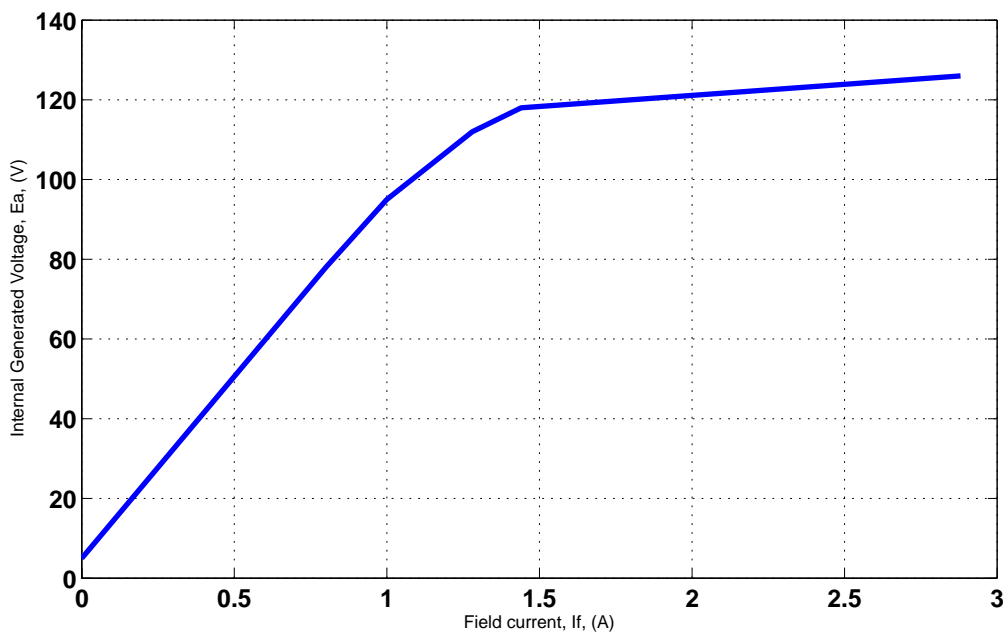


Fig. 1. Magnetization characteristic of the dc machine at 1000 rpm

- What is the speed of this motor when it is running at the rated conditions specified above?
- The output power from the motor is 10-hp at the rated conditions. What is net the output (load) torque of this motor?
- What are the copper losses ( $P_{Cu}$ ) and rotational losses ( $P_{rot}$ ) in the motor at full-load?



- d) What is the efficiency of the motor at full-load?
- e) If the motor loses its load, i.e. becomes unloaded, what is the no-load speed of the motor (Terminal voltage and total field resistance do not change)?
- f) Suppose that the motor is running at the no-load conditions described in part (e). What would happen to the motor if its field circuit were to open? Ignoring armature reaction, what would the final steady-state speed of the motor be under those conditions?

2. A DC machine with a shunt field winding is operated as a self-excited dc generator at a constant shaft speed of 1200 rpm. The magnetization characteristic of the machine, obtained by exciting the shunt field winding separately by a dc source and keeping the shaft speed constant at 1200 rpm, is approximated by two straight lines as given below:

$$\begin{aligned} E_a &\cong 10 \text{ V} && \text{for } I_f = 0 \\ E_a &\cong 250I_f && \text{for } 0 < I_f \leq 0.8 \text{ A} \\ E_a &\cong 125I_f + 100 && \text{for } I_f > 0.8 \text{ A} \end{aligned}$$

Armature winding resistance  $R_a$  and total field winding resistance  $R_f$  are measured as  $1 \Omega$  and  $165.3 \Omega$ , respectively.

- a) Calculate the no-load terminal voltage of the generator.
- b) The self-excited dc generator above is now loaded, and supplies a constant load current of  $I_L = 50 \text{ A}$ . Calculate the induced armature emf  $E_a$ , field current  $I_f$ , armature current  $I_a$  and terminal voltage  $V_t$ .