



V. DC Machines

Introduction


DC machines are used in applications requiring a wide range of speeds by means of various combinations of their field windings

Types of DC machines:

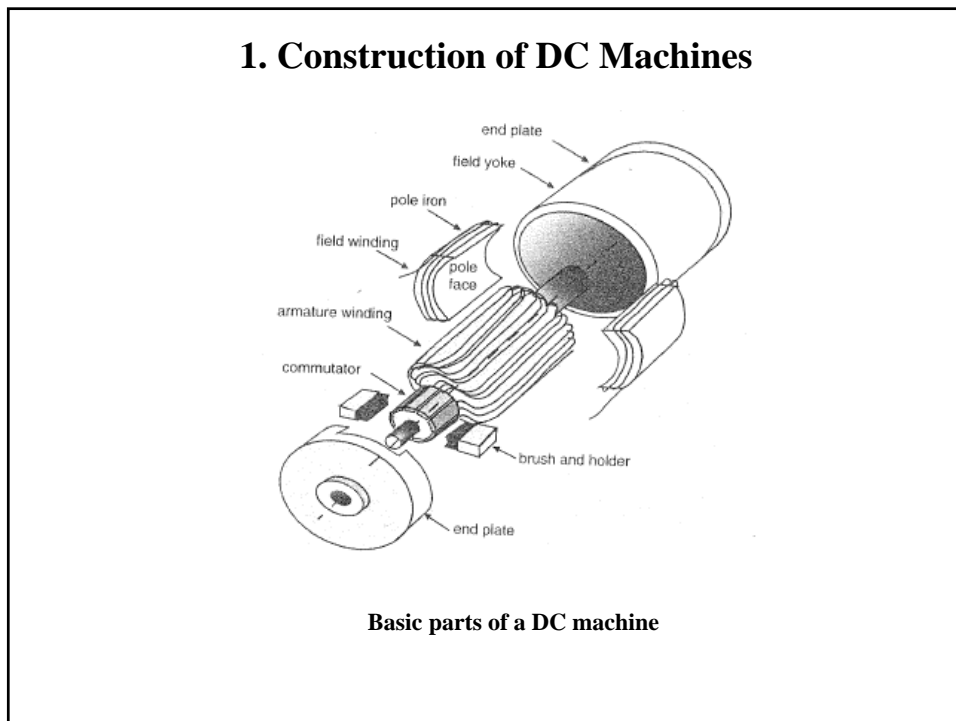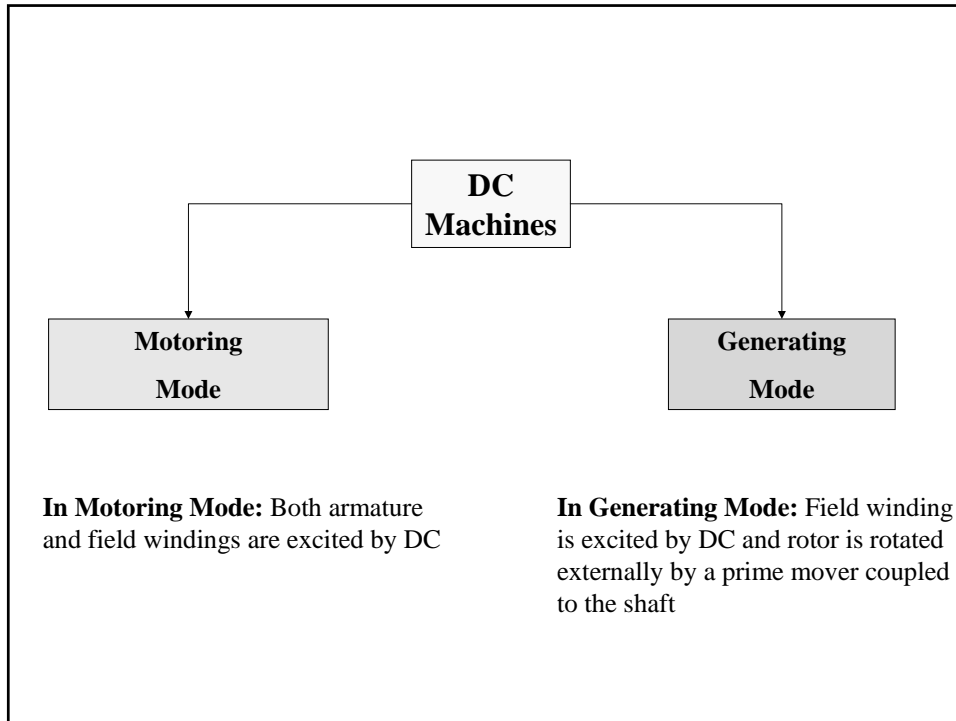- Separately-excited
- Shunt
- Series
- Compound





Construction of DC Machines

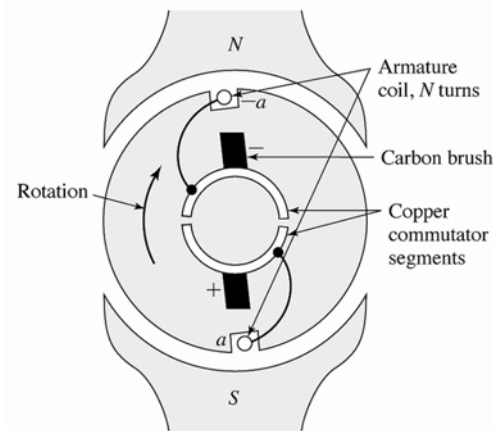

Copper commutator segment and carbon brushes are used for:

- (i) for mechanical rectification of induced armature emfs
- (ii) for taking stationary armature terminals from a moving member

Elementary DC machine with commutator.

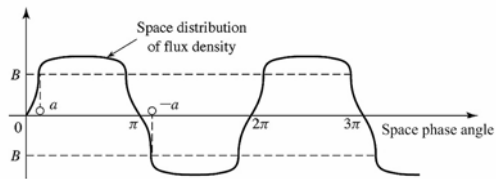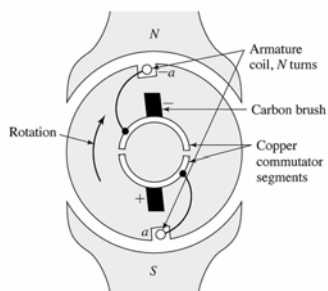


(a) Space distribution of air-gap flux density in an elementary dc machine;



Average gives us a DC voltage, E_a



$$E_a = K_g \phi_f \omega_r$$

$$T_e = K_g \phi_f I_a = K_d I_f I_a$$

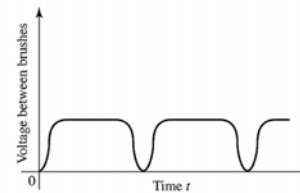

(b) waveform of voltage between brushes.

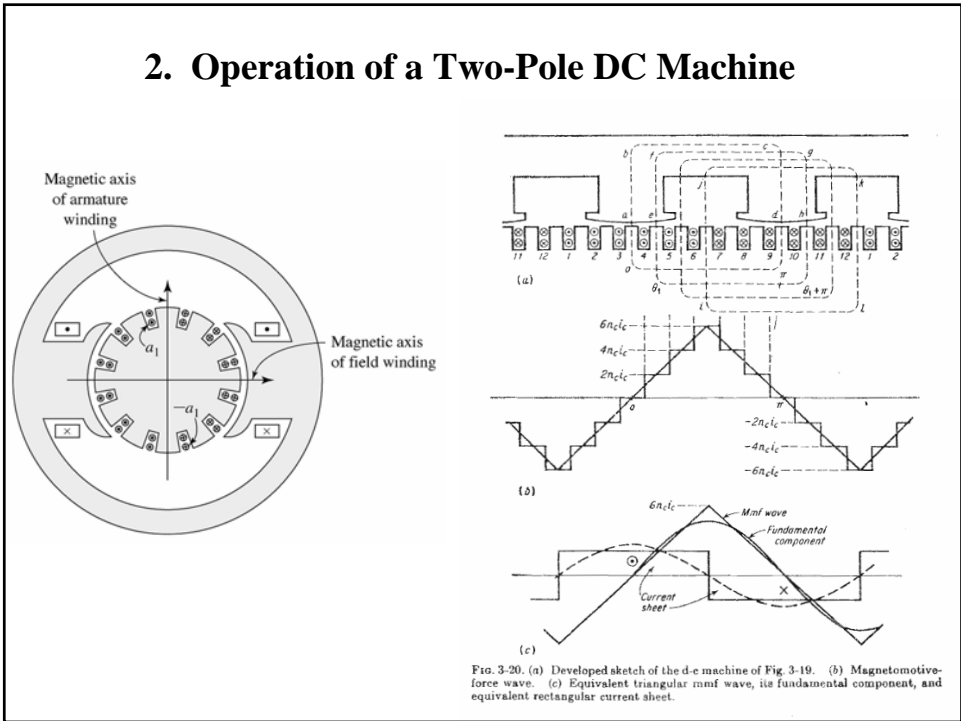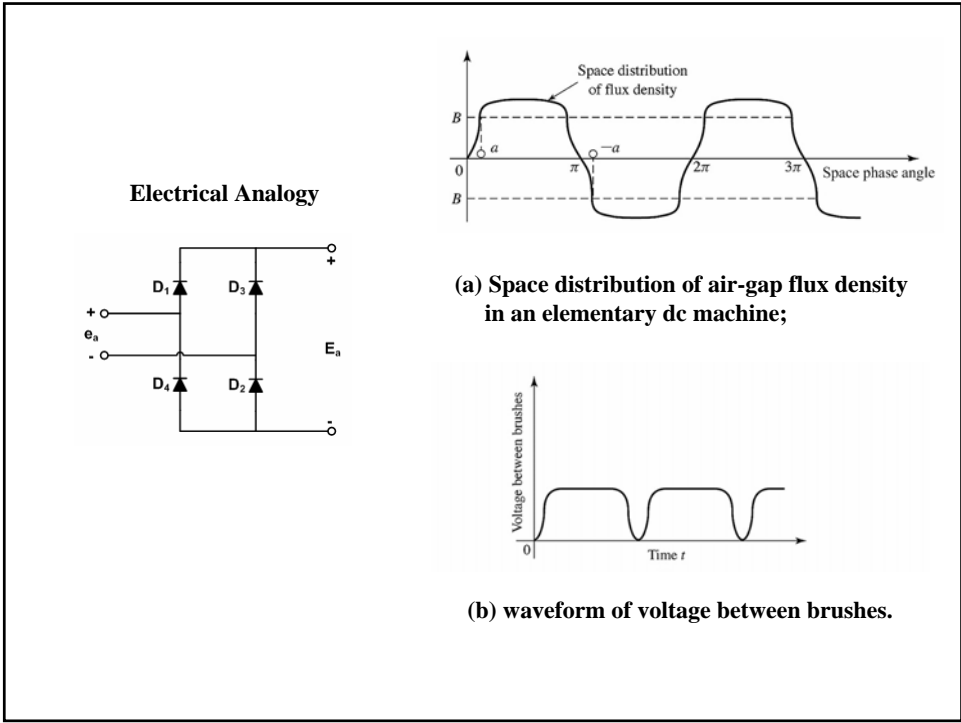

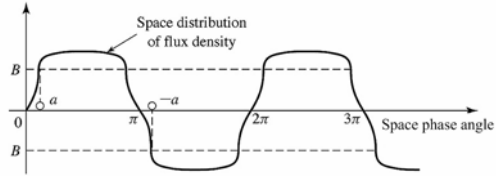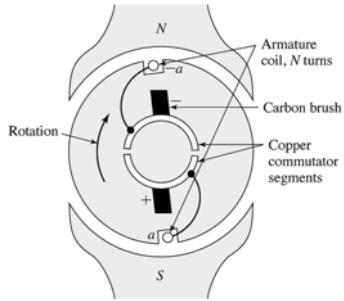

Space distribution of air-gap flux density, B_f in an elementary dc machine;

One pole spans 180° electrical in space



$$B_f = B_{peak} \sin(\theta)$$

Mean air gap flux per pole: $\phi_{avg / pole} = B_{avg} A_{per\ pole}$ $A_{per\ pole}$: surface area spanned by a pole

$$= \int_0^\pi B_{peak} \sin(\theta) dA$$

$$= \int_0^\pi B_{peak} \sin(\theta) \ell r d\theta$$

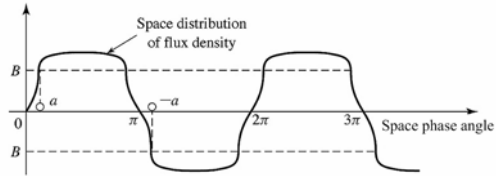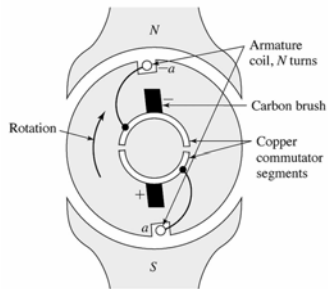For a two pole DC machine, $\phi_{avg / pole} = 2B_{peak} \ell r$



Space distribution of air-gap flux density, B_f in an elementary dc machine;

One pole spans 180° electrical in space

$$B_f = B_{peak} \sin(\theta)$$

Flux linkage λ_a : $\lambda_a = N \phi_{avg / pole} \cos(\alpha)$ α : phase angle between the magnetic axes of the rotor and the stator

with $\alpha_0 = 0$ $\lambda_a = N \phi_{avg / pole} \cos(\omega_r t)$ $\alpha(t) = \omega_r t + \alpha_0$

$$e_a = \frac{d\lambda_a}{dt} = -\omega_r N \phi_{avg / pole} \sin(\omega_r t)$$

$$E_a = \frac{1}{\pi} \int_0^\pi e_a(t) dt$$

For a two pole DC machine: $E_a = \frac{2}{\pi} \omega_r N \phi_{avg / pole}$

In general: $E_a = K_g \phi_f \omega_r$


K_g : winding factor

ϕ_f : mean airgap flux per pole

ω_r : shaft-speed in mechanical rad/sec

$$\omega_r = 2\pi \frac{n_r}{60} \quad n_r: \text{shaft-speed in revolutions per minute (rpm)}$$

DC machines with number of poles > 2

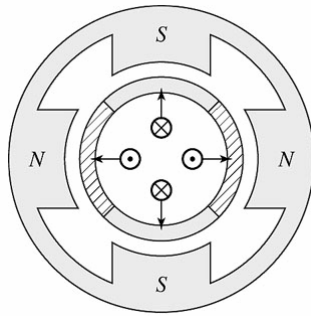


$$f_{elec} = \frac{P n_r}{2 \cdot 60} = \frac{P n_r}{120} \quad P: \text{number of poles}$$

$$\phi_{avg / pole} = \frac{2}{P} 2B_{peak} \ell r$$


$$E_a = \frac{P}{2} \frac{2}{\pi} N \omega_r \phi_{avg / pole} = K_g \phi_f \omega_r$$

A four-pole DC machine

Schematic representation of a DC machine

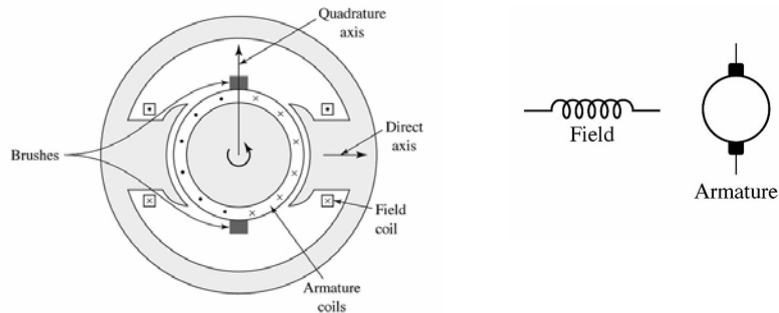

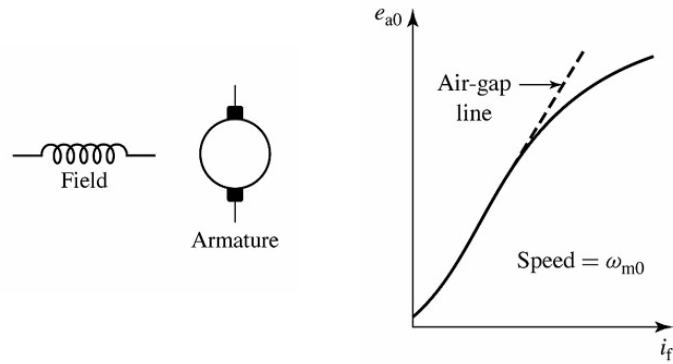Typical magnetization curve of a DC machine




Torque expression in terms of mutual inductance

$$T_e = \frac{1}{2} i_f^2 \frac{dL_f}{d\theta} + \frac{1}{2} i_a^2 \frac{dL_a}{d\theta} + i_f i_a \frac{dM_{fa}}{d\theta}$$

$$T_e = i_f i_a \frac{dM_{fa}}{d\theta} \quad M_{fa} = \hat{M} \cos \theta$$

$$|T_e| = \hat{M} i_f i_a$$

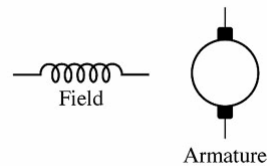

Alternatively, electromagnetic torque T_e can be derived from power conversion equations

$$P_{mech} = P_{elec}$$

$$T_e \omega_m = E_a I_a$$


$$T_e \omega_m = K_g \phi_f \omega_m I_a$$

$$E_a = K_g \phi_f \omega_m$$


$$T_e = K_g \phi_f I_a$$

In a linear magnetic circuit

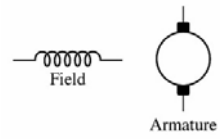
$$T_e = K_g K_f I_f I_a \quad \text{where} \quad \phi_f = K_f I_f$$




Field-circuit connections of DC machines

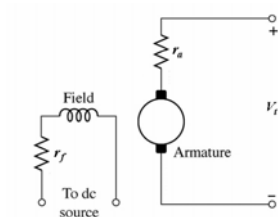


(a) separately-excited

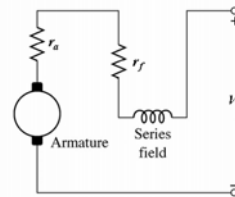

(b) series

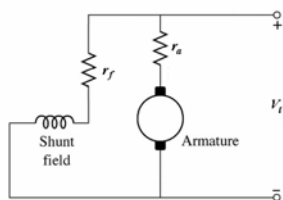


(c) shunt

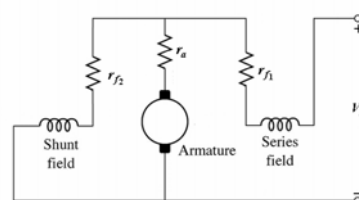

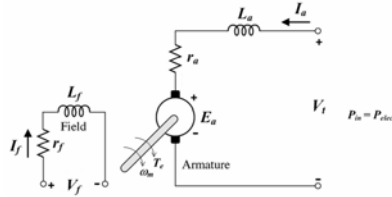(d) compound

Separately-excited DC machine circuit in motoring mode



$$\underbrace{P_{mech}}_{\substack{\text{internal electromechanical power} \\ \text{or gross output power}}} = \underbrace{P_{out}}_{\text{output power produced}} + \underbrace{P_{f\&w}}_{\text{friction and windage}}$$


$$E_a = K_g \phi_f \omega_m \quad K_g = \frac{p C_a}{2 \pi a}$$

$E_a \leq V_t$

p : number of poles
 C_a : total number of conductors in armature winding
 a : number of parallel paths through armature winding

T_e produces rotation (T_e and ω_m are in the same direction) $P_{mech} > 0, T_e > 0$ and $\omega_m > 0$

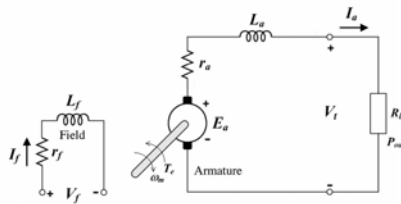Separately-excited DC machine circuit in generating mode



$$E_a > V_t$$


T_e and ω_m are in the opposite direction $P_{mech} < 0, T_e < 0$ and $\omega_m > 0$

Generating mode

- Field excited by I_f (dc)
- Rotor is rotated by a mechanical prime-mover at ω_m .
- As a result E_a and I_a are generated

3. Analysis of DC Generators


Separately-Excited DC Generator

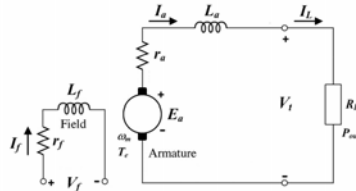

$$V_t = E_a - I_a r_a \quad \text{where} \quad E_a = K_g \phi_f \omega_m$$


$$\text{also} \quad V_t = I_L R_L \quad \text{where} \quad I_L = I_a$$

Terminal V-I Characteristics

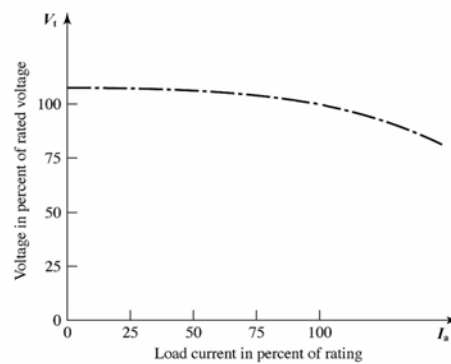


Terminal voltage (V_t) decreases slightly as load current increases
(due to $I_a R_a$ voltage drop)

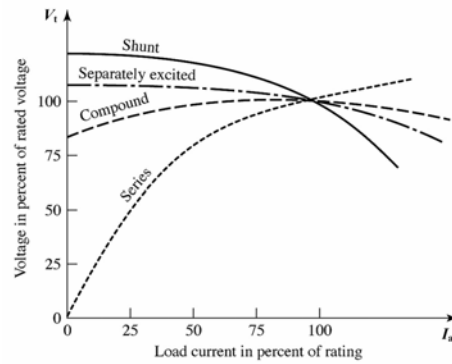Terminal voltage characteristics of DC generators



Series generator is not used due to poor voltage regulation

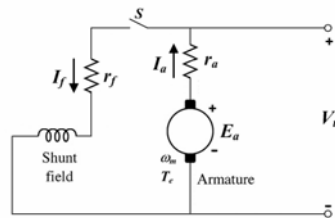
Shunt DC Generator (Self-excited DC Generator)



- Initially the rotor is rotated by a mechanical prime-mover at ω_m while the switch (S) is open.
- Then the switch (S) is closed.


When the switch (S) is closed
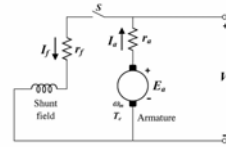
$$E_a = (r_a + r_f) I_f \quad \text{Load line of electrical circuit}$$



Self-excitation uses the residual magnetization & saturation properties of ferromagnetic materials.

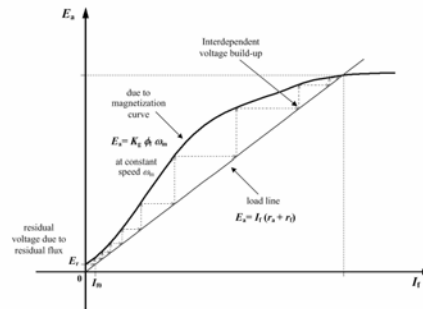
- when S is closed $E_a = E_r$ and $I_f = I_{f0}$
- interdependent build-up of I_f and E_a continues
- comes to a stop at the intersection of the two curve as shown in the figure below



Solving for the exciting current, I_f

$$E_a = K_g \phi_f \omega_m \quad \text{where} \quad \phi_f = K_f I_f$$
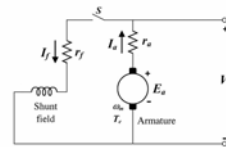
$$E_a = K_d I_f \omega_m \quad \text{where} \quad K_d = K_g K_f$$



Integrating with the electrical circuit equations

$$K_d i_f \omega_m = (L_a + L_f) \frac{di_f}{dt} + (r_a + r_f) i_f$$

Applying Laplace transformation we obtain

$$K_d \omega_m I_f(s) = (L_a + L_f) s I_f(s) + (r_a + r_f) I_f(s) - (L_a + L_f) I_{f0}$$

So the time domain solution is given by

$$i_f(t) = I_{f0} e^{-\left(\frac{r_a + r_f - K_d \omega_m}{L_a + L_f}\right)t}$$


$$i_f(t) = I_{f0} e^{-\left(\frac{r_a + r_f - K_d \omega_m}{L_a + L_f}\right)t}$$

Let us consider the following 3 situations

(i) $(r_a + r_f) > K_d \omega_m$

$$\lim_{t \rightarrow \infty} i_f(t) = 0$$


Two curves do not intersect.

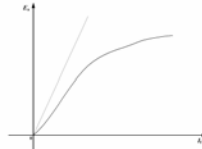

(ii) $(r_a + r_f) = K_d \omega_m$


$$i_f(t) = I_{f0}$$

Self excitation can just start

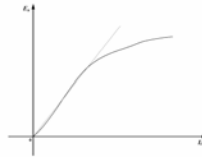


(iii) $(r_a + r_f) < K_d \omega_m$

Generator can self-excite

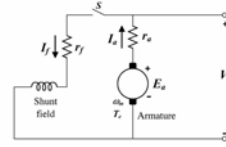

Self-excited DC generator under load

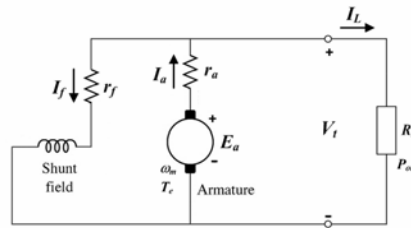


$$I_a = I_f + I_L \quad V_t = E_a - r_a I_a = r_f I_f$$


$$E_a = r_a I_a + r_f I_f$$

$$E_a = (r_a + r_f) I_f + r_a I_L$$

Load line of electrical circuit

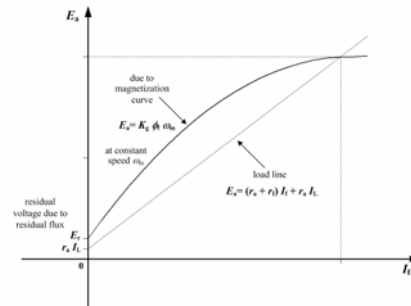


Series DC Generator

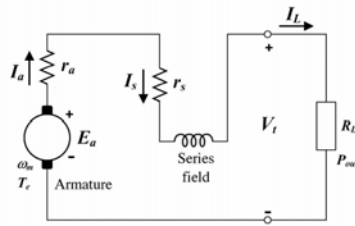

$$V_t = E_a - I_a(r_a + r_s) \quad \text{where} \quad E_a = K_g \phi_f \omega_m$$

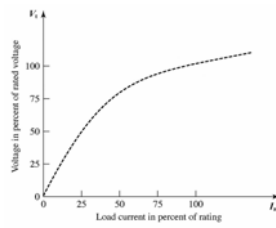
$$\text{also } V_t = I_L R_L \quad \text{and} \quad I_L = I_a = I_s$$



Not used in practical, due to poor voltage regulation

Compound DC Generators

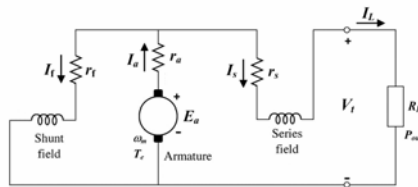
(a) Short-shunt connected compound DC generator



$$V_t = E_a - I_a r_a + I_s r_s \quad \text{where} \quad E_a = K_g \phi_f \omega_m$$

$$\text{also } V_t = I_L R_L \quad \text{and} \quad I_L = I_s \quad \text{and} \quad I_a = I_t + I_s$$

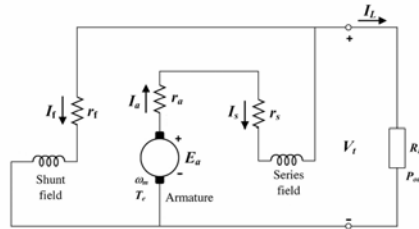(b) Long-shunt connected compound DC generator



$$V_t = E_a - I_a(r_a + r_s) \quad \text{where} \quad E_a = K_g \phi_f \omega_m$$

$$\text{also} \quad V_t = I_L R_L \quad \text{and} \quad I_L = I_a + I_t \quad \text{and} \quad I_a = I_s$$

Types of Compounding

(i) Cumulatively-compounded DC generator (additive compounding)

$$\underbrace{\mathcal{F}_d}_{\text{field mmf}} = \underbrace{\mathcal{F}_f}_{\text{shunt field mmf}} + \underbrace{\mathcal{F}_s}_{\text{series field mmf}}$$

for linear M.C. (or in the linear region of the magnetization curve, i.e. unsaturated magnetic circuits)

$$\phi_d = \phi_f + \phi_s$$

(ii) Differentially-compounded DC generator (subtractive compounding)


$$\mathcal{F}_d = \mathcal{F}_f - \mathcal{F}_s$$

for linear M.C. (or in the linear region of the magnetization curve, i.e. unsaturated magnetic circuits)

$$\phi_d = \phi_f - \phi_s$$


Differentially-compounded generator is not used in practical, as it exhibits poor voltage regulation

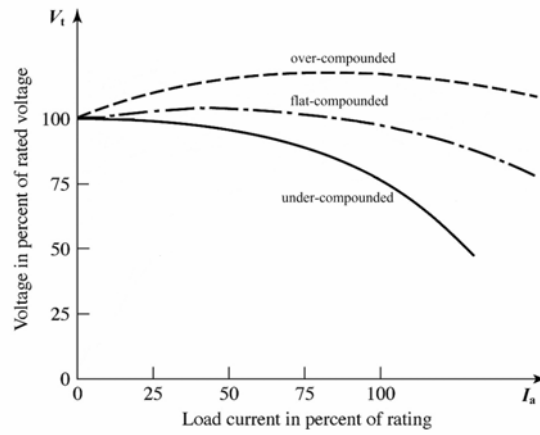Terminal V-I Characteristics of Compound Generators



Above curves are for cumulatively-compounded generators

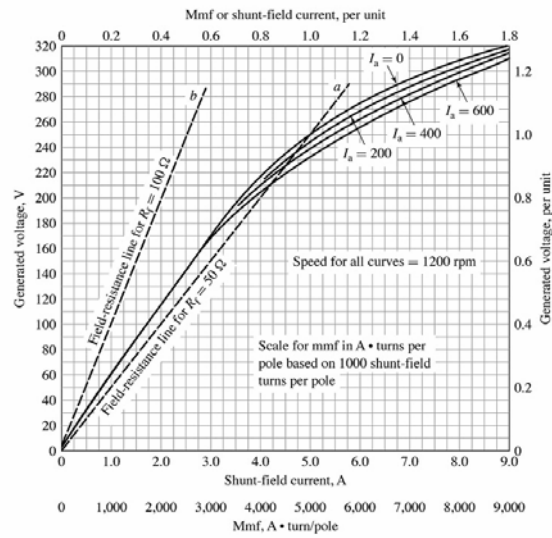Magnetization curves for a 250-V 1200-r/min dc machine. Also field-resistance lines for the discussion of self-excitation are shown



Examples


1. A 240kW, 240V, 600 rpm separately excited DC generator has an armature resistance, $r_a = 0.01\Omega$ and a field resistance $r_f = 30\Omega$. The field winding is supplied from a DC source of $V_f = 100V$. A variable resistance R is connected in series with the field winding to adjust field current I_f . The magnetization curve of the generator at 600 rpm is given below:

I_f (A)	1	1.5	2	2.5	3	4	5	6
E_a (V)	165	200	230	250	260	285	300	310


If DC generator is delivering rated voltage and is driven at 600 rpm determine:

- a) Induced armature emf, E_a
- b) The internal electromagnetic power produced (gross power)
- c) The internal electromagnetic torque
- d) The applied torque if rotational loss is $P_{rot} = 10kW$
- e) Efficiency of generator
- f) Voltage regulation

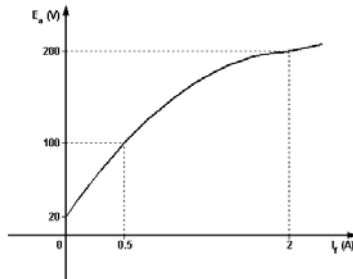
2. A shunt DC generator has a magnetization curve at $n_r = 1500$ rpm as shown below. The armature resistance $r_a = 0.2 \Omega$, and field total resistance $r_f = 100 \Omega$.
- a) Find the terminal voltage V_t and field current I_f of the generator when it delivers 50A to a resistive load
 - b) Find V_t and I_f when the load is disconnected (i.e. no-load)



Solution:

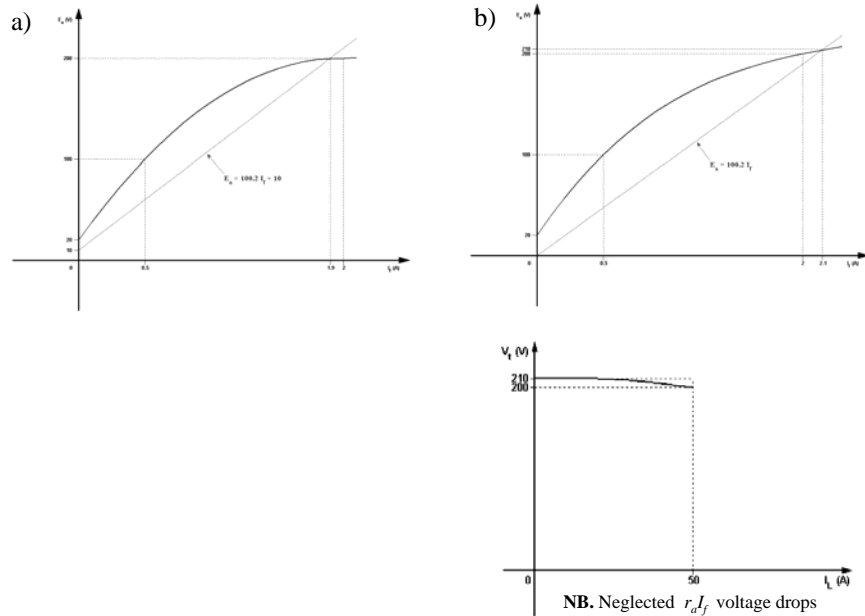


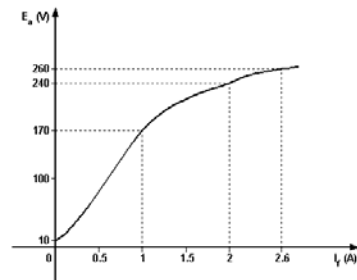3. The magnetization curve of a DC shunt generator at 1500 rpm is given below, where the armature resistance $r_a = 0.2 \Omega$, and field total resistance $r_f = 100 \Omega$, the total friction & windage loss at 1500 rpm is 400W.
- Find no-load terminal voltage at 1500 rpm
 - For the self-excitation to take place
 - Find the highest value of the total shunt field resistance at 1500 rpm
 - The minimum speed for $r_f = 100 \Omega$.
 - Find terminal voltage V_t , efficiency η and mechanical torque applied to the shaft when $I_a = 60$ A at 1500 rpm.




Solution:


a)

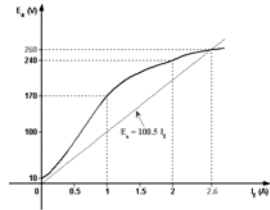

b) (i)

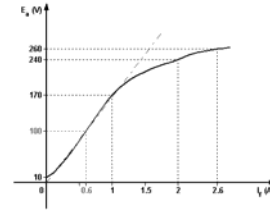

b) (ii)

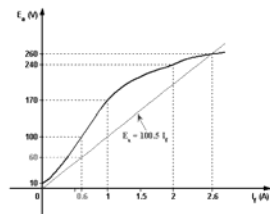



4. Analysis of DC Motors

DC motors are adjustable speed motors. A wide range of torque-speed characteristics ($T_e - \omega_m$) is obtainable depending on the motor types given below:



- Series DC motor
- Separately-excited DC motor
- Shunt DC motor
- Compound DC motor

DC Motors Overview



(a) Series DC Motors

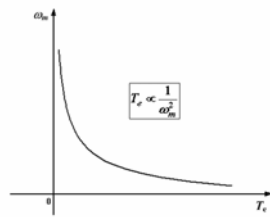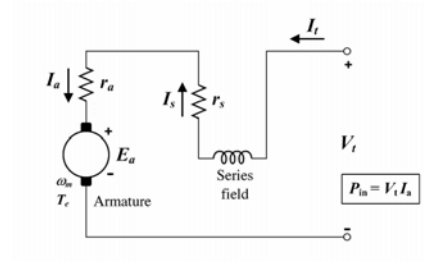



(b) Separately-excited DC Motors

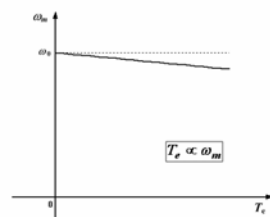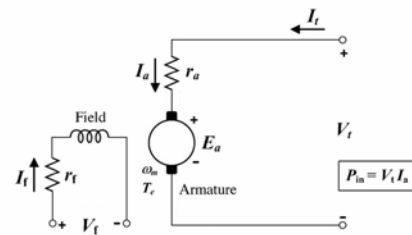

(c) Shunt DC Motors

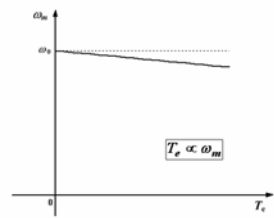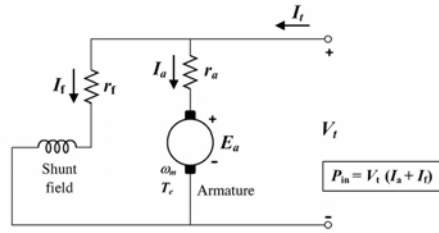


(d) Compound DC Motors

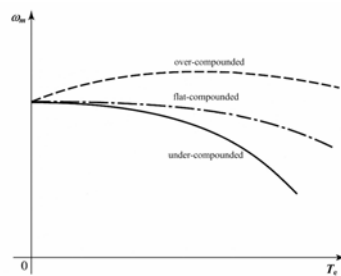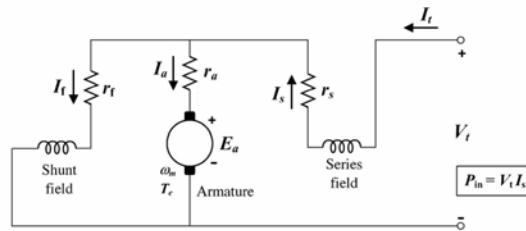

DC Motors

(a) Series DC Motors

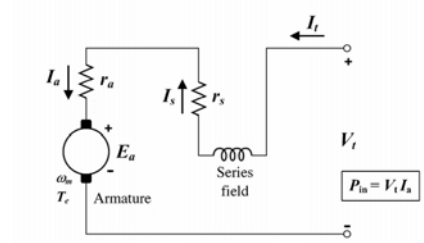

The back e.m.f: $E_a = K_g \phi_f \omega_m$

Electromagnetic torque: $T_e = K_g \phi_f I_a$

Terminal voltage equation: $V_t = E_a + I_a(r_a + r_s)$

$I_a = I_s$

Assuming linear equation: $\phi_f = K_f I_s$

$$T_e = K_g \phi_f I_a$$


$$T_e = K_g K_f I_s I_a$$

$$T_e = K_d I_a^2$$

$$K_g \phi_f = K_d I_a$$

$$\dots \phi_f = K_f I_s$$

$$\dots I_a = I_s$$

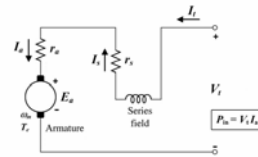

$$\omega_m = \frac{E_a}{K_g \phi_f} = \frac{V_t - I_a(r_a + r_s)}{K_g \phi_f}$$

$$\dots E_a = K_g \phi_f \omega_m, \quad V_t = E_a + I_a(r_a + r_s)$$

$$\omega_m = \frac{V_t - I_a(r_a + r_s)}{K I_a}$$

$$\dots K_g \phi_f = K I_a$$


$$E_a = K_d I_a \omega_m = V_t - I_a(r_a + r_s)$$

$$\dots E_a = K_g \phi_f \omega_m$$

$$I_a = \frac{V_t}{K_d \omega_m + (r_a + r_s)}$$

$$T_e = \frac{K_d V_t^2}{[K_d \omega_m + (r_a + r_s)]^2}$$

$$\dots T_e = K_d I_a^2$$

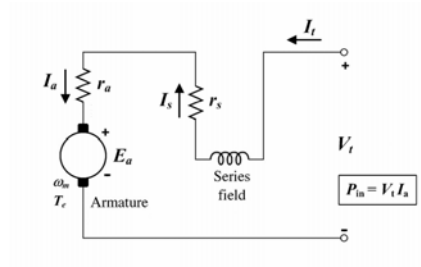


$$T_e = \frac{K_d V_t^2}{[K_d \omega_m + (r_a + r_s)]^2} \quad \text{thus} \quad T_e \propto \frac{1}{\omega_m^2}$$

Note that: A series DC motor should never run no load!

$$T_e \rightarrow 0 \Rightarrow \omega_m = \infty \quad \text{overspeeding!}$$

(b) Separately-excited DC Motors

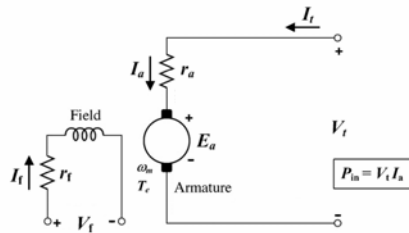

The back e.m.f: $E_a = K_g \phi_f \omega_m$

Electromagnetic torque: $T_e = K_g \phi_f I_a$

Terminal voltage equation: $V_t = E_a + I_a r_a$

Assuming linear equation: $\phi_f = K_f I_f$



$$V_t = E_a + I_a r_a$$

$$V_t = K_g \phi_f \omega_m + \frac{T_e r_a}{K_g \phi_f} \quad \dots \quad E_a = K_g \phi_f \omega_m, \quad T_e = K_g \phi_f I_a$$

$$\frac{V_t}{K_g \phi_f} = \omega_m + \frac{T_e r_a}{(K_g \phi_f)^2}$$

$$\omega_m = \frac{V_t}{K_g \phi_f} - \frac{r_a}{(K_g \phi_f)^2} T_e$$

$$\omega_m = \omega_0 - K_t T_e$$

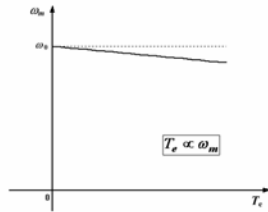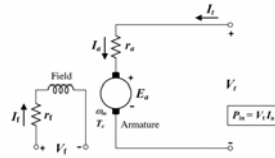


No load (i.e. $T_e = 0$) speed: $\omega_0 = \frac{V_t}{K_g \phi_f}$

Slope: $K_t = \frac{r_a}{(K_g \phi_f)^2}$ very small!

Slightly dropping ω_m with load

(c) Shunt DC Motors

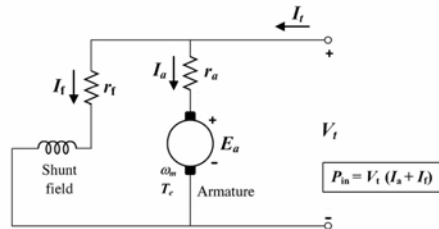

The back e.m.f: $E_a = K_g \phi_f \omega_m$

Electromagnetic torque: $T_e = K_g \phi_f I_a$

Terminal voltage equation: $V_t = E_a + I_a r_a$

Assuming linear equation: $\phi_f = K_f I_f$

$$V_t = E_a + I_a r_a$$



$$V_t = K_g \phi_f \omega_m + \frac{T_e r_a}{K_g \phi_f} \quad \dots \quad E_a = K_g \phi_f \omega_m, \quad T_e = K_g \phi_f I_a$$

$$\frac{V_t}{K_g \phi_f} = \omega_m + \frac{T_e r_a}{(K_g \phi_f)^2}$$

$$\omega_m = \frac{V_t}{K_g \phi_f} - \frac{r_a}{(K_g \phi_f)^2} T_e$$

$$\omega_m = \omega_0 - K_I T_e$$


Same as separately excited motor

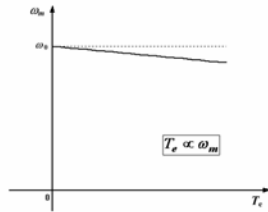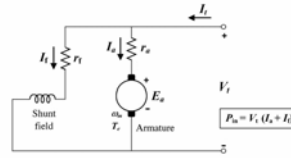

$$\text{No load (i.e. } T_e = 0) \text{ speed: } \omega_0 = \frac{V_t}{K_g \phi_f}$$

$$\text{Slope: } K_I = \frac{r_a}{(K_g \phi_f)^2} \quad \text{very small!}$$

Slightly dropping ω_m with load

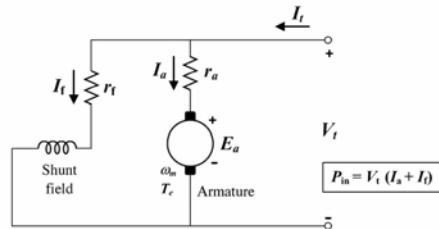

$$\omega_m = \omega_0 - K_I T_e$$

Note that: In the shunt DC motors, if suddenly the field terminals are disconnected from the power, supply while the motor was running, overspeeding problem will occur

$$E_a = K_g \phi_f \omega_m \quad E_a \text{ is momentarily constant, but } \phi \text{ will decrease rapidly.}$$


$$\text{so } \phi_f \rightarrow 0 \Rightarrow \omega_m \rightarrow \infty \quad \text{overspeeding!}$$

Motor Speed Control Methods

(a) Controlling separately-excited DC motors

Shaft speed can be controlled by

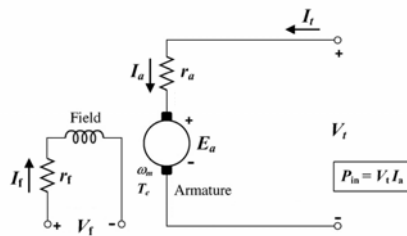- i. Changing the terminal voltage
- ii. Changing the field current (magnetic flux)




i. Changing the terminal voltage

$$\omega_m = \omega_0 - K_t T_e \quad \omega_0 = \frac{V_t}{K_g \phi_f} \quad V_t = E_a + I_a r_a$$

$$T_e = K_g \phi_f I_a$$
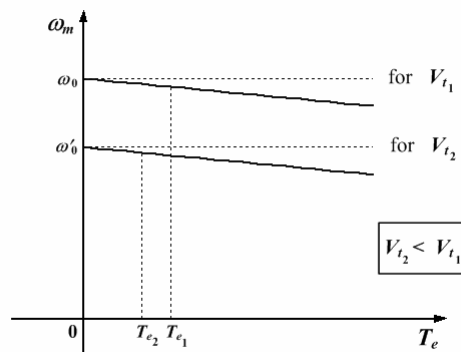
$$V_t \downarrow \Rightarrow \omega_0 \downarrow, T_e \downarrow$$




ii. Changing the field current

$$\omega_m = \omega_0 - K_t T_e \quad \omega_0 = \frac{V_t}{K_g \phi_f}$$


$$T_e = K_g \phi_f I_a$$

$$\phi_f = K_f I_f \quad (\text{linear magnetic circuit})$$

$$I_f \downarrow \Rightarrow \phi_f \downarrow, \omega_0 \uparrow, T_e \downarrow$$

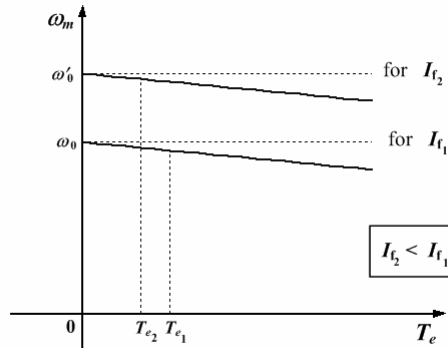

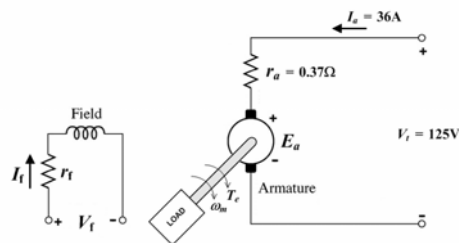Ex1: A separately excited DC motor drives the load at $n_r = 1150$ rpm.



- Find the gross output power (electromechanical power output) produced by the dc motor.
- If the speed control is to be achieved by armature voltage control and the new operating condition is given by:


$$n_r = 1150 \text{ rpm} \quad \text{and} \quad T_e = 30 \text{ Nm}$$

find the new terminal voltage V_t' while ϕ_f is kept constant.


(b) Controlling series DC motors

Shaft speed can be controlled by

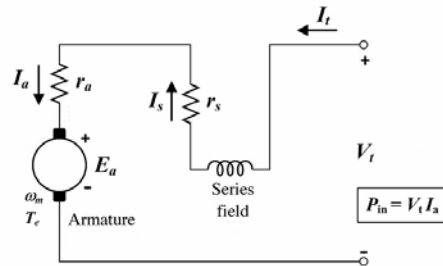- i. Adding a series resistance
- ii. Adding a parallel field diverter resistance
- iii. Using a potential divider at the input (i.e. changes the effective terminal voltage)



i. Adding a series resistance

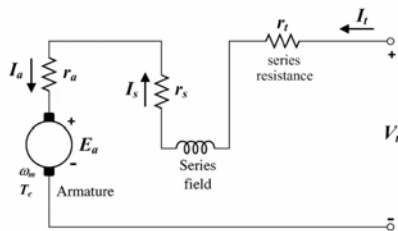

For the same T_e produced

E_a drops, I_a stays the same

$$E_a = V_t - I_a(r_a + r_s + r_t)$$

For the same T_e ,


ϕ_f is constant

but ω_m drops since $E_a = K_g \phi_f \omega_m$.


New value of the motor speed, ω_m is given by

$$\begin{aligned} \omega_m &= \frac{E_a}{K_g \phi_f} & \dots & T_e = K_g \phi_f I_a \\ & & \dots & E_a = K_g \phi_f \omega_m \end{aligned}$$
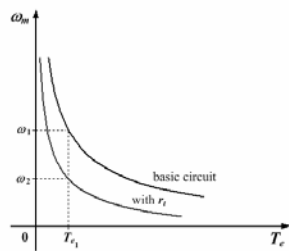
$$r_t \uparrow \Rightarrow E_a \downarrow, \omega_m \downarrow$$



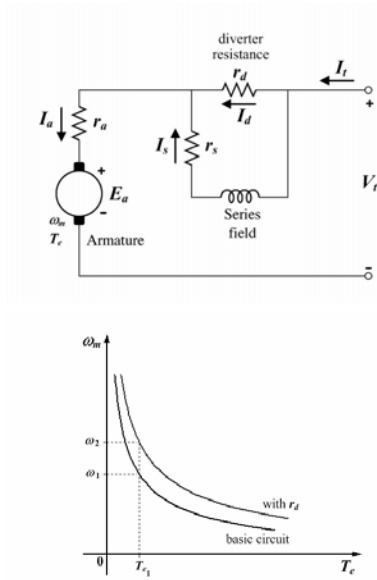ii. Adding a parallel field diverter resistance



When we add the diverter resistance

$$I_s \text{ drops i.e. } I_s < I_a.$$

E_a remains constant,

For the same T_e produced, I_a increases

$$I_a = \frac{V_t - E_a}{r_a + (r_s \parallel r_d)} \quad \dots \quad r_s \parallel r_d < r_s$$


When series field flux drops, the motor speed $\omega_m = E_a / K_g \phi_f$ should rise, while driving the same load.

$$\omega_m = \frac{E_a}{K_g \phi_f} \quad \dots \quad E_a = K_g \phi_f \omega_m$$

$$\dots \quad \phi_f = K_f I_s$$

$$r_d \downarrow \Rightarrow I_s \downarrow, I_a \uparrow, \phi_f \downarrow, \omega_m \uparrow$$

iii. Using a potential divider

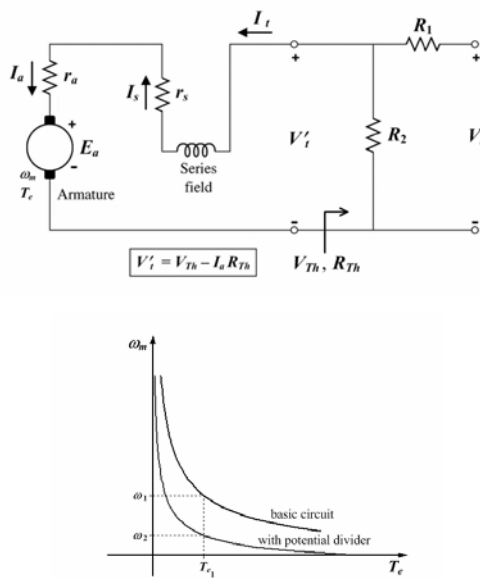

Let us apply Thévenin theorem to the right of V'_t

$$V_{Th} = \frac{R_2}{R_1 + R_2} V_t \quad R_{Th} = R_1 \parallel R_2$$

This system like the speed control by adding series resistance as explained in section (i) where $r_t \equiv R_{Th}$ and $V_t \equiv V_{Th}$.

For the same T_e produced

E_a drops rapidly, I_a stays the same

$$E_a = V_{Th} - I_a (r_a + r_s + R_{Th})$$

For the same T_e ,

ϕ_f is constant

but ω_m drops rapidly since $E_a = K_g \phi_f \omega_m$.

New value of the motor speed, ω_m is given by

$$\omega_m = \frac{E_a}{K_g \phi_f} \quad \dots \quad T_e = K_g \phi_f I_a$$

$$\dots \quad E_a = K_g \phi_f \omega_m$$

$$V'_t \downarrow \Rightarrow E_a \downarrow \downarrow, \omega_m \downarrow \downarrow$$

If the load increases, T_e and I_a increases and E_a decreases, thus motor speed ω_m drops down more.