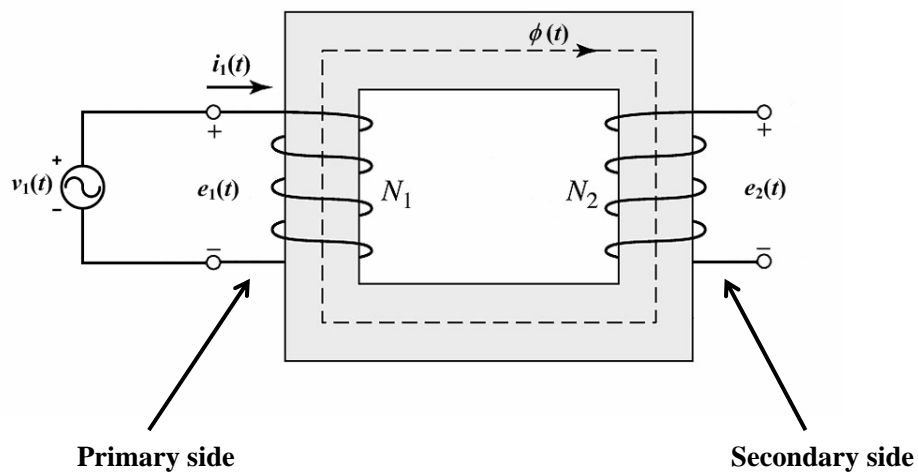


II. Transformers


Transformer

Transformer comprises two or more windings coupled by a common magnetic circuit (M.C.).

If the primary side is connected to an AC voltage source $v_1(t)$, an AC flux $\phi(t)$ will be produced in the M.C.



Ideal transformer voltage relationship

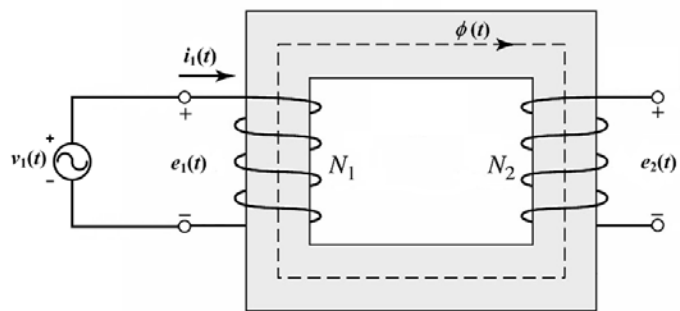


$$e_1(t) = N_1 \frac{d\phi(t)}{dt}$$

$$e_2(t) = N_2 \frac{d\phi(t)}{dt}$$


$$\frac{e_1}{e_2} = \frac{N_1}{N_2}$$

Ideal transformer symbol

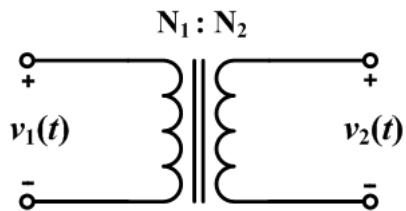


$$\frac{v_1}{v_2} = \frac{N_1}{N_2}$$

Another representation

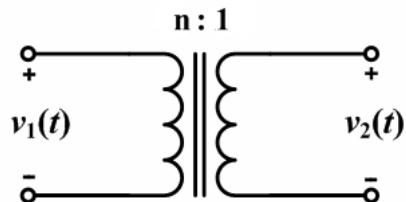


$$n = \frac{N_1}{N_2}$$


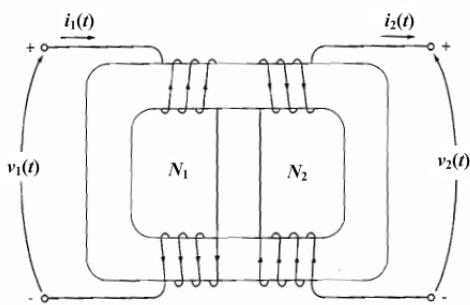
There are two common types of transformer construction:



(a) core-type


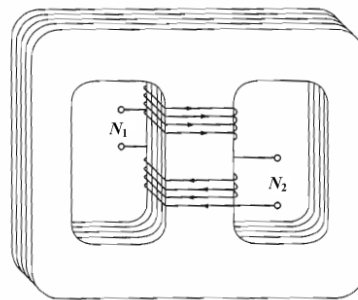


(b) shell-type

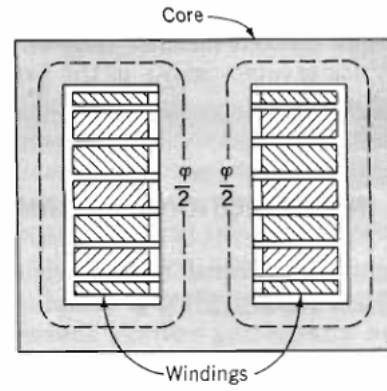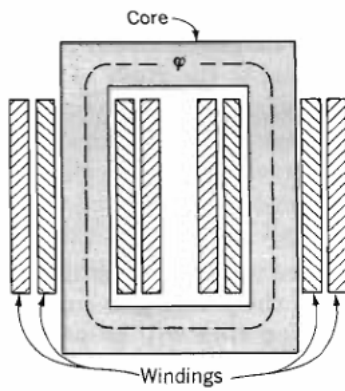


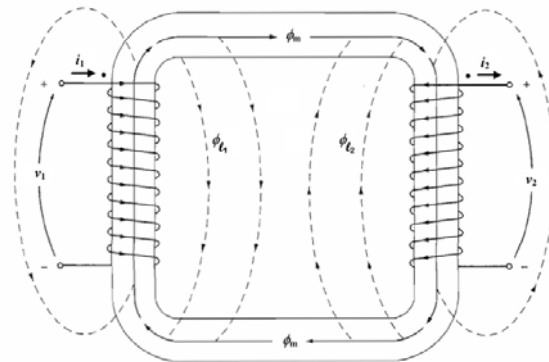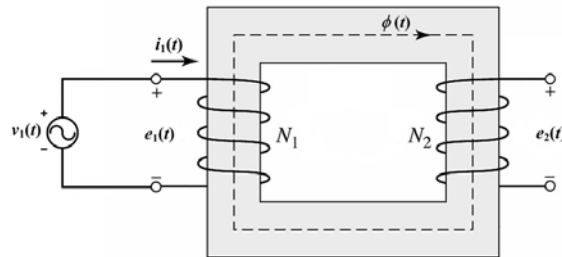1. Analysis of the transformer with no-load

Secondary side open-circuited:
(no sec. current)



Modelling of Magnetic Core

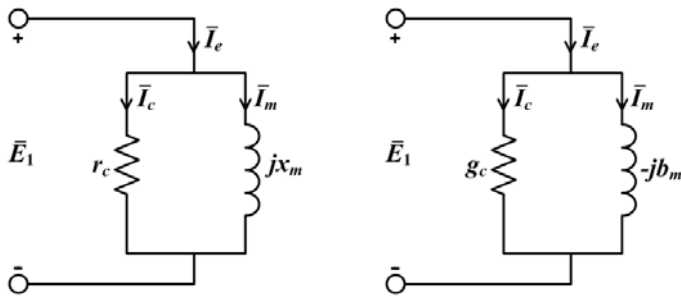

r_c : core loss resistance
(hysteresis & eddy-current loss)

x_m : magnetizing reactance

I_e : exciting current

g_c : core loss conductance

$g_c - jb_m$: magnetizing admittance


b_m : magnetizing susceptance

$$g_c = \frac{1}{r_c}$$

$$-jb_m = \frac{1}{jx_m}$$

Phasor diagram

$$\bar{I}_e = \bar{I}_c + \bar{I}_m$$

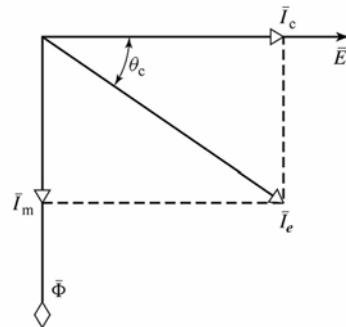

\bar{I}_m lags \bar{E}_1 by 90°


\bar{I}_c in phase with \bar{E}_1

Modelling of Leakage Flux

Let us express the voltage drop due to leakage flux in the primary winding below

$$v_{\ell_1} = \frac{d\lambda_{\ell_1}}{dt} = \frac{d\lambda_{\ell_1}}{di_e} \frac{di_e}{dt} = L_{\ell_1} \frac{di_e}{dt} \quad \text{where} \quad \lambda_{\ell_1} = N_1 \phi_{\ell_1}$$

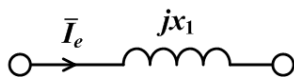
$$v_{\ell_1} = L_{\ell_1} \frac{di_e}{dt} \quad L_{\ell_1} : \text{leakage inductance of primary winding}$$



primary leakage reactance: $x_1 = \omega L_{\ell_1}$


$$\omega = 2\pi f$$

Modelling of Copper Loss

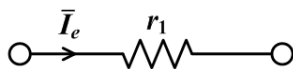

r_1 : resistance of primary winding

Equivalent circuit model of primary side

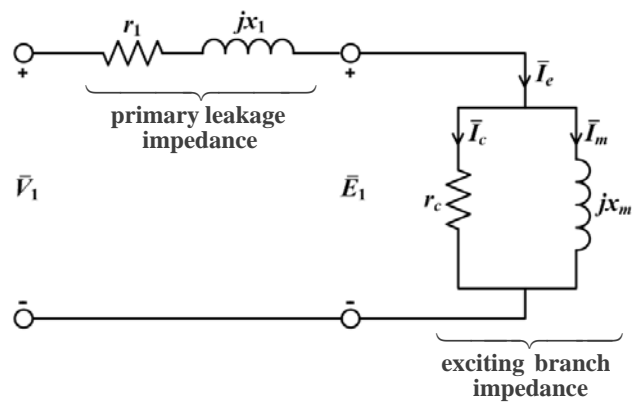

Exciting current is only a few percent of rated primary current of the transformer

2. Ideal Transformer Operation

- No leakage fluxes
- Negligible winding internal resistances
- B-H characteristic of the magnetic material is single-valued, and linear
 - No hysteresis loss
- Magnetic core has a very high μ_r , i.e. Core reluctance is negligible.
- No copper, no core losses (Efficiency $\eta = 100\%$)
- Interwinding capacitances are negligible at power frequencies (50Hz, 60Hz)

Basic Relations

1. From Faraday's Law: $e_1 = N_1 d\phi/dt$, and
 $e_2 = N_2 d\phi/dt$

So,

$$\frac{e_1}{e_2} = \frac{N_1}{N_2}$$


2. Since winding resistances & leakage fluxes are negligible:

$$\frac{v_1}{v_2} = \frac{N_1}{N_2}$$

3. $\mathcal{F}_1 = \mathcal{F}_2$

$$\frac{i_1}{i_2} = \frac{N_2}{N_1}$$


4. Ideal transformer symbol

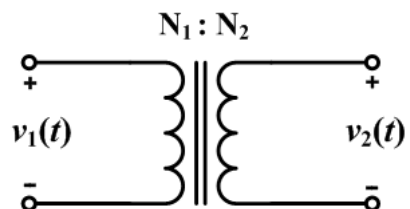


4. No power loss

Conservation of power: $v_1 i_1 = v_2 i_2$

5. Under Load

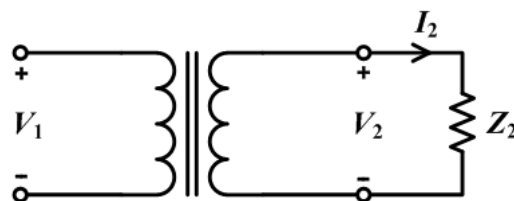

Ideal transformer under load

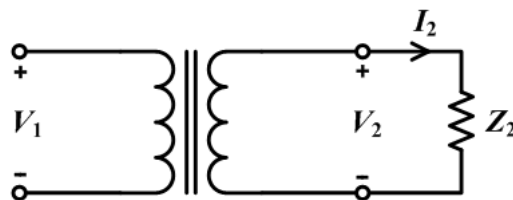


$$\frac{v_1}{v_2} = \frac{N_1}{N_2}$$


$$\frac{i_1}{i_2} = \frac{N_2}{N_1}$$

$$v_1 i_1 = v_2 i_2$$

$$v_2 = i_2 Z_2$$

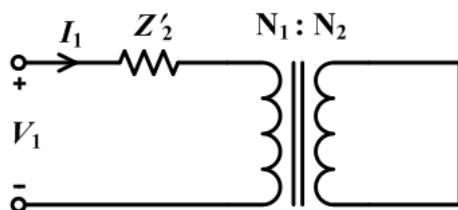

⇒

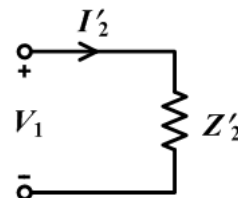

$$I_1 = I'_2$$

Eqv. crt. referred to primary

Secondary impedance referred to primary side:

$$Z'_2 = \left(\frac{N_1}{N_2} \right)^2 Z_2 = n^2 Z_2$$

Terminology

V_1, I_1, Z_1 : actual primary quantities

V_2, I_2, Z_2 : actual secondary quantities


V'_1, I'_1, Z'_1 : primary quantities referred to secondary side

V'_2, I'_2, Z'_2 : secondary quantities referred to primary side

$$V'_1 = \frac{N_2}{N_1} V_1, \quad I'_1 = \frac{N_1}{N_2} I_1, \quad Z'_1 = \left(\frac{N_2}{N_1} \right)^2 Z_1$$


$$V'_2 = \frac{N_1}{N_2} V_2, \quad I'_2 = \frac{N_2}{N_1} I_2, \quad Z'_2 = \left(\frac{N_1}{N_2} \right)^2 Z_2$$

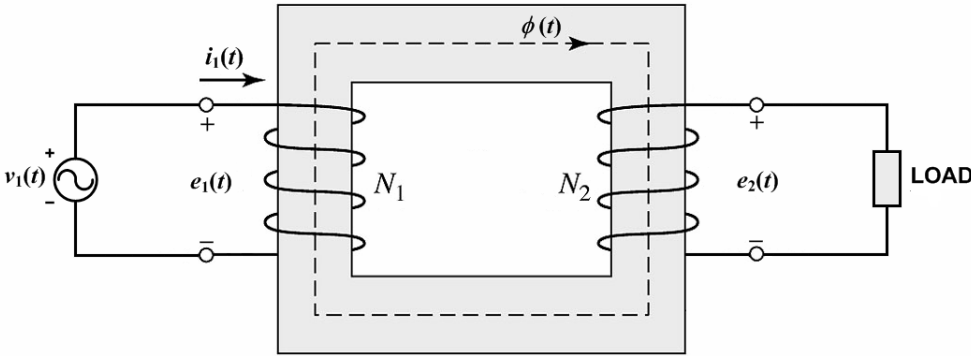3. Equivalent circuit representation of a practical transformer



Transformer under load

Equivalent Circuit representation

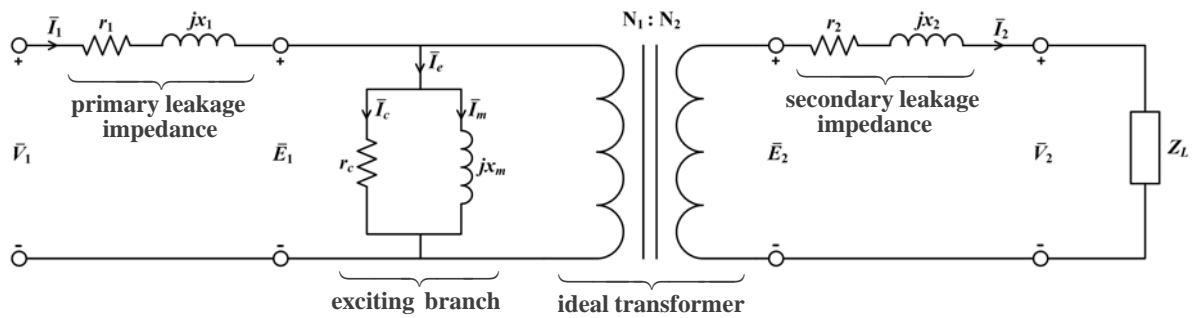


r_1 : Primary winding internal resistance (Ω) r_2 : Secondary winding internal resistance (Ω)

x_1 : Primary winding leakage reactance (Ω) x_2 : Secondary winding leakage reactance (Ω)

r_c : Core-loss resistance (Ω)

x_m : Magnetizing reactance (Ω)

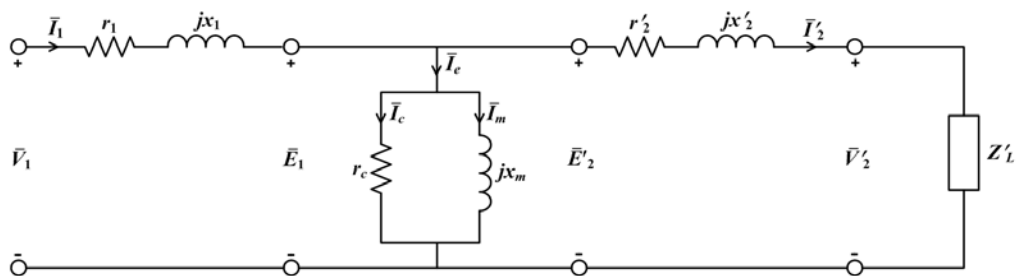Equivalent circuit referred to primary side



r'_2 : Secondary winding internal resistance referred to primary side

x'_2 : Secondary winding leakage reactance referred to primary side

I'_2 : Secondary winding current referred to primary side

V'_2 : Secondary winding voltage referred to primary side

Z'_L : Load impedance referred to primary side

$$r'_2 = n^2 r_2$$

$$x'_2 = n^2 x_2$$

$$I'_2 = \frac{I_2}{n}$$


$$V'_2 = n V_2$$

$$Z'_L = n^2 Z_L$$

$$n = \frac{N_1}{N_2}$$

$$E_1 = E'_2 = n E_2$$

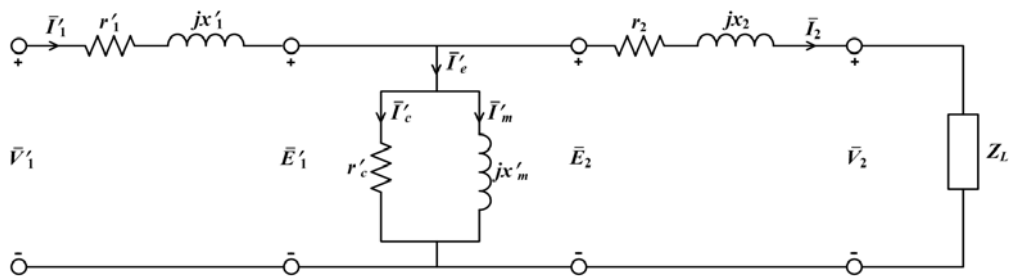Equivalent circuit referred to secondary side



r_1' : Primary winding internal resistance referred to secondary side

$$r_1' = \frac{r_1}{n^2}$$

$$n = \frac{N_1}{N_2}$$

x_1' : Primary winding leakage reactance referred to secondary side

$$x_1' = \frac{x_1}{n^2}$$

$$I_1' = nI_1$$

I_1' : Primary winding current referred to secondary side

$$r_c' = \frac{r_c}{n^2}$$

$$V_1' = \frac{V_1}{n}$$

V_1' : Primary winding voltage referred to secondary side


r_c' : Core-loss resistance referred to sec. side

$$x_m' = \frac{x_m}{n^2}$$

$$E_2 = E_1' = \frac{E_1}{n}$$

x_m' : Magnetizing reactance referred to sec. side

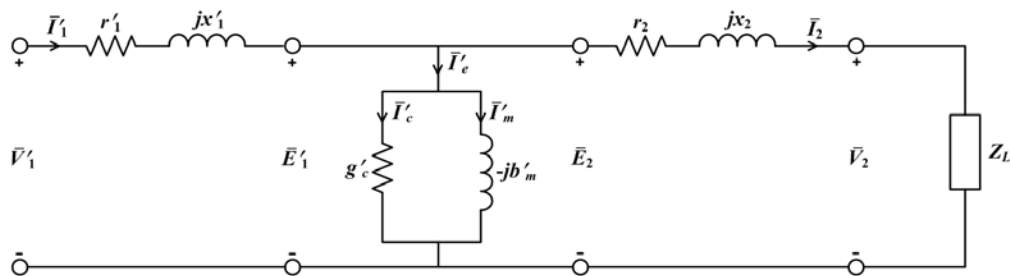Equivalent circuit referred to secondary side



g'_c : Core-loss conductance referred to sec. side

b'_m : Magnetizing admittance referred to sec. side

$$n = \frac{N_1}{N_2}$$


$$g'_c = \frac{1}{r'_c}$$

$$-jb'_m = \frac{1}{jx'_m}$$


$$g'_c = n^2 g_c$$

$$b'_m = n^2 b_m$$

Simplification

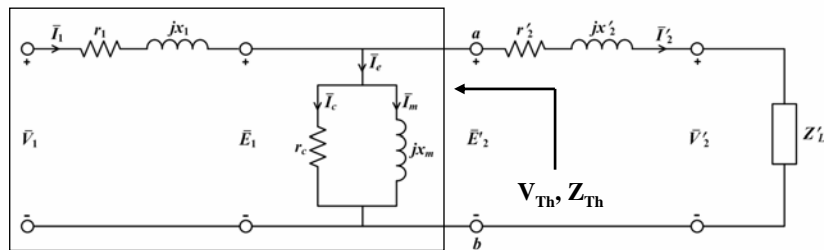

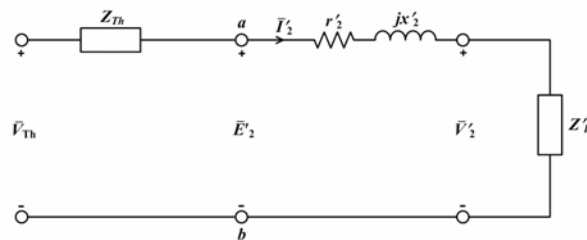Let us apply Thévenin equivalent circuit to the primary side



$$r_c \parallel jx_m = \frac{1}{g_c - jb_m}$$



$$\bar{V}_{Th} = \bar{V}_1 \frac{r_c \parallel jx_m}{(r_1 + jx_1) + (r_c \parallel jx_m)} \cong \bar{V}_1 \quad \text{where } |r_c \parallel jx_m| \gg |r_1 + jx_1|$$

$$\boxed{\bar{V}_{Th} \cong \bar{V}_1}$$

$$Z_{Th} = (r_1 + jx_1) \parallel (r_c \parallel jx_m) \cong r_1 + jx_1$$

$$\boxed{Z_{Th} \cong r_1 + jx_1}$$

Simplification

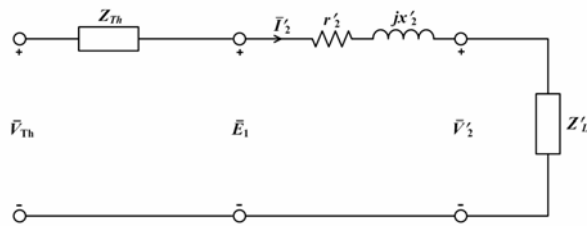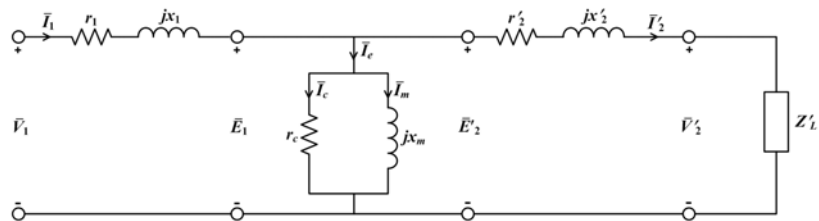


$$\bar{E}_1 = \bar{V}_{Th} - \cancel{Z_{Th} \bar{I}_2} \cong \bar{V}_{Th} \cong \bar{V}_1 \quad \text{where } Z_{Th} \cong r_1 + jx_1$$


$$\boxed{\bar{E}_1 \cong \bar{V}_1}$$

Error made in approximations is at most 1% – 2% compared to actual values.

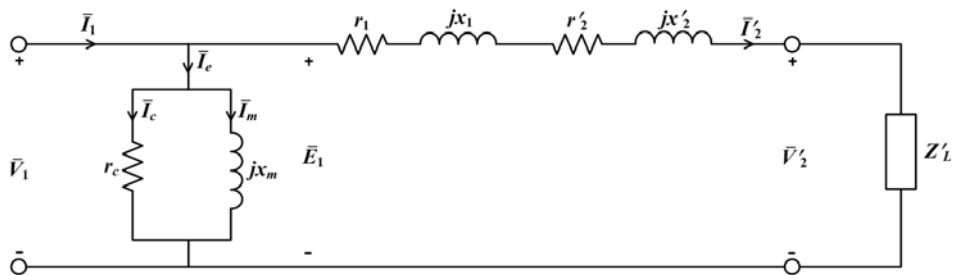Approximate Equivalent Circuit referred to primary side



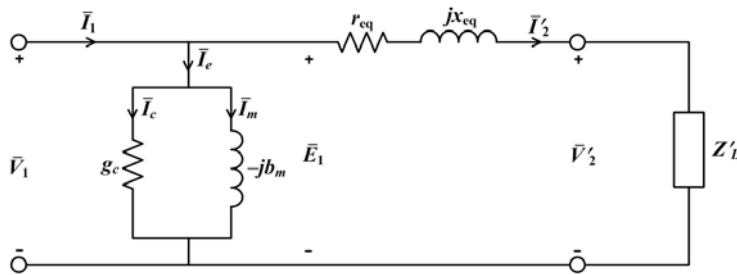
Further simplification gives us the figure below




$$r_{eq} = r_1 + r'_2$$

$$x_{eq} = x_1 + x'_2$$

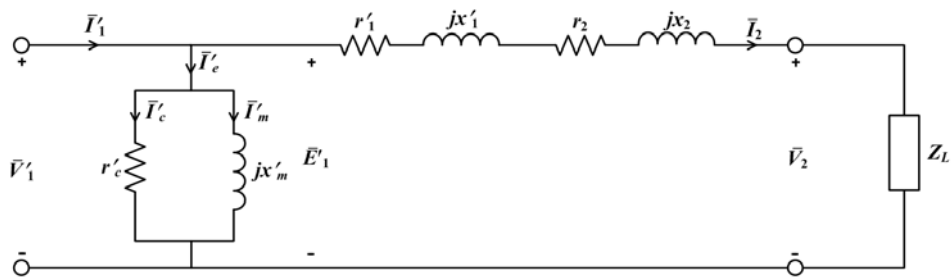Approximate Equivalent Circuit referred to secondary side




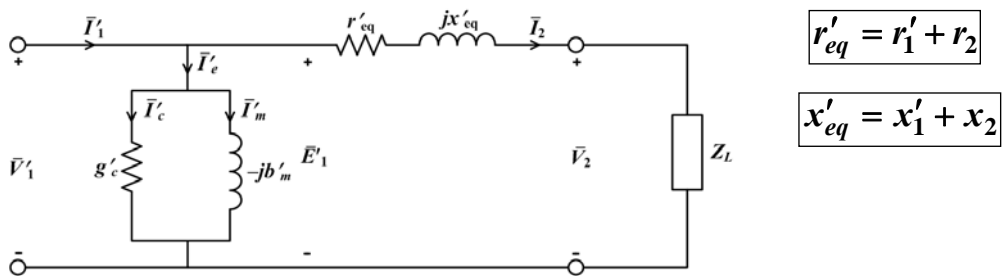Further simplification gives us the figure below




Approximate Equivalent Circuits for Large Transformers (referred to primary side)

(of a few 100 kVAs)

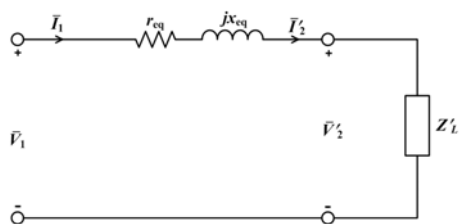


$|r_c \parallel jx_m|$ is very large

(in the MVA range)

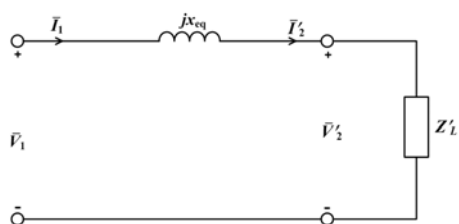

$x_{eq} \gg r_{eq}$ (4 - 10 times)

AC Power

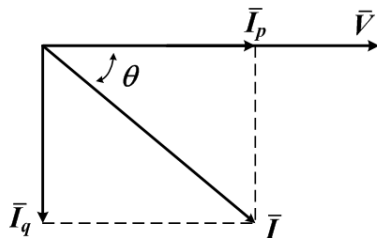

θ : angle between voltage \bar{V} and current \bar{I}

Real Power : $P = V_{\text{rms}} I_{\text{rms}} \cos \theta$ [W, Watts]


Reactive Power : $Q = V_{\text{rms}} I_{\text{rms}} \sin \theta$ [VAR, Volt Ampere Reactive]
(Imaginary Power)

Complex Power : $S = P + jQ$

Apparent Power : $|S| = V_{\text{rms}} I_{\text{rms}}$ [VA, Volt Ampere]

Power Factor : $\cos \theta = \frac{P}{|S|}$

Transformer Power Flow

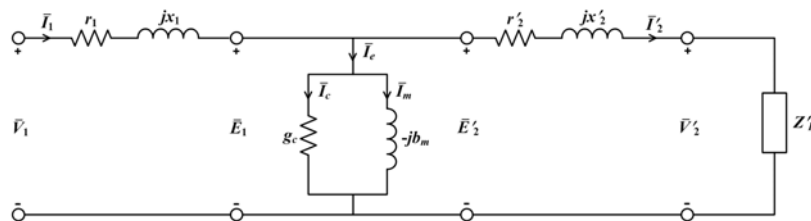

$$P_{\text{in}} = V_1 I_1 \cos \theta_1$$

$$P_{\text{out}} = P_{\text{load}} = V_2' I_2' \cos \theta_2$$

$$P_{\text{in}} = P_{\text{cu}_1} + P_{\text{core}} + P_{\text{cu}_2} + P_{\text{load}}$$

P_{cu} : Copper loss

P_{core} : Core loss

$$P_{\text{cu}_1} = I_1^2 r_1 = I_1'^2 r_1'$$

$$P_{\text{core}} = E_1^2 g_c = E_1'^2 g_c'$$


$$P_{\text{core}} \cong V_1^2 g_c$$

$$P_{\text{cu}_2} = I_2^2 r_2 = I_2'^2 r_2'$$


4. Short-circuit and Open-circuit Tests

- Measure voltage (V), current (I) and power (P) in order to determine the equivalent circuit parameters of the transformer:
 - For leakage impedance parameters
 - with secondary short circuited
 - For exciting branch parameters
 - with secondary open circuited


i. Short-circuit Test

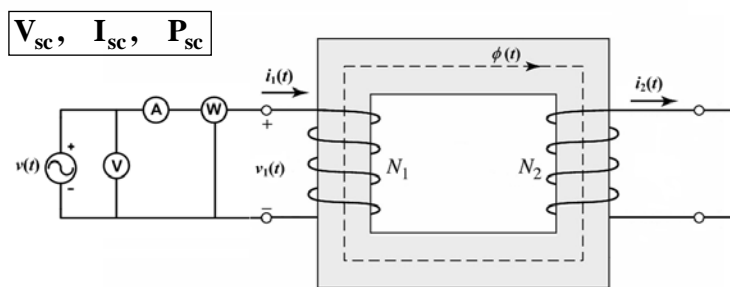

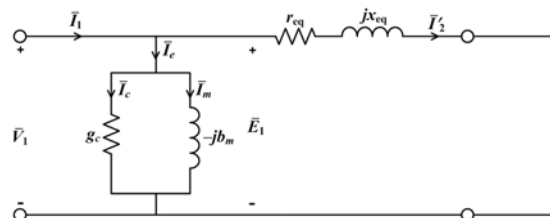A reduced voltage \vec{V}_{sc} of 2% - 10 % of rated voltage is applied to allow rated primary current.




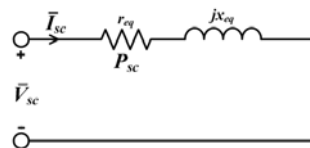where $\frac{1}{g_c - jb_m} \gg r_{eq} + jx_{eq}$



Short circuit equivalent circuit

Short-circuit Test

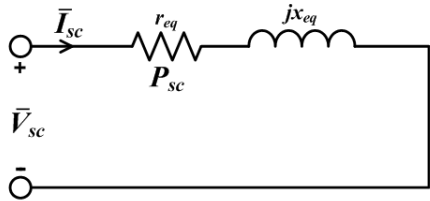

$$r_{eq} = \frac{P_{sc}}{I_{sc}^2}$$

$$|z_{eq}| = \frac{V_{sc}}{I_{sc}}$$

where $z_{eq} = r_{eq} + jx_{eq}$

$$x_{eq} = \sqrt{|z_{eq}|^2 - r_{eq}^2}$$

$$r_{eq} = r_1 + r'_2 \quad \text{where } r_1 \cong r'_2$$

$$r_1 = r'_2 \cong \frac{r_{eq}}{2}$$


$$x_{eq} = x_1 + x'_2 \quad \text{where } x_1 \cong x'_2$$

$$x_1 = x'_2 \cong \frac{x_{eq}}{2}$$


at 50 Hz $r_{1,AC} = 1.1 r_{1,DC}$ ← Measured DC resistance
 Form factor $r_{2,AC} = 1.1 r_{2,DC}$ ←

ii. Open-circuit Test


V_{oc} , I_{oc} , P_{oc}

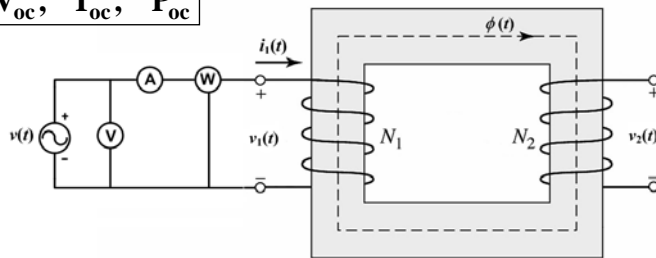

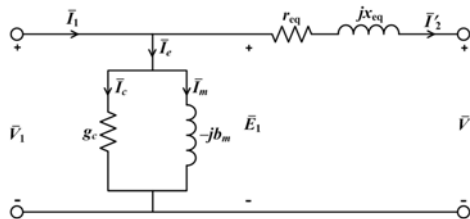Rated voltage is applied to the transformer under no-load and exciting current flows, which is a few percent of rated current.




where $I_2' = 0$ and $I_e = I_1$

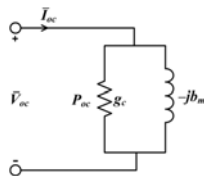

Open circuit equivalent circuit

Open-circuit Test

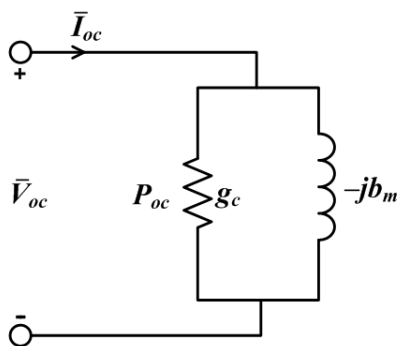

$$g_c = \frac{P_{oc}}{V_{oc}^2}$$

$$|Y_c| = \frac{I_{oc}}{V_{oc}}$$

$$\text{where } Y_c = g_c - j b_m$$

$$b_m = \sqrt{|Y_c|^2 - g_c^2}$$

$$\text{where } g_c = \frac{1}{r_c} \quad \text{and} \quad b_m = \frac{1}{x_m}$$

5. Voltage regulation (VR%)


- The change in secondary terminal voltage (load voltage) from no-load to full-load
 - expressed as a percentage (%) of the rated value
 - ideally $VR\% = 0$.

$$VR\% = \frac{V_1 - V_2'}{V_{1(\text{rated})}} \times 100\%$$

or

$$VR\% = \frac{V_1' - V_2}{V_{2(\text{rated})}} \times 100\%$$


Simplification by approximation

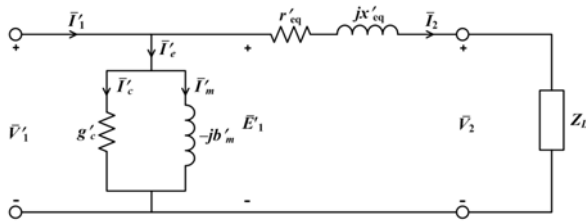

$$\bar{V}'_1 = \bar{V}_2 + (r'_{eq} + j x'_{eq}) \bar{I}_2$$

$$V'_1 \approx V_2 + I_2 r'_{eq} \cos \theta + I_2 x'_{eq} \sin \theta$$
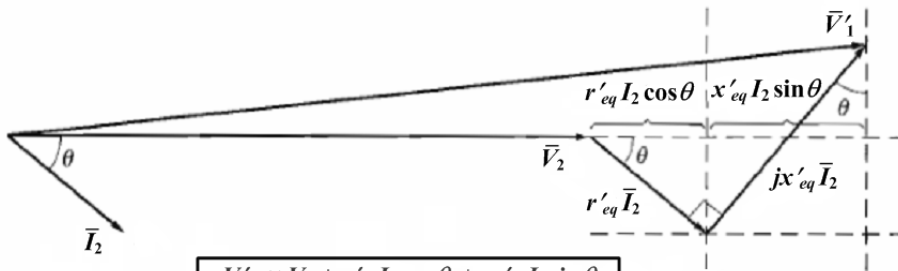
$$\mathbf{VR}\% = \frac{I_2 r'_{eq} \cos \theta + I_2 x'_{eq} \sin \theta}{V_2} \times 100\%$$



$$V'_1 \cong V_2 + r'_{eq} I_2 \cos \theta + x'_{eq} I_2 \sin \theta$$

Zero regulation, i.e. VR% = 0

- For zero regulation, phase angle (θ) of the load is given by

$$\text{VR}\% = \frac{I_2}{V_2} (r'_{eq} \cos \theta + x'_{eq} \sin \theta) \times 100\%$$

$$r'_{eq} \cos \theta + x'_{eq} \sin \theta = 0$$

$$\theta = -\tan^{-1} \left(\frac{r'_{eq}}{x'_{eq}} \right)$$

Note that $\theta < 0$, so

Load must be capacitive for zero regulation

NOTE

- For an inductive load, $\mathbf{Z}_L = \mathbf{R}_L + j\mathbf{X}_L$
 - Always $V'_1 > V_2$, i.e. $\mathbf{VR}\% > 0$
- For a capacitive load, $\mathbf{Z}_L = \mathbf{R}_L - j\mathbf{X}_L$
 - Usually $V'_1 \leq V_2$, i.e. $\mathbf{VR}\% \leq 0$ (where $-x'_{eq} \sin \theta \geq r'_{eq} \cos \theta$)

6. Efficiency ($\eta\%$)

- The ratio of the output power given to the load and the input power taken from the electrical supply
 - expressed as a percentage (%)

$$\eta = \frac{P_{\text{out}}}{P_{\text{in}}} 100\%$$

$$\eta = \frac{P_{\text{out}}}{P_{\text{out}} + P_{\text{losses}}} 100\%$$

$$\eta = \frac{P_{\text{out}}}{P_{\text{out}} + P_{\text{losses}}} 100\%$$

$$P_{\text{losses}} = P_{\text{cu}} + P_{\text{core}}$$

$$\eta = \frac{P_{\text{out}}}{P_{\text{out}} + P_{\text{cu}_1} + P_{\text{cu}_2} + P_{\text{core}}} 100\%$$

$$P_{\text{cu}} = P_{\text{cu}_1} + P_{\text{cu}_2}$$

$$\eta = \frac{V_2 I_2 \cos \theta}{V_2 I_2 \cos \theta + I_1^2 r_1 + I_2^2 r_2 + V_1^2 g_c} 100\%$$

$$P_{\text{cu}} \approx I_2^2 r'_{eq}$$

$$\eta = \frac{V_2 I_2 \cos \theta}{V_2 I_2 \cos \theta + I_2^2 r'_{eq} + V_1^2 g_c} 100\%$$

or

$$\eta = \frac{V_2' I_2' \cos \theta}{V_2' I_2' \cos \theta + I_2'^2 r_{eq} + V_1^2 g_c} 100\%$$

Maximum efficiency

Let us find the value of I_2 which maximizes the efficiency $\frac{d\eta}{dI_2} = 0$

$$\text{where } \eta = \frac{V_2 I_2 \cos \theta}{V_2 I_2 \cos \theta + I_2^2 r'_{eq} + P_{\text{core}}} \cdot 100\%$$

$$\frac{d\eta}{dI_2} = 0 \Rightarrow V_2 \cos \theta (V_2 I_2 \cos \theta + I_2^2 r'_{eq} + P_{\text{core}}) - (V_2 \cos \theta + 2I_2 r'_{eq}) V_2 I_2 \cos \theta = 0$$

$$V_2 I_2 \cos \theta + I_2^2 r'_{eq} + P_{\text{core}} - (V_2 \cos \theta + 2I_2 r'_{eq}) I_2 = 0$$

$$P_{\text{core}} - I_2^2 r'_{eq} = 0$$

$$P_{\text{core}} = I_2^2 r'_{eq}$$

$$\boxed{P_{\text{core}} = P_{\text{cu}}}$$

$$\text{i.e., } V_1^2 g_c = I_2^2 r'_{eq} = I_2'^2 r_{eq}$$

Thus, maximum efficiency is achieved if core loss equals to the copper loss.

Examples

1. A 12kVA, 220/440V, 50 Hz single phase transformer has the following test data:
 - No-load test: 220V, 2A, 165W (measured at primary side)
 - Short-circuit test: 12V, 15A, 60W (measured at secondary side)
- a) Calculate the equivalent circuit parameters referred to primary side
- b) Calculate the primary terminal voltage on full-load at a power factor of: 0.8 pf lagging.

2. Given a 250kVA, 4160:480V, 60 Hz transformer, the following parameters are obtained by tests

- $r_1 = 0.09 \Omega$ and $x_1 = 1.7 \Omega$
- $r_2 = 1.2 \times 10^{-3} \Omega$ and $x_2 = 2.26 \times 10^{-2} \Omega$

Neglecting core losses,

- a) Calculate the primary voltage and voltage regulation for rated load at 76% pf lagging
- b) Repeat a) for a load of 76% pf leading
- c) Calculate the transformer efficiency for parts a) and b) with a core loss $P_{\text{core}} = 547\text{W}$.

3. The parameters of the exact equivalent circuit of a 150kVA, 2400/240V transformer are

- $r_1 = r'_2 = 0.2 \Omega$
- $x_1 = x'_2 = 0.45 \Omega$
- $r_c = 10 \text{ k}\Omega$ and $x_m = 1.55 \text{ k}\Omega$

Using both the exact and approximate equivalent circuit of the transformer, determine

a) Voltage regulation

b) Efficiency

for rated load at 0.8pf lagging

4. At 10kVA, 8000:230V transformer has a leakage impedance referred to primary of $90 + j400\Omega$. Exciting branch parameters are
- $r_c = 500\text{ k}\Omega$ and $x_m = 60\text{ k}\Omega$
- a) If primary voltage $V_1 = 7967\text{V}$ and actual load impedance $Z_L = 4.2 + j3.15\Omega$, find the secondary voltage of the transformer
- b) If the load is disconnected, and a capacitor of $-j6\Omega$ is connected in its place, what will be the load voltage?