

ECE 450 Lecture 4 :


Transmission Line Matching

Prof. Logan Liu

ECE Department

University of Illinois at Urbana-Champaign

Standing Wave Ratio

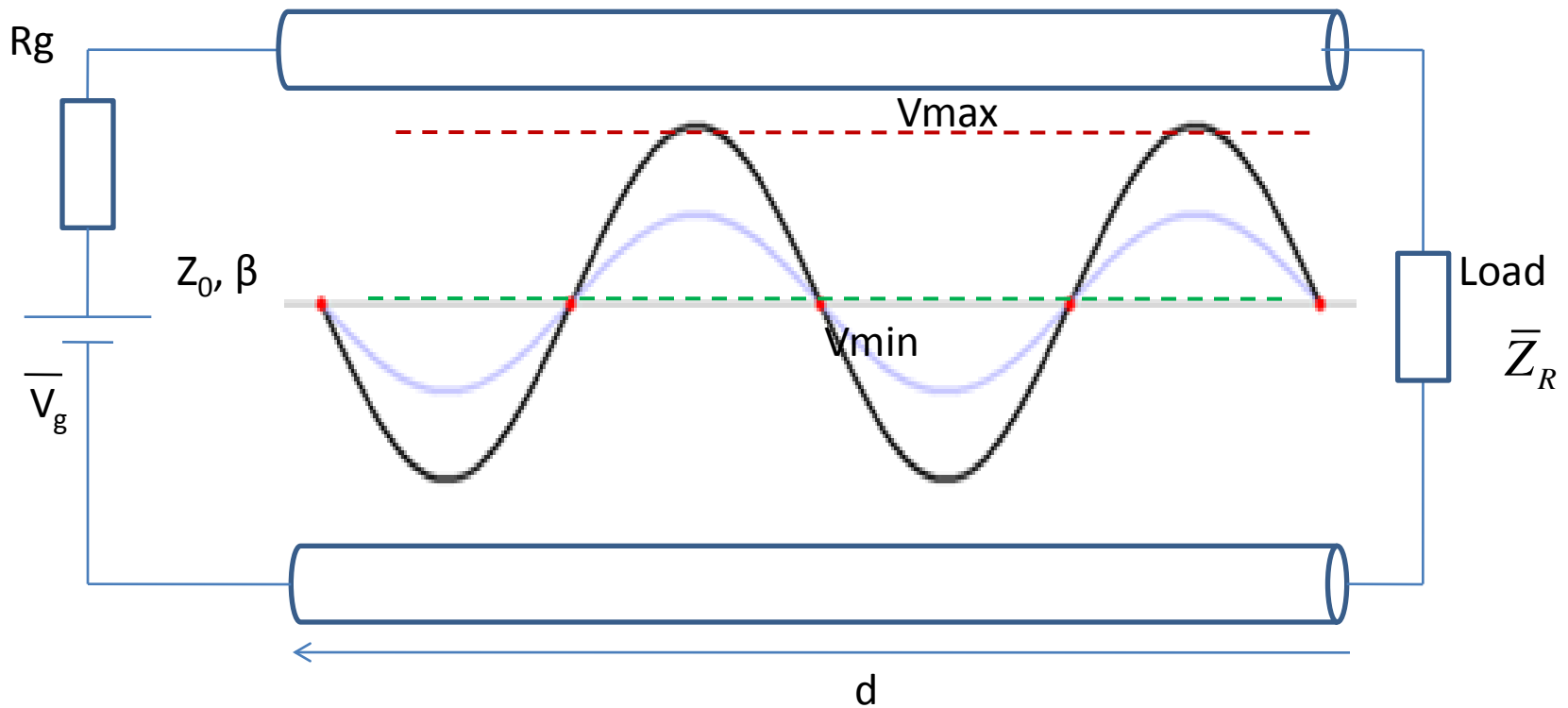



[Pg.452, Eqn. 7.25a]

$$|V(d)| = |V^+| |1 + \Gamma_R e^{-j2\beta d}|$$

[Pg.454, Eqn. 7.26]

$$SWR = \frac{V(d)_{max}}{V(d)_{min}} = \frac{|V^+| (1 + |\bar{\Gamma}_R|)}{|V^+| (1 - |\bar{\Gamma}_R|)}$$

Meaning of SWR

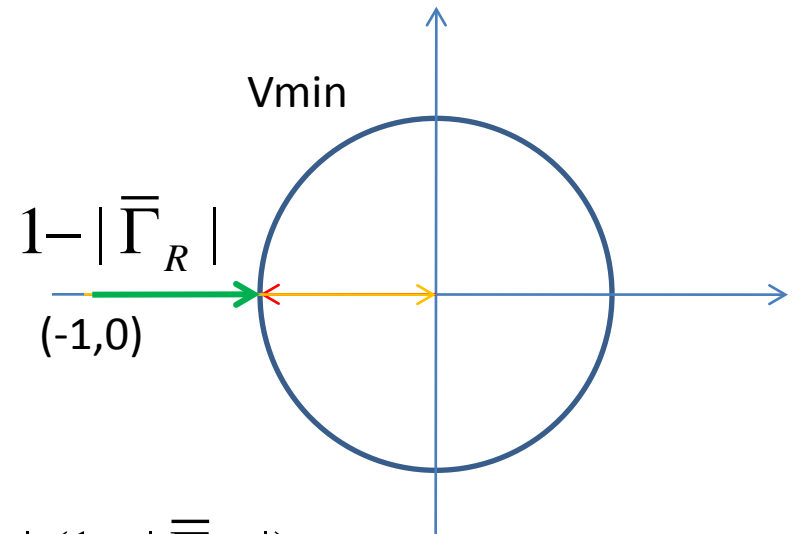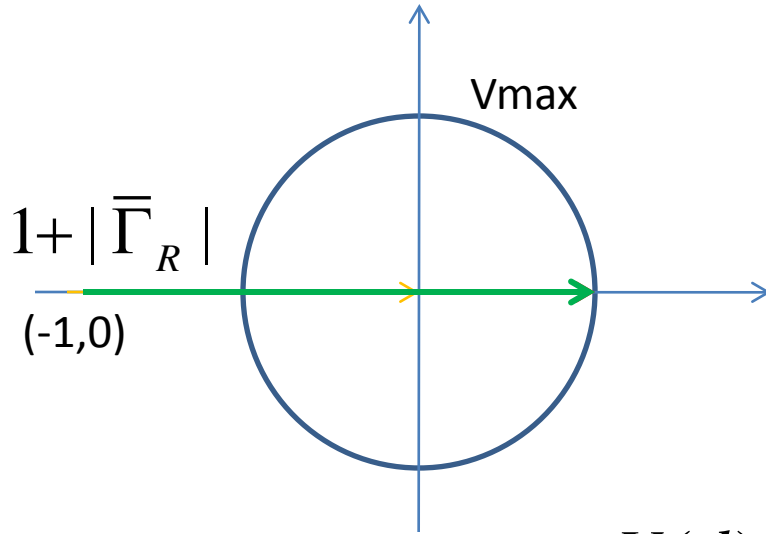


$$SWR = \frac{V(d)_{\max}}{V(d)_{\min}} = \frac{|V^+| (1 + |\bar{\Gamma}_R|)}{|V^+| (1 - |\bar{\Gamma}_R|)}$$

- | | | | | |
|--------------------------|-----------------------|---------------|--------------------------|------------------------|
| 1. Short circuit line | $\bar{\Gamma}_R = -1$ | \Rightarrow | $SWR \rightarrow \infty$ | Complete standing wave |
| 2. open circuit line | $\bar{\Gamma}_R = 1$ | \Rightarrow | $SWR \rightarrow \infty$ | |
| 3. Terminated with Z_0 | $\bar{\Gamma}_R = 0$ | \Rightarrow | $SWR = 1$ | NO standing wave |

$SWR < 1$?

SWR and Reflection Coefficient



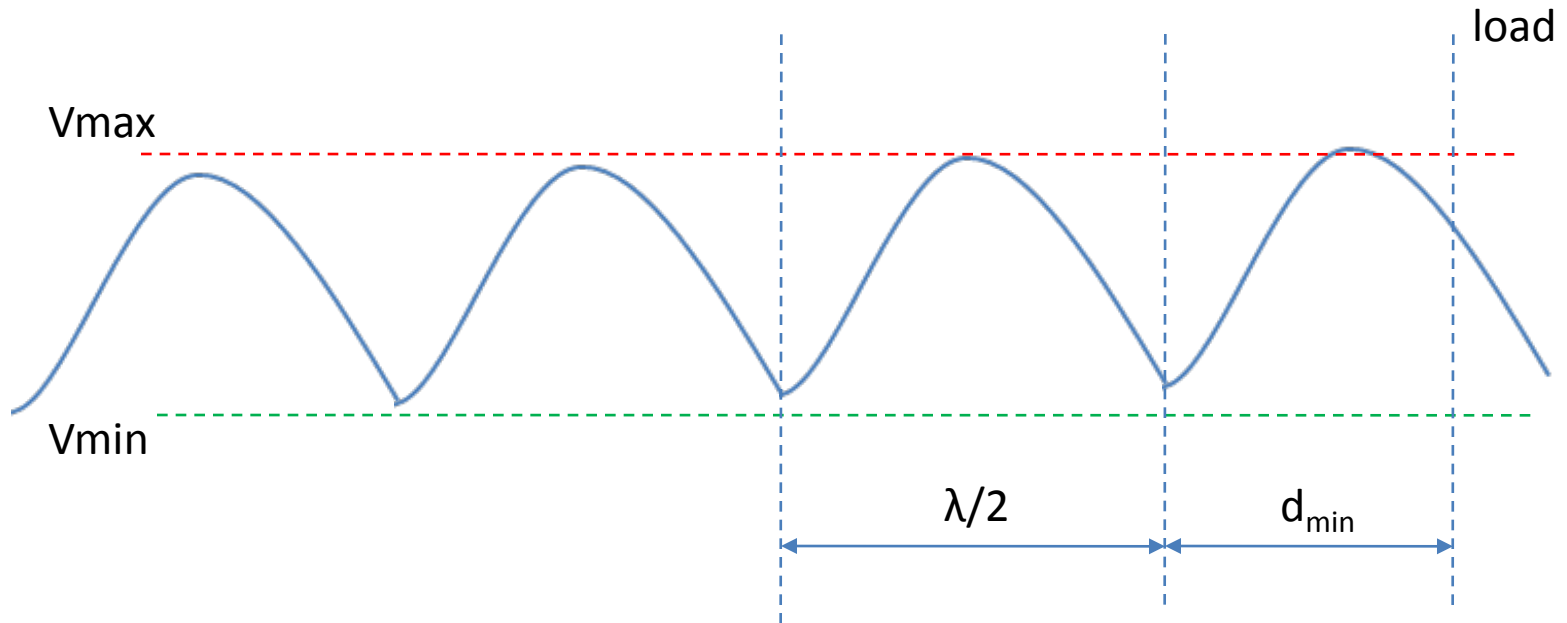


$$|\Gamma_R| = \frac{SWR - 1}{SWR + 1}$$

$$d_{\min} = \frac{\lambda}{4\pi} (\theta + \pi)$$

$$\bar{Z}_R = Z_0 \frac{1 + \bar{\Gamma}_R}{1 - \bar{\Gamma}_R}$$


SWR and Slotted Line

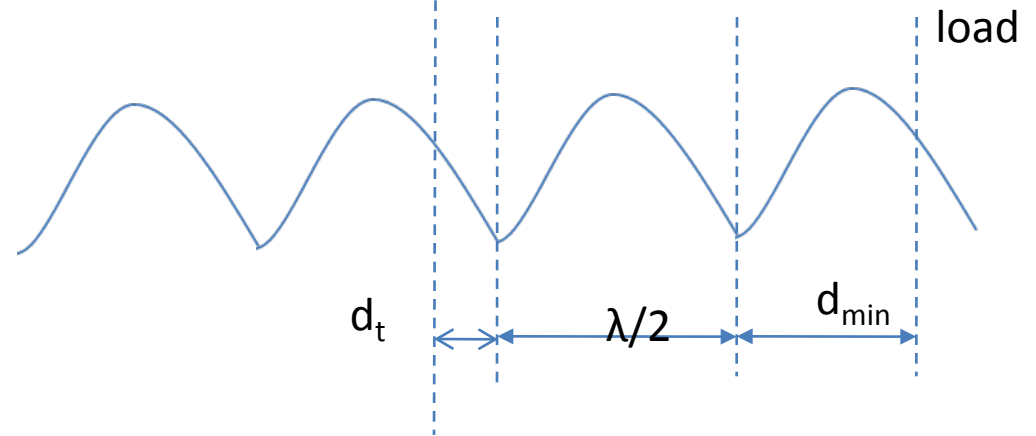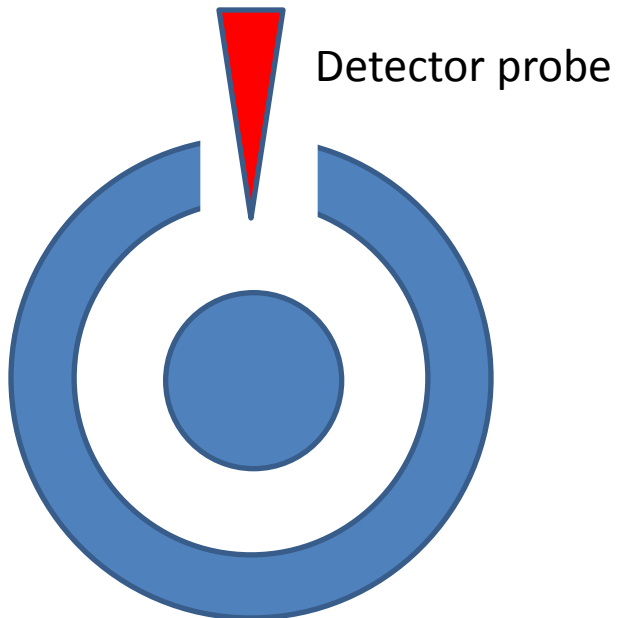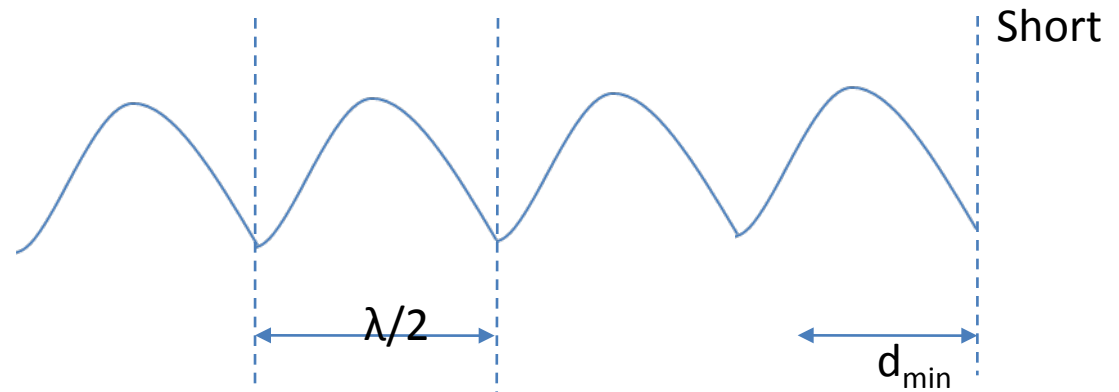

$$d_{\min} = \lambda / 2 - d_t$$


What is “T-line Matching”

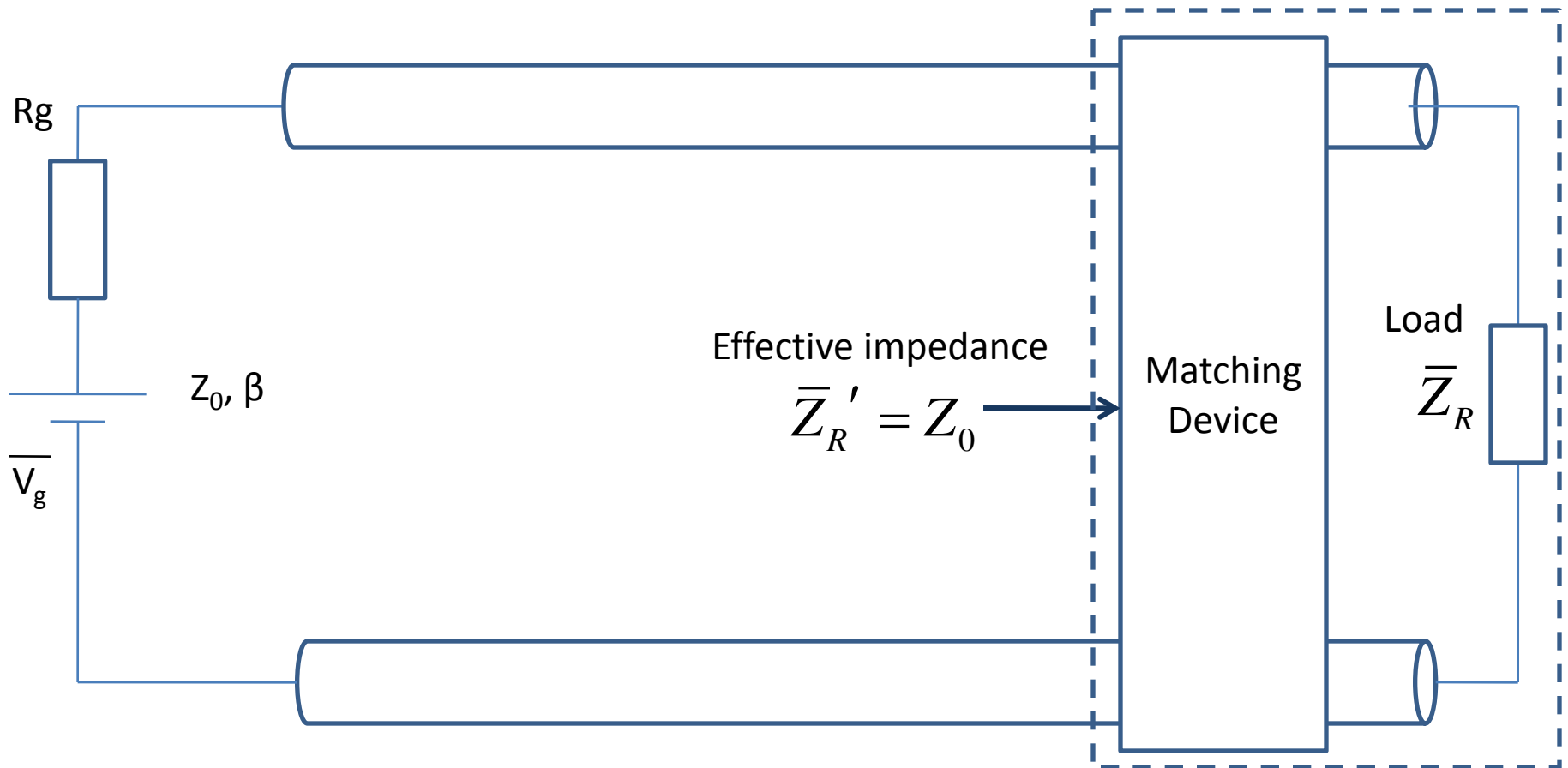- Match the effective impedance of the load to the T-line characteristic impedance Z_0 after adding a “matching device” near the load



Why “T-line Matching” I

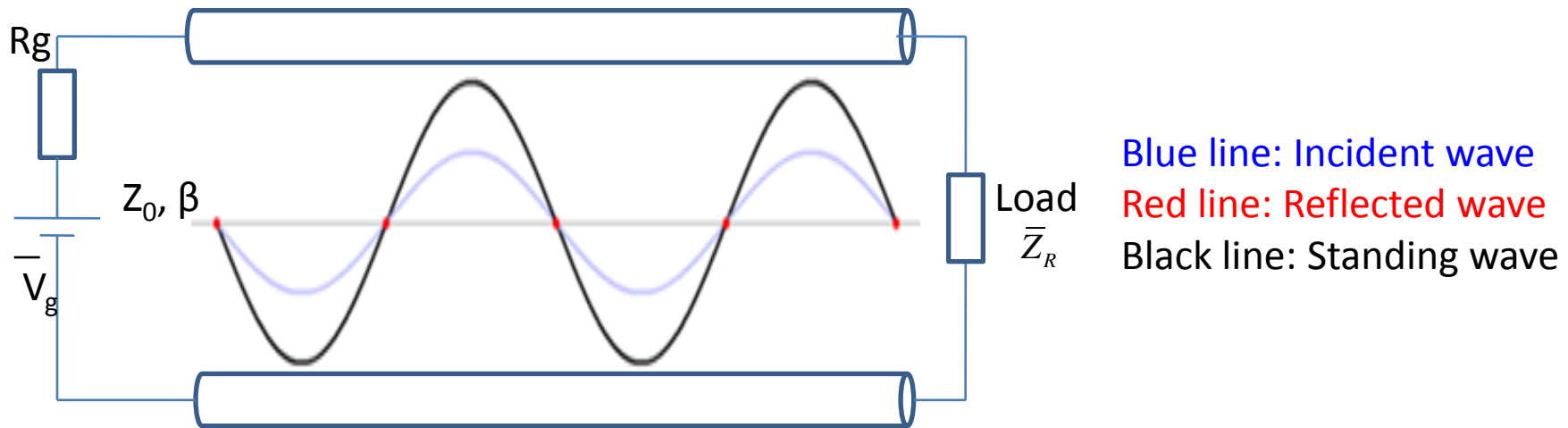- Standing waves in T-line “lock up” energy in the line and prevent good “transmission”




Reflection coefficient $\bar{\Gamma}_R = \frac{\bar{Z}_R - Z_0}{\bar{Z}_R + Z_0}$

“Matching” = “Zero Reflection”

$\Rightarrow \boxed{Z_R' = Z_0}$

Why “T-line Matching” II

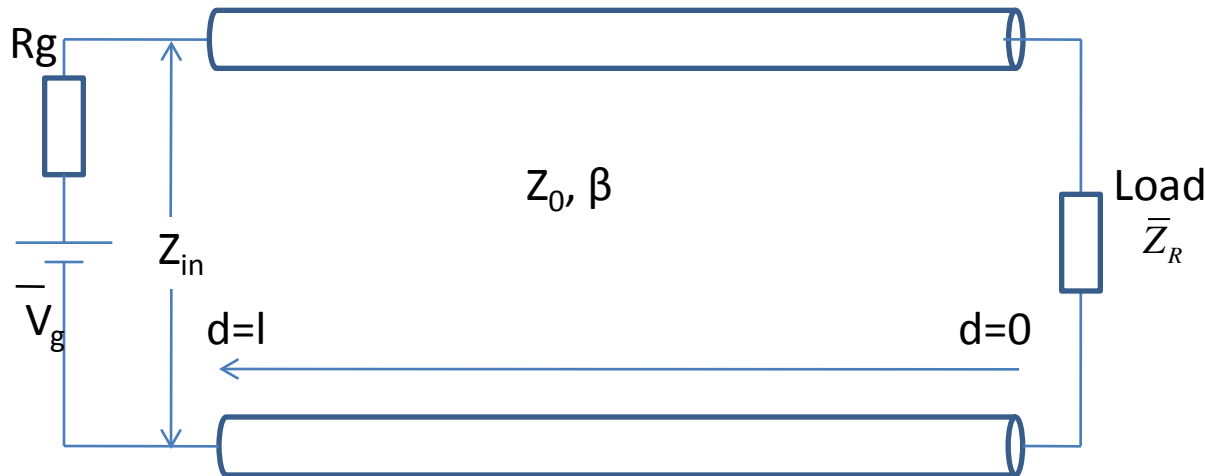- Without matching, transmitted power varies with the length of the line and impedance of the load



$$\bar{V}(R) = \bar{V}^+ (1 + \bar{\Gamma}_R)$$

$$\bar{I}(R) = \bar{V}^+ (1 + \bar{\Gamma}_R) / Z_0$$


$$\bar{Z}_{in} = \bar{Z}(l) = Z_0 \frac{1 + \bar{\Gamma}(l)}{1 - \bar{\Gamma}(l)}$$

$$\bar{V}^+ = \bar{V}_{in} = \bar{I}_{in} \bar{Z}(l) = \frac{\bar{V}_g}{\bar{Z}_g + \bar{Z}(l)} \bar{Z}(l)$$

Matching Technique I


- Quarter-wave Transformer (QWT) --- A matching device with the length of quarter wavelength.

Matching Condition $\bar{Z}_1 = Z_0$

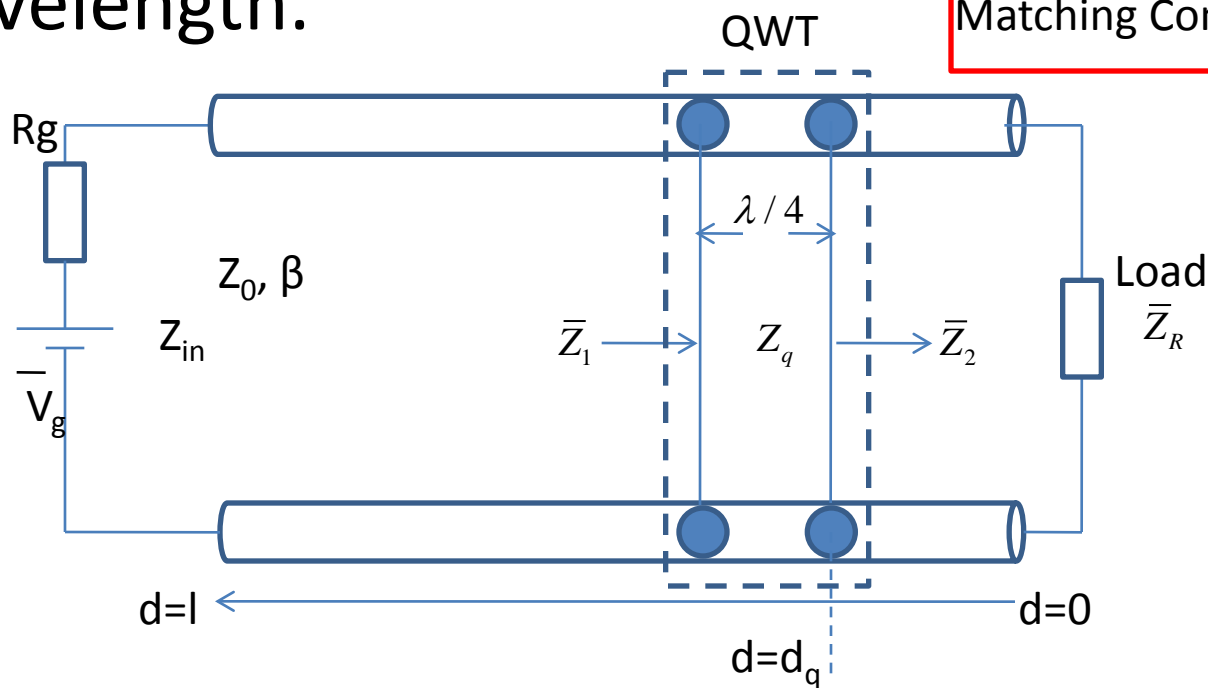

Design Parameters : 1. QWT impedance Z_q ; 2. QWT distance from the load, d_q

Quarter-wave Transformer

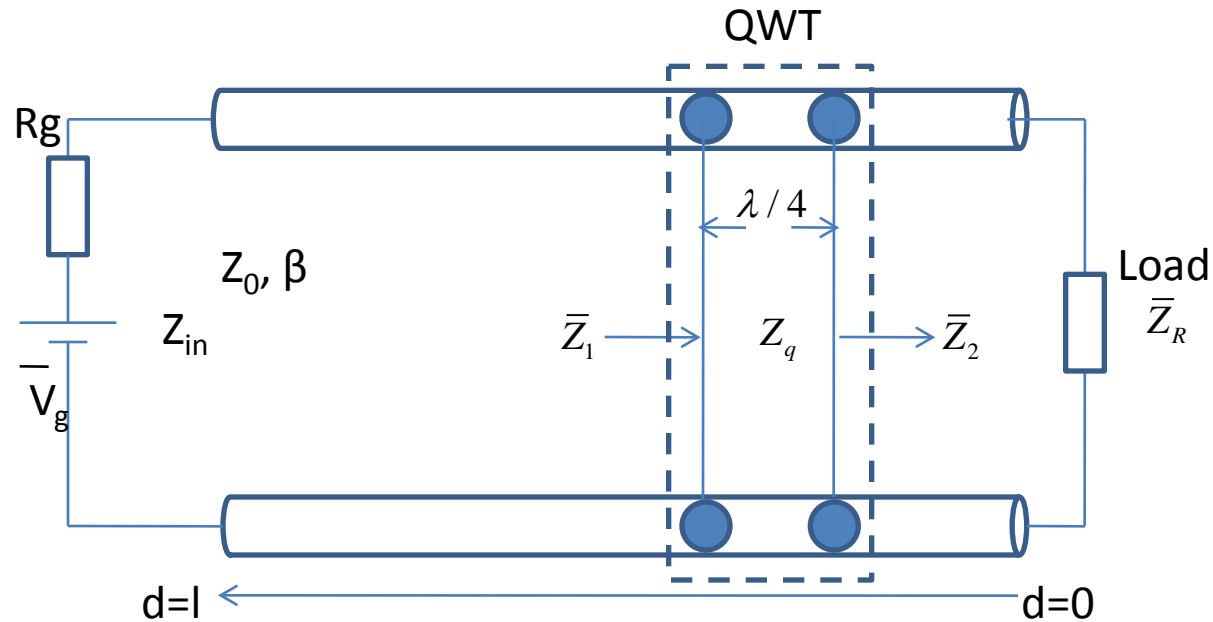

$$\bar{Z}_1 = \bar{Z}(d_q + \lambda / 4)$$

$$\bar{Z}_2 = \bar{Z}(d_q)$$


Property of quarter wave transformer

$$\bar{Z}_1 \bar{Z}_2 = Z_q^2 \quad [\text{Pg.460, Eqn. 7.33}]$$

Loss-less Transmission Line

$$\bar{Z}_2 = Z_q^2 / \bar{Z}_1 = Z_q^2 / Z_0 \quad (\text{A Real Value})$$

Quarter-wave Transformer

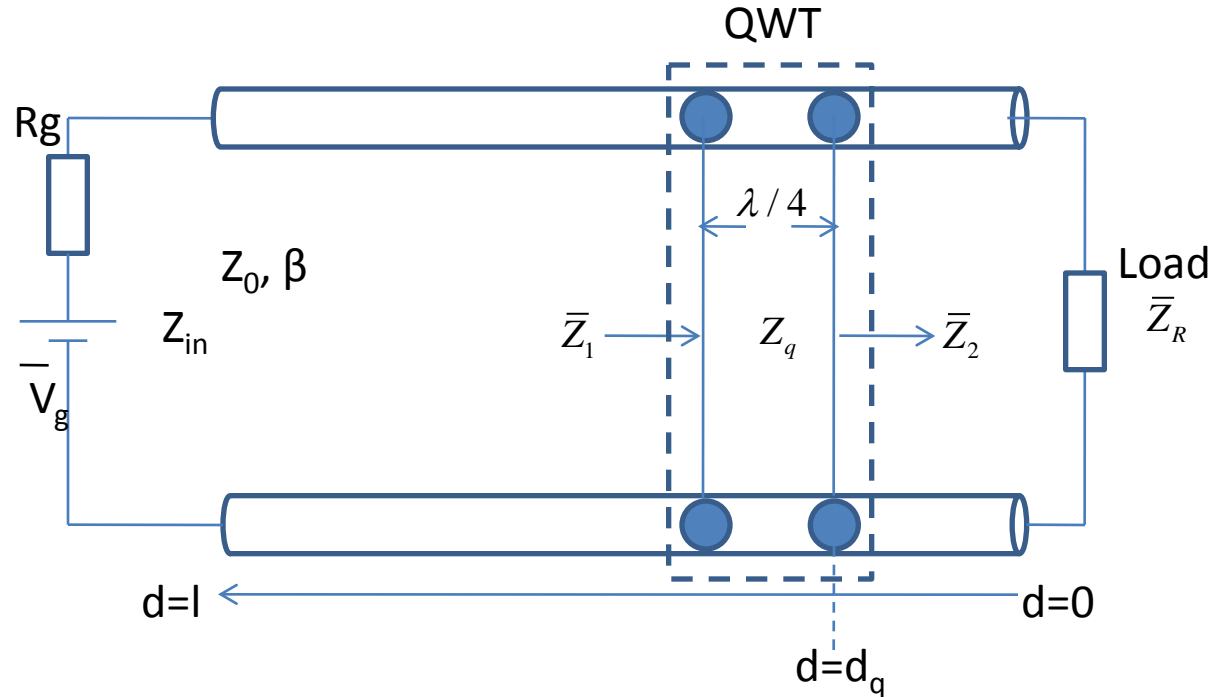

[Pg.452, Eqn. 7.25]

For Z_2 to be real

$$|\bar{Z}_2| = |Z(d_q)| = |V(d_q)| / |I(d_q)|$$


$$|V(d_q)| = |V^+| |1 + \Gamma_R e^{-j2\beta d_q}|$$

$$|I(d_q)| = \frac{|V^+|}{Z_0} |1 + \Gamma_R e^{-j2\beta d_q}|$$

$$d_q^{(1)} = \frac{(2n+1)\lambda}{4\pi} (\theta + \pi), n = 0, 1, 2, 3, \dots$$

$$d_q^{(2)} = \frac{(2n+1)\lambda}{4\pi} (\theta + \pi \pm \pi), n = 0, 1, 2, 3, \dots$$

Quarter-wave Transformer

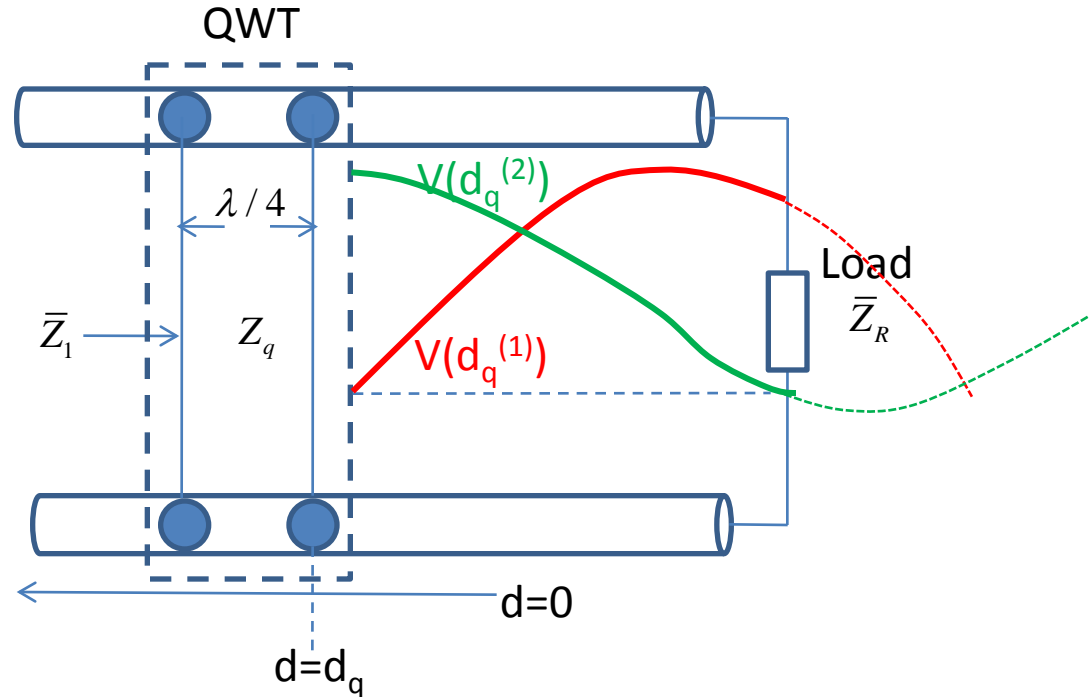

d_q should be the minimally possible value, why?

Hint: Is there standing wave pattern between QWT and the load ?

$$d_q^{(1)} = \frac{\lambda}{4\pi} (\theta + \pi)$$


$$d_q^{(2)} = \frac{\lambda}{4\pi} (\theta + \pi \pm \pi)$$



$$|V(d_q^{(1)})| = |V^+| |1 - \Gamma_R| = |V(d_q)|_{\min}$$

$$|V(d_q^{(2)})| = |V^+| |1 + \Gamma_R| = |V(d_q)|_{\max}$$

Quarter-wave Transformer

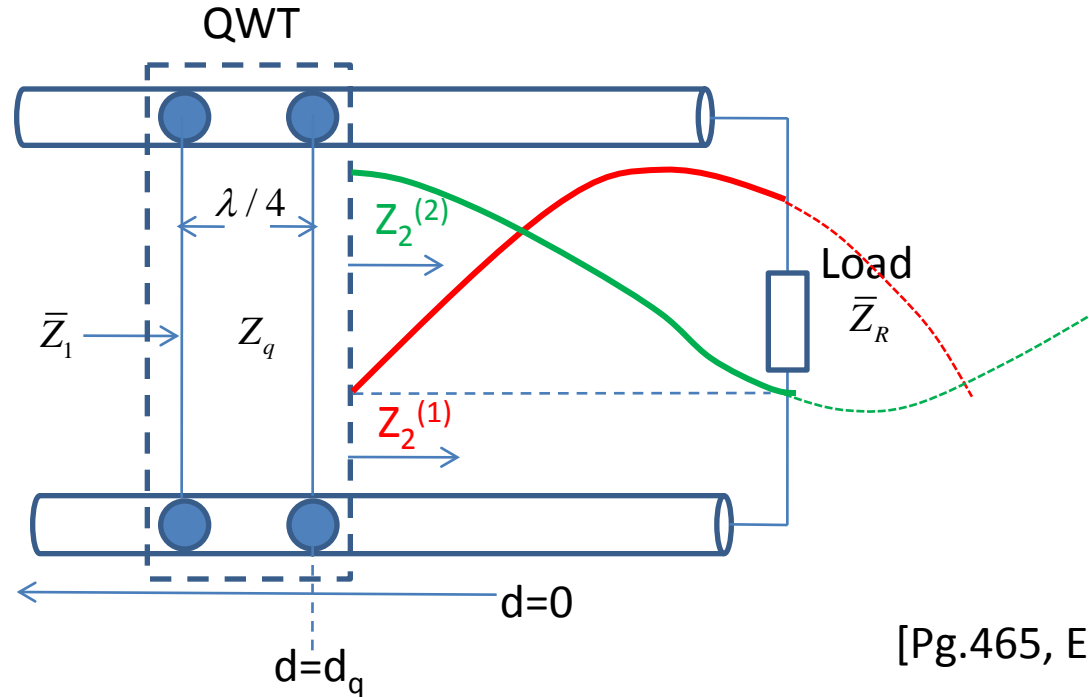

[Pg.465, Eqn. 7.42, 7.44]

$$d_q^{(1)} = \frac{\lambda}{4\pi} (\theta + \pi)$$

$$d_q^{(2)} = \frac{\lambda}{4\pi} (\theta + \pi \pm \pi)$$

$$\bar{Z}_2^{(1)} = Z_0 \frac{1 - |\Gamma_R|}{1 + |\Gamma_R|}$$

$$\bar{Z}_2^{(2)} = Z_0 \frac{1 + |\Gamma_R|}{1 - |\Gamma_R|}$$

$$\therefore \bar{Z}_1 = Z_0$$

$$\therefore \bar{Z}_1 \bar{Z}_2 = Z_q^2$$

$$Z_q^{(1)} = Z_0 \sqrt{\frac{1 - |\Gamma_R|}{1 + |\Gamma_R|}}$$

$$Z_q^{(2)} = Z_0 \sqrt{\frac{1 + |\Gamma_R|}{1 - |\Gamma_R|}}$$

QWT Design Finished ! Z_q is purely resistive

Matching Technique II

- Single-Stub Matching --- Parallel shorted-circuit line (purely reactive)

