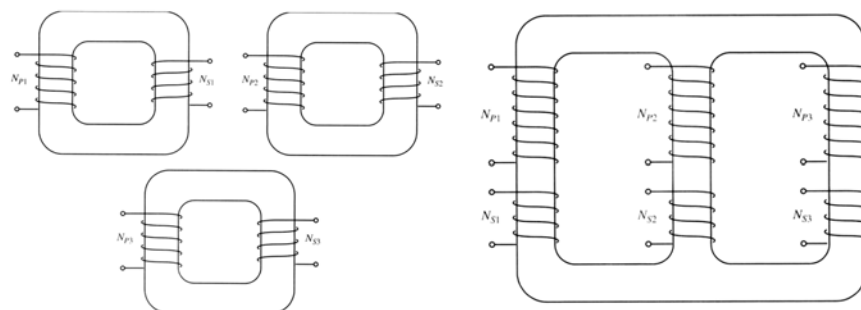


IV. Three-Phase Transformers

Three-Phase Transformers

The majority of the power generation/distribution systems in the world are 3-phase systems. The transformers for such circuits can be constructed either as a **3-phase bank of independent identical transformers** (can be replaced independently) or as a single transformer wound on a **single 3-legged core** (lighter, smaller, cheaper and slightly more efficient).




We assume that any single transformer in a 3-phase transformer (bank) behaves exactly as a single-phase transformer. The impedance, voltage regulation, efficiency, and other calculations for 3-phase transformers are done on a per-phase basis, using the techniques studied previously for single-phase transformers.

Four possible connections for a 3-phase transformer bank are:

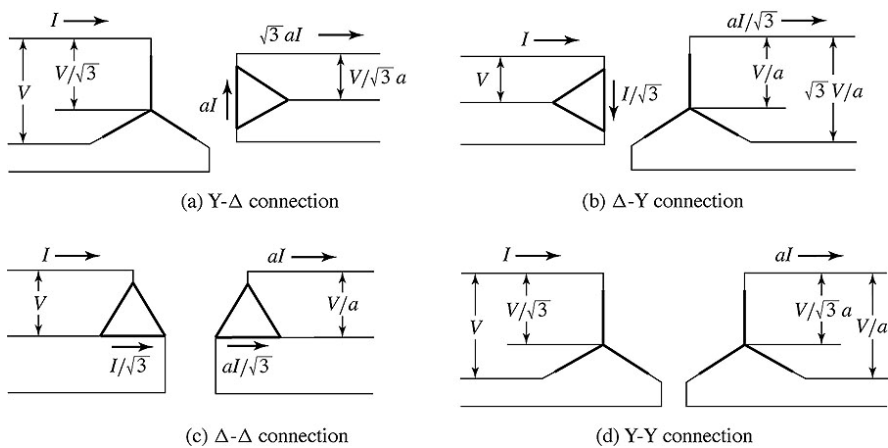- 1) Y-Y
- 2) Y- Δ
- 3) Δ - Δ
- 4) Δ -Y

Common three-phase transformer connections. The transformer windings are indicated by the heavy lines.



1) Y-Y connection

The primary voltage on each phase of the transformer is:


$$V_{\phi P} = \frac{V_{LP}}{\sqrt{3}}$$

The secondary phase voltage is:

$$V_{LS} = \sqrt{3}V_{\phi S}$$

The overall voltage ratio is:
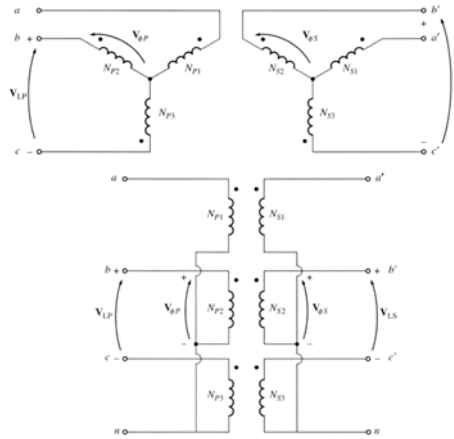
$$\frac{V_{LP}}{V_{LS}} = \frac{\sqrt{3}V_{\phi P}}{\sqrt{3}V_{\phi S}} = a$$



The Y-Y connection is seldom used as it has two very serious problems:

- a) If loads on one of the transformer circuits are unbalanced, the voltages on the phases of the transformer **can** become **severely unbalanced**.
- b) The **third harmonic** issue. The voltages in any phase of an Y-Y transformer are 120° apart from the voltages in any other phase. However, the third-harmonic components of each phase will be in phase with each other. **Nonlinearities in the transformer core always lead to generation of third harmonic!** These components will add up resulting in large (can be even larger than the fundamental component) third harmonic component.

Both problems can be solved by one of two techniques:

- i) **Solidly ground the neutral** of the transformers (especially, the primary side). The third harmonic will flow in the neutral and a return path will be established for the unbalanced loads.
- ii) **Add a third Δ-connected winding**. A circulating current at the third harmonic will flow through it suppressing the third harmonic in other windings.

2) Y-Δ connection

The primary voltage on each phase of the transformer is:


$$V_{\phi P} = \frac{V_{LP}}{\sqrt{3}}$$

The secondary phase voltage is:

$$V_{LS} = V_{\phi S}$$

The overall voltage ratio is:
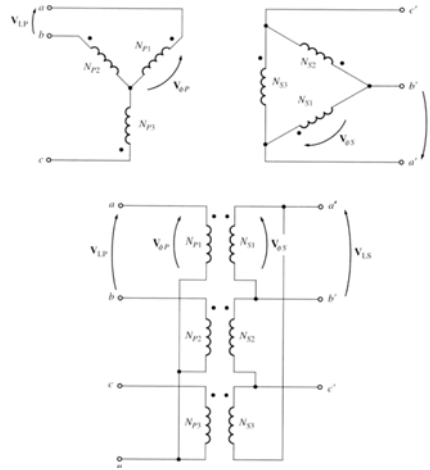
$$\frac{V_{LP}}{V_{LS}} = \frac{\sqrt{3}V_{\phi P}}{V_{\phi S}} = \sqrt{3}a$$



The Y-Δ connection has no problem with third harmonic components, since they are consumed in a circulating current on the Δ side. It is also more stable to unbalanced loads since the Δ partially redistributes any imbalance that occurs.

One problem associated with this connection is that the **secondary voltage is shifted by 30°** with respect to the primary voltage. This can cause problems when paralleling 3-phase transformers since transformers secondary voltages must be in-phase to be paralleled. Therefore, we must pay attention to these shifts.


In the U.S., it is common (actually it is a standard now) to make the secondary voltage to lag the primary voltage. The connection shown in the previous slide will do it.

The Y-Δ connection is generally used in **stepping down** from a high voltage to a medium or low voltage. One reason is that a neutral is thereby provided for grounding on the high-voltage side, a procedure which can be shown to be desirable in many cases.

3) Δ -Y connection


The primary voltage on each phase of the transformer is:

$$V_{\phi P} = V_{LP}$$

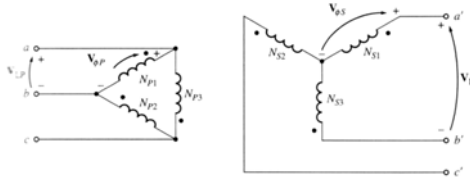

The secondary phase voltage is:

$$V_{LS} = \sqrt{3}V_{\phi S}$$

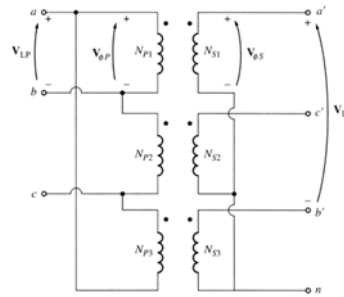

The overall voltage ratio is:

$$\frac{V_{LP}}{V_{LS}} = \frac{V_{\phi P}}{\sqrt{3}V_{\phi S}} = \frac{a}{\sqrt{3}}$$


The Δ -Y connection has the same advantages and the same phase shift as the Y- Δ connection.

The Δ -Y connection is commonly used for **stepping up** to a high voltage.

4) Δ - Δ connection


The primary voltage on each phase of the transformer is:

$$V_{\phi P} = V_{LP}$$

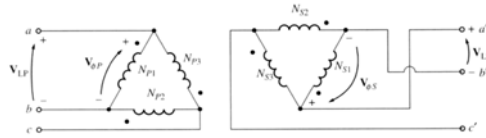

The secondary phase voltage is:

$$V_{LS} = V_{\phi S}$$

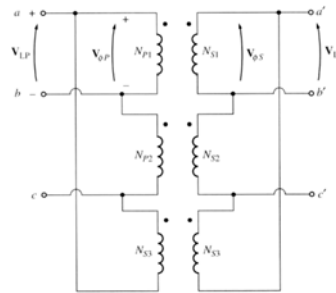

The overall voltage ratio is:

$$\frac{V_{LP}}{V_{LS}} = \frac{V_{\phi P}}{V_{\phi S}} = a$$

The Δ - Δ connection has no phase shift and no problems with unbalanced loads or harmonics.

The Δ - Δ connection has the advantage that one transformer can be removed for repair or maintenance while the remaining two continue to function as a three-phase bank with the rating reduced to 58% of that of the original bank; this is known as the *open-delta*, or *V*, connection.

Analyzing Three-Phase Transformer Circuits

1. For fixed line-to-line voltages and total fixed kVA rating of the 3-phase transformer, the kVA rating of each transformer is $1/3^{\text{rd}}$ of total kVA rating of bank regardless of the connection type.
2. Voltage and current values of individual transformers depend on connection type (\mathbf{Y} or $\mathbf{\Delta}$)
3. Circuit computations involving 3-phase transformer banks can be made by dealing with only one phase and recognizing that conditions are the same for other 3 phases except a 120° phase displacement
4. Computations are carried out on a per-phase \mathbf{Y} line-to-neutral basis, since the transformer impedances in a \mathbf{Y} -connected can be added directly in series with transmission line impedance
5. The impedances of transmission lines can be referred from one side to other by the use of square of ideal line-to-line voltage ratio of the bank.
6. In dealing with $\mathbf{Y}\text{-}\mathbf{\Delta}$ or $\mathbf{\Delta}\text{-}\mathbf{Y}$ banks, all quantities should be referred to \mathbf{Y} -connected side for simplicity
7. In dealing with $\mathbf{\Delta}\text{-}\mathbf{\Delta}$ banks in series with transmission lines, it is convenient to replace $\mathbf{\Delta}$ -connected transformer impedance into \mathbf{Y} -connected ones.

Per-Unit System for Three-Phase Transformers

The per-unit system applies to the 3-phase transformers as well as to single-phase transformers.

If the total base VA value of the transformer bank is S_{base} , the base VA value of one of the transformers will be

$$S_{1\phi, \text{base}} = \frac{S_{\text{base}}}{3}$$

Therefore, the base phase current and impedance of the transformer are

$$I_{\phi, \text{base}} = \frac{S_{1\phi, \text{base}}}{V_{\phi, \text{base}}} = \frac{S_{\text{base}}}{3V_{\phi, \text{base}}}$$

$$Z_{\text{base}} = \frac{(V_{\phi, \text{base}})^2}{S_{1\phi, \text{base}}} = \frac{3(V_{\phi, \text{base}})^2}{S_{\text{base}}}$$

The line quantities on 3-phase transformer banks can also be represented in per-unit system.

$$\text{If the windings are in } \Delta: V_{L,base} = V_{\phi,base}$$

$$\text{If the windings are in Y: } V_{L,base} = \sqrt{3}V_{\phi,base}$$

And the base line current in a 3-phase transformer bank is:

$$I_{L,base} = \frac{S_{base}}{\sqrt{3}V_{L,base}}$$

The application of the per-unit system to 3-phase transformer problems is similar to its application in single-phase situations.

The voltage regulation of the transformer bank is the same.

Ex 1. A 50 kVA, 13800/208V Δ -Y transformer has a resistance of 1% and a reactance of 7% per unit.

- What is the transformer's phase impedance referred to the high voltage side?
- What is the transformer's voltage regulation at full load and 0.8 pf lagging, using the calculated high-side impedance?
- What is the transformer's voltage regulation under the same conditions, using the per-unit system?

- The high-voltage side of the transformer has the base voltage 13 800 V and a base apparent power of 50 kVA. Since the primary side is Δ -connected, its phase voltage and the line voltage are the same.

The base impedance is:

$$Z_{base} = \frac{3(V_{\phi,base})^2}{S_{base}} = \frac{3(13\,800)^2}{50\,000} = 11\,426 \, \Omega$$

The per-unit impedance of the transformer is: $Z_{eq,pu} = 0.01 + j0.07 pu$

Therefore, the high-side impedance in ohms is:

$$Z_{eq} = Z_{eq,pu} Z_{base} = (0.01 + j0.07) \cdot 11426 = 114 + j800 \Omega$$

b) The voltage regulation of a 3-phase transformer equals to a voltage regulation of a single transformer:

$$VR = \frac{V_{\phi P} - aV_{\phi S}}{aV_{\phi S}} \cdot 100\%$$

The rated phase current on the primary side can be found as:

$$I_{\phi} = \frac{S}{3V_{\phi}} = \frac{50000}{3 \cdot 13800} = 1.208 A$$

The rated phase voltage on the secondary of the transformer is

$$V_{\phi S} = \frac{208}{\sqrt{3}} = 120 V$$

When referred to the primary (high-voltage) side, this voltage becomes

$$V_{\phi S}' = aV_{\phi S} = 13800 V$$

Assuming that the transformer secondary winding is working at the rated voltage and current, the resulting primary phase voltage is

$$\begin{aligned} V_{\phi P} &= aV_{\phi S} + R_{eq}I_{\phi} + jX_{eq}I_{\phi} = 13800\angle 0^{\circ} + 114.2 \cdot 1.208\angle \cos^{-1}(-0.8) + j \cdot 800 \cdot 1.208\angle \cos^{-1}(-0.8) \\ &= 14490 + j690.3 = 14506\angle 2.73^{\circ} V \end{aligned}$$

The voltage regulation, therefore, is

$$VR = \frac{|V_{\phi P}| - aV_{\phi S}}{aV_{\phi S}} \cdot 100\% = \frac{14506 - 13800}{13800} \cdot 100\% = 5.1\%$$

c) In the per-unit system, the output voltage is $1\angle 0^\circ$, and the current is $1\angle \cos^{-1}(-0.8)$. Therefore, the input voltage is

$$V_{\phi P} = 1\angle 0^\circ + 0.01 \cdot 1\angle \cos^{-1}(0.8) + j0.07 \cdot 1\angle \cos^{-1}(0.8) = 1.051\angle 2.73^\circ$$

Thus, the voltage regulation in per-unit system will be

$$VR = \frac{1.051 - 1.0}{1.0} \cdot 100\% = 5.1\%$$

The voltage regulation in per-unit system is the same as computed in volts...

Ex 2. Three 2400:240V single-phase transformers connected in Δ - Δ and supplied with power through a 3-phase feeder (i.e. cable) connected at high-voltage side whose reactance is $j0.8 \Omega/\text{phase}$. The equivalent reactance of each transformer referred to high-voltage side is $j1.82 \Omega/\text{phase}$. Other circuit resistances are negligible. At its sending end (i.e. primary-side), the feeder is connected to the secondary terminals of a Y - Δ connected 3-phase transformer whose rating is 500kVA 24000:2400V. The equivalent reactance of sending end transformer is $j2.76\Omega/\text{phase}$ referred to 2400V side. The voltage applied to primary of the sending end transformer is 24kV. A 3-phase short-circuit occurs at 240V terminals of the receiving end transformer (i.e. load side). Compute the steady-state short-circuit current in the feeder wires, primary of receiving end and actual value of the short circuit current.

