

## Mesh and Nodal Analysis

Here, two very powerful analysis methods will be introduced for analysing any circuit:


1. Node analysis (Node-voltage method)
2. Mesh analysis (Mesh-current method)

These methods are based on the systematic application of Kirchhoff's laws (KVL and KCL).

### Nodal Analysis


- Six steps:
  1. Chose one node as the reference node
  2. Label remaining nodes  $V_1, V_2,$  etc.
  3. Label any known voltages
  4. Apply Kirchhoff's current law to each unknown node
  5. Solve simultaneous equations to determine voltages
  6. If necessary calculate required currents

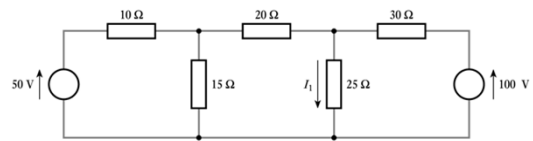**Example:** Determine the current  $I_1$  in the following circuit


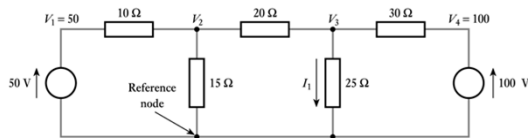
### Solution:

– first we pick a reference node and label the various node voltages, assigning values where these are known



– next we sum the currents flowing into the nodes for which the node voltages are unknown. This gives

$$\frac{50 - V_2}{10} + \frac{V_3 - V_2}{20} + \frac{0 - V_2}{15} = 0 \quad \frac{V_2 - V_3}{20} + \frac{100 - V_3}{30} + \frac{0 - V_3}{25} = 0$$

### Solution: (continued)


– solving these two equations gives

$$\begin{aligned} V_2 &= 32.34 \text{ V} \\ V_3 &= 40.14 \text{ V} \end{aligned}$$


– and the required current is given by

$$I_1 = \frac{V_3}{25 \Omega} = \frac{40.14 \text{ V}}{25 \Omega} = 1.6 \text{ A}$$

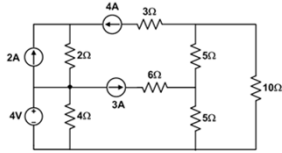**Example:** Using nodal analysis, determine the power delivered to the 10Ω resistor.



**Solution:**

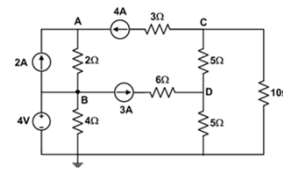

It is sufficient to write KCL equations for Node C and Node D.


$$I_{CA} + I_{CD} + I_{C,GND} = 0$$

$$I_{DB} + I_{DC} + I_{D,GND} = 0$$

Thus

$$4A + \frac{V_C - V_D}{5} + \frac{V_C - 0}{10} = 0$$
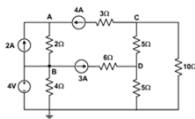
$$-3A + \frac{V_D - V_C}{5} + \frac{V_D - 0}{5} = 0$$



Let us rearrange the equations by eliminating the denominators

$$40 + 3V_C - 2V_D = 0$$

$$-15 + 2V_D - V_C = 0$$

After solving these two equations simultaneously for  $V_C$ , we find  $V_C$  as

$$V_C = -12.5 \text{ V.}$$

Thus, the power delivered to the 10Ω resistor is given by

$$P_{10\Omega} = \frac{V_C^2}{10\Omega}$$


$$= \frac{(-12.5)^2}{10}$$

$$= 15.625 \text{ W.}$$

### Mesh Analysis


- Four steps:
  1. Identify the meshes and assign a clockwise-flowing current to each. Label these  $I_1, I_2$ , etc.
  2. Apply Kirchhoff's voltage law to each mesh
  3. Solve the simultaneous equations to determine the currents  $I_1, I_2$ , etc.
  4. Use these values to obtain voltages if required

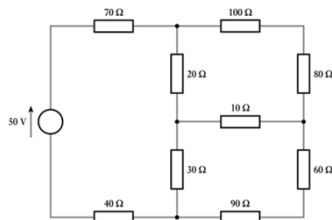**Example:** Determine the voltage across the 10 Ω resistor



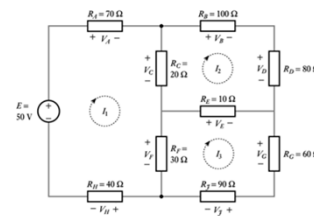**Solution:**

– first assign mesh currents and label voltages



– next apply Kirchhoff's law to each loop. This gives

$$E - V_A - V_C - V_F - V_H = 0$$

$$V_C - V_B - V_D + V_E = 0$$

$$V_F - V_E - V_G - V_J = 0$$

**Solution:** (continued)

– which gives the following set of simultaneous equations

$$\begin{aligned} 50 - 70I_1 - 20(I_1 - I_2) - 30(I_1 - I_3) - 40I_1 &= 0 \\ 20(I_1 - I_2) - 100I_2 - 80I_2 + 10(I_3 - I_2) &= 0 \\ 30(I_1 - I_3) - 10(I_3 - I_2) - 60I_3 - 90I_3 &= 0 \end{aligned}$$

– these can be rearranged to give

$$\begin{aligned} 50 - 160I_1 + 20I_2 + 30I_3 &= 0 \\ 20I_1 - 210I_2 + 10I_3 &= 0 \\ 30I_1 + 10I_2 - 190I_3 &= 0 \end{aligned}$$

– which can be solved to give

$$\begin{aligned} I_1 &= 326 \text{ mA} \\ I_2 &= 34 \text{ mA} \\ I_3 &= 53 \text{ mA} \end{aligned}$$

**Solution:** (continued)

– the voltage across the 10 Ω resistor is therefore given by

$$\begin{aligned} V_E &= R_E(I_3 - I_2) \\ &= 10(0.053 - 0.034) \\ &= 0.19 \text{ V} \end{aligned}$$

– since the calculated voltage is positive, the polarity is as shown on the figure with the left hand end of the resistor more positive than the right hand end

**Solving Simultaneous Circuit Equations**

• Both nodal analysis and mesh analysis produce a series of **simultaneous equations**

– can be solved ‘by hand’ or by using matrix methods  
– e.g.

$$\begin{aligned} 50 - 160I_1 + 20I_2 + 30I_3 &= 0 \\ 20I_1 - 210I_2 + 10I_3 &= 0 \\ 30I_1 + 10I_2 - 190I_3 &= 0 \end{aligned}$$

– can be rearranged as

$$\begin{aligned} 160I_1 - 20I_2 - 30I_3 &= 50 \\ 20I_1 - 210I_2 + 10I_3 &= 0 \\ 30I_1 + 10I_2 - 190I_3 &= 0 \end{aligned}$$

**Solving Simultaneous Circuit Equations**

– these equations can be expressed as


$$\begin{bmatrix} 160 & -20 & -30 \\ 20 & -210 & 10 \\ 30 & 10 & -190 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 50 \\ 0 \\ 0 \end{bmatrix}$$

– which can be solved by hand (e.g. **Cramer’s rule**)


– or can use automated tools

- e.g. scientific calculators
- computer-based packages such as **MATLAB** or **Mathcad**

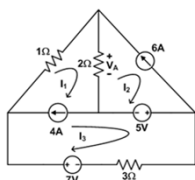**Example:** Using **mesh analysis**, determine the mesh currents  $I_1$ ,  $I_2$  and  $I_3$  and then find the voltage  $V_A$ .



**Solution:**

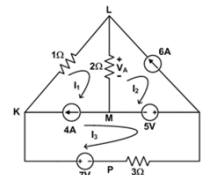

We have three unknowns  $I_1$ ,  $I_2$  and  $I_3$ , so we need three equations.

From the figure, the second mesh current  $I_2$  is given by


$$I_2 = -6 \text{ A.}$$

Also, from the circuit

$$I_1 - I_3 = 4 \text{ A.} \quad (\text{Hence, } I_3 = I_1 - 4)$$

Let us write the third equation as a KVL equation for a loop containing only resistors and voltage sources (i.e., around the Loop KLMNPK),
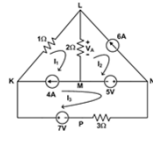
$$\begin{aligned} V_{KP} + V_{LK} + V_{ML} + V_{NM} + V_{PN} &= 0 \\ 7 - 1(I_1) - 2(I_1 - I_2) + 5 - 3(I_3) &= 0 \end{aligned}$$



Then simplify this equation to find  $I_1$

$$\begin{aligned} 7 - I_1 - 2(I_1 + 6) + 5 - 3(I_1 - 4) &= 0 \\ 12 - 6I_1 &= 0 \\ I_1 &= 2 \text{ A} \end{aligned}$$

Consequently,

$$I_3 = I_1 - 4 = 2 - 4 = -2 \text{ A}.$$

Finally, the voltage  $V_A$  is given by

$$V_A = (I_1 - I_2) 2\Omega = (2 + 6) 2 = 16 \text{ V}.$$

### Choice of Techniques

- How do we choose the right technique?
  - nodal and mesh analysis will work in a wide range of situations but are not necessarily the simplest methods
  - no simple rules
  - often involves looking at the circuit and seeing which technique seems appropriate