

## Contents

### BJT Small-Signal Analysis

#### Purpose of SSAC Analysis

##### BJT SSAC Analysis Steps

#### BJT Small-Signal Models

##### Hybrid Equivalent Model

#### Common-Emitter Fixed-Bias Configuration

##### Input Resistance

##### Voltage Gain

##### Output Resistance

##### Phase Relationship

#### Common-Emitter Voltage-Divider Bias Configuration

##### Input Resistance

##### Voltage Gain

##### Output Resistance

##### Phase Relationship

#### Common-Emitter Unbypassed-Emitter Bias Configuration

##### Input Resistance

##### Voltage Gain

##### Output Resistance

##### Phase Relationship

#### Emitter-Follower Configuration

##### Input Resistance

##### Voltage Gain

##### Output Resistance

##### Phase Relationship

#### Common-Emitter Collector Feedback Configuration

##### Input Resistance

##### Voltage Gain

##### Output Resistance

##### Phase Relationship

#### Common-Base Configuration

##### Input Resistance


##### Voltage Gain

##### Output Resistance

##### Phase Relationship
 
## Purpose of SSAC Analysis


The purpose of small-signal AC (SSAC) analysis is to determine the **three** parameters of an amplifier **input resistance**, **output resistance** and **gain**. In this course, we are mostly interested in the two-port voltage-gain amplifier model shown below.



- Input resistance  $R_i$  is defined by the no-load input voltage of the amplifier divided by the no-load input current to the amplifier, i.e.,

$$R_i = \left. \frac{v_i}{i_i} \right|_{R_L = \infty}$$

 NOTE: Input resistance **cannot** include the source resistance  $R_s$ .




- Output resistance  $R_o$  is obtained by the test-voltage method, i.e., by dividing the test voltage value with the measured test current value. In the test-voltage method, load is replaced with a test voltage  $v_{\text{test}}$  and the independent power sources ( $v_s$  or  $i_s$ ) are killed, i.e.,  $v_s = 0$  or  $i_s = 0$ . Thus, output resistance  $R_o$  is given by

$$R_o = \frac{v_{\text{test}}}{i_{\text{test}}} \Big|_{v_s=0, R_L=v_{\text{test}}}$$

NOTE: Output resistance **cannot** include the load resistance  $R_L$ .

- No-load voltage gain  $A_v$  (or  $A_{V_{NL}}$ ) is defined by

$$A_v = \frac{v_o}{v_i} \Big|_{R_L=\infty}$$

 

- When load is connected, the voltage gain will decrease due to the voltage-divider consisting of  $R_L$  and  $R_o$ . So, voltage gain with load,  $A_V$ , is given by

$$A_V = \frac{v_o}{v_i} = \left( \frac{v_o}{A_v v_i} \right) \left( \frac{A_v v_i}{v_i} \right) = \frac{R_L}{R_o + R_L} A_v$$

- Current gain  $A_i$  is defined by the output current versus the input current, i.e.,

$$A_i = \frac{i_o}{i_i} = \frac{v_o/R_L}{v_i/R_i} = \frac{R_i}{R_L} A_V = \frac{R_i}{R_o + R_L} A_v$$

- Finally, overall voltage gain  $A_{V_s}$  is given by

$$A_{V_s} = \frac{v_o}{v_s} = \frac{R_L}{R_o + R_L} A_v \frac{R_i}{R_s + R_i}$$

## BJT SSAC Analysis Steps

1. Draw the SSAC equivalent circuit
  - a) Draw the AC equivalent circuit (signal frequency is infinity, i.e.,  $f = \infty$ )
    - i. Capacitors are short circuit, i.e.,  $X_C \rightarrow 0$ .
    - ii. Kill the DC power sources (i.e., AC value of DC sources is zero).
  - b) Replace BJT with its small-signal equivalent model (e.g., hybrid equivalent model or  $r_e$  model).
2. Calculate the three amplifier parameters:  $R_i$ ,  $R_o$  and  $A_v$ 
  - a) Calculate no-load input resistance,  $R_i = \left. \frac{v_i}{i_i} \right|_{R_L = \infty}$ .
  - b) Calculate output resistance,  $R_o$ .
  - c) Calculate no-load voltage gain,  $A_v = \left. \frac{v_o}{v_i} \right|_{R_L = \infty}$ .

## BJT Small-Signal Models

A small-signal model is an equivalent circuit that represents the SSAC characteristics of the transistor. It uses circuit elements that approximate the behavior of the transistor.

Two commonly used models used in SSAC analysis of BJTs are given below:


- hybrid equivalent model
- $r_e$  model

Mostly, we are going to use the **hybrid equivalent model**. But, we are going to introduce and provide results for the  $r_e$  model as well.

**NOTE:** Small-signal equivalent model and its analysis are the same for both *npn* and *pnp* transistors.
 
# Hybrid Equivalent Model


Parameters of the hybrid equivalent circuit provide the entire set on the specification sheet of a BJT and cover all operating conditions. Generalized hybrid equivalent circuit for any transistor configuration is provided below.



Here,

- $h_i$ : input resistance
- $h_r$ : reverse transfer voltage ratio ( $v_i/v_o$ )
- $h_f$ : forward transfer current ratio ( $i_o/i_i$ )
- $h_o$ : output conductance

 
For a specific configuration, the model parameters modified with the label of the common-mode terminal in their subscript. So, common-emitter and common-base configurations and their hybrid equivalent models are shown below, respectively.




- For the common-collector configuration, we always use the common-emitter hybrid equivalent model.
 
## Simplified Hybrid Equivalent Model


Because  $h_r$  is normally a relatively small quantity, its removal is approximated by  $h_r \approx 0$  and  $h_r v_o = 0$ , resulting in the simplified hybrid equivalent circuit shown below. In this course, we are going to use the **simplified hybrid equivalent model**.



 This circuit, can be further simplified if a value for the parameter  $h_o$  or  $1/h_o$  is not provided. In that case, we can safely assume that  $h_o = 0$  or  $1/h_o = \infty$  resulting in the approximate hybrid equivalent circuit shown below.


 
## Common-Emitter Hybrid Equivalent Model




Here, the  $h$ -parameters are defined as below

$$h_{ie} = \left. \frac{\partial V_{BE}}{\partial I_B} \right|_{Q\text{-point}} = \frac{\gamma}{I_{BQ}} \quad \dots \text{see diode dynamic resistance section}$$

$$h_{fe} = \left. \frac{\partial I_C}{\partial I_B} \right|_{Q\text{-point}} = \beta_{ac}$$

$$1/h_{oe} = \left. \frac{\partial V_{CE}}{\partial I_C} \right|_{Q\text{-point}} = \frac{V_A + V_{CEQ}}{I_{CQ}} \quad \dots V_A \text{ is the early voltage and } V_A \gg V_{CEQ}$$

 Typical values of  $h_{fe}$  run from 50 to 200,  $h_{ie}$  run from  $500\ \Omega$  to  $7\ \text{k}\Omega$ , and  $1/h_{oe}$  run from  $40\ \text{k}\Omega$  to  $100\ \text{k}\Omega$ .




Note that, as  $I_{CQ} = \beta I_{BQ}$  and  $I_{EQ} = (\beta + 1) I_{BQ}$ , we can also express  $h_{ie}$  in terms of  $I_{CQ}$  or  $I_{EQ}$  as follows

$$\begin{aligned} h_{ie} &= \frac{\gamma}{I_{BQ}} \\ &= h_{fe} \frac{\gamma}{I_{CQ}} \\ &= (h_{fe} + 1) \frac{\gamma}{I_{EQ}} \end{aligned}$$

where  $\gamma = kT/q$  is the thermal voltage and have fixed values for a given temperature, e.g.,  $\gamma = 26 \text{ mV}$  at room temperature  $T = 300 \text{ K}$ .

## Common-Emitter $r_e$ Equivalent Model

 


One-to-one correspondence with the  $h$ -parameters are given below,

$$\begin{aligned} h_{fe} &= \beta \\ h_{ie} &= (\beta + 1) r_e \cong \beta r_e \\ 1/h_{oe} &= r_o. \end{aligned}$$

Thus,  $\beta = h_{fe}$ ,  $\beta r_e = h_{ie}$  and  $r_o = 1/h_{oe}$ .

# Common-Base Hybrid Equivalent Model

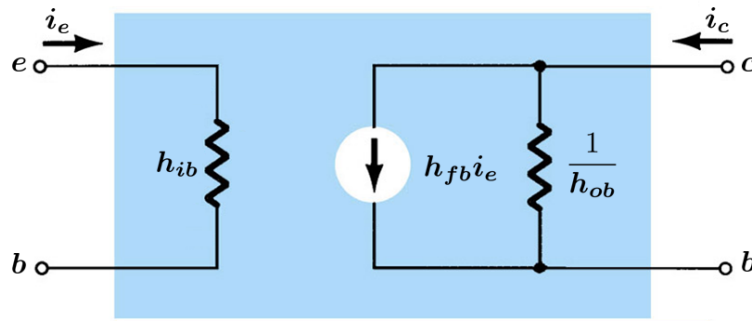


Here, the  $h$ -parameters are defined as below,

$$h_{ib} = \left. \frac{\partial V_{BE}}{\partial I_E} \right|_{Q\text{-point}} = \frac{\gamma}{I_{EQ}} \quad \dots \text{see diode dynamic resistance section}$$

$$h_{fb} = - \left. \frac{\partial I_C}{\partial I_E} \right|_{Q\text{-point}} = -\alpha_{ac} \cong -1$$

$$1/h_{ob} = \left. \frac{\partial V_{CB}}{\partial I_C} \right|_{Q\text{-point}} \approx \infty$$

 Typically,  $h_{fb} = -1$ , and  $h_{ib}$  run from  $5\Omega$  to  $50\Omega$ , and  $1/h_{ob}$  is in the megohm range. Thus,  $1/h_{ob} \gg 1/h_{oe}$ .




Note that, the relationship between  $h_{ib}$  and  $h_{ie}$  is given below

$$h_{ie} = (h_{fe} + 1) h_{ib}$$

$$\text{or } h_{ib} = \frac{h_{ie}}{h_{fe} + 1}$$

## Common-Base $r_e$ Equivalent Model

 

One-to-one correspondence with the  $h$ -parameters are given below

$$\begin{aligned} h_{fb} &= -\alpha \\ h_{ib} &= r_e \\ 1/h_{ob} &= r_o. \end{aligned}$$

Thus,  $\alpha = -h_{fb} \cong 1$ ,  $r_e = h_{ib}$  and  $r_o = 1/h_{ob} \cong \infty$ . Note that, minus sign is due to the direction of the current source.

## Phase Relationship


The phase relationship between input and output depends on the amplifier configuration circuit as listed below.

- Common-Emitter: 180 degrees
- Common-Base: 0 degrees
- Common-Collector: 0 degrees (Emitter-Follower)




 
# Common-Emitter Fixed-Bias Configuration


Common-emitter fixed-bias configuration is given below



  Let us start SSAC analysis by drawing the AC equivalent circuit as shown below



 
Then, we are going to replace BJT with its common-emitter hybrid equivalent model as shown below



- Obtain  $h_{fe}$  and  $1/h_{oe}$  from the specification sheet of the transistor or by testing the transistor using a curve tracer. Calculate  $h_{ie}$  using the DC analysis values as

$$h_{ie} = \frac{26 \text{ mV}}{I_{BQ}} = h_{fe} \frac{26 \text{ mV}}{I_{CQ}}$$

## Input Resistance

 


Input resistance  $R_i$  is given as

$$R_i = \left. \frac{v_i}{i_i} \right|_{R_L = \infty} = R_B \parallel h_{ie}$$

- If  $R_B \geq 10h_{ie}$ , then  $R_i$  simplifies to  $R_i = h_{ie}$ .
- Input resistance  $R_i$  according to the  $r_e$  model is given by

$$R_i = R_B \parallel \beta r_e$$

## Voltage Gain

 


No-load voltage gain  $A_v$  is given by

$$\begin{aligned} A_v &= \left. \frac{v_o}{v_i} \right|_{R_L = \infty} = \left( \frac{v_o}{h_{fe}i_b} \right) \left( \frac{h_{fe}i_b}{i_b} \right) \left( \frac{i_b}{v_i} \right) \\ &= (-R_C \parallel 1/h_{oe}) (h_{fe}) \left( \frac{1}{h_{ie}} \right) \\ &= -\frac{h_{fe} (R_C \parallel 1/h_{oe})}{h_{ie}} \end{aligned}$$

- No-load voltage gain  $A_v$  according to the  $r_e$  model is given by

$$A_v = -\frac{R_C \parallel r_o}{r_e}$$

 

- If  $1/h_{oe} \geq 10R_C$ , no-load voltage gain  $A_v$  reduces to

$$A_v = -\frac{h_{fe}R_C}{h_{ie}} \quad \dots r_e \text{ model: } A_v = -\frac{R_C}{r_e}$$


- For the circuit above, we can obtain the current gain  $A_i$  as follows

$$\begin{aligned} A_i &= \frac{i_o}{i_i} = \frac{v_o/R_C}{v_i/R_i} = \frac{R_i}{R_C} \frac{v_o}{v_i} \\ &= \frac{R_i}{R_C} A_v \end{aligned}$$

- If  $1/h_{oe} \geq 10R_C$  and  $R_B \geq 10h_{ie}$ , current gain  $A_i$  reduces to

$$A_i = -h_{fe} \quad \dots r_e \text{ model: } A_i = -\beta$$

## Output Resistance

 


Output resistance, i.e., Thévenin equivalent resistance,  $R_o$  is calculated using the test voltage circuit above. Note that in the circuit  $i_b = 0$ , so  $h_{fe}i_b = 0$  as well.

$$R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}} = R_C || 1/h_{oe}$$

- If  $1/h_{oe} \geq 10R_C$ , then  $R_o$  simplifies to  $R_o = R_C$ .
- Output resistance  $R_o$  according to the  $r_e$  model is given by

$$R_o = R_C || r_o$$


# Phase Relationship

 


- The phase relationship between input and output is 180 degrees as shown above.
- The negative sign used in the voltage gain formulas indicates the inversion.
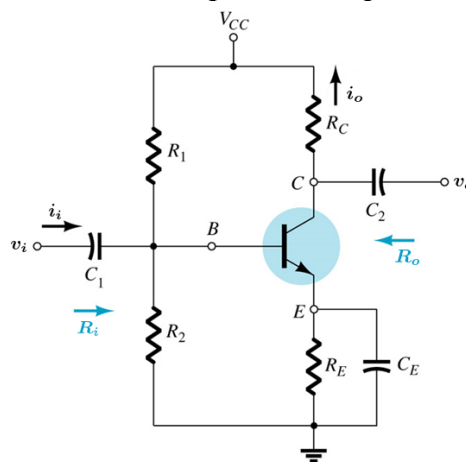
# CE Voltage-Divider Bias Configuration


Common-emitter voltage-divider bias configuration is given below



 Corresponding SSAC equivalent circuit is shown below



## Input Resistance

 


Input resistance  $R_i$  is given as

$$R_i = \left. \frac{v_i}{i_i} \right|_{R_L = \infty} = R_1 || R_2 || h_{ie}$$

- Input resistance  $R_i$  according to the  $r_e$  model is given by

$$R_i = R_1 || R_2 || \beta r_e$$

## Voltage Gain

 


No-load voltage gain  $A_v$  is given by

$$\begin{aligned} A_v &= \left. \frac{v_o}{v_i} \right|_{R_L = \infty} = \left( \frac{v_o}{h_{fe} i_b} \right) \left( \frac{h_{fe} i_b}{i_b} \right) \left( \frac{i_b}{v_i} \right) \\ &= (-R_C || 1/h_{oe}) (h_{fe}) \left( \frac{1}{h_{ie}} \right) \\ &= - \frac{h_{fe} (R_C || 1/h_{oe})}{h_{ie}} \end{aligned}$$

- No-load voltage gain  $A_v$  according to the  $r_e$  model is given by

$$A_v = - \frac{R_C || r_o}{r_e}$$

 

- If  $1/h_{oe} \geq 10R_C$ , no-load voltage gain  $A_v$  reduces to

$$A_v = -\frac{h_{fe}R_C}{h_{ie}} \quad \dots r_e \text{ model: } A_v = -\frac{R_C}{r_e}$$


- For the circuit above, we can obtain the current gain  $A_i$  as follows

$$\begin{aligned} A_i &= \frac{i_o}{i_i} = \frac{v_o/R_C}{v_i/R_i} = \frac{R_i}{R_C} \frac{v_o}{v_i} \\ &= \frac{R_i}{R_C} A_v \end{aligned}$$

- If  $1/h_{oe} \geq 10$ , and given  $R' = R_1 || R_2$ , current gain  $A_i$  reduces to

$$A_i = -h_{fe} \frac{R'}{R' + h_{ie}} \quad \dots r_e \text{ model: } A_i = -\frac{R'}{R'/\beta + r_e}$$

## Output Resistance

 

Output resistance, i.e., Thévenin equivalent resistance,  $R_o$  is calculated using the test voltage circuit above. Note that in the circuit  $i_b = 0$ , so  $h_{fe}i_b = 0$  as well.

$$R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}} = R_C || 1/h_{oe}$$

- If  $1/h_{oe} \geq 10R_C$ , then  $R_o$  simplifies to  $R_o = R_C$ .
- Output resistance  $R_o$  according to the  $r_e$  model is given by


$$R_o = R_C || r_o$$

## Phase Relationship

- Phase relationship between input and output of a common-emitter amplifier configuration is always 180 degrees. This is independent of the type of the bias-configuration.

 
## CE Unbypassed-Emitter Bias Configuration

Common-emitter unbypassed-emitter bias configuration and its SSAC equivalent circuit are given on the left and right figures below, respectively.



- When  $R_E$  is not bypassed, we normally assume  $1/h_{oe} = \infty$  in order to reduce the calculation complexity. Because of the feedback, even  $1/h_{oe} \neq \infty$  the results do not really change at all.

# Input Resistance

 

Input resistance  $R_i$  is given as


$$R_i = \left. \frac{v_i}{i_i} \right|_{R_L=\infty} = R_B \parallel R_b \quad \dots R_b = h_{ie} + (h_{fe} + 1) R_E$$

$$= R_B \parallel [h_{ie} + (h_{fe} + 1) R_E]$$

- Input resistance  $R_i$  according to the  $r_e$  model is given by

$$R_i = R_B \parallel (\beta + 1)(r_e + R_E) \cong R_B \parallel \beta(r_e + R_E)$$

# Voltage Gain

 

No-load voltage gain  $A_v$  is given by

$$A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = \left( \frac{v_o}{h_{fe}i_b} \right) \left( \frac{h_{fe}i_b}{i_b} \right) \left( \frac{i_b}{v_i} \right)$$


$$= (-R_C)(h_{fe}) \left( \frac{1}{R_b} \right)$$

$$= -\frac{h_{fe}R_C}{h_{ie} + (h_{fe} + 1) R_E}$$

- No-load voltage gain  $A_v$  according to the  $r_e$  model is given by

$$A_v = -\frac{R_C}{r_e + R_E}$$



 

- If  $(h_{fe} + 1) R_E \geq 10h_{ie}$ , no-load voltage gain  $A_v$  reduces to

$$A_v = -\frac{R_C}{R_E} \quad \dots r_e \text{ model: } A_v = -\frac{R_C}{R_E}$$


- For the circuit above, we can obtain the current gain  $A_i$  as follows

$$A_i = \frac{i_o}{i_i} = \frac{v_o/R_C}{v_i/R_i} = \frac{R_i}{R_C} \frac{v_o}{v_i} = \frac{R_i}{R_C} A_v$$

- Resultant current gain  $A_i$  is given by

$$A_i = -h_{fe} \frac{R_B}{R_B + R_b} \quad \dots r_e \text{ model: } A_i = -\frac{R_B}{R_B/\beta + r_e + R_E}$$

## Output Resistance

 

Output resistance, i.e., Thévenin equivalent resistance,  $R_o$  is calculated using the test voltage circuit above. Note that in the circuit  $i_b = 0$ , so  $h_{fe}i_b = 0$  as well.

$$R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}} = R_C$$

- Output resistance  $R_o$  according to the  $r_e$  model is given by


$$R_o = R_C$$

## Phase Relationship

- Phase relationship between input and output of a common-emitter amplifier configuration is always 180 degrees. This is independent of the type of the bias-configuration.

 
## Emitter-Follower Configuration

Emitter-follower (common-collector) configuration and its SSAC equivalent circuit are given on the left and right figures below, respectively.



- When  $R_E$  is not bypassed, we normally assume  $1/h_{oe} = \infty$  in order to reduce the calculation complexity.

# Input Resistance

 

Input resistance  $R_i$  is given as


$$R_i = \left. \frac{v_i}{i_i} \right|_{R_L = \infty} = R_B \parallel R_b \quad \dots R_b = h_{ie} + (h_{fe} + 1) R_E$$

$$= R_B \parallel [h_{ie} + (h_{fe} + 1) R_E]$$

■ Input resistance  $R_i$  according to the  $r_e$  model is given by

$$R_i = R_B \parallel (\beta + 1)(r_e + R_E) \cong R_B \parallel \beta(r_e + R_E)$$

# Voltage Gain

 

No-load voltage gain  $A_v$  is given by


$$A_v = \left. \frac{v_o}{v_i} \right|_{R_L = \infty} = \left( \frac{v_o}{i_b} \right) \left( \frac{i_b}{v_i} \right)$$

$$= [(h_{fe} + 1) R_E] \left( \frac{1}{R_b} \right) \quad \dots R_b = h_{ie} + (h_{fe} + 1) R_E$$

$$= \frac{(h_{fe} + 1) R_E}{h_{ie} + (h_{fe} + 1) R_E} \cong 1$$

■ No-load voltage gain  $A_v$  according to the  $r_e$  model is given by

$$A_v = \frac{R_E}{r_e + R_E} \cong 1$$

 


- For the circuit above, we can obtain the current gain  $A_i$  as follows

$$A_i = \frac{i_o}{i_i} = \frac{v_o/R_E}{v_i/R_i} = \frac{R_i}{R_E} \frac{v_o}{v_i} = \frac{R_i}{R_E} A_v$$

- Resultant current gain  $A_i$  is given by,

$$A_i = (h_{fe} + 1) \frac{R_B}{R_B + R_b} \quad \dots r_e \text{ model: } A_i = \frac{R_B}{R_B/(\beta + 1) + r_e + R_E}$$

## Output Resistance

 

Output resistance, i.e., Thévenin equivalent resistance,  $R_o$  is calculated using the test voltage circuit above.

$$R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}} = R_E \parallel \frac{h_{ie}}{h_{fe} + 1}$$

- Output resistance  $R_o$  according to the  $r_e$  model is given by

$$R_o = R_E \parallel r_e$$


- If  $1/h_{oe} \neq \infty$ , then replace  $R_E$  with  $(R_E \parallel 1/h_{oe})$  in  $R_i$ ,  $A_v$  and  $R_o$  calculations.
- If a voltage source with source resistance  $R_s$  is connected to the input, replace  $h_{ie}$  with  $(h_{ie} + R_B \parallel R_s)$  in  $R_o$  calculations.

## Phase Relationship


- Emitter-follower (common-collector) configuration has **no phase shift** between input and output.
 
## CE Collector Feedback Configuration


Common-emitter collector feedback bias configuration is given below



 Corresponding SSAC equivalent circuit is shown below



## Input Resistance

 

Input resistance  $R_i$  is given as


$$R_i = \left. \frac{v_i}{i_i} \right|_{R_L=\infty} = \frac{h_{ie}}{1 + \frac{h_{ie} + h_{fe}R_C}{R_F + R_C}} \quad \dots i_f = -\frac{h_{ie} + h_{fe}R_C}{R_F + R_C} i_b$$

$$\cong \frac{h_{ie}}{1 + \frac{h_{fe}R_C}{R_F + R_C}} \quad \dots h_{fe}R_C \gg h_{ie}$$

■ Input resistance  $R_i$  according to the  $r_e$  model is given by

$$R_i \cong \frac{\beta r_e}{1 + \frac{\beta R_C}{R_F + R_C}}$$

## Voltage Gain

 

No-load voltage gain  $A_v$  is given by


$$A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = \left( \frac{h_{fe}R_F - h_{ie}}{R_F + R_C} \right) \left( \frac{-R_C}{h_{ie}} \right) \quad \dots i_f = -\frac{h_{ie} + h_{fe}R_C}{R_F + R_C} i_b$$

$$\cong \left( \frac{h_{fe}R_F}{R_F + R_C} \right) \left( \frac{-R_C}{h_{ie}} \right) \quad \dots h_{fe}R_F \gg h_{ie}$$

$$\approx -\frac{h_{fe}R_C}{h_{ie}} \quad \dots R_F \gg R_C$$

■ No-load voltage gain  $A_v$  according to the  $r_e$  model is given by

$$A_v \approx -\frac{R_C}{r_e}$$

 


- For the circuit above, we can obtain the current gain  $A_i$  as follows

$$A_i = \frac{i_o}{i_i} = \frac{v_o/R_C}{v_i/R_i} = \frac{R_i}{R_C} \frac{v_o}{v_i} = \frac{R_i}{R_C} A_v$$

- Resultant current gain  $A_i$  is given by,

$$A_i \cong -\frac{h_{fe}(R_F + R_C)}{R_F + (h_{fe} + 1)R_C} \quad \dots r_e \text{ model: } A_i = -\frac{R_F + R_C}{R_F/\beta + R_C}$$

## Output Resistance

 

Output resistance, i.e., Thévenin equivalent resistance,  $R_o$  is calculated using the test voltage circuit above. Note that in the circuit  $i_b = 0$ , so  $h_{fe}i_b = 0$  as well.

$$R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}} = R_C || R_F$$

- Output resistance  $R_o$  according to the  $r_e$  model is given by

$$R_o = R_C || R_F$$


- If  $1/h_{oe} \neq \infty$ , then replace  $R_C$  with  $(R_C || 1/h_{oe})$  in  $R_i$ ,  $A_v$  and  $R_o$  calculations.
- If a voltage source with source resistance  $R_s$  is connected to the input, replace  $R_F$  with  $[R_F(R_s + h_{ie}) / (h_{fe}R_s + h_{ie})]$  in  $R_o$  calculations.

# Phase Relationship


- Phase relationship between input and output of a common-emitter amplifier configuration is always 180 degrees. This is independent of the type of the bias-configuration.

# Common-Base Configuration

Common-base configuration is given below

 

 
Corresponding SSAC equivalent circuit is shown below



- Here,  $h_{ib} = \frac{h_{ie}}{h_{fe} + 1} = \frac{26 \text{ mV}}{I_{EQ}}$  and  $h_{fb} = -\alpha_{ac} = -1$ .



# Input Resistance

 


Input resistance  $R_i$  is given as

$$R_i = \frac{v_i}{i_i} \Big|_{R_L=\infty} = R_E || h_{ib}$$

- If  $R_E \geq 10h_{ib}$ , then  $R_i$  simplifies to  $R_i = h_{ib}$ .
- Input resistance  $R_i$  according to the  $r_e$  model is given by

$$R_i = R_E || r_e$$

# Voltage Gain

 


No-load voltage gain  $A_v$  is given by

$$\begin{aligned} A_v &= \frac{v_o}{v_i} \Big|_{R_L=\infty} = \left( \frac{v_o}{h_{fb} i_e} \right) \left( \frac{h_{fb} i_e}{i_e} \right) \left( \frac{i_e}{v_i} \right) \\ &= (-R_C) (h_{fb}) \left( \frac{1}{h_{ib}} \right) \\ &= \frac{R_C}{h_{ib}} \end{aligned} \quad \dots h_{fb} = -1$$

- No-load voltage gain  $A_v$  according to the  $r_e$  model is given by

$$A_v = \frac{R_C}{r_e}$$

 


- For the circuit above, we can obtain the current gain  $A_i$  as follows

$$A_i = \frac{i_o}{i_i} = \frac{v_o/R_C}{v_i/R_i} = \frac{R_i}{R_C} \frac{v_o}{v_i} \\ = \frac{R_i}{R_C} A_v$$

- Resultant current gain  $A_i$  is given by,

$$A_i = \frac{R_E || h_{ib}}{h_{ib}} \approx 1 \quad \dots r_e \text{ model: } A_i = \frac{R_E || r_e}{r_e} \approx 1$$

## Output Resistance

 

Output resistance, i.e., Thévenin equivalent resistance,  $R_o$  is calculated using the test voltage circuit above. Note that in the circuit  $i_e = 0$ , so  $h_{fb}i_e = 0$  as well.

$$R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}} = R_C$$


- Output resistance  $R_o$  according to the  $r_e$  model is given by

$$R_o = R_C$$

- If  $1/h_{ob} \neq \infty$ , then replace  $R_C$  with  $(R_C || 1/h_{ob})$  in  $R_i$ ,  $A_v$  and  $R_o$  calculations.

# Phase Relationship


- A common-base amplifier configuration has **no phase shift** between input and output

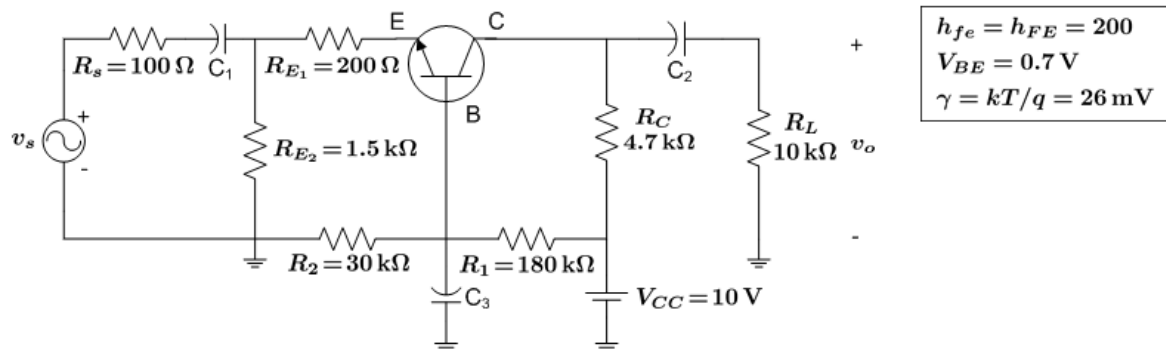

 **Example 1:** Consider the common-base BJT amplifier in the figure above.

- Perform DC analysis and find the  $Q$ -point.
- Evaluate the overall voltage gain  $A_{V_s}$  and the current gain  $A_i$ .
- Sketch  $v_o$  on the AC+DC load line graph when
  - $v_s = 100 \sin(\omega t)$  mV,
  - $v_s = 900 \sin(\omega t)$  mV.

**Solution:** a) Let us first draw the DC equivalent circuit first as shown below,



Here,  $R_E = R_{E1} + R_{E2} = 0.2k + 1.5k = 1.7k\Omega$ .

Now, let us calculate  $V_{BB}$ ,  $R_{BB}$ ,  $I_{CQ}$ ,  $V_{CEQ}$  and  $V_{CBQ}$

$$V_{BB} = \left( \frac{30k}{30k + 180k} \right) (10) = 1.43V,$$

$$R_{BB} = 30k || 180k = 25.71k\Omega,$$

$$I_{CQ} \cong I_{EQ} = \frac{1.43 - 0.7}{25.71k/201 + 1.7k} = 0.4mA,$$


$$V_{CEQ} = 10 - (0.4m)(4.7k + 1.7k) = 7.44V,$$

$$V_{CBQ} = 7.44 - 0.7 = 6.74V.$$

 b) In order to calculate the voltage gain, we need to draw the common-base SSAC equivalent circuit. As it is not given  $1/h_{ob} = \infty$ . Let us now calculate  $h_{ib}$  as

$$h_{ib} = \frac{26m}{0.4m} = 65\Omega.$$


So, the small-signal equivalent circuit is given below



Now, let us calculate input resistance  $R_i$  and voltage gain with load  $A_V$  as follows

$$R_i = R_{E2} || (R_{E1} + h_{ib}) = 1.5k || (200 + 65) \cong 225\Omega$$

$$\begin{aligned} A_V &= \frac{v_o}{v_i} = \left( \frac{v_o}{h_{fb}i_e} \right) \left( \frac{h_{fb}i_e}{i_e} \right) \left( \frac{i_e}{v_i} \right) \\ &= (-R_C || R_L) (h_{fb}) \left( \frac{1}{R_{E1} + h_{ib}} \right) = \frac{R_C || R_L}{R_{E1} + h_{ib}} \\ &= \frac{4.7k || 10k}{200 + 65} = \frac{3.2k}{0.265k} = 12.08. \end{aligned}$$

 

Thus, overall voltage gain  $A_{V_s}$  and current gain  $A_i$  are given by

$$A_{V_s} = \frac{v_o}{v_s} = \left(\frac{v_o}{v_i}\right) \left(\frac{v_i}{v_s}\right) = A_V \frac{R_i}{R_s + R_i} = (12.08) \left(\frac{225}{100 + 225}\right) = 8.36,$$

$$A_i = \frac{i_o}{i_i} = \frac{v_o/R_L}{v_i/R_i} = A_V \frac{R_i}{R_L} = (12.08) \left(\frac{0.225k}{10k}\right) = 0.27.$$

c) Let us write down the AC load line equation for this common-base amplifier, noting that  $v_o = v_{cb} = -i_c(R_C || R_L) = -i_c R_{ac}$  and  $v_{cb} = v_{ce} - v_{be} = v_{ce} - \frac{h_{ib}}{R_{E1} + h_{ib}} v_i \approx v_{ce}$

$$\begin{aligned} v_{CB} &= -i_c R_{ac} + V_{CBQ} + I_{CQ} R_{ac} & \dots V_{CBQ} &= V_{CEQ} - V_{BEQ} \\ v_{CE} - V_{BEQ} &= -i_c R_{ac} + V_{CEQ} - V_{BEQ} + I_{CQ} R_{ac} & \dots v_{CB} &\approx v_{CE} - V_{BEQ} \\ v_{CE} &= -i_c R_{ac} + V_{CEQ} + I_{CQ} R_{ac} \end{aligned}$$


So,  $R_{ac} = R_C || R_L = 4.7k || 10k = 3.2 k\Omega$ , and similarly we obtain  $R_{DC}$  from the C-E loop as  $R_{DC} = R_C + R_E = 4.7k + 1.7k = 6.4 k\Omega$ .

Note that, maximum available undistorted swing amplitude is

$$\min(V_{CEQ}, I_{CQ} R_{ac}) = \min(7.44, (0.4m)(3.2k)) = \min(7.44, 1.28) = 1.28 V.$$

Thus, as  $A_{V_s} = 8.36$ , maximum input source amplitude which gives an undistorted output is  $\max(v_{s(p)}) = 1.28/8.36 = 153.1 mV$ . If the input source amplitude exceeds this value, we will observe distortion at the output.

 i. For  $v_s = 100 \sin(\omega t)$  mV, we are going to observe an undistorted sinusoidal output with an amplitude of 0.836 V around  $V_{CBQ} = 6.74 V$  as shown below.



ii. For  $v_s = 900 \sin(\omega t)$  mV, we are going to observe a distorted output as shown below.

