 


Contents

- BJT Small-Signal Analysis
- Purpose of SSAC Analysis
- BJT SSAC Analysis Steps
- BJT Small-Signal Models
 - Hybrid Equivalent Model
- Common-Emitter Fixed-Bias Configuration
 - Input Resistance
 - Voltage Gain
 - Output Resistance
 - Phase Relationship
- Common-Emitter Voltage-Divider Bias Configuration
 - Input Resistance
 - Voltage Gain
 - Output Resistance
 - Phase Relationship
- Common-Emitter Unbypassed-Emitter Bias Configuration
 - Input Resistance
 - Voltage Gain
 - Output Resistance
 - Phase Relationship
- Emitter-Follower Configuration
 - Input Resistance
 - Voltage Gain
 - Output Resistance
 - Phase Relationship
- Common-Emitter Collector Feedback Configuration
 - Input Resistance
 - Voltage Gain
 - Output Resistance
 - Phase Relationship
- Common-Base Configuration
 - Input Resistance
 - Voltage Gain
 - Output Resistance
 - Phase Relationship

Purpose of SSAC Analysis


The purpose of small-signal AC (SSAC) analysis to determine the three parameters of an amplifier **input resistance**, **output resistance** and **gain**. In this course, we are mostly interested in the two-port voltage-gain amplifier model shown below.



■ Input resistance R_i is defined by the no-load input voltage of the amplifier divided by the no-load input current to the amplifier, i.e.,

$$R_i = \left. \frac{v_i}{i_i} \right|_{R_L=\infty}$$

 NOTE: Input resistance **cannot** include the source resistance R_s .




■ Output resistance R_o is obtained by the test-voltage method, i.e., by dividing the test voltage value with the measured test current value. In the test-voltage method, load is replaced with a test voltage v_{test} and the independent power sources (v_s or i_s) are killed, i.e., $v_s = 0$ or $i_s = 0$. Thus, output resistance R_o is given by

$$R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}}$$

NOTE: Output resistance **cannot** include the load resistance R_L .

■ No-load voltage gain A_v (or A_{VNL}) is defined by

$$A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty}$$

 

■ When load is connected, the voltage gain will decrease due to the voltage-divider consisting of R_L and R_o . So, voltage gain with load, A_V , is given by

$$A_V = \left. \frac{v_o}{v_i} \right|_{R_L} = \left(\frac{v_o}{A_v v_i} \right) \left(\frac{A_v v_i}{v_i} \right) = \frac{R_L}{R_o + R_L} A_v$$

■ Current gain A_i is defined by the output current versus the input current, i.e.,

$$A_i = \left. \frac{i_o}{i_i} \right|_{v_i/R_i} = \frac{v_o/R_L}{v_i/R_i} = \frac{R_i}{R_L} A_V = \frac{R_i}{R_o + R_L} A_v$$

■ Finally, overall voltage gain A_{Vs} is given by

$$A_{Vs} = \left. \frac{v_o}{v_s} \right|_{R_L} = \frac{R_L}{R_o + R_L} A_v \frac{R_i}{R_s + R_i}$$

BJT SSAC Analysis Steps

1. Draw the SSAC equivalent circuit
 - a) Draw the AC equivalent circuit (signal frequency is infinity, i.e., $f = \infty$)
 - i. Capacitors are short circuit, i.e., $X_C \rightarrow 0$.
 - ii. Kill the DC power sources (i.e., AC value of DC sources is zero).
 - b) Replace BJT with its small-signal equivalent model (e.g., hybrid equivalent model or r_e model).
2. Calculate the three amplifier parameters: R_i , R_o and A_v
 - a) Calculate no-load input resistance, $R_i = \left. \frac{v_i}{i_i} \right|_{R_L=\infty}$
 - b) Calculate output resistance, R_o .
 - c) Calculate no-load voltage gain, $A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty}$.

A small-signal model is an equivalent circuit that represents the SSAC characteristics of the transistor. It uses circuit elements that approximate the behavior of the transistor. Two commonly used models in SSAC analysis of BJTs are given below:

■ hybrid equivalent model


■ r_e model

Mostly, we are going to use the **hybrid equivalent model**. But, we are going to introduce and provide results for the r_e model as well.

NOTE: Small-signal equivalent model and its analysis are the same for both *npn* and *pnp* transistors.

Hybrid Equivalent Model

 
Parameters of the hybrid equivalent circuit provide the entire set on the specification sheet of a BJT and cover all operating conditions. Generalized hybrid equivalent circuit for any transistor configuration is provided below.



Here,

- h_i : input resistance
- h_r : reverse transfer voltage ratio (v_i/v_o)
- h_f : forward transfer current ratio (i_o/i_i)
- h_o : output conductance

 
For a specific configuration, the model parameters modified with the label of the common-mode terminal in their subscript. So, common-emitter and common-base configurations and their hybrid equivalent models are shown below, respectively.




- For the common-collector configuration, we always use the common-emitter hybrid equivalent model.

Simplified Hybrid Equivalent Model

 
Because h_r is normally a relatively small quantity, its removal is approximated by $h_r \approx 0$ and $h_r v_o = 0$, resulting in the simplified hybrid equivalent circuit shown below. In this course, we are going to use the simplified hybrid equivalent model.



 This circuit can be further simplified if a value for the parameter h_o or $1/h_o$ is not provided. In that case, we can safely assume that $h_o = 0$ or $1/h_o = \infty$ resulting in the approximate hybrid equivalent circuit shown below.




Common-Emitter Hybrid Equivalent Model

 

Here, the h -parameters are defined as below

$$\begin{aligned} h_{ie} &= \frac{\partial V_{BE}}{\partial I_B} \Big|_{Q\text{-point}} &= \frac{\gamma}{I_{BQ}} & \dots \text{see diode dynamic resistance section} \\ h_{fe} &= \frac{\partial I_C}{\partial I_B} \Big|_{Q\text{-point}} &= \beta_{ac} \\ 1/h_{oe} &= \frac{\partial V_{CE}}{\partial I_C} \Big|_{Q\text{-point}} &= \frac{V_A + V_{CEQ}}{I_{CQ}} & \dots V_A \text{ is the early voltage and } V_A \gg V_{CEQ} \end{aligned}$$

 Typical values of h_{fe} run from 50 to 200, h_{ie} run from 500Ω to $7k\Omega$, and $1/h_{oe}$ run from $40k\Omega$ to $100k\Omega$.




Note that, as $I_{CQ} = \beta I_{BQ}$ and $I_{EQ} = (\beta + 1) I_{BQ}$, we can also express h_{ie} in terms of I_{CQ} or I_{EQ} as follows

$$\begin{aligned} h_{ie} &= \frac{\gamma}{I_{BQ}} \\ &= h_{fe} \frac{\gamma}{I_{CQ}} \\ &= (h_{fe} + 1) \frac{\gamma}{I_{EQ}} \end{aligned}$$

where $\gamma = kT/q$ is the thermal voltage and have fixed values for a given temperature, e.g., $\gamma = 26\text{ mV}$ at room temperature $T = 300\text{ K}$.

Common-Emitter r_e Equivalent Model

 


One-to-one correspondence with the h -parameters are given below,

$$\begin{aligned} h_{fe} &= \beta \\ h_{ie} &= (\beta + 1) r_e \cong \beta r_e \\ 1/h_{oe} &= r_o \end{aligned}$$

Thus, $\beta = h_{fe}$, $\beta r_e = h_{ie}$ and $r_o = 1/h_{oe}$.


Common-Base Hybrid Equivalent Model

 

Here, the h -parameters are defined as below,

$$\begin{aligned} h_{ib} &= \left. \frac{\partial V_{BE}}{\partial I_E} \right|_{Q\text{-point}} = \frac{\gamma}{I_{EQ}} & \dots \text{see diode dynamic resistance section} \\ h_{fb} &= -\left. \frac{\partial I_C}{\partial I_E} \right|_{Q\text{-point}} = -\alpha_{ac} \cong -1 \\ 1/h_{ob} &= \left. \frac{\partial V_{CB}}{\partial I_C} \right|_{Q\text{-point}} \approx \infty \end{aligned}$$

 Typically, $h_{fb} = -1$, and h_{ib} run from 5Ω to 50Ω , and $1/h_{ob}$ is in the megohm range. Thus, $1/h_{ob} \gg 1/h_{oe}$.




Note that, the relationship between h_{ib} and h_{ie} is given below

$$h_{ie} = (h_{fe} + 1) h_{ib}$$

$$\text{or } h_{ib} = \frac{h_{ie}}{h_{fe} + 1}.$$

Common-Base r_e Equivalent Model

 

One-to-one correspondence with the h -parameters are given below

$$\begin{aligned} h_{fb} &= -\alpha \\ h_{ib} &= r_e \\ 1/h_{ob} &= r_o. \end{aligned}$$

Thus, $\alpha = -h_{fb} \cong 1$, $r_e = h_{ib}$ and $r_o = 1/h_{ob} \cong \infty$. Note that, minus sign is due to the direction of the current source.


Phase Relationship

The phase relationship between input and output depends on the amplifier configuration circuit as listed below.



- Common-Emitter: 180 degrees
- Common-Base: 0 degrees
- Common-Collector: 0 degrees (Emitter-Follower)

Common-Emitter Fixed-Bias Configuration

 
Common-emitter fixed-bias configuration is given below



  Let us start SSAC analysis by drawing the AC equivalent circuit as shown below



 
Then, we are going to replace BJT with its common-emitter hybrid equivalent model as shown below



- Obtain h_{fe} and $1/h_{oe}$ from the specification sheet of the transistor or by testing the transistor using a curve tracer. Calculate h_{ie} using the DC analysis values as

$$h_{ie} = \frac{26\text{ mV}}{I_{BQ}} \frac{26\text{ mV}}{I_{CQ}}.$$

Input Resistance

 

Input resistance R_i is given as


$$R_i = \left. \frac{v_i}{i_i} \right|_{R_L=\infty} = R_B \parallel h_{ie}$$

If $R_B \geq 10h_{ie}$, then R_i simplifies to $R_i = h_{ie}$.

Input resistance R_i according to the r_e model is given by

$$R_i = R_B \parallel \beta r_e$$

Voltage Gain

 


No-load voltage gain A_v is given by

$$\begin{aligned} A_v &= \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = \left(\frac{v_o}{h_{fe}i_b} \right) \left(\frac{i_b}{i_i} \right) \\ &= (-R_C \parallel 1/h_{oe}) (h_{fe}) \left(\frac{1}{h_{ie}} \right) \\ &= -\frac{h_{fe} (R_C \parallel 1/h_{oe})}{h_{ie}} \end{aligned}$$

No-load voltage gain A_v according to the r_e model is given by

$$A_v = -\frac{R_C \parallel r_o}{r_e}$$

 

If $1/h_{oe} \geq 10R_C$, no-load voltage gain A_v reduces to

$$A_v = -\frac{h_{fe}R_C}{h_{ie}} \quad \dots r_e \text{ model: } A_v = -\frac{R_C}{r_e}$$


For the circuit above, we can obtain the current gain A_i as follows

$$\begin{aligned} A_i &= \frac{i_o}{i_i} = \frac{v_o/R_C}{v_i/R_i} = \frac{R_i}{R_C} \frac{v_o}{v_i} \\ &= \frac{R_i}{R_C} A_v \end{aligned}$$

If $1/h_{oe} \geq 10R_C$ and $R_B \geq 10h_{ie}$, current gain A_i reduces to

$$A_i = -h_{fe} \quad \dots r_e \text{ model: } A_i = -\beta$$

Output Resistance

 

Output resistance, i.e., Thévenin equivalent resistance, R_o is calculated using the test voltage circuit above. Note that in the circuit $i_b = 0$, so $h_{fe}i_b = 0$ as well.


$$R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}} = R_C \parallel 1/h_{oe}$$

If $1/h_{oe} \geq 10R_C$, then R_o simplifies to $R_o = R_C$.

Output resistance R_o according to the r_e model is given by

$$R_o = R_C \parallel r_o$$

Phase Relationship

 


The phase relationship between input and output is 180 degrees as shown above.


The negative sign used in the voltage gain formulas indicates the inversion.

CE Voltage-Divider Bias Configuration

 
Common-emitter voltage-divider bias configuration is given below



 Corresponding SSAC equivalent circuit is shown below



Input Resistance

 


Input resistance R_i is given as

$$R_i = \left. \frac{v_i}{i_i} \right|_{R_L=\infty} = R_1 || R_2 || h_{ie}$$

■ Input resistance R_i according to the r_e model is given by

$$R_i = R_1 || R_2 || \beta r_e$$

Voltage Gain

 


No-load voltage gain A_v is given by

$$\begin{aligned} A_v &= \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = \left(\frac{v_o}{h_{fe} i_b} \right) \left(\frac{i_b}{v_i} \right) \\ &= (-R_C || 1/h_{oe}) (h_{fe}) \left(\frac{1}{h_{ie}} \right) \\ &= -\frac{h_{fe} (R_C || 1/h_{oe})}{h_{ie}} \end{aligned}$$

■ No-load voltage gain A_v according to the r_e model is given by

$$A_v = -\frac{R_C || r_o}{r_e}$$

 

■ If $1/h_{oe} \geq 10R_C$, no-load voltage gain A_v reduces to

$$A_v = -\frac{h_{fe} R_C}{h_{ie}} \quad \dots r_e \text{ model: } A_v = -\frac{R_C}{r_e}$$


■ For the circuit above, we can obtain the current gain A_i as follows

$$\begin{aligned} A_i &= \frac{i_o}{i_i} = \frac{v_o/R_C}{v_i/R_i} = \frac{R_i}{R_C} \frac{v_o}{v_i} \\ &= \frac{R_i}{R_C} A_v \end{aligned}$$

■ If $1/h_{oe} \geq 10$, and given $R' = R_1 || R_2$, current gain A_i reduces to

$$A_i = -h_{fe} \frac{R'}{R' + h_{ie}} \quad \dots r_e \text{ model: } A_i = -\frac{R'}{R' + \beta + r_e}$$

Output Resistance

 

Output resistance, i.e., Thévenin equivalent resistance, R_o is calculated using the test voltage circuit above. Note that in the circuit $i_b = 0$, so $h_{fe} i_b = 0$ as well.

$$R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}} = R_C || 1/h_{oe}$$

■ If $1/h_{oe} \geq 10R_C$, then R_o simplifies to $R_o = R_C$.

■ Output resistance R_o according to the r_e model is given by

$$R_o = R_C || r_o$$


Phase Relationship

■ Phase relationship between input and output of a common-emitter amplifier configuration if always 180 degrees. This is independent of the type of the bias-configuration.




CE Unbypassed-Emitter Bias Configuration

 Common-emitter unbypassed-emitter bias configuration and its SSAC equivalent circuit are given on the left and right figures below, respectively.



■ When R_E is not bypassed, we normally assume $1/h_{oe} = \infty$ in order to reduce the calculation complexity. Because of the feedback, even $1/h_{oe} \neq \infty$ the results do not really change at all.

Input Resistance

 


Input resistance R_i is given as

$$\begin{aligned} R_i &= \frac{v_i}{i_i} \Big|_{R_L=\infty} = R_B || R_E \\ &= R_B || [h_{ie} + (h_{fe} + 1) R_E] \end{aligned}$$

■ Input resistance R_i according to the r_e model is given by

$$R_i = R_B || (\beta + 1)(r_e + R_E) \cong R_B || \beta(r_e + R_E)$$

Voltage Gain

 


No-load voltage gain A_v is given by

$$\begin{aligned} A_v &= \frac{v_o}{v_i} \Big|_{R_L=\infty} = \left(\frac{v_o}{h_{fe} i_b} \right) \left(\frac{i_b}{i_i} \right) \left(\frac{i_i}{v_i} \right) \\ &= (-R_C) (h_{fe}) \left(\frac{1}{R_B} \right) \\ &= -\frac{h_{fe} R_C}{h_{ie} + (h_{fe} + 1) R_E} \end{aligned}$$

■ No-load voltage gain A_v according to the r_e model is given by

$$A_v = -\frac{R_C}{r_e + R_E}$$

 

■ If $(h_{fe} + 1) R_E \geq 10 h_{ie}$, no-load voltage gain A_v reduces to

$$A_v = -\frac{R_C}{R_E} \quad \dots r_e \text{ model: } A_v = -\frac{R_C}{R_E}$$


■ For the circuit above, we can obtain the current gain A_i as follows

$$\begin{aligned} A_i &= \frac{i_o}{i_i} = \frac{v_o/R_C}{v_i/R_i} = \frac{R_i}{R_C} \frac{v_o}{v_i} \\ &= \frac{R_i}{R_C} A_v \end{aligned}$$

■ Resultant current gain A_i is given by

$$A_i = -h_{fe} \frac{R_B}{R_B + R_E} \quad \dots r_e \text{ model: } A_i = -\frac{R_B}{R_B/\beta + r_e + R_E}$$

Output Resistance

 

Output resistance, i.e., Thévenin equivalent resistance, R_o is calculated using the test voltage circuit above. Note that in the circuit $i_b = 0$, so $h_{fe} i_b = 0$ as well.

$$R_o = \frac{v_{test}}{i_{test}} \Big|_{v_s=0, R_L=v_{test}} = R_C$$

■ Output resistance R_o according to the r_e model is given by

$$R_o = R_C$$


Phase Relationship

■ Phase relationship between input and output of a common-emitter amplifier configuration if always 180 degrees. This is independent of the type of the bias-configuration.




Emitter-Follower Configuration

 Emitter-follower (common-collector) configuration and its SSAC equivalent circuit are given on the left and right figures below, respectively.



■ When R_E is not bypassed, we normally assume $1/h_{oe} = \infty$ in order to reduce the calculation complexity.

Input Resistance

 


Input resistance R_i is given as

$$\begin{aligned} R_i &= \frac{v_i}{i_i} \Big|_{R_L=\infty} = R_B || R_b \\ &= R_B \parallel [h_{ie} + (h_{fe} + 1) R_E] \end{aligned}$$

■ Input resistance R_i according to the r_e model is given by

$$R_i = R_B \parallel (\beta + 1)(r_e + R_E) \cong R_B \parallel \beta(r_e + R_E)$$

Voltage Gain

 


No-load voltage gain A_v is given by

$$\begin{aligned} A_v &= \frac{v_o}{v_i} \Big|_{R_L=\infty} = \left(\frac{v_o}{i_b} \right) \left(\frac{i_b}{v_i} \right) \\ &= [(h_{fe} + 1) R_E] \left(\frac{1}{R_b} \right) \\ &= \frac{(h_{fe} + 1) R_E}{h_{ie} + (h_{fe} + 1) R_E} \cong 1 \end{aligned}$$

■ No-load voltage gain A_v according to the r_e model is given by

$$A_v = \frac{R_E}{r_e + R_E} \cong 1$$

 


■ For the circuit above, we can obtain the current gain A_i as follows

$$\begin{aligned} A_i &= \frac{i_o}{i_i} = \frac{v_o/R_E}{v_i/R_i} = \frac{R_i}{R_E} \frac{v_o}{v_i} \\ &= \frac{R_i}{R_E} A_v \end{aligned}$$

■ Resultant current gain A_i is given by,

$$A_i = (h_{fe} + 1) \frac{R_B}{R_B + R_b} \quad \dots r_e \text{ model: } A_i = \frac{R_B}{R_B / (\beta + 1) + r_e + R_E}$$

Output Resistance

 

Output resistance, i.e., Thévenin equivalent resistance, R_o is calculated using the test voltage circuit above.

$$R_o = \frac{v_{test}}{i_{test}} \Big|_{v_s=0, R_L=v_{test}} = R_E \parallel \frac{h_{ie}}{h_{fe} + 1}$$

■ Output resistance R_o according to the r_e model is given by

$$R_o = R_E \parallel r_e$$


■ If $1/h_{oe} \neq \infty$, then replace R_E with $(R_E \parallel 1/h_{oe})$ in R_i , A_v and R_o calculations.

■ If a voltage source with source resistance R_s is connected to the input, replace h_{ie} with $(h_{ie} + R_B \parallel R_s)$ in R_o calculations.


Phase Relationship

■ Emitter-follower (common-collector) configuration has no phase shift between input and output.

 
Common-emitter collector feedback bias configuration is given below



 Corresponding SSAC equivalent circuit is shown below



Input Resistance

 

Input resistance R_i is given as


$$R_i = \frac{v_i}{i_i} \Big|_{R_L=\infty} = \frac{h_{ie}}{1 + \frac{h_{ie} + h_{fe}R_C}{R_F + R_C}} \quad \dots i_f = -\frac{h_{ie} + h_{fe}R_C}{R_F + R_C} i_b$$

$$\cong \frac{h_{ie}}{1 + \frac{h_{fe}R_C}{R_F + R_C}} \quad \dots h_{fe}R_C \gg h_{ie}$$

■ Input resistance R_i according to the r_e model is given by

$$R_i \cong \frac{\beta r_e}{1 + \frac{\beta R_C}{R_F + R_C}}$$

Voltage Gain

 

No-load voltage gain A_v is given by


$$A_v = \frac{v_o}{v_i} \Big|_{R_L=\infty} = \left(\frac{h_{fe}R_F - h_{ie}}{R_F + R_C} \right) \left(\frac{-R_C}{h_{ie}} \right) \quad \dots i_f = -\frac{h_{ie} + h_{fe}R_C}{R_F + R_C} i_b$$

$$\cong \left(\frac{h_{fe}R_F}{R_F + R_C} \right) \left(\frac{-R_C}{h_{ie}} \right) \quad \dots h_{fe}R_F \gg h_{ie}$$

$$\approx -\frac{h_{fe}R_C}{h_{ie}} \quad \dots R_F \gg R_C$$

■ No-load voltage gain A_v according to the r_e model is given by

$$A_v \approx -\frac{R_C}{r_e}$$

 

■ For the circuit above, we can obtain the current gain A_i as follows


$$A_i = \frac{i_o}{i_i} = \frac{v_o/R_C}{v_i/R_i} = \frac{R_i}{R_C} \frac{v_o}{v_i}$$

$$= \frac{R_i}{R_C} A_v$$

■ Resultant current gain A_i is given by,

$$A_i \cong -\frac{h_{fe}(R_F + R_C)}{R_F + (h_{fe} + 1)R_C} \quad \dots r_e \text{ model: } A_i = -\frac{R_F + R_C}{R_F/\beta + R_C}$$

Output Resistance

 

Output resistance, i.e., Thévenin equivalent resistance, R_o is calculated using the test voltage circuit above. Note that in the circuit $i_b = 0$, so $h_{fe}i_b = 0$ as well.

$$R_o = \frac{v_{test}}{i_{test}} \Big|_{v_s=0, R_L=v_{test}} = R_C || R_F$$

■ Output resistance R_o according to the r_e model is given by

$$R_o = R_C || R_F$$

■ If $1/h_{oe} \neq \infty$, then replace R_C with $(R_C || 1/h_{oe})$ in R_i , A_v and R_o calculations.


■ If a voltage source with source resistance R_s is connected to the input, replace R_F with $[R_F(R_s + h_{ie}) / (h_{fe}R_s + h_{ie})]$ in R_o calculations.

Phase Relationship


■ Phase relationship between input and output of a common-emitter amplifier configuration if always 180 degrees. This is independent of the type of the bias-configuration.

Common-Base Configuration

Common-base configuration is given below

 


 Corresponding SSAC equivalent circuit is shown below



$$\text{■ Here, } h_{ib} = \frac{h_{ie}}{h_{fe} + 1} = \frac{26 \text{ mV}}{I_{EQ}} \text{ and } h_{fb} = -\alpha_{ac} = -1.$$

 Solution: a) Let us first draw the DC equivalent circuit first as shown below.



Here, $R_E = R_{E1} + R_{E2} = 0.2k + 1.5k = 1.7\text{k}\Omega$.

Now, let us calculate V_{BB} , R_{BB} , I_{CQ} , V_{CEQ} and V_{CBQ}

$$V_{BB} = \left(\frac{30k}{30k + 180k} \right) (10) = 1.43\text{ V},$$

$$R_{BB} = 30k \parallel 180k = 25.71\text{ k}\Omega,$$

$$I_{CQ} \cong I_{EQ} = \frac{1.43 - 0.7}{25.71k/201 + 1.7k} = 0.4\text{ mA},$$


$$V_{CEQ} = 10 - (0.4m)(4.7k + 1.7k) = 7.44\text{ V},$$

$$V_{CBQ} = 7.44 - 0.7 = 6.74\text{ V}.$$

 b) In order to calculate the voltage gain, we need to draw the common-base SSAC equivalent circuit. As it is not given $1/h_{ob} = \infty$. Let us now calculate h_{ib} as

$$h_{ib} = \frac{26m}{0.4m} = 65\text{ }\Omega.$$

So, the small-signal equivalent circuit is given below




Now, let us calculate input resistance R_i and voltage gain with load A_V as follows

$$R_i = R_{E2} \parallel (R_{E1} + h_{ib}) = 1.5k \parallel (200 + 65) \cong 225\text{ }\Omega$$

$$A_V = \frac{v_o}{v_i} = \left(\frac{v_o}{h_{fb}i_e} \right) \left(\frac{h_{fb}i_e}{i_e} \right) \left(\frac{i_e}{v_i} \right)$$

$$= (-R_C \parallel R_L) \left(\frac{1}{R_{E1} + h_{ib}} \right) = \frac{R_C \parallel R_L}{R_{E1} + h_{ib}}$$
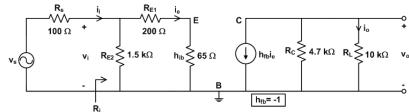
$$= \frac{4.7k \parallel 10k}{200 + 65} = \frac{3.2k}{0.265k} = 12.08.$$



Thus, overall voltage gain A_{Vs} and current gain A_i are given by

$$A_{Vs} = \frac{v_o}{v_s} = \left(\frac{v_o}{v_i} \right) \left(\frac{v_i}{v_s} \right) = A_V \frac{R_i}{R_s + R_i} = (12.08) \left(\frac{225}{100 + 225} \right) = 8.36,$$

$$A_i = \frac{i_o}{i_i} = \frac{v_o / R_L}{v_i / R_i} = A_V \frac{R_i}{R_L} = (12.08) \left(\frac{0.225k}{10k} \right) = 0.27.$$

c) Let us write down the AC load line equation for this common-base amplifier, noting that $v_o = v_{cb} = -i_c(R_C \parallel R_L) = -i_c R_{ac}$ and $v_{cb} = v_{ce} - v_{be} = v_{ce} - \frac{h_{ib}}{R_{E1} + h_{ib}} v_i \approx v_{ce}$

$$v_{CB} = -i_c R_{ac} + V_{CBQ} + I_{CQ} R_{ac} \quad \dots V_{CBQ} = V_{CEQ} - V_{BEQ}$$

$$v_{CE} - V_{BEQ} = -i_c R_{ac} + V_{CEQ} - V_{BEQ} + I_{CQ} R_{ac} \quad \dots v_{CB} \approx v_{CE} - V_{BEQ}$$

$$v_{CE} = -i_c R_{ac} + V_{CEQ} + I_{CQ} R_{ac}$$


So, $R_{ac} = R_C \parallel R_L = 4.7k \parallel 10k = 3.2k\Omega$, and similarly we obtain R_{DC} from the C-E loop as $R_{DC} = R_C + R_E = 4.7k + 1.7k = 6.4k\Omega$.

Note that, maximum available undistorted swing amplitude is

$$\min(V_{CEQ}, I_{CQ} R_{ac}) = \min(7.44, (0.4m)(3.2k)) = \min(7.44, 1.28) = 1.28\text{ V}.$$

Thus, as $A_{Vs} = 8.36$, maximum input source amplitude which gives an undistorted output is $\max(v_{s(p)}) = 1.28/8.36 = 153.1\text{ mV}$. If the input source amplitude exceeds this value, we will observe distortion at the output.

 i. For $v_s = 100 \sin(\omega t)\text{ mV}$, we are going to observe an undistorted sinusoidal output with an amplitude of 0.836V around $V_{CBQ} = 6.74\text{ V}$ as shown below.



ii. For $v_s = 900 \sin(\omega t)\text{ mV}$, we are going to observe a distorted output as shown below.

