

## Contents


- FET Small-Signal Analysis
  - FET SSAC Analysis Steps
  - FET Small-Signal Model
  - Common-Source Fixed-Bias Configuration
    - Input Resistance
    - Voltage Gain
    - Output Resistance
  - Common-Source Self-Bias Configuration
    - Input Resistance
    - Voltage Gain
    - Output Resistance
  - Common-Source Voltage-Divider Bias Configuration
    - Input Resistance
    - Voltage Gain
    - Output Resistance
  - Common-Source Unbypassed Self-Bias Configuration
    - Input Resistance
    - Voltage Gain
    - Output Resistance
  - Source-Follower Configuration
    - Input Resistance
    - Voltage Gain
    - Output Resistance
  - Common-Source Drain Feedback Configuration
    - Input Resistance
    - Voltage Gain
    - Output Resistance
  - Common-Gate Configuration
    - Input Resistance
    - Voltage Gain
    - Output Resistance

## FET SSAC Analysis Steps

1. Draw the SSAC equivalent circuit
  - a) Draw the AC equivalent circuit (signal frequency is infinity, i.e.,  $f = \infty$ )
    - i. Capacitors are short circuit, i.e.,  $X_C \rightarrow 0$ .
    - ii. Kill the DC power sources (i.e., AC value of DC sources is zero).
  - b) Replace FET with its small-signal equivalent model.
2. Calculate the three amplifier parameters:  $R_i$ ,  $R_o$  and  $A_v$ 
  - a) Calculate no-load input resistance,  $R_i = \left. \frac{v_i}{i_i} \right|_{R_L = \infty}$ .
  - b) Calculate output resistance,  $R_o$ .
  - c) Calculate no-load voltage gain,  $A_v = \left. \frac{v_o}{v_i} \right|_{R_L = \infty}$ .
 
## FET Small-Signal Model

Small-signal equivalent model for a FET transistor is provided below. This model and its analysis is the same for all FET types, i.e., JFET, DMOSFET, EMOSFET,  $n$ -channel and  $p$ -channel.




Here,

- $g_m = g_{fs} = y_{fs} = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{Q\text{-point}}$  is the forward transfer conductance,
- $r_{ds} = \frac{1}{g_{os}} = \frac{1}{y_{os}} = \left. \frac{\partial V_{DS}}{\partial I_D} \right|_{Q\text{-point}}$  is the output resistance.

Forward transfer conductance  $g_m$  is mostly called as the **transconductance** parameter.

 When  $r_{ds} \neq \infty$ , we can also use the voltage-controlled voltage source model (via Norton-to-Thévenin transformation) as shown below. We mostly use this model for the common-gate and unbypassed self-bias configurations.



Here  $\mu = g_m r_{ds}$  is the forward transfer-voltage gain.


- Typical values of  $g_m$  run from 1 mS to 5 mS,
- Typical values of  $r_{ds}$  run from 20 kΩ to 100 kΩ,
- Consequently, typical values of  $\mu$  run from 20 to 500.

## Transconductance Parameter ( $g_m$ )

Transconductance parameter  $g_m$  is given by

$$g_m = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{Q\text{-point}} \cong \frac{\Delta I_D}{\Delta V_{GS}} \Big|_{Q\text{-point}}$$

 In other words,  $g_m$  is the slope of the characteristics at the point of operation as shown below.



- Let us derive  $g_m$  for the JFET equation,  $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$

$$\begin{aligned} g_m &= \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{Q\text{-point}} = \frac{2I_{DSS}}{|V_P|} \left(1 - \frac{V_{GS}}{V_P}\right) \Big|_{Q\text{-point}} \\ &= \frac{2I_{DSS}}{|V_P|} \left(1 - \frac{V_{GSQ}}{V_P}\right) \\ &= \frac{2I_{DSS}}{|V_P|} \sqrt{\frac{I_{DQ}}{I_{DSS}}} \quad \dots I_{DQ} = I_{DSS} \left(1 - \frac{V_{GSQ}}{V_P}\right)^2 \\ &= g_{m0} \sqrt{\frac{I_{DQ}}{I_{DSS}}} \quad \dots g_{m0} = \frac{2I_{DSS}}{|V_P|} \end{aligned}$$

- Let us derive  $g_m$  for the MOSFET equation,  $I_D = k(V_{GS} - V_{GS(Th)})^2$

$$\begin{aligned} g_m &= \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{Q\text{-point}} = 2k(V_{GS} - V_{GS(Th)}) \Big|_{Q\text{-point}} \\ &= 2k(V_{GSQ} - V_{GS(Th)}) \\ &= 2\sqrt{k} \sqrt{I_{DQ}} \quad \dots I_{DQ} = k(V_{GS} - V_{GS(Th)})^2 \end{aligned}$$


## Phase Relationship

The phase relationship between input and output depends on the amplifier configuration circuit as listed below.


- Common-Source: 180 degrees
- Common-Gate: 0 degrees
- Common-Drain: 0 degrees (Source-Follower)
 
## Common-Source Fixed-Bias Configuration


Common-source fixed-bias configuration is given below



 Corresponding SSAC equivalent circuit is shown below




## Input Resistance

 

Input resistance  $R_i$  is given as

$$R_i = \left. \frac{v_i}{i_i} \right|_{R_L = \infty} = R_G$$

## Voltage Gain

 


No-load voltage gain  $A_v$  is given by

$$\begin{aligned} A_v &= \left. \frac{v_o}{v_i} \right|_{R_L = \infty} = \left( \frac{v_o}{g_m v_{gs}} \right) \left( \frac{g_m v_{gs}}{v_{gs}} \right) \left( v_{gs} \right) \\ &= (-R_D || r_{ds}) (g_m) (1) \\ &= -g_m (R_D || r_{ds}) \end{aligned}$$

- If  $r_{ds} \geq 10R_D$ , voltage gain  $A_v$  reduces to

$$A_v = -g_m R_D$$

 


- For the circuit above, we can obtain the current gain  $A_i$  as follows

$$\begin{aligned} A_i &= \frac{i_o}{i_i} = \frac{v_o/R_D}{v_i/R_i} = \frac{R_i}{R_D} \frac{v_o}{v_i} \\ &= \frac{R_i}{R_D} A_v \end{aligned}$$

- If  $r_{ds} \geq 10R_D$ , current gain  $A_i$  reduces to

$$A_i = -g_m R_G$$

## Output Resistance

 


Output resistance, i.e., Thévenin equivalent resistance,  $R_o$  is calculated using the test voltage circuit above. Note that in the circuit  $v_{gs} = 0$ , so  $g_m v_{gs} = 0$  as well.

$$R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_{gs}=0, R_L=v_{test}} = R_D || r_{ds}$$


- If  $r_{ds} \geq 10R_D$ , then  $R_o$  simplifies to  $R_o = R_D$ .
 
### CS Self-Bias Configuration


Common-source self-bias configuration is given below



 Corresponding SSAC equivalent circuit is shown below




### Input Resistance

 

Input resistance  $R_i$  is given as

$$R_i = \frac{v_i}{i_i} \Big|_{R_L = \infty} = R_G$$


### Voltage Gain

 

No-load voltage gain  $A_v$  is given by

$$A_v = \frac{v_o}{v_i} \Big|_{R_L = \infty} = \left( \frac{v_o}{g_m v_{gs}} \right) \left( \frac{g_m v_{gs}}{v_{gs}} \right) \left( v_{gs} \right) = (-R_D || r_{ds}) (g_m) (1) = -g_m (R_D || r_{ds})$$

 ■ If  $r_{ds} \geq 10R_D$ , no-load voltage gain  $A_v$  reduces to  $A_v = -g_m R_D$




■ For the circuit above, we can obtain the current gain  $A_i$  as follows

$$A_i = \frac{i_o}{i_i} = \frac{v_o / R_D}{v_i / R_i} = \frac{R_i}{R_D} \frac{v_o}{v_i} = \frac{R_i}{R_D} A_v$$

■ If  $r_{ds} \geq 10R_D$ , current gain  $A_i$  reduces to

$$A_i = -g_m R_G$$

### Output Resistance

 


Output resistance, i.e., Thévenin equivalent resistance,  $R_o$  is calculated using the test voltage circuit above. Note that in the circuit  $v_{gs} = 0$ , so  $g_m v_{gs} = 0$  as well.

$$R_o = \frac{v_{test}}{i_{test}} \Big|_{v_{gs}=0, R_L=v_{test}} = R_D || r_{ds}$$


■ If  $r_{ds} \geq 10R_D$ , then  $R_o$  simplifies to  $R_o = R_D$ .
 
### CS Voltage-Divider Bias Configuration


Common-source voltage-divider bias configuration is given below



 Corresponding SSAC equivalent circuit is shown below




### Input Resistance

 

Input resistance  $R_i$  is given as

$$R_i = \left. \frac{v_i}{i_i} \right|_{R_L = \infty} = R_1 \parallel R_2$$

### Voltage Gain

 


No-load voltage gain  $A_v$  is given by

$$A_v = \left. \frac{v_o}{v_i} \right|_{R_L = \infty} = \left( \frac{v_o}{g_m v_{gs}} \right) \left( \frac{g_m v_{gs}}{v_{gs}} \right) \left( \frac{v_{gs}}{v_i} \right) = (-R_D \parallel r_{ds}) (g_m) (1) = -g_m (R_D \parallel r_{ds})$$

■ If  $r_{ds} \geq 10R_D$ , no-load voltage gain  $A_v$  reduces to

$$A_v = -g_m R_D$$

 


■ For the circuit above, we can obtain the current gain  $A_i$  as follows

$$A_i = \frac{i_o}{i_i} = \frac{v_o/R_D}{v_i/R_i} = \frac{R_i v_o}{R_D v_i} = \frac{R_i}{R_D} A_v$$

■ If  $r_{ds} \geq 10R_D$ , current gain  $A_i$  reduces to

$$A_i = -g_m (R_1 \parallel R_2)$$

### Output Resistance

 


Output resistance, i.e., Thévenin equivalent resistance,  $R_o$  is calculated using the test voltage circuit above. Note that in the circuit  $v_{gs} = 0$ , so  $g_m v_{gs} = 0$  as well.

$$R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_{gs}=0, R_L=v_{test}} = R_D \parallel r_{ds}$$

■ If  $r_{ds} \geq 10R_D$ , then  $R_o$  simplifies to  $R_o = R_D$ .

 
### CS Unbypassed Self-Bias Configuration

Common-source unbypassed self-bias configuration and its SSAC equivalent circuit are given on the left and right figures below, respectively.



■ When  $R_S$  is not bypassed, we normally use the voltage-controlled voltage source model in the small-signal equivalent circuit as shown above.


### Input Resistance

 

Input resistance  $R_i$  is given as


$$R_i = \left. \frac{v_i}{i_i} \right|_{R_L = \infty} = R_G$$

### Voltage Gain

 

No-load voltage gain  $A_v$  is given by

$$\begin{aligned}
 A_v &= \left. \frac{v_o}{v_i} \right|_{R_L = \infty} = \left( \frac{v_o}{i_d} \right) \left( \frac{i_d}{v_{gs}} \right) \left( \frac{v_{gs}}{v_i} \right) \\
 &= (-R_D) \left( \frac{\mu}{R_S + R_D + r_{ds}} \right) \left( \frac{v_{gs}}{v_{gs} + i_d R_S} \right) \quad \dots i_d = \frac{\mu v_{gs}}{R_S + R_D + r_{ds}} \\
 &= (-R_D) \left( \frac{\mu}{R_S + R_D + r_{ds}} \right) \left( \frac{1}{1 + \frac{\mu R_S}{R_S + R_D + r_{ds}}} \right) \\
 &= -\frac{\mu R_D}{(\mu + 1) R_S + R_D + r_{ds}} \quad \dots \mu = g_m r_{ds} \\
 &= -\frac{g_m R_D}{1 + g_m R_S + \frac{R_S + R_D}{r_{ds}}}
 \end{aligned}$$

 

■ If  $r_{ds} \geq 10(R_D + R_S)$ , no-load voltage gain  $A_v$  reduces to

$$A_v = -\frac{g_m R_D}{1 + g_m R_S}$$


■ If  $r_{ds} \geq 10(R_D + R_S)$  and  $g_m R_S \gg 1$ , no-load voltage gain  $A_v$  reduces to

$$A_v \approx -\frac{R_D}{R_S}$$

■ For the circuit above, we can obtain the current gain  $A_i$  as follows

$$\begin{aligned}
 A_i &= \frac{i_o}{i_i} = \frac{v_o/R_D}{v_i/R_i} = \frac{R_i}{R_D} \frac{v_o}{v_i} \\
 &= \frac{R_i}{R_D} A_v
 \end{aligned}$$

### Output Resistance

 


Output resistance, i.e., Thévenin equivalent resistance,  $R_o$  is calculated using the test voltage circuit above.


$$\begin{aligned}
 R_o &= \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}} = \frac{v_{test}}{R_D} + i_d \\
 &= \frac{v_{test}}{R_D} - \frac{v_{gs}}{R_S} \quad \dots v_s = -v_{gs}, i_d = \frac{-v_{gs}}{R_S} \\
 &= \frac{v_{test}}{R_D} + \frac{v_{test}}{(\mu + 1) R_S + r_{ds}} \quad \dots v_{gs} = -\frac{v_{test}}{(\mu + 1) + r_{ds}/R_S} \\
 &= R_D \parallel [(\mu + 1) R_S + r_{ds}] \quad \dots \mu = g_m r_{ds} \\
 &= R_D \parallel [(g_m R_S + 1) r_{ds} + R_S] \\
 &\cong R_D
 \end{aligned}$$
 
### Source-Follower Configuration


Source-follower (common-drain) configuration is given below



 Corresponding SSAC equivalent circuit is shown below




### Input Resistance

 

Input resistance  $R_i$  is given as


$$R_i = \left. \frac{v_i}{i_i} \right|_{R_L = \infty} = R_G$$

### Voltage Gain

 

No-load voltage gain  $A_v$  is given by

$$\begin{aligned}
 A_v &= \left. \frac{v_o}{v_i} \right|_{R_L = \infty} = \left( \frac{v_o}{v_{gs}} \right) \left( \frac{v_{gs}}{v_i} \right) \\
 &= [g_m (R_S \parallel r_{ds})] \left( \frac{1}{1 + g_m (R_S \parallel r_{ds})} \right) \quad \dots v_i = v_{gs} + v_o \\
 &= \frac{g_m (R_S \parallel r_{ds})}{1 + g_m (R_S \parallel r_{ds})} \\
 &\cong 1
 \end{aligned}$$

 


■ For the circuit above, we can obtain the current-gain  $A_i$  as follows

$$A_i = \frac{i_o}{i_i} = \frac{v_o/R_S}{v_i/R_i} = \frac{R_i}{R_S} \frac{v_o}{v_i}$$

$$= \frac{R_i}{R_S} A_v$$

### Output Resistance

 

Output resistance, i.e., Thévenin equivalent resistance,  $R_o$  is calculated using the test voltage circuit above.

$$R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_{gs}=0, R_L=v_{test}} = \frac{v_{test}}{R_S || r_{ds}} - g_m v_{gs}$$

$$= \frac{v_{test}}{R_S || r_{ds}} + g_m v_{test} \quad \dots v_{test} = -v_{gs}$$

$$= \frac{v_{test}}{R_S || r_{ds}} + \frac{v_{test}}{1/g_m}$$


$$= R_S || r_{ds} || \frac{1}{g_m}$$

■ If  $(R_S || r_{ds}) \geq 10/g_m$ , output resistance  $R_o$  reduces to


$$R_o \cong \frac{1}{g_m}$$
 
### CS Drain Feedback Configuration


Common-source drain feedback bias configuration is given below



 Corresponding SSAC equivalent circuit is shown below



### Input Resistance

 


Input resistance  $R_i$  is given as

$$R_i = \left. \frac{v_i}{i_i} \right|_{R_L=\infty} = \frac{v_{gs}}{g_m v_{gs} + v_o / (R_D || r_{ds})} \quad \dots v_i = v_{gs}$$

$$= \frac{R_F + R_D || r_{ds}}{1 + g_m (R_D || r_{ds})} \quad \dots v_o = \frac{(1 - g_m R_F) (R_D || r_{ds}) v_{gs}}{R_F + R_D || r_{ds}}$$

$$\cong \frac{R_F}{1 + g_m (R_D || r_{ds})} \quad \dots R_F \gg R_D || r_{ds}$$

### Voltage Gain

 

No-load voltage gain  $A_v$  is given by

$$A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = \frac{(1 - g_m R_F) (R_D || r_{ds})}{R_F + R_D || r_{ds}} \quad \dots v_i = v_{gs}$$


$$\cong -g_m (R_D || r_{ds}) || R_F \quad \dots g_m R_F \gg 1$$

■ For the circuit above, we can obtain the current-gain  $A_i$  as follows

$$A_i = \frac{i_o}{i_i} = \frac{v_o/R_D}{v_i/R_i} = \frac{R_i}{R_D} \frac{v_o}{v_i}$$

$$= \frac{R_i}{R_D} A_v$$

### Output Resistance

 


Output resistance, i.e., Thévenin equivalent resistance,  $R_o$  is calculated using the test voltage circuit above. Note that in the circuit  $v_{gs} = 0$ , so  $g_m v_{gs} = 0$  as well.

$$R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}} = R_D || r_{ds} || R_F$$


- If a voltage source with source resistance  $R_s$  is connected to the input, replace  $R_F$  with  $[(R_F + R_s) / (1 + g_m R_s)]$  in  $R_o$  calculations.

### Common-Gate Configuration


Common-gate configuration is given below

 

 Corresponding SSAC equivalent circuit is shown below



### Input Resistance

 

Input resistance  $R_i$  is given as


$$R_i = \left. \frac{v_i}{i_i} \right|_{R_L=\infty} = \frac{v_i}{v_i/R_S - i_d} \quad \dots v_i = -v_{gs}$$

$$= \frac{v_i}{v_i/R_S + v_i / \left( \frac{R_D + r_{ds}}{\mu + 1} \right)} \quad \dots i_d = \frac{(\mu + 1) v_{gs}}{R_D + r_{ds}}$$

$$= R_S || \frac{R_D + r_{ds}}{1 + g_m r_{ds}} \quad \dots \mu = g_m r_{ds}$$

$$\cong R_S || \frac{1}{g_m} \quad \dots r_{ds} \geq 10R_D \text{ and } g_m r_{ds} \gg 1$$

### Voltage Gain

 


No-load voltage gain  $A_v$  is given by

$$A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = \frac{-i_d R_D}{-v_{gs}} \quad \dots v_i = -v_{gs}$$

$$= \frac{(\mu + 1) R_D}{R_D + r_{ds}} \quad \dots i_d = \frac{(\mu + 1) v_{gs}}{R_D + r_{ds}}$$

$$= \frac{(g_m r_{ds} + 1) R_D}{R_D + r_{ds}} \quad \dots \mu = g_m r_{ds}$$
 
$$\cong g_m R_D \quad \dots r_{ds} \geq 10R_D \text{ and } g_m r_{ds} \gg 1$$



■ For the circuit above, we can obtain the current-gain  $A_i$  as follows


$$A_i = \frac{i_o}{i_i} = \frac{v_o/R_D}{v_i/R_i} = \frac{R_i}{R_D} \frac{v_o}{v_i}$$

$$= \frac{R_i}{R_D} A_v$$

■ If  $r_{ds} \geq 10R_D$  and  $g_m r_{ds} \gg 1$ , current-gain  $A_i$  reduces to

$$A_i = g_m \left( R_S || \frac{1}{g_m} \right) \approx 1$$

### Output Resistance

 

Output resistance, i.e., Thévenin equivalent resistance,  $R_o$  is calculated using the test voltage circuit above. Note that in the circuit  $v_{gs} = 0$ , so  $g_m v_{gs} = 0$  as well.

$$R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}} = R_D || r_{ds}$$

- If  $r_{ds} \geq 10R_D$ , then  $R_o$  simplifies to  $R_o = R_D$ .
- If a voltage source with source resistance  $R_s$  is connected to the input, replace  $r_{ds}$  with  $([1 + g_m (R_s || R_G)] r_{ds} + R_s || R_G)$  in  $R_o$  calculations. We can say that  $R_o \approx R_D$  in most cases.