

ELE 230 Electronics I

Hacettepe University

Dr. Umut Sezen
Dr. Dinçer Gökçen

27 May 2018

1. These lecture notes are complete and regularly updated at the address below:
<http://www.ee.hacettepe.edu.tr/~usezen/ele230/>.
2. These lecture notes use material from several other sources like Prof. Selçuk Geçim's lecture notes, "Electronic Devices and Circuit Theory, 11th ed." by Boylestad and Nashelsky and its instructor materials.

Contents

List of Figures	xvi
List of Examples	xviii
List of Homeworks	xix
Textbook	xx
1 Semiconductor Diodes	1
1.1 Circuit Symbol	1
1.2 Ideal Diode Model	1
1.2.1 Determining State of an Ideal Diode	3
1.3 <i>p-n</i> Junction Diodes	4
1.3.1 No Bias Condition	5
1.3.2 Reverse Bias Condition	6
1.3.3 Forward Bias Condition	7
1.3.4 Diode Characteristic Equation	8
1.3.5 Zener Region (or Avalanche Breakdown Region)	10
1.3.6 Peak Inverse Voltage (PIV) Rating	11
1.3.7 Forward Bias Turn-On Voltage ($V_{D(ON)}$)	11
1.3.8 Temperature Effects	12
1.3.9 Load Line and Operating Point (<i>Q</i> -point)	12
1.3.10 DC Resistance (Static Resistance)	14
1.3.11 AC Resistance (Dynamic Resistance)	15
1.3.12 DC and Small-Signal AC (SSAC) Analysis	16
1.3.13 Average AC Resistance	18
1.4 Piecewise-Linear Diode Model	19
1.5 Simplified Diode Model	19
1.5.1 Determining State of a Diode	20
1.6 Diode Specification Sheets	23
1.6.1 Semiconductor Notation	24
1.6.2 Capacitance	25
1.7 Other Types of Diodes	26
1.8 Zener Diode	26
1.9 Light Emitting Diode (LED)	27

2	Diode Applications	28
2.1	Clippers	28
2.1.1	Parallel Clippers	31
2.2	Clampers	33
2.3	Voltage Multiplier Circuits	37
2.3.1	Peak Rectifier	37
2.3.2	Voltage Doubler	38
2.3.3	Voltage Tripler and Quadrupler	39
2.4	Zener Diode	40
2.4.1	Zener Regulator	40
2.4.2	Other Zener Diode Regulators	42
2.4.3	Zener Diode Parameters	42
2.5	Practical Applications of Diode Circuits	43
3	Rectifiers and Voltage Regulating Filters	44
3.1	Properties of Electrical Signals	44
3.1.1	DC Component (Average Value) and AC Component	44
3.1.2	Effective Value (RMS Value)	47
3.2	Half-Wave Rectifier	52
3.3	Full-Wave Rectifier	53
3.3.1	Center-Tapped Transformer Full-Wave Rectifier	54
3.3.2	Full-Wave Bridge Rectifier	55
3.4	Rectifier Summary	57
3.5	Voltage Regulation and Ripple Factor	58
3.5.1	Voltage Regulation	58
3.5.2	Ripple Factor	59
3.6	Capacitor Filter	60
3.6.1	Ripple Factor of Capacitor Filter	62
3.6.2	Diode Conduction Period and Peak Diode Current	64
3.7	Additional RC Filter	66
3.7.1	DC Operation	67
3.7.2	AC Operation	67
3.8	π -Filter	70
4	Bipolar Junction Transistor (BJT)	72
4.1	Bipolar Junction Transistor	72
4.2	Common-Base Configuration	74
4.2.1	Input and Output Characteristics	75
4.2.2	Three Modes of Operation	76
4.2.3	Currents	77
4.2.4	Alpha (α)	77
4.2.5	Simplification (Active Mode)	78
4.2.6	AC Amplification	79
4.3	Common-Emitter Configuration	80
4.3.1	Input and Output Characteristics	80
4.3.2	Currents	81

4.3.3	Beta (β)	82
4.3.3.1	Determining β from a graph	82
4.3.4	Relationship between β and α	83
4.3.5	Simplification (Active Mode)	83
4.4	Common-Collector Configuration	83
4.5	Operating Limits	84
4.6	Simplified BJT Model	85
5	DC Biasing of BJTs	87
5.1	DC Biasing	87
5.2	Three States of Operation	88
5.3	BJT DC Analysis	88
5.4	DC Biasing Circuits	89
5.4.1	Fixed-Bias Circuit	89
5.4.1.1	Base-Emitter Loop	90
5.4.1.2	Collector-Emitter Loop	90
5.4.1.3	Saturation	91
5.4.1.4	DC Load Line	92
5.4.2	Emitter-Stabilized Bias Circuit	96
5.4.2.1	Base-Emitter Loop	96
5.4.2.2	Collector-Emitter Loop	98
5.4.2.3	DC Load Line	98
5.4.2.4	Improved Biased Stability	99
5.4.3	Voltage Divider Bias Circuit	100
5.4.3.1	Base-Emitter Loop (Exact Analysis)	101
5.4.3.2	Base-Emitter Loop (Approximate Analysis)	102
5.4.3.3	Collector-Emitter Loop and DC Load line	103
5.4.4	Collector Feedback Bias Circuit	104
5.4.4.1	Base-Emitter Loop	104
5.4.4.2	Collector-Emitter Loop	105
5.4.4.3	DC Load line	106
5.4.5	Various Different Bias Circuits	106
5.4.6	<i>pnp</i> Transistors	107
5.5	Bias Stabilization	107
5.5.1	Stability Factors	108
5.5.1.1	Derivation of Stability Factors (Voltage-Divider Bias Circuit)	109
5.5.1.2	Stability Factors for Other Bias Circuits	110
5.5.2	Stability of Transistor Circuits with Active Components	112
5.6	Practical Applications	114
5.6.1	Relay Driver	114
5.6.2	Transistor Switch	114
5.6.3	Transistor Switching Networks	115
5.6.4	Logic Gates	117
5.6.5	Current Mirror	117
5.6.6	Voltage Level Indicator	118

6	AC-DC Load Lines of BJT Circuits	119
6.1	BJT AC Analysis	119
6.1.1	DC Load Line	120
6.1.2	Distortion	121
6.1.3	AC Load Line	122
6.1.4	AC-DC Load Lines	123
6.1.4.1	Maximum Symmetric Undistorted Swing Design	124
6.1.4.2	Other Amplifier Configurations	125
7	Field Effect Transistors (FETs)	131
7.1	Similarities and Differences with BJTs	131
7.2	FET Types	132
7.3	FET Operation	132
7.4	Junction Field-Effect Transistor (JFET)	133
7.4.1	Construction	133
7.4.2	Operating Characteristics	133
7.4.2.1	$V_{GS} = 0$ and $V_{DS} > 0$	134
7.4.2.2	$V_{GS} < 0$ and $V_{DS} > 0$	135
7.4.2.3	Voltage-Controlled Resistor (Ohmic Region)	136
7.4.3	p -channel JFET	137
7.4.3.1	Characteristics	137
7.4.4	Circuit Symbol	138
7.4.5	Transfer Characteristics	138
7.5	Metal-Oxide-Semiconductor Field-Effect Transistors (MOSFETs)	140
7.5.1	Depletion-Type MOSFET (DMOSFET)	140
7.5.1.1	Construction	140
7.5.1.2	Operating Characteristics	141
7.5.1.3	Transfer Characteristics	142
7.5.1.4	p -channel DMOSFET	143
7.5.2	Circuit Symbol	143
7.5.3	Enhancement-Type MOSFET (EMOSFET)	144
7.5.3.1	Construction	144
7.5.3.2	Transfer Characteristics	145
7.5.3.3	p -channel EMOSFET	146
7.5.4	Circuit Symbol	146
7.5.5	MOSFET Handling	147
7.6	Summary	147
8	DC Biasing of FETs	150
8.1	DC Biasing	150
8.2	FET DC Analysis	150
8.3	DC Biasing Circuits	150
8.3.1	Fixed-Bias Configuration	151
8.3.1.1	Gate-Source Loop	152
8.3.1.2	Drain-Source Loop	153
8.3.2	Self-Bias Configuration	153

8.3.2.1	Gate-Source Loop	154
8.3.2.2	Drain-Source Loop	155
8.3.3	Voltage-Divider Bias Configuration	157
8.3.3.1	Gate-Source Loop	158
8.3.3.2	Drain-Source Loop	159
8.3.4	Voltage-Feedback Bias Configuration	163
8.3.4.1	Gate-Source Loop	164
8.3.4.2	Drain-Source Loop	165
8.3.5	<i>p</i> -channel FETs	166
8.4	Practical Applications	168
8.5	Summary	168
9	AC-DC Load Lines of FET Circuits	170
9.1	FET AC Analysis	170
9.1.1	AC and DC Load Lines	170
9.1.2	Maximum Symmetric Undistorted Swing Design	171
9.1.3	Other Amplifier Configurations	172
10	BJT Small-Signal Analysis	173
10.1	Purpose of SSAC Analysis	173
10.1.1	BJT SSAC Analysis Steps	174
10.2	BJT Small-Signal Models	175
10.2.1	Hybrid Equivalent Model	175
10.2.1.1	Simplified Hybrid Equivalent Model	176
10.2.1.2	Common-Emitter Hybrid Equivalent Model	177
10.2.1.3	Common-Emitter r_e Model	178
10.2.1.4	Common-Base Hybrid Equivalent Model	178
10.2.1.5	Common-Base r_e Model	179
10.2.1.6	Phase Relationship	180
10.3	Common-Emitter Fixed-Bias Configuration	180
10.3.1	Input Resistance	182
10.3.2	Voltage Gain	182
10.3.3	Output Resistance	183
10.3.4	Phase Relationship	183
10.4	Common-Emitter Voltage-Divider Bias Configuration	184
10.4.1	Input Resistance	184
10.4.2	Voltage Gain	185
10.4.3	Output Resistance	185
10.4.4	Phase Relationship	186
10.5	Common-Emitter Unbypassed-Emitter Bias Configuration	186
10.5.1	Input Resistance	187
10.5.2	Voltage Gain	187
10.5.3	Output Resistance	188
10.5.4	Phase Relationship	189
10.6	Emitter-Follower Configuration	189
10.6.1	Input Resistance	190

10.6.2	Voltage Gain	190
10.6.3	Output Resistance	191
10.6.4	Phase Relationship	192
10.7	Common-Emitter Collector Feedback Configuration	192
10.7.1	Input Resistance	193
10.7.2	Voltage Gain	193
10.7.3	Output Resistance	194
10.7.4	Phase Relationship	194
10.8	Common-Base Configuration	194
10.8.1	Input Resistance	195
10.8.2	Voltage Gain	195
10.8.3	Output Resistance	196
10.8.4	Phase Relationship	196
11	FET Small-Signal Analysis	201
11.0.1	FET SSAC Analysis Steps	201
11.1	FET Small-Signal Model	201
11.1.0.1	Transconductance Parameter (g_m)	203
11.1.0.2	Phase Relationship	204
11.2	Common-Source Fixed-Bias Configuration	204
11.2.1	Input Resistance	205
11.2.2	Voltage Gain	205
11.2.3	Output Resistance	205
11.3	Common-Source Self-Bias Configuration	206
11.3.1	Input Resistance	207
11.3.2	Voltage Gain	207
11.3.3	Output Resistance	207
11.4	Common-Source Voltage-Divider Bias Configuration	208
11.4.1	Input Resistance	209
11.4.2	Voltage Gain	209
11.4.3	Output Resistance	209
11.5	Common-Source Unbypassed Self-Bias Configuration	210
11.5.1	Input Resistance	211
11.5.2	Voltage Gain	211
11.5.3	Output Resistance	212
11.6	Source-Follower Configuration	212
11.6.1	Input Resistance	213
11.6.2	Voltage Gain	213
11.6.3	Output Resistance	214
11.7	Common-Source Drain Feedback Configuration	215
11.7.1	Input Resistance	215
11.7.2	Voltage Gain	216
11.7.3	Output Resistance	216
11.8	Common-Gate Configuration	217
11.8.1	Input Resistance	217
11.8.2	Voltage Gain	218

11.8.3	Output Resistance	218
12	Frequency Response of Amplifiers	220
12.1	First-Order RC Filters	220
12.1.1	First-Order Highpass RC Filter	220
12.1.1.1	Cutoff Frequency	221
12.1.1.2	Bode Plot	222
12.1.1.3	Decibels (dB)	222
12.1.2	First-Order Lowpass RC Filter	224
12.1.2.1	Cutoff Frequency	225
12.1.2.2	Bode Plot	226
12.2	Typical Frequency Response	227
12.3	Low Frequency Response	229
12.3.1	BJT Amplifiers	229
12.3.1.1	Effect of Coupling Capacitor C_1	230
12.3.1.2	Effect of Coupling Capacitor C_2	230
12.3.1.3	Effect of Bypass Capacitor C_3	231
12.3.1.4	Combined Effect of C_1 , C_2 and C_3	231
12.3.2	FET Amplifiers	232
12.3.2.1	Effect of Coupling Capacitor C_1	233
12.3.2.2	Effect of Coupling Capacitor C_2	233
12.3.2.3	Effect of Bypass Capacitor C_3	234
12.3.2.4	Combined Effect of C_1 , C_2 and C_3	234
12.4	Miller Effect	235
12.4.0.1	Miller Input Capacitance C_{M_i}	235
12.4.0.2	Miller Output Capacitance C_{M_o}	236
12.4.0.3	Miller Representation	237
12.5	High Frequency Response	238
12.5.1	BJT Amplifiers	238
12.5.1.1	Input Circuit Cutoff Frequency f_{H_1}	238
12.5.1.2	Output Circuit Cutoff Frequency f_{H_2}	239
12.5.1.3	h_{fe} (or β) Variation Cutoff Frequency f_β	239
12.5.1.4	Combined Effect of f_{H_1} , f_{H_2} and f_β	240
12.5.2	FET Amplifiers	241
12.5.2.1	Input Circuit Cutoff Frequency f_{H_1}	242
12.5.2.2	Output Circuit Cutoff Frequency f_{H_2}	242
12.5.2.3	Combined Effect of f_{H_1} and f_{H_2}	243
12.6	Gain-Bandwidth Product	243
13	Multistage (Cascaded) Amplifiers	244
13.1	Cascaded Systems	244
13.2	AC-Coupled Multistage Amplifiers	246
13.3	DC-Coupled Multistage Amplifiers	248
13.4	Cascode Amplifier	254
13.5	Darlington Pair	256
13.6	Feedback Pair	257

List of Figures

1.1	Diode circuit symbol.	1
1.2	Ideal diode is short circuit when it is forward biased.	2
1.3	Ideal diode is open circuit when it is reverse biased.	2
1.4	Characteristics curve of the ideal diode.	2
1.5	Diode circuit for Example 1.1.	3
1.6	A p - n junction.	4
1.7	Depletion layer in a p - n junction.	5
1.8	p - n junction under no bias.	5
1.9	Diode behaviour under no bias.	6
1.10	p - n junction under reverse bias.	6
1.11	Diode behaviour under reverse bias.	7
1.12	p - n junction under forward bias.	7
1.13	Diode behaviour under forward bias.	8
1.14	Diode characteristics curve	8
1.15	Zener region (or avalanche breakdown region)	10
1.16	Change of diode characteristics with temperature	12
1.17	Series diode configuration: (a) circuit, (b) diode characteristics curve.	12
1.18	Drawing the load line and finding the point of operation.	13
1.19	Determining the DC resistance of a diode at a particular operating point.	14
1.20	Defining the dynamic or AC resistance around an operating point	15
1.21	Diode circuit with AC and DC sources.	16
1.22	DC equivalent circuit of the circuit in Figure 1.21.	17
1.23	SSAC equivalent circuit of the circuit in Figure 1.21.	17
1.24	Determining the average AC resistance between indicated limits.	18
1.25	Piecewise-linear characteristics curve (blue line on the left) and piecewise-linear equivalent circuit (on the right) of the diode.	19
1.26	Simplified characteristics curve (on the left) and simplified equivalent circuit (on the right) of the diode.	19
1.27	Diode circuit for Example 1.2.	21
1.28	Simplified circuit for the diode circuit in Figure 1.27.	21
1.29	Diode circuit for Example 1.3.	22
1.30	Simplified circuit for the diode circuit in Figure 1.29.	22
1.31	Diode circuit for Example 1.4.	23
1.32	Semiconductor diode notation.	24
1.33	Some diode types and packagings.	25
1.34	Transition and diffusion capacitance versus applied bias for a Silicon diode.	25

1.35	Zener diode symbol.	26
1.36	Circuit symbol of an LED.	27
1.37	Litronix 7-segment LED display	27
1.38	Relative intensity versus wavelength.	27
2.1	A series clipper circuit.	28
2.2	Voltage transfer characteristics (VTC) curve of the series clipper circuit Figure 2.1.	29
2.3	Positive half-cycle operation of the series clipper circuit in Figure 2.1.	29
2.4	Negative half-cycle operation of the series clipper circuit in Figure 2.1.	29
2.5	A series clipper circuit with a DC supply.	30
2.6	Input and output of the series clipper circuit in Figure 2.5.	30
2.7	Various series clipper examples (diodes are ideal).	31
2.8	A parallel clipper circuit.	31
2.9	Sample input and output waveforms of the parallel clipper circuit in Figure 2.8.	32
2.10	A parallel clipper circuit with a DC supply.	32
2.11	A diode limiter circuit.	32
2.12	Outputs of the circuit in Figure 2.11: (a) VTC diagram, (b) output waveform.	33
2.13	Various parallel clipper examples (diodes are ideal).	33
2.14	A clamper circuit.	34
2.15	Charging operation of the clamper circuit in Figure 2.14.	35
2.16	Discharging operation of the clamper circuit in Figure 2.14.	35
2.17	A clamper circuit with a square wave input.	36
2.18	Output of the circuit given in Figure 2.17.	36
2.19	A clamper circuit with a sinusoidal input.	36
2.20	Output of the circuit given in Figure 2.19.	37
2.21	Various clamper examples (diodes are ideal and capacitors are charged).	37
2.22	A peak rectifier circuit.	38
2.23	For the circuit in Figure 2.22: (a) input waveform, (b) output waveform.	38
2.24	Voltage doubler circuit.	39
2.25	Operation of the circuit in Figure 2.24 at (a) first positive half-cycle, and (b) first negative half-cycle.	39
2.26	Voltage tripler/quadrupler circuit.	39
2.27	Zener diode operation: (a) ON (b) OFF.	40
2.28	A general Zener diode circuit.	40
2.29	Zener diode circuit for Example 2.9.	41
2.30	Single Zener diode clipper.	42
2.31	Dual Zener diode clipper.	42
3.1	Ideal half-wave rectifier output of a sinusoidal input $v_i(t) = V_m \sin(2\pi t/T)$	45
3.2	Ideal full-wave rectifier output of a sinusoidal input $v_i(t) = V_m \sin(2\pi t/T)$	45
3.3	Triangular waveform.	46
3.4	AC component of the triangular waveform in Figure 3.3.	47
3.5	Triangular waveform and its analytical expression.	49
3.6	A half-wave rectifier circuit.	52
3.7	Input and ideal output waveforms for the half-wave rectifier given in Figure 3.6.	52
3.8	Input and output waveforms for the half-wave rectifier when $V_{D(ON)} = 0.7 \text{ V}$	53

3.9	Input and ideal output waveforms of the full-wave rectifier.	53
3.10	Center-tapped transformer full-wave rectifier.	54
3.11	Positive half-cycle operation of the center-tapped transformer full-wave rectifier in Figure 3.10.	55
3.12	Negative half-cycle operation of the center-tapped transformer full-wave rectifier in Figure 3.10.	55
3.13	Full-wave bridge rectifier.	56
3.14	Positive half-cycle operation of the full-wave bridge rectifier in Figure 3.13.	56
3.15	Negative half-cycle operation of the full-wave bridge rectifier in Figure 3.13.	56
3.16	Positive-half cycle operation and full output of the full-wave bridge rectifier when $V_{D(ON)} = 0.7\text{ V}$	57
3.17	Block diagram showing parts of a power supply.	58
3.18	Filter voltage waveform showing DC and ripple voltages.	59
3.19	Simple capacitor filter.	60
3.20	Capacitor filter after a center-tapped transformer full-wave rectifier.	60
3.21	Capacitor filter operation: (a) ideal full-wave rectifier output, (b) filtered output voltage.	60
3.22	Capacitor filter output after a full-wave rectifier: (a) actual output, (b) approximate output where ripple waveform is approximated by a triangular waveform.	61
3.23	Capacitor filter output (after a full-wave rectifier) with charging and discharging timings.	62
3.24	Capacitor filter output voltage and diode current waveforms for a half-wave rectifier: (a) small C , (b) large C	64
3.25	Capacitor filter circuit for Example 3.15.	65
3.26	Additional RC filter stage.	66
3.27	Center-tapped transformer full-wave rectifier and RC filter circuit.	66
3.28	DC equivalent circuit of the additional RC filter stage in Figure 3.26.	67
3.29	AC equivalent circuit of the additional RC filter stage in Figure 3.26.	67
3.30	Capacitor filter circuit for Example 3.16.	68
3.31	Capacitor filter circuit for Example 3.17.	69
3.32	π -filter stage.	70
4.1	Types of transistors: (a) npn , (b) npn	72
4.2	Biasing a transistor: (a) base-emitter forward-biased, (b) base-collector reverse-biased.	73
4.3	Current flow in a properly biased npn transistor.	74
4.4	Notation and symbols used with the common-base configuration: (a) npn transistor, (b) npn transistor.	75
4.5	Characteristics of an npn common-base amplifier: a) Input characteristics, b) Output characteristics.	76
4.6	Output characteristics of a common-base amplifier.	76
4.7	Common-base cutoff current (or reverse saturation current), I_{CBO}	77
4.8	Simplified output characteristics of a common-base amplifier.	78
4.9	Simplified input characteristics of a common-base amplifier.	79
4.10	AC equivalent circuit of a common-base amplifier.	79
4.11	Notation and symbols used with the common-emitter configuration: (a) npn transistor, (b) npn transistor.	80
4.12	Characteristics of an npn common-emitter amplifier: a) Input characteristics, b) Output characteristics.	81

4.13	Common-emitter cutoff current, I_{CEO} .	81
4.14	Determining β_{DC} and β_{ac} from the output characteristics.	82
4.15	Notation and symbols used with the common-collector configuration: (a) <i>npn</i> transistor, (b) <i>pnp</i> transistor.	84
4.16	Defining the region of operation for a transistor.	84
4.17	An example BJT packaging.	85
4.18	States of the simplified <i>npn</i> BJT model: (a) Cutoff, (b) Active, (c) Saturation	86
5.1	Various operating points within the limits of operation of a BJT transistor.	87
5.2	Fixed-bias BJT circuit.	89
5.3	DC equivalent circuit of the fixed-bias circuit in Figure 5.2.	89
5.4	Base-emitter loop of the fixed-bias circuit in Figure 5.2.	90
5.5	Collector-emitter loop of the fixed-bias circuit in Figure 5.2.	90
5.6	Saturation regions: (a) actual, (b) approximate.	91
5.7	Determining $I_{C(sat)}$ for the fixed-bias configuration. Example 5.0.	92
5.8	Fixed-bias circuit for Example 5.1.	92
5.9	Load line of the fixed-bias circuit in Figure 5.2.	93
5.10	Movement of the Q -point with increasing level of I_B .	94
5.11	Effect of an increasing level of R_C on the load line and the Q -point.	94
5.12	Effect of lower values of V_{CC} on the load line and the Q -point.	95
5.13	Fixed-bias load line for Example 5.2.	95
5.14	Emitter-stabilized bias circuit.	96
5.15	DC equivalent circuit of the emitter-stabilized bias circuit in Figure 5.14.	96
5.16	Base-emitter loop of the emitter-stabilized bias circuit in Figure 5.14: (a) normal circuit, (b) equivalent circuit for common base current.	97
5.17	Equivalent circuit for common emitter current for the base-emitter loop of the emitter-stabilized bias circuit in Figure 5.14.	97
5.18	Collector-emitter loop of the emitter-stabilized bias circuit in Figure 5.14.	98
5.19	Load line of the emitter-stabilized bias circuit in Figure 5.14.	99
5.20	Emitter-stabilized bias circuit for Example 5.3.	99
5.21	Voltage divider bias BJT circuit.	100
5.22	DC equivalent circuit of the voltage divider bias circuit in Figure 5.21.	101
5.23	Base-emitter loop of the voltage divider bias circuit in Figure 5.21: (a) normal circuit, (b) Thévenin equivalent circuit.	101
5.24	Thévenin analysis circuits for the circuit in Figure 5.23(a): (a) Open-circuit voltage calculation, (b) Test-voltage method for Thévenin resistance calculation.	102
5.25	Voltage-divider bias circuit for Example 5.4.	103
5.26	Collector feedback bias circuit.	104
5.27	DC equivalent circuit of the collector feedback circuit in Figure 5.26.	104
5.28	Base-emitter loop of the collector feedback circuit in Figure 5.26.	105
5.29	Collector-emitter loop of the collector feedback circuit in Figure 5.26.	105
5.30	Common-collector bias circuit for Example 5.5.	106
5.31	<i>pnp</i> transistor in a voltage-divider bias configuration Example 5.6.	107
5.32	Shift in operating point (Q -point) due to change in temperature: (a) 25 °C, (b) 100 °C.	108
5.33	Equivalent circuit for the voltage-divider configuration.	109
5.34	Active V_{BE} compensation using a reverse-biased diode at the emitter.	113

5.35	Active I_{CO} compensation replacing R_2 with a reverse-biased diode.	113
5.36	Active I_C compensation using a current mirror.	113
5.37	Relay driver in the absence of protective device.	114
5.38	Relay driver protected with a diode across the relay coil.	114
5.39	Using the BJT as a switch to control the on/off states of a bulb with a limiting resistor.	115
5.40	A BJT inverter circuit and its operation.	115
5.41	Load-line of the inverter circuit in Figure 5.40.	116
5.42	Defining the time intervals of a pulse waveform.	116
5.43	BJT logic OR gate.	117
5.44	BJT logic AND gate.	117
5.45	BJT logic OR gate.	118
5.46	Voltage level indicator.	118
6.1	A voltage-divider common-emitter BJT circuit.	119
6.2	DC and AC equivalent circuits of the common-emitter circuit in Figure 6.1: (a) DC equivalent circuit (b) AC equivalent circuit.	120
6.3	DC equivalent circuit of Figure 6.1.	120
6.4	Input and output swings around the Q -points: (a) input swing (b) output swing.	121
6.5	Distorted output swings: (a) incorrect Q -point (b) incorrect input (i.e., high input).	122
6.6	AC-equivalent circuit of Figure 6.1.	122
6.7	AC-DC load lines.	123
6.8	Maximum undistorted swing design with Q -point in the middle of the AC load line.	124
6.9	BJT amplifier circuit for Example 6.1.	126
6.10	AC-DC load-lines for Example 6.1.	127
6.11	BJT amplifier circuit for Example 6.2.	127
6.12	AC-DC load-lines for Example 6.2.	128
6.13	BJT amplifier circuit for Example 6.3.	129
6.14	AC-DC load-lines for Example 6.3.	130
7.1	BJT (npn) and FET (n -channel) comparison: (a) current-controlled device (BJT), (b) voltage-controlled device (FET).	132
7.2	Water analogy for the FET control mechanism.	132
7.3	n -channel junction field-effect transistor (JFET) construction.	133
7.4	JFET at $V_{GS} = 0\text{ V}$ and $V_{DS} > 0\text{ V}$: (a) DC biasing, (b) variation of the gate-channel junction reverse-bias voltages through the channel.	134
7.5	Pinch-off ($V_{GS} = 0\text{ V}$, $V_{DS} = -V_P$).	134
7.6	Output characteristics, i.e., I_D versus V_{DS} , for $V_{GS} = 0\text{ V}$	135
7.7	Output characteristics of an n -Channel JFET with $I_{DSS} = 8\text{ mA}$ and $V_P = -4\text{ V}$	136
7.8	p -Channel JFET biasing.	137
7.9	Output characteristics of an p -Channel JFET with $I_{DSS} = 6\text{ mA}$ and $V_P = +6\text{ V}$	138
7.10	JFET circuit symbols: (a) n -channel, (b) p -channel.	138
7.11	Transfer and output characteristics curves together for an n -channel JFET.	139
7.12	Scaled transfer characteristics curve.	139
7.13	n -channel depletion-type MOSFET construction.	140

7.14	Change in channel width (and depletion region) for a fixed value of V_{GS} (V_{GS} determines the initial channel width) with $V_{DS} > 0$	141
7.15	Increase (or enhancement) in initial channel width when $V_{GS} > 0$	142
7.16	Transfer and output characteristics curves together for an n -channel DMOSFET.	142
7.17	p -channel DMOSFET with $I_{DSS} = 6 \text{ mA}$ and $V_P = +6 \text{ V}$: (a) construction, (b) transfer characteristics, (c) output characteristics.	143
7.18	DMOSFET circuit symbols: (a) n -channel, (b) p -channel.	144
7.19	n -channel enhancement-type MOSFET construction.	144
7.20	Transfer and output characteristics curves together for an n -channel EMOSFET.	145
7.21	p -channel EMOSFET with $V_{GS(Th)} = 2 \text{ V}$ and $k = 0.5 \text{ mA/V}^2$: (a) construction, (b) transfer characteristics, (c) output characteristics.	146
7.22	EMOSFET circuit symbols: (a) n -channel, (b) p -channel.	147
7.23	n -channel FET summary.	148
7.24	Circuit behaviour of the n -channel FET model: (a) Cutoff state, (b) Saturation state	149
8.1	Fixed-bias JFET circuit.	151
8.2	DC equivalent circuit (with $I_G = 0$) of the fixed-bias configuration in Figure 8.1.	152
8.3	Graphical solution (for transfer load-line and transfer characteristics equations) for the fixed-bias configuration in Figure 8.1.	153
8.4	Self-bias JFET circuit.	154
8.5	DC equivalent circuit (with $I_G = 0$) of the self-bias configuration in Figure 8.4.	154
8.6	Graphical solution (for transfer load-line and transfer characteristics equations) for the self-bias configuration in Figure 8.4.	155
8.7	Self-bias JFET circuit for Example 8.1.	156
8.8	Obtaining I_{DQ} graphically for the circuit in Figure 8.7.	157
8.9	Voltage-divider bias JFET circuit.	157
8.10	DC equivalent circuit of the voltage-divider configuration in Figure 8.9.	158
8.11	Graphical solution (for transfer load-line and transfer characteristics equations) for the voltage-divider configuration in Figure 8.9.	158
8.12	Voltage-divider bias JFET circuit for Example 8.2.	159
8.13	Obtaining I_{DQ} graphically for the circuit in Figure 8.12.	160
8.14	Voltage-divider bias DMOSFET circuit for Example 8.3.	160
8.15	Obtaining I_{DQ} graphically for the circuit in Figure 8.14 with $R_S = 750 \Omega$	161
8.16	Obtaining I_{DQ} graphically for the circuit in Figure 8.14 with $R_S = 150 \Omega$	162
8.17	Voltage-divider bias EMOSFET circuit for Example 8.4.	162
8.18	Obtaining I_{DQ} graphically for the circuit in Figure 8.17.	163
8.19	Voltage-feedback bias EMOSFET circuit.	163
8.20	DC equivalent circuit (with $I_G = 0$) of the voltage-feedback configuration in Figure 8.19.	164
8.21	Graphical solution (for transfer load-line and transfer characteristics equations) for the voltage-feedback configuration in Figure 8.19.	164
8.22	Voltage-feedback bias EMOSFET circuit for Example 8.5.	165
8.23	Obtaining I_{DQ} graphically for the circuit in Figure 8.22.	166
8.24	Voltage-divider bias JFET circuit for Example 8.6.	167
8.25	Obtaining I_{DQ} graphically for the circuit in Figure 8.24.	167
8.26	n -channel JFET bias circuits.	168
8.27	n -channel MOSFET bias circuits.	169

9.1	AC-DC load lines for FETs.	171
9.2	Maximum undistorted swing design for FETs with Q -point in the middle of the AC load line.	172
10.1	Two-port voltage-gain amplifier model.	173
10.2	Complete hybrid equivalent circuit.	175
10.3	Common-emitter configuration and its complete hybrid equivalent circuit.	176
10.4	Common-base configuration and its complete hybrid equivalent circuit.	176
10.5	Simplified hybrid equivalent circuit.	176
10.6	Approximate hybrid equivalent circuit.	177
10.7	Common-emitter simplified hybrid equivalent circuit.	177
10.8	Common-emitter r_e model.	178
10.9	Common-base simplified hybrid equivalent circuit.	179
10.10	Common-base r_e model.	180
10.11	Common-emitter fixed-bias configuration.	181
10.12	AC equivalent circuit of the fixed-bias circuit in Figure 10.11.	181
10.13	Small-signal equivalent circuit of the fixed-bias circuit in Figure 10.11.	181
10.14	Test voltage circuit of Figure 10.13 in order to calculate the output resistance R_o	183
10.15	Demonstrating the 180° phase shift between input and output waveforms.	183
10.16	Common-emitter voltage-divider bias configuration.	184
10.17	Small-signal equivalent circuit of the voltage-divider bias circuit in Figure 10.16.	184
10.18	Test voltage circuit of Figure 10.17 in order to calculate the output resistance R_o	185
10.19	Common-emitter unbypassed-emitter bias configuration.	186
10.20	Small-signal equivalent circuit of the unbypassed-emitter bias circuit in Figure 10.19.	187
10.21	Test voltage circuit of Figure 10.20 in order to calculate the output resistance R_o	188
10.22	Emitter-follower configuration.	189
10.23	Small-signal equivalent circuit of the emitter-follower circuit in Figure 10.22.	190
10.24	Test voltage circuit of Figure 10.23 in order to calculate the output resistance R_o	191
10.25	Common-emitter collector feedback bias configuration.	192
10.26	Small-signal equivalent circuit of the collector feedback bias circuit in Figure 10.25.	192
10.27	Test voltage circuit of Figure 10.26 in order to calculate the output resistance R_o	194
10.28	Common-base configuration.	194
10.29	Small-signal equivalent circuit of the common-base circuit in Figure 10.28.	195
10.30	Test voltage circuit of Figure 10.29 in order to calculate the output resistance R_o	196
10.31	BJT amplifier circuit for Example 10.1.	197
10.32	DC equivalent circuit of Figure 10.31: (a) as it is (b) Thévenin applied.	197
10.33	Small-signal equivalent circuit of Figure 10.31.	198
10.34	AC-DC load-lines for Example 10.1 with input $v_s = 100 \sin(\omega t)$ mV.	199
10.35	AC-DC load-lines for Example 10.1 with input $v_s = 900 \sin(\omega t)$ mV.	200
11.1	FET small-signal equivalent circuit.	202
11.2	FET small-signal equivalent circuit with the voltage-controlled voltage source.	202
11.3	Graphical definition of the transconductance g_m	203
11.4	Common-source fixed-bias configuration.	204
11.5	Small-signal equivalent circuit of the fixed-bias circuit in Figure 11.4.	204
11.6	Test voltage circuit of Figure 11.5 in order to calculate the output resistance R_o	205

11.7	Common-source self-bias configuration.	206
11.8	Small-signal equivalent circuit of the self-bias circuit in Figure 11.7.	206
11.9	Test voltage circuit of Figure 11.8 in order to calculate the output resistance R_o	207
11.10	Common-source voltage-divider bias configuration.	208
11.11	Small-signal equivalent circuit of the voltage-divider bias circuit in Figure 11.10.	208
11.12	Test voltage circuit of Figure 11.11 in order to calculate the output resistance R_o	209
11.13	Common-source unbypassed self-bias configuration.	210
11.14	Small-signal equivalent circuit of the unbypassed self-bias circuit in Figure 11.13.	210
11.15	Test voltage circuit of Figure 11.14 in order to calculate the output resistance R_o	212
11.16	Source-follower configuration.	213
11.17	Small-signal equivalent circuit of the source-follower circuit in Figure 11.16.	213
11.18	Test voltage circuit of Figure 11.17 in order to calculate the output resistance R_o	214
11.19	Common-source drain feedback bias configuration.	215
11.20	Small-signal equivalent circuit of the drain feedback bias circuit in Figure 11.19.	215
11.21	Test voltage circuit of Figure 11.20 in order to calculate the output resistance R_o	216
11.22	Common-gate configuration.	217
11.23	Small-signal equivalent circuit of the common-gate circuit in Figure 11.22.	217
11.24	Test voltage circuit of Figure 11.23 in order to calculate the output resistance R_o	218
12.1	First order highpass RC filter.	220
12.2	Asymptotic Bode plot (scalar) of the first order highpass RC filter in Figure 12.1.	222
12.3	Asymptotic Bode plot (dB) of the first order highpass RC filter in Figure 12.1.	223
12.4	Magnitude (top) and phase (bottom) responses of the first order highpass RC filter in Figure 12.1.	224
12.5	First order lowpass RC filter.	225
12.6	Asymptotic Bode plot (dB) of the first order lowpass RC filter in Figure 12.5.	226
12.7	Magnitude (top) and phase (bottom) responses of the first order lowpass RC filter in Figure 12.5.	227
12.8	Typical magnitude response of a transistor amplifier.	228
12.9	Normalized scalar plot of the magnitude response given in Figure 12.8.	229
12.10	Normalized decibel plot of the magnitude response given in Figure 12.8.	229
12.11	A common-emitter voltage-divider bias BJT circuit.	230
12.12	Low-frequency plot for the circuit given in Figure 12.11.	232
12.13	A common-source self-bias JFET circuit.	233
12.14	Low-frequency plot for the circuit given in Figure 12.13.	235
12.15	Circuit employed in the derivation of an equation for the Miller input capacitance C_{M_i} , where $A_v < 0$	236
12.16	Circuit employed in the derivation of an equation for the Miller output capacitance C_{M_o} , where $A_v < 0$	237
12.17	Miller representation of the feedback capacitance in negative gain amplifiers.	238
12.18	A common-emitter voltage-divider bias BJT circuit with the capacitors that affect the high-frequency response.	238
12.19	h_{fe} and h_{fb} versus frequency in the high-frequency region.	240
12.20	Normalized magnitude response (normalized gain vs. frequency) for the circuit given in Figure 12.18.	241

12.21	A common-source self-bias JFET circuit with the capacitors that affect the high-frequency response.	242
13.1	A cascaded (or multistage) system.	244
13.2	Overall representation of the system as a single voltage-gain amplifier.	244
13.3	A two-stage cascaded system for Example 13.1.	245
13.4	An AC-coupled two-stage FET amplifier for Example 13.2.	246
13.5	An AC-coupled two-stage BJT amplifier for Example 13.3.	247
13.6	An AC-coupled two-stage BJT amplifier for Example 13.4.	248
13.7	A DC-coupled two-stage BJT amplifier for Example 13.5.	249
13.8	AC-DC load-line for the first transistor in Example 13.5.	250
13.9	AC-DC load-line for the second transistor in Example 13.5.	251
13.10	A DC-coupled two-stage BJT amplifier for Example 13.6.	252
13.11	A DC-coupled two-stage BJT amplifier for Example 13.7.	253
13.12	A cascode configuration.	254
13.13	A cascode amplifier circuit for Example 13.8.	255
13.14	SSAC equivalent circuit for Example 13.8.	256
13.15	Darlington combination.	256
13.16	Single <i>nnp</i> transistor representation of the Darlington pair.	257
13.17	Feedback pair connection.	257
13.18	Single <i>pnp</i> transistor representation of the feedback pair.	258

List of Examples

Example 1.1	(Diode Example 1)	3
Example 1.2	(Diode Example 2)	20
Example 1.3	(Diode Example 3)	21
Example 1.4	(Diode Example 4)	22
Example 2.1	(Series Clipper with a DC source)	30
Example 2.2	(Various Series Clippers)	31
Example 2.3	(Parallel Clipper with a DC source)	32
Example 2.4	(Diode Limiter or Dual-Diode Parallel Clipper)	32
Example 2.5	(Various Parallel Clippers)	33
Example 2.6	(Clamper Example 1)	35
Example 2.7	(Clamper Example 2)	36
Example 2.8	(Various Clampers)	37
Example 2.9	(Zener Regulator)	41
Example 3.1	(DC Component of Half-Wave Rectifier Output)	45
Example 3.2	(DC Component of Full-Wave Rectifier Output)	45
Example 3.3	(DC Component of Triangular Waveform)	46
Example 3.4	(AC Component of Triangular Waveform)	46
Example 3.5	(RMS value of an AC+DC signal)	48
Example 3.6	(RMS value of Triangular Waveform)	49
Example 3.7	(RMS value of Half-Wave Rectifier Output)	50
Example 3.8	(RMS value of Full-Wave Rectifier Output)	50
Example 3.9	(RMS value of AC component - Triangular Waveform)	50
Example 3.10	(RMS value of AC component - Half-wave Rectifier Output)	51
Example 3.11	(RMS value of AC component - Full-wave Rectifier Output)	51
Example 3.12	(Voltage Regulation)	58
Example 3.13	(Ripple Factor of Half-Wave Rectifier Output)	59

Example 3.14	(Ripple Factor of Full-Wave Rectifier Output)	59
Example 3.15	(Capacitor Filter)	65
Example 3.16	(RC Filter Example 1)	68
Example 3.17	(RC Filter Example 2)	69
Example 3.18	(π Filter)	70
Example 4.1	(Amplification in Common-Base Configuration)	79
Example 4.2	(Determining β)	82
Example 5.1	(Fixed-Bias BJT Circuit)	92
Example 5.2	(Fixed-Bias Load Line)	95
Example 5.3	(Emitter-Stabilized Bias BJT Circuit)	99
Example 5.4	(Voltage-Divider Bias BJT Circuit)	103
Example 5.5	(Common-Collector Bias Circuit)	106
Example 5.6	(Voltage-Divider Bias <i>pnp</i> Circuit)	107
Example 5.7	(Bias Stabilization)	111
Example 6.1	(AC-DC Load Lines Example 1)	126
Example 6.2	(AC-DC Load Lines Example 2)	127
Example 6.3	(AC-DC Load Lines Example 3)	129
Example 8.1	(Self-Bias JFET Circuit)	156
Example 8.2	(Voltage-Divider JFET Circuit)	159
Example 8.3	(Voltage-Divider DMOSFET Circuit)	160
Example 8.4	(Voltage-Divider EMOSFET Circuit)	162
Example 8.5	(Voltage-Feedback EMOSFET Circuit)	165
Example 8.6	(<i>p</i> -channel JFET Circuit)	166
Example 10.1	(Small-Signal Common-Base Example)	197
Example 13.1	(Two-stage Cascaded System)	245
Example 13.2	(AC-Coupled FET Amplifier)	246
Example 13.3	(AC-Coupled BJT Amplifier 1)	247
Example 13.4	(AC-Coupled BJT Amplifier 2)	248
Example 13.5	(DC-Coupled BJT Amplifier 1)	249
Example 13.6	(DC-Coupled BJT Amplifier 2)	252
Example 13.7	(DC-Coupled BJT Amplifier 3)	253
Example 13.8	(Cascode Amplifier)	255

List of Homeworks

Homework 1.1	(Diodes)	23
Homework 2.1	(Parallel Clipper 1)	32
Homework 2.2	(Parallel Clipper 2)	32
Homework 3.1	(Full-Wave Rectifiers)	57
Homework 5.1	(Current Mirror)	118
Homework 6.1	(AC-DC Load Lines)	123
Homework 7.1	(MOSFET)	145
Homework 13.1	(Two-Stage Cascaded System)	246
Homework 13.2	(AC-Coupled BJT Amplifier)	248
Homework 13.3	(DC-Coupled BJT Amplifier 1)	252
Homework 13.4	(DC-Coupled BJT Amplifier 2)	253
Homework 13.5	(Cascode Amplifier)	256
Homework 13.6	(Darlington Pair)	257
Homework 13.7	(Feedback Pair)	258

Textbook

Textbooks:

1. Boylestad and Nashelsky, *Electronic Devices and Circuit Theory*, Prentice Hall, 11th ed, 2012.
2. Sedra and Smith, *Microelectronic Circuits*, Oxford Press, 2009 (6th ed.)

Supplementary books:

1. Millman and Halkias, *Integrated Electronics*, McGraw-Hill.
2. Horowitz and Hill, *The Art of Electronics*, Cambridge, 3rd ed.

Chapter 1

Semiconductor Diodes

1.1 Circuit Symbol

Diode is a nonlinear two-terminal device whose circuit symbol is like an arrowhead shown in Figure 1.1 below.

 


Figure 1.1: Diode circuit symbol.

- Voltage across the diode, V_D , is normally defined as the voltage difference between back end of the arrowhead and front end of the arrowhead (voltage difference between terminal A and terminal B), i.e.,

$$\boxed{V_D = V_A - V_B} \quad (1.1.1)$$

- Current through the diode, I_D , is defined in the direction of the arrowhead (flowing from terminal A to terminal B), i.e.,

$$\boxed{I_D = I_{AB}} \quad (1.1.2)$$

- Diode is called **forward biased** (FB) when $V_A \geq V_B$, i.e., $V_D \geq 0$, and called **reverse biased** (RB) when $V_A < V_B$, i.e., $V_D < 0$.

1.2 Ideal Diode Model

Ideally diode conducts current in only one direction and blocks current in the opposite direction. Thus,

- Ideal diode is **short circuit** (i.e., ON) when it is **forward biased**.

 


Figure 1.2: Ideal diode is short circuit when it is forward biased.

and **open circuit** (i.e., OFF) when it is **reverse biased**.

 


Figure 1.3: Ideal diode is open circuit when it is reverse biased.

Consequently, characteristics curve of the ideal diode is given by

 


Figure 1.4: Characteristics curve of the ideal diode.

We can summarize the ideal diode with its state and circuit behaviour with

$$\text{Ideal diode state} = \begin{cases} ON, & \text{if } V_D \geq 0 \\ OFF, & \text{if } V_D < 0 \end{cases} \quad (1.2.3)$$

and

Ideal Diode Model		
State	Circuit Behaviour	Test Condition
ON	$V_D = 0$	$I_D \geq 0$
OFF	$I_D = 0$	$V_D < 0$

If you make a **wrong assumption** about the state of the diode, then you will find that the **test condition will fail** (once you calculate the circuit voltage and currents).

- For example, if you have assumed the diode to be ON while it should be OFF, then you will find $I_D < 0$, failing the test condition.
- Similarly, if you have assumed the diode to be OFF while it should be ON, then you will find $V_D \geq 0$, failing the test condition.

1.2.1 Determining State of an Ideal Diode

Using circuit behaviour and the test condition for the OFF state, let us devise a method to determine the state of the ideal diode.

Determining State of an Ideal Diode

1. Obtain the expression for V_D in terms of the diode current I_D from the electronic circuit.
2. Insert $I_D = 0$ in to this expression
3. Then, the diode state is given by

$$\text{Ideal diode state} = \begin{cases} ON, & \text{if } V_D|_{I_D=0} \geq 0 \\ OFF, & \text{if } V_D|_{I_D=0} < 0 \end{cases} \quad (1.2.4)$$

Example 1.1: Consider the circuit below and find I_D and V_D . Assume the diode is **ideal**.

 


Figure 1.5: Diode circuit for Example 1.1.

Solution: First we need to determine the state of the ideal diode (i.e., ON or OFF). So, let us write down the KVL equation and obtain V_D

$$V_D = 5 - 5 I_D$$

From the equation above, $V_D|_{I_D=0} = 5 \geq 0$. So, the diode is ON. Thus,

$$V_D = 0 \text{ V} \quad \dots \text{from circuit behaviour}$$
$$I_D = \frac{5 - V_D}{5} = \frac{5 - 0}{5} = 1 \text{ A.}$$

1.3 *p-n* Junction Diodes

In an ***n*-type** semiconductor, **majority carriers** are **electrons** and **minority carriers** are **holes**.

Similarly, in a ***p*-type** semiconductor, **majority carriers** are **holes** and **minority carriers** are **electrons**.

When we join *n*-type and *p*-type semiconductors (Silicon or Germanium) together, we obtain a *p-n* junction as shown in Figure 1.6 below.

 


Figure 1.6: A *p-n* junction.

Current formed due to the movement of majority carriers across the junction is called the **majority carrier current**, I_{majority} .

Similarly, current formed due to the movement of minority carriers across the junction is called the **minority carrier current**, I_s . Note that, minority carrier and majority carrier currents flow in **opposite** directions.

When the materials are joined, the negatively charged atoms of the *n*-type side are attracted to the positively charged atoms of the *p*-type side.

Electrons in the *n*-type material migrate across the junction to the *p*-type material (electron flow).

Or, you could also say that holes in the *p*-type material migrate across the junction to the *n*-type material (conventional current flow).

The result is the formation of a **depletion layer** around the junction intersection, as shown in Figure 1.7 below.

 


Figure 1.7: Depletion layer in a p - n junction.

Normally, depletion layer is not symmetric around the intersection as the doping levels of n -side and p -side are usually not the same.

Operating Conditions

- **No Bias:** No voltage is applied and no current is flowing.
- **Reverse Bias:** Negative voltage (i.e., opposite polarity with the p - n junction) is applied.
- **Forward Bias:** Positive voltage (i.e., same polarity with the p - n junction) is applied.

1.3.1 No Bias Condition

- No external voltage is applied to the p - n junction as shown in Figure 1.8 below. So, $V_D = 0$ V and no current is flowing $I_D = 0$ A. Under no bias, only a modest depletion layer exists as seen in Figure 1.8 below.

 


Figure 1.8: p - n junction under no bias.

- No bias circuit behaviour is also shown in Figure 1.9 below

 


Figure 1.9: Diode behaviour under no bias.

1.3.2 Reverse Bias Condition

- External voltage is applied across the p - n junction in the opposite polarity of the p - and n -type materials, as shown in Figure 1.10 below.
- This causes the depletion layer to widen as shown below, as electrons in the n -type material are attracted towards the positive terminal and holes in the p -type material are attracted towards the negative terminal. Thus, the majority carrier current is zero, i.e., $I_{\text{majority}} = 0$.
- However, minority carriers move along the electric field across the junction forming the **minority carrier current**, I_s . Sometimes, this current is also called as the **reverse saturation current**.

 


Figure 1.10: p - n junction under reverse bias.

- Reverse bias circuit behaviour is also shown in Figure 1.11 below

 


Figure 1.11: Diode behaviour under reverse bias.

- Thus, diode current I_D under reverse bias is given by

$$I_D = I_{\text{majority}} - I_s = 0 - I_s = -I_s. \quad (1.3.5)$$

1.3.3 Forward Bias Condition

- External voltage is applied across the p - n junction in the same polarity of the p - and n -type materials, as shown in Figure 1.12 below.
- The depletion layer is narrow. So, electrons from the n -type material and holes from the p -type material have sufficient energy to cross the junction forming the **majority carrier current**, I_{majority}
- Minority carrier current I_s is still present in the opposite direction

 


Figure 1.12: p - n junction under forward bias.

- Forward bias circuit behaviour is also shown in Figure 1.13 below

 


Figure 1.13: Diode behaviour under forward bias.

- Thus, diode current I_D under forward bias is given by

$$I_D = I_{\text{majority}} - I_s. \quad (1.3.6)$$

- Normally $I_{\text{majority}} \gg I_s$, so diode current I_D under forward bias is approximately equal to the majority carrier current, i.e.,

$$I_D \approx I_{\text{majority}}. \quad (1.3.7)$$

1.3.4 Diode Characteristic Equation

Empirically obtained diode **characteristics curve** covering all three operating conditions is shown in Figure 1.14 below

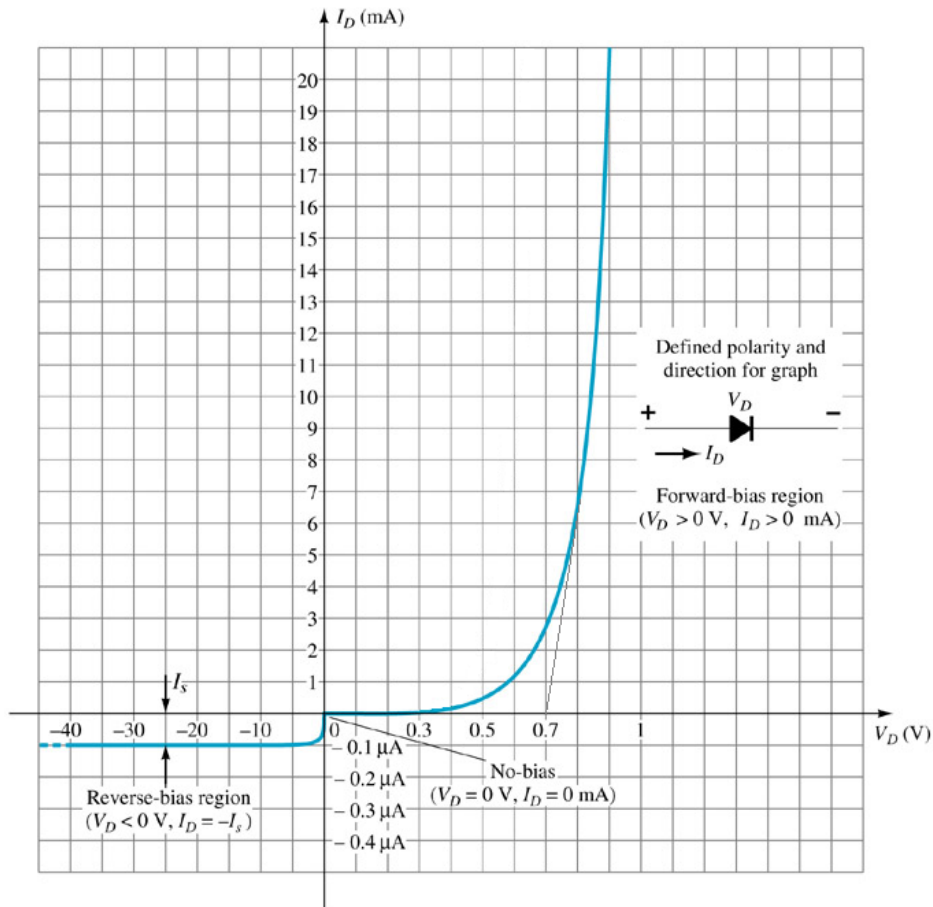


Figure 1.14: Diode characteristics curve

- Diode characteristic equation (also known as the Shockley diode equation) describing the diode characteristics curve is given below

$$\boxed{I_D = I_s (e^{V_D/\gamma} - 1)} \quad (1.3.8)$$

where γ , sometimes expressed as V_T , is the **thermal voltage** given by

$$\gamma = \frac{kT}{q} \quad (1.3.9)$$

with k , q and T being the Boltzman constant, the charge of an electron and temperature in Kelvins, respectively. Note that, $\frac{k}{q}$ is constant given by

$$\frac{k}{q} = \eta 8.6173 \times 10^{-5} \text{ V/K} \quad (1.3.10)$$

where $\eta = 1$ for Ge and $\eta = 2$ for Si for relatively low levels of diode current (at or below the knee of the curve) and $\eta = 1$ for Ge and Si for higher levels of diode current (in the rapidly increasing section of the curve). We can safely assume $\eta = 1$ for most cases.

- Under forward bias, diode characteristic equation simplifies (as $e^{V_D/\gamma} \gg 1$) to the **simplified forward bias diode equation** below

$$I_D \approx I_s e^{V_D/\gamma} \quad (1.3.11)$$

- Under reverse bias, diode characteristic equation simplifies (as $e^{V_D/\gamma} \ll 1$) to the following

$$I_D \approx -I_s \quad (1.3.12)$$

- Note that, γ only depends on the temperature (expressed in Kelvin units).

So, thermal voltage γ at room temperature $T = 300 \text{ K}$ (i.e., $T = 27^\circ\text{C}$) is given by

$$\boxed{\gamma = \gamma|_{T=300\text{K}} = 26 \text{ mV}.} \quad (1.3.13)$$

If we take the room temperature as $T = 25^\circ\text{C}$, then thermal voltage becomes

$$\gamma|_{T=298\text{K}} = 25 \text{ mV}. \quad (1.3.14)$$

NOTE: Temperature in Kelvin (T) is obtained from the temperature in Celsius (T_C) as follows

$$T = T_C + 273 \quad (1.3.15)$$

1.3.5 Zener Region (or Avalanche Breakdown Region)

 


Figure 1.15: Zener region (or avalanche breakdown region)

Even though the scale of Figure 1.14 is in tens of volts in the negative region, there is a point where the application of too negative a voltage will result in a sharp change in the characteristics, as shown in Figure 1.15. The current increases at a very rapid rate in a direction opposite to that of the positive voltage region. The reverse-bias potential that results in this dramatic change in characteristics is called the Zener potential and is given the symbol V_Z .

As the voltage across the diode increases in the reverse-bias region, the velocity of the minority carriers responsible for the reverse saturation current I_s will also increase. Eventually, their velocity and associated kinetic energy will be sufficient to release additional carriers (i.e., avalanche effect) through collisions with otherwise stable atomic structures. That is, an ionization process will result whereby valence electrons absorb sufficient energy to leave the parent atom. These additional carriers can then aid the ionization process to the point where a high avalanche current is established and the **avalanche breakdown** region determined.

The avalanche region (V_Z) can be brought closer to the vertical axis by increasing the doping levels in the p - and n -type materials. However, as V_Z decreases to very low levels, such as 5 V, another mechanism, called **Zener breakdown**, will contribute to the sharp change in the characteristic.

It occurs because there is a strong electric field in the region of the junction that can disrupt the bonding forces within the atom and generate carriers generally **via tunnelling** (sometimes called as tunnelling breakdown) of the majority carriers under reverse-bias electric field when the valence band of the highly doped p -region is aligned with the conduction band of the highly doped n -region.

Although the Zener breakdown mechanism is a significant contributor only at lower levels of V_Z , this sharp change in the characteristic at any level is called the Zener region and diodes employing this unique portion of the characteristic of a p - n junction are called **Zener diodes**.

1.3.6 Peak Inverse Voltage (PIV) Rating

Avalanche breakdown region of the semiconductor diode must be avoided if the diode is supposed to work as an ON and OFF device.

The maximum reverse-bias potential that can be applied before entering the avalanche breakdown region is called the **peak inverse voltage** (referred to simply as the **PIV rating**) or the **peak reverse voltage** (denoted by **PRV rating**).

If an application requires a PIV rating greater than that of a single unit, a number of diodes of the same characteristics can be connected in series.

Similarly, diodes can be also connected in parallel to increase the current-carrying capacity.

1.3.7 Forward Bias Turn-On Voltage ($V_{D(ON)}$)

The point at which the diode changes from No Bias condition to Forward Bias condition happens when the electron and holes are given sufficient energy to cross the p - n junction. This energy comes from the external voltage applied across the diode.

This voltage (can be deduced from the diode characteristics curve) is called the **turn-on voltage** or the **threshold voltage**, and denoted by $V_{D(ON)}$ (V_T or V_0 notations are also used).

The forward bias voltage required to turn on the diode for a

- Silicon diode: $V_{D(ON)} = 0.7 \text{ V}$
- Germanium diode: $V_{D(ON)} = 0.3 \text{ V}$

1.3.8 Temperature Effects

 


Figure 1.16: Change of diode characteristics with temperature

- As temperature increases it adds energy to the diode. From Figure 1.16 above, as temperature increases
 - It **reduces** the required **turn-on voltage** ($V_{D(ON)}$) in forward bias condition,
 - It **increases** the amount of **reverse saturation current** (I_s) in reverse bias condition,
 - It **increases** the **avalanche breakdown voltage** in reverse bias condition.
- Germanium diodes are more sensitive to temperature variations than Silicon diodes.

1.3.9 Load Line and Operating Point (Q -point)

 


Figure 1.17: Series diode configuration: (a) circuit, (b) diode characteristics curve.

From Figure 1.17(a) above, we obtain

$$V_D = E - I_D R \quad (1.3.16)$$

- We can rearrange the circuit equation (1.3.16) above to get I_D on the left-hand side of the equation, i.e.,

$$I_D = \frac{-1}{R} V_D + \frac{E}{R} \quad (1.3.17)$$

- This equation obtained from the diode circuit is called the **load line equation**.

The **load line** equation gives us all the possible current (I_D) values for all the possible voltage (V_D) values obtained across the diode in a given circuit.

- Once we draw the load line over the diode characteristics curve given in Figure 1.17(b), and the intersection point will give us the solution (I_{DQ}, V_{DQ}) of the diode current and diode voltages I_D and V_D for the given circuit, respectively. The result is shown in Figure 1.18 below.

 


Figure 1.18: Drawing the load line and finding the point of operation.

- This plot is called the **load line plot**. Also, the intersection point of the load line and the diode characteristics curve is called the **operating point** or the **Q-point** specified by the (I_{DQ}, V_{DQ}) pair. Note that Q stands for quiescent (i.e., still).
- For some examples, see Examples 2.1, 2.2 and 2.3 in the Boylestad and Nashelsky textbook (8th ed.).

A load line plot like Figure 1.18 is actually the graphical way of solving the diode characteristics equation

$$I_D = I_S (e^{V_D/\gamma} - 1)$$

and the electrical circuit equation, i.e., load line equation

$$I_D = -\frac{V_D}{R} + \frac{E}{R}$$

simultaneously. Load line plots are very practical and more efficient than solving these two equations analytically.

1.3.10 DC Resistance (Static Resistance)

 


Figure 1.19: Determining the DC resistance of a diode at a particular operating point.

- For a specific applied DC voltage V_{DQ} , the diode will have a specific current I_{DQ} , and consequently a specific resistance R_{DQ} . The amount of resistance R_{DQ} , depends on the applied DC voltage and current.
- For a given operating point as shown in Figure 1.19 above, we can find the DC resistance as follows

$$\begin{aligned} R_{DQ} &= \left. \frac{V_D}{I_D} \right|_{Q\text{-point}} \\ &= \frac{V_{DQ}}{I_{DQ}} \end{aligned} \quad (1.3.18)$$

1.3.11 AC Resistance (Dynamic Resistance)

 


Figure 1.20: Defining the dynamic or AC resistance around an operating point

- Dynamic resistance r_d is determined around a Q -point (see Figure 1.20 above) as the ratio of given very small voltage variation ΔV_d to the current variation ΔI_d obtained, i.e.,

$$r_d \cong \left. \frac{\Delta V_d}{\Delta I_d} \right|_{Q\text{-point}}$$

- As the magnitude of these small voltage and current variations go to zero this equation for the dynamic resistance r_d approaches to the following partial derivative

$$\boxed{r_d = \left. \frac{\partial V_D}{\partial I_D} \right|_{Q\text{-point}}} \quad (1.3.19)$$

- In the **forward bias region**, we can use the simplified forward bias diode equation

$$I_D \approx I_s e^{V_D/\gamma}$$

as given in (1.3.11)

Then, the forward bias dynamic resistance is obtained as

$$\begin{aligned} r_d &= \left. \frac{\partial V_D}{\partial I_D} \right|_{Q\text{-point}} = \left. \frac{1}{\frac{\partial I_D}{\partial V_D}} \right|_{Q\text{-point}} \approx \frac{1}{\frac{1}{\gamma} \underbrace{I_s e^{V_{DQ}/\gamma}}_{I_{DQ}}} \\ &= \frac{\gamma}{I_{DQ}} \end{aligned}$$

The forward bias dynamic resistance depends on the Q -point current I_{DQ} and the temperature, i.e.,

$$r_d = \frac{\gamma}{I_{DQ}} \quad (1.3.20)$$

We know that $\gamma = 26 \text{ mV}$ at room temperature (300 K), so the diode dynamic resistance can be calculated as

$$r_d = \frac{26 \text{ mV}}{I_{DQ}} \quad (1.3.21)$$

- In the **reverse bias region**, diode current is approximately constant

$$I_D \approx -I_s$$

as given in (1.3.12)

So, the reverse bias dynamic resistance is essentially infinite, i.e.,

$$r_d = \infty. \quad (1.3.22)$$

1.3.12 DC and Small-Signal AC (SSAC) Analysis

 


Figure 1.21: Diode circuit with AC and DC sources.

- Here, it is given that $V_{DC} - \text{peak}(v_{ac}(t)) > V_{D(ON)}$ and $V_{DC} \gg \text{peak}(v_{ac}(t))$.

First condition ensures that the diode state do not change for any value of the AC signal (i.e., diode is always ON) and the second condition ensures that diode behaviour is approximately linear around the Q -point.

The two conditions together provide **linearity** (approximately), so that we can employ the **superposition theorem**. Remember that, superposition theorem can only be employed in linear systems.

- Then, we can apply the **superposition theorem** and express the diode current and voltages as follows

$$i_D(t) = I_{DQ} + i_d(t) \quad (1.3.23)$$

$$v_D(t) = V_{DQ} + v_d(t). \quad (1.3.24)$$

- Diode is always ON and magnitude of the AC signal is very small compared to the DC signal (e.g., 10 mV vs. 10 V). So, we can apply the **law of superposition** and perform DC analysis and small-signal AC (SSAC) analysis **separately**, that is, we obtain I_{DQ} and $i_d(t)$ independently using different circuits.
- We obtain **DC equivalent circuit** by killing the AC sources as shown in Figure 1.22 below

 


Figure 1.22: DC equivalent circuit of the circuit in Figure 1.21.

In DC analysis, I_{DQ} and V_{DQ} are found using the **load-line analysis**, i.e., by solving the diode characteristic equation and load-line equation simultaneously.

- We obtain **SSAC equivalent circuit** by killing the DC sources and replacing the diode with its **SSAC model (r_d)** where

$$r_d = \frac{26 \text{ mV}}{I_{DQ}}$$

as shown in Figure 1.23 below

 


Figure 1.23: SSAC equivalent circuit of the circuit in Figure 1.21.

- In SSAC analysis, diode is replaced by its dynamic resistance r_d and we can finally find $i_d(t)$ and $v_d(t)$ as follows

$$i_d(t) = \frac{v_{ac}(t)}{R + r_d} \tag{1.3.25}$$

$$v_d(t) = \frac{r_d}{R + r_d} v_{ac}(t). \tag{1.3.26}$$

1.3.13 Average AC Resistance

 


Figure 1.24: Determining the average AC resistance between indicated limits.

- Average AC resistance can be determined by picking two points on the characteristic curve developed for a particular circuit where the voltage and current variations (i.e., ΔV_d and ΔI_d) are large, as shown in Figure 1.24 above. It is used to develop the piecewise-linear diode model.
- Thus, the average AC resistance r_{av} is calculated as

$$r_{av} = \frac{\Delta V_D}{\Delta I_D} \quad (\text{point-to-point}) \quad (1.3.27)$$

1.4 Piecewise-Linear Diode Model

 


Figure 1.25: Piecewise-linear characteristics curve (blue line on the left) and piecewise-linear equivalent circuit (on the right) of the diode.

- Piecewise-linear approximation of the diode characteristics curve is obtained and depicted as the blue lines on the left of Figure 1.25 above.
- Similarly, obtained piecewise-linear equivalent circuit is shown on the right of Figure 1.25 above.
- Here, r_{av} is the forward bias average AC resistance (i.e., **internal resistance**) of the diode.

1.5 Simplified Diode Model

 


Figure 1.26: Simplified characteristics curve (on the left) and simplified equivalent circuit (on the right) of the diode.

- Simplified diode characteristics curve is obtained and shown on the left of Figure 1.26 above.
- Similarly, obtained simplified equivalent circuit is shown on the right of Figure 1.26 above.

We can summarize the simplified diode model with its state and circuit behaviour with

$$\text{Diode state} = \begin{cases} ON, & \text{if } V_D \geq V_{D(ON)} \\ OFF, & \text{if } V_D < V_{D(ON)} \end{cases} \quad (1.5.28)$$

and

Simplified Diode Model		
State	Circuit Behaviour	Test Condition
ON	$V_D = V_{D(ON)}$	$I_D \geq 0$
OFF	$I_D = 0$	$V_D < V_{D(ON)}$

- For the ideal diode model, the turn-on voltage is zero, i.e., $V_{D(ON)} = 0 \text{ V}$.

In this course, we will mostly use the simplified diode model unless otherwise stated.

1.5.1 Determining State of a Diode

- Using circuit behaviour and the test condition for the OFF state, let us devise a method to determine the state of a diode under simplified diode model.

Determining State of a Diode

1. Obtain the expression for V_D in terms of the diode current I_D from the electronic circuit.
2. Insert $I_D = 0$ in to this expression
3. Then, the diode state is given by

$$\text{Ideal diode state} = \begin{cases} ON, & \text{if } V_D|_{I_D=0} \geq V_{D(ON)} \\ OFF, & \text{if } V_D|_{I_D=0} < V_{D(ON)} \end{cases} \quad (1.5.29)$$

Example 1.2: Consider the circuit below and find I_D and V_D with $V_{D(ON)} = 0.7 \text{ V}$ and $E > 0.7 \text{ V}$.

 


Figure 1.27: Diode circuit for Example 1.2.

Solution: First we need to determine the state of the diode (i.e., ON or OFF). So, let us write down the KVL equation and obtain V_D

$$V_D = E - I_D R$$

From the equation above, $V_D|_{I_D=0} = E \geq V_{D(ON)}$. So, the diode is ON. Thus,

$$\begin{aligned}
 V_D &= V_{D(ON)} = 0.7 \text{ V} && \dots \text{from circuit behaviour} \\
 I_D &= \frac{E - V_D}{R} = \frac{E - 0.7}{R} \\
 V_R &= E - V_D = E - 0.7
 \end{aligned}$$

Thus, our diode circuit in Figure 1.27 is simplified to the circuit shown in Figure 1.28 below

 


Figure 1.28: Simplified circuit for the diode circuit in Figure 1.27.

Note that $I_R = I_D$.

Example 1.3: Consider the circuit below and find I_D and V_D with $V_{D(ON)} = 0.7 \text{ V}$ and $E > 0.7 \text{ V}$.

 


Figure 1.29: Diode circuit for Example 1.3.

Solution: First we need to determine the state of the diode (i.e., ON or OFF). So, let us write down the KVL equation and obtain V_D

$$V_D = -E - I_D R$$

From the equation above, $V_D|_{I_D=0} = -E < V_{D(ON)}$. So, the diode is OFF. Thus,

$$\begin{aligned}
 I_D &= 0 \text{ A} && \dots \text{from circuit behaviour} \\
 V_D &= -E - I_D R = -E \\
 V_R &= -I_D R = 0 \text{ V}
 \end{aligned}$$

Thus, our diode circuit in Figure 1.29 is simplified to the circuit shown in Figure 1.30 below

 


Figure 1.30: Simplified circuit for the diode circuit in Figure 1.29.

Note that $I_R = -I_D = 0 \text{ A}$.

Example 1.4: Consider the circuit below and find I_1 , V_o , I_{D_1} and I_{D_2} with $V_{D(ON)} = 0.7 \text{ V}$ and $D_1 \equiv D_2$.

 


Figure 1.31: Diode circuit for Example 1.4.

Solution: First we need to determine the state of the diodes (i.e., ON or OFF). As the diodes are parallel, we let us make the following definitions

$$V_D = V_{D_1} = V_{D_2}$$

$$I_D = I_{D_1} + I_{D_2} = I_1$$

So, let us write down the KVL equation and obtain V_D

$$V_D = E - I_D R = 10 - 0.33k I_D$$

From the equation above, $V_D|_{I_D=0} = 10 \geq V_{D(ON)}$. So, both diodes are ON.

Thus,

$$V_{D_1} = V_{D(ON)} = 0.7 \text{ V} \quad \dots \text{from circuit behaviour}$$

$$V_{D_2} = V_{D(ON)} = 0.7 \text{ V} \quad \dots \text{from circuit behaviour}$$

$$V_o = V_D = 0.7 \text{ V}$$

$$I_1 = \frac{E - V_D}{R} = \frac{10 - 0.7}{0.33k} = 28.18 \text{ mA}$$

$$I_{D_1} = I_{D_2} = \frac{I_1}{2} = 14.09 \text{ mA} \quad \dots \text{as } D_1 \equiv D_2$$

Homework 1.1: What will happen if D_2 is replaced by a Germanium diode and D_1 remains as a Silicon diode?

1.6 Diode Specification Sheets

Data about a diode is presented uniformly for many different diodes. This makes cross-matching of diodes for replacement or design easier.

Some of the key elements is listed below:

1. V_F : forward voltage at a specific current and temperature
2. I_F : maximum forward current at a specific temperature

3. I_R : maximum reverse current at a specific temperature
4. PIV or PRV or VBR: maximum reverse voltage at a specific temperature
5. Power Dissipation: maximum power dissipated at a specific temperature
6. C : Capacitance levels in reverse bias
7. t_{rr} : reverse recovery time
8. Temperatures: operating and storage temperature ranges

1.6.1 Semiconductor Notation


 


Figure 1.32: Semiconductor diode notation.

- Anode is abbreviated as A.
- Cathode is abbreviated as K (because the Cathode end of the diode symbol looks like a backwards K).

 Examples of some diode types and packagings are shown in Figure 1.33 below.



Types of Diode

Figure 1.33: Some diode types and packagings.

1.6.2 Capacitance

 


Figure 1.34: Transition and diffusion capacitance versus applied bias for a Silicon diode.

- In **reverse bias**, the depletion layer is very large. The diode's strong positive and negative polarities create capacitance, C_T . The amount of capacitance depends on the reverse voltage applied.
- In **forward bias**, storage capacitance or diffusion capacitance (C_D) exists as the diode voltage increases

1.7 Other Types of Diodes

Other types of diodes we like to mention are listed below

1. Zener Diode
2. Light Emitting Diode

1.8 Zener Diode

 


Figure 1.35: Zener diode symbol.

- A Zener is a diode operated in reverse bias at the Peak Inverse Voltage (PIV) called the **Zener voltage** (V_Z).
- Common Zener voltages: 1.8 V to 200 V.
- We are going to cover Zener diodes in more detail later in the course.

1.9 Light Emitting Diode (LED)

 


Figure 1.36: Circuit symbol of an LED.

- This diode when forward biased emits photons. These can be in the visible spectrum.
- The forward bias turn-on voltage is higher, usually around 2-3 V.
- A Litronix 7-segment LED display is shown in Figure 1.37 below

 


Figure 1.37: Litronix 7-segment LED display

- Relative intensity of each color versus wavelength appears in Figure 1.38 below.

 


Figure 1.38: Relative intensity versus wavelength.

Chapter 2

Diode Applications

2.1 Clippers

Clipper diode circuits have the ability to *clip* off a portion of the input signal without distorting the remaining part of the alternating waveform.

Depending on the orientation of the diode, the positive or negative region of the input signal is *clipped* off.

There are two general categories of clippers: **series** and **parallel**. The series configuration is defined as one where the diode is in series with the load as shown in Figure 2.1 below, while the parallel variety has the diode in a branch parallel to the load.

 


Figure 2.1: A series clipper circuit.

- Let us write down the KVL equation for the circuit in Figure 2.1 above

$$v_i - v_D - i_D R = 0 \quad \Rightarrow \quad v_D = v_i - i_D R \quad (2.1.1)$$

As $v_D|_{i_D=0} = v_i$, we have

$$\text{Diode state} = \begin{cases} ON, & \text{if } v_i \geq V_{D(ON)} \\ OFF, & \text{if } v_i < V_{D(ON)} \end{cases} \quad (2.1.2)$$

As the **output** v_o is across the resistor R , i.e., $v_o = i_D R = v_i - v_D$, we have

$$v_o = \begin{cases} v_i - V_{D(ON)}, & \text{if } v_i \geq V_{D(ON)} \\ 0, & \text{if } v_i < V_{D(ON)} \end{cases} \quad (2.1.3)$$

- Let us plot equation (2.1.3) above, as a **voltage transfer characteristics (VTC)** curve, i.e., output versus input plot, in order to understand the clipper behaviour visually, as shown in Figure 2.2 below.

 


Figure 2.2: Voltage transfer characteristics (VTC) curve of the series clipper circuit Figure 2.1.

- Let us analyse the operation of the series clipper circuit Figure 2.1 for a sinusoidal input, using the **ideal diode** model, i.e., $V_{D(ON)} = 0$.

 


Figure 2.3: Positive half-cycle operation of the series clipper circuit in Figure 2.1.

 


Figure 2.4: Negative half-cycle operation of the series clipper circuit in Figure 2.1.

As we see from Figure 2.3 and Figure 2.4 above, negative half-cycle portion of the signal is clipped off while the positive half-cycle portion remains intact.

Example 2.1: By adding a DC source to the circuit as shown in Figure 2.5, the voltage required to forward bias the diode can be changed.

 


Figure 2.5: A series clipper circuit with a DC supply.

Consequently, the output will be given by

$$v_o = \begin{cases} v_i + 5 \text{ V} - V_{D(ON)}, & \text{if } v_i \geq V_{D(ON)} - 5 \text{ V} \\ 0, & \text{if } v_i < V_{D(ON)} - 5 \text{ V} \end{cases} \quad (2.1.4)$$

Let us sketch the output of the series clipper circuit Figure 2.5 for a sinusoidal input, using the **ideal diode** model, as shown in Figure 2.6 below.


 


Figure 2.6: Input and output of the series clipper circuit in Figure 2.5.


Example 2.2: Various series clipper examples are shown in Figure 2.7 below (diodes are ideal).

Simple Series Clippers (Ideal Diodes)

POSITIVE

 

NEGATIVE

 

Biased Series Clippers (Ideal Diodes)

 
 


Figure 2.7: Various series clipper examples (diodes are ideal).

2.1.1 Parallel Clippers

By taking the output across the diode shown in Figure 2.8 below, the output equals to the input voltage when the diode is not conducting.

 


Figure 2.8: A parallel clipper circuit.

Hence, the output for this circuit will be given by

$$v_o = \begin{cases} V_{D(ON)}, & \text{if } v_i \geq V_{D(ON)} \\ v_i, & \text{if } v_i < V_{D(ON)} \end{cases} \tag{2.1.5}$$

Example input and output waveforms of the parallel clipper circuit Figure 2.8 for the **ideal diode** model are shown in Figure 2.9 below.

 


Figure 2.9: Sample input and output waveforms of the parallel clipper circuit in Figure 2.8.

Example 2.3: A DC source can also be added to change the diode's required forward bias voltage, as shown in Figure 2.10

 


Figure 2.10: A parallel clipper circuit with a DC supply.

Consequently, the output will be given by

$$v_o = \begin{cases} -V_{D(ON)} - V_{BB}, & \text{if } v_i \leq -V_{D(ON)} - V_{BB} \\ v_i, & \text{if } v_i > -V_{D(ON)} - V_{BB} \end{cases} \quad (2.1.6)$$

Homework 2.1: Draw the VTC diagram of the parallel clipper circuit given in Figure 2.10 above.

Homework 2.2: Draw the output waveform and the VTC diagram when the diode is reversed.

Example 2.4: For the circuit shown in Figure 2.11 below, find the output for a sinusoidal input $v_i(t) = V_m \sin(2\pi t/T)$ where $(V_{B1}, V_{B2}) < V_m$ and draw the VTC diagram.

 


Figure 2.11: A diode limiter circuit.

Consequently, the output is given below and also shown in Figures 2.12(a) and 2.12(b) below

$$v_o = \begin{cases} V_{D(ON)} + V_{B1}, & \text{if } v_i \geq V_{D(ON)} + V_{B1}, \\ -V_{D(ON)} - V_{B2}, & \text{if } v_i \leq -V_{D(ON)} - V_{B2}, \\ v_i, & \text{else.} \end{cases} \quad (2.1.7)$$

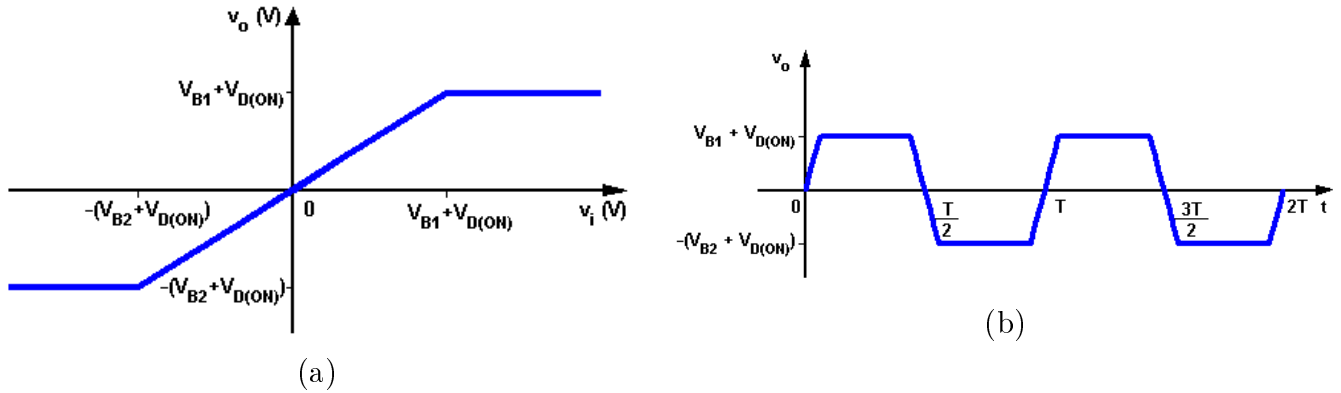


Figure 2.12: Outputs of the circuit in Figure 2.11: (a) VTC diagram, (b) output waveform.

Example 2.5: Various parallel clipper examples are shown in Figure 2.13 below (diodes are ideal).

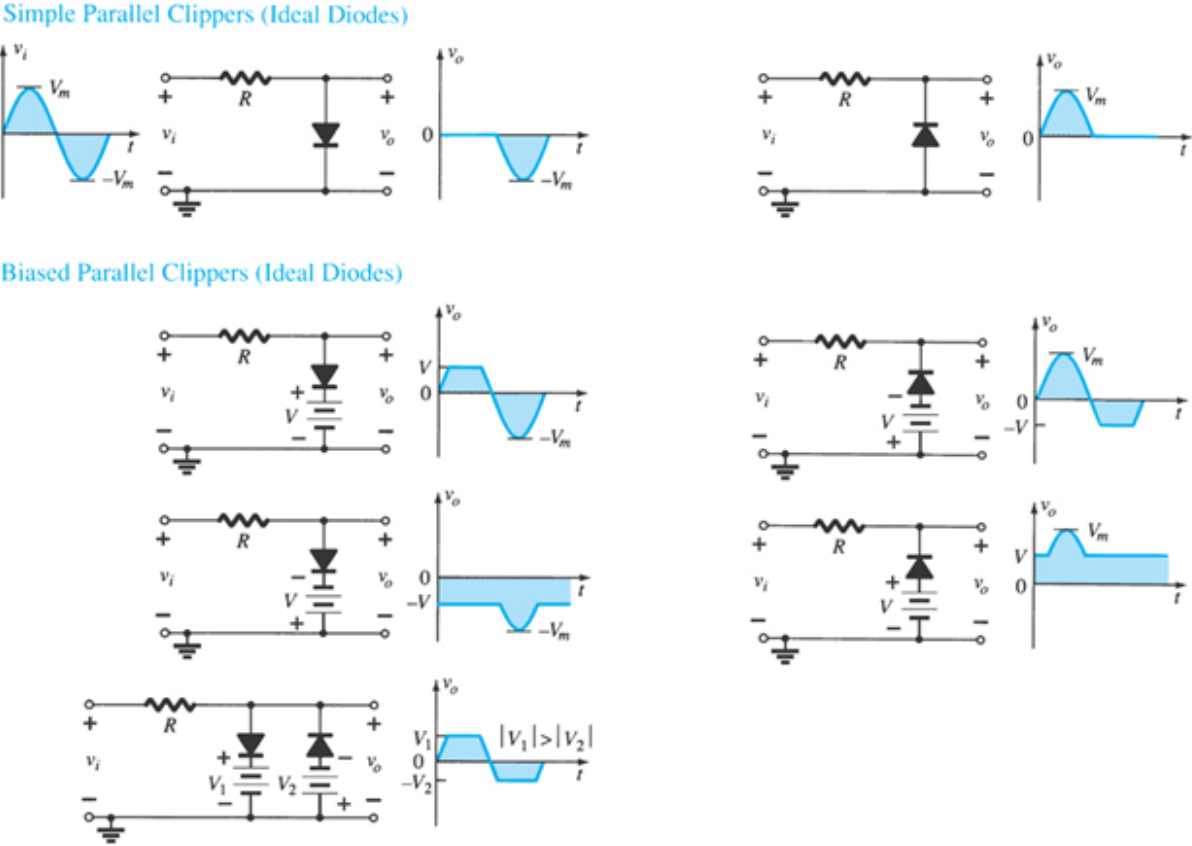


Figure 2.13: Various parallel clipper examples (diodes are ideal).

2.2 Clampers

Clamper circuits *clamp* a signal to different DC levels. The circuit must have a capacitor, a diode, and a resistive element as shown in Figure 2.14 below, but it can also employ an independent DC supply to introduce an additional shift.

 


Figure 2.14: A clamper circuit.

Throughout the analysis, we will assume that for all practical purposes the **capacitor** will **fully discharge** in **five time constants**, i.e., $5\tau_{\text{discharge}}$, where time constant $\tau_{\text{discharge}} = RC$.

The magnitude of R and C must be chosen such that the **time constant** $\tau_{\text{discharge}} = RC$ is **large enough** to ensure that the voltage across the **capacitor** does not discharge significantly during the interval the **diode** is **nonconducting**.

For the circuit in Figure 2.14 above, the diode state is given by

$$\text{Diode state} = \begin{cases} ON, & \text{if } v_i \geq V_{D(ON)} + V_C \\ OFF, & \text{if } v_i < V_{D(ON)} + V_C \end{cases} \quad (2.2.8)$$

where V_C is the voltage across the capacitor C .

The clamper output is given by

$$v_o = v_i - V_C. \quad (2.2.9)$$

- Consequently, when the capacitor is charged at the maximum voltage, i.e., $V_C = V_m - V_{D(ON)}$ and diode is OFF, the clamper output will be

$$v_o = v_i - (V_m - V_{D(ON)}). \quad (2.2.10)$$

IMPORTANT: The clamper **shifts** the signal **in the direction of the diode arrowhead** by an amount of $(V_m - V_{D(ON)})$.

- Let us generate steps for the clamper operation for the circuit in Figure 2.14 above, assuming capacitor is fully discharged initially, i.e., at $t = 0$, using the **ideal diode** model.
 1. The diode will be ON in the **first** positive half cycle as $V_C = 0$ and the capacitor will charge up very quickly to the peak value V_m with a time constant $\tau_{\text{charge}} = Cr_{av} \cong 0$ where $r_{av} \cong 0\Omega$ is the internal resistance of the diode as shown in Figure 2.15 below.

 


Figure 2.15: Charging operation of the clamper circuit in Figure 2.14.

2. Once the capacitor is charged, i.e., $V_C = V_m$. then the diode turns OFF, as shown in Figure 2.16 below.

 


Figure 2.16: Discharging operation of the clamper circuit in Figure 2.14.

3. Capacitor will discharge until the input waveform gets larger than the capacitor voltage, i.e., $v_i(t) > v_C(t)$. Thus, the discharging period ($\frac{T}{2}$) must be much smaller than the fully discharge constant $5\tau_{\text{discharge}}$ in order to keep the voltage across the capacitor almost constant at $V_C \cong V_m$, i.e.,

$$5\tau_{\text{discharge}} \gg \frac{T}{2} \quad (2.2.11)$$

So, if take ($5\tau_{\text{discharge}} \geq 50 \frac{T}{2}$), then we obtain the following condition for the clamping operation

$$\boxed{\tau_{\text{discharge}} \geq 5T} \quad (2.2.12)$$

where T is the period of the input signal v_i .

- **For a clamping operation, selected capacitor C and resistor R values should satisfy the discharge condition in (2.2.12).**
- **IMPORTANT:** If it is not explicitly stated we are going to assume that **capacitor is already charged**, e.g., $V_C = V_m - V_{D(ON)}$.

Example 2.6: Consider the clamping circuit below and plot the output waveform. Assume the diode is **ideal**.

 


Figure 2.17: A clamer circuit with a square wave input.

Solution: As this is a clamping circuit, i.e., $\tau_{\text{discharge}} \leq 5T$, we obtain the following output

$$v_o = v_i - V + V_{D(ON)}$$

where $V_{D(ON)} = 0\text{ V}$. The resulting waveform is shown in Figure 2.18 below.

 


Figure 2.18: Output of the circuit given in Figure 2.17.

Example 2.7: Consider the clamping circuit below and plot the output waveform. Assume the diode is **ideal**.

 


Figure 2.19: A clamer circuit with a sinusoidal input.

Solution: Assuming the capacitor is already charged at $V_C = -V_m + V_{D(ON)} + V_{BB} = -20 + 0 + 10 = -10\text{ V}$, we obtain the following output

$$\begin{aligned} v_o &= v_i - (-V_m + V_{D(ON)} + V_{BB}) = v_i + V_m - V_{D(ON)} - V_{BB} = v_i + 20 - 0 - 10 \\ &= v_i + 10\text{ V}. \end{aligned}$$

The resulting waveform is shown in Figure 2.20 below.

 


Figure 2.20: Output of the circuit given in Figure 2.19.

Example 2.8: Various clamper examples are shown in Figure 2.21 below (diodes are ideal).

Clamping Networks (Ideal Diodes)

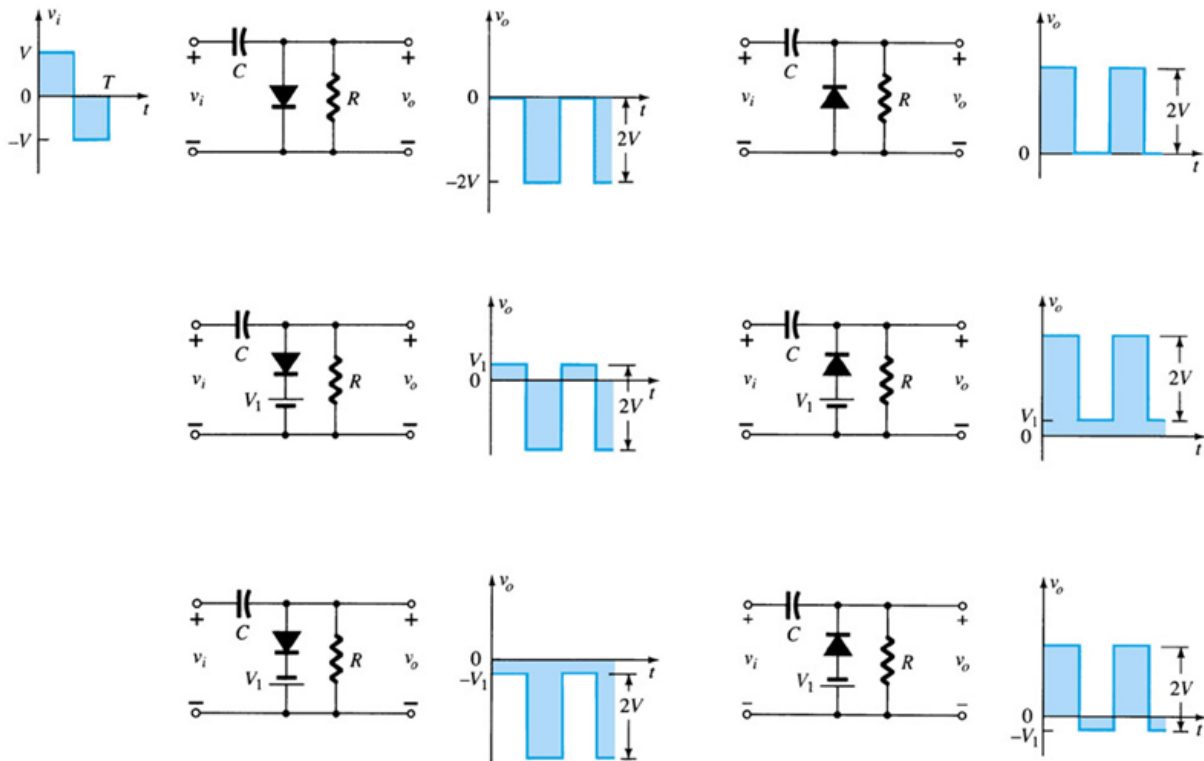


Figure 2.21: Various clamper examples (diodes are ideal and capacitors are charged).

2.3 Voltage Multiplier Circuits

2.3.1 Peak Rectifier

Once we consider a clamper circuit and take the output over the capacitor instead of the diode, we obtain the **peak rectifier** circuit shown in Figure 2.22 below producing a DC output at peak value of the input signal.

 


Figure 2.22: A peak rectifier circuit.

Corresponding input and output are also shown in figures 2.23(a) and 2.23(b) below. The capacitor is charged to the maximum value ($V_m - V_{D(ON)}$) in the first positive half cycle (i.e., between 0 and $T/4$), then the diode turns OFF and capacitor cannot discharge retaining the charged value. This value is equal to the **peak value** V_m for the **ideal diode**.

 


Figure 2.23: For the circuit in Figure 2.22: (a) input waveform, (b) output waveform.

- When a load R_L is connected, the discharge constant $\tau_{discharge} = R_L C$ should have a very high value compared to the half period ($\frac{T}{2}$) of the signal, otherwise ripples are observed at the output voltage, i.e., R_L should have a very large value.
- Using a combination of diodes and capacitors we can step up the output voltage of rectifier circuits. These circuits (some listed below) are called **voltage multiplier circuits**.
 1. Voltage Doubler
 2. Voltage Tripler
 3. Voltage Quadrupler

2.3.2 Voltage Doubler

A voltage doubler circuit is shown in Figure 2.24 below.

 


Figure 2.24: Voltage doubler circuit.

Using the **ideal diode** model, operation of the voltage doubler circuit are shown for the first positive and negative half-cycles in figures 2.25(a) and 2.25(b) below, respectively. After the first cycle, both diodes retain their OFF state.

 


Figure 2.25: Operation of the circuit in Figure 2.24 at (a) first positive half-cycle, and (b) first negative half-cycle.

2.3.3 Voltage Tripler and Quadrupler

By adding more diode-capacitor networks the voltage can be increased as shown in Figure 2.26 below.

 


Figure 2.26: Voltage tripler/quadrupler circuit.

2.4 Zener Diode

Zener diode **operates** in **reverse bias** (RB) at the Zener Voltage (V_Z). Zener diode is ON when it operates on the Zener region, i.e., $-V_D \geq V_Z$, and is OFF when $0 < -V_D < V_Z$, as shown in figures 2.27(a) and 2.27(b) below.

 


Figure 2.27: Zener diode operation: (a)ON (b) OFF.

- Although Zener diode behaves like a normal diode in forward bias, Zener diode is not normally used in forward bias.
- Zener diode also needs some minimum current $I_{Z(min)}$ in order to turn ON, although voltage threshold $-V_D \geq V_Z$ is satisfied. If not given, $I_{Z(min)} = 0$ A.
- There is also a maximum power limit $P_{Z(max)}$ for the Zener diode. Note that, maximum power limit results in a maximum current limit $I_{Z(max)}$ given by $I_{Z(max)} = \frac{P_{Z(max)}}{V_Z}$.

2.4.1 Zener Regulator

 


Figure 2.28: A general Zener diode circuit.

In a Zener regulator circuit likein Figure 2.28 above, Zener diode must be always ON in order to continuously regulate the voltage over the load R_L . So, let us derive the necessary equations for the two limiting factors $I_{Z(min)}$ and $I_{Z(max)}$ using

$$\boxed{I_Z = I_1 - I_L} \tag{2.4.13}$$

- Let us first write down the equation for $I_{Z(min)}$

$$\boxed{I_{Z(min)} = I_{1(min)} - I_{L(max)}} \quad (2.4.14)$$

where $I_{L(max)}$ and $I_{1(min)}$ are given by

$$I_{L(max)} = \frac{V_Z}{R_{L(min)}} \quad (2.4.15)$$

$$I_{1(min)} = \frac{V_{s(min)} - V_Z}{R_{1(max)}} \quad (2.4.16)$$

- Similarly, we can also write down the equation for $I_{Z(max)}$

$$\boxed{I_{Z(max)} = I_{1(max)} - I_{L(min)}} \quad (2.4.17)$$

where $I_{L(min)}$ and $I_{1(max)}$ are given by

$$I_{L(min)} = \frac{V_Z}{R_{L(max)}} \quad (2.4.18)$$

$$I_{1(max)} = \frac{V_{s(max)} - V_Z}{R_{1(min)}} \quad (2.4.19)$$

- Note that the values of V_Z , $I_{Z(min)}$ and $I_{Z(max)}$ (or $P_{Z(min)}$ and $P_{Z(max)}$) are specified in the specification sheet (or data sheet) of a Zener diode.

Example 2.9: (2004-2005 MI) In the figure below, V_s is an unregulated voltage that varies between 6 V and 7 V while the Zener diode voltage is $V_Z = 5$ V. The load resistor R_L can have a value from 100Ω to ∞ (i.e., open circuit). Also you can take $I_{Z(min)} \cong 0$ A.

- Find the **maximum** value of R_1 so that the load voltage V_L would be still kept constant at 5 V **for all values** of R_L and V_s .
- Provide a symbolic expression for the **maximum power** dissipated by the Zener diode.
- Determine the **minimum** value of R_1 so that the power dissipated by the Zener diode never exceeds 1 W **for all values** of R_L and V_s .

 


Figure 2.29: Zener diode circuit for Example 2.9.

Solution:

a) As $I_{Z(min)} = I_1(min) - I_{L(max)} = 0$, $I_1(min) = I_{L(max)}$, i.e.,

$$\frac{V_{s(min)} - V_Z}{R_{1(max)}} = \frac{V_Z}{R_{L(min)}}$$

$$R_{1(max)} = \frac{V_{s(min)} - V_Z}{V_Z} R_{L(min)} = \frac{6 - 5}{5} 100 = \underline{20\Omega}.$$

b) $P_{Z(max)} = V_Z I_{Z(max)}$.

c) It is given that $P_{Z(max)} = 1 \text{ W}$, so

$$I_{Z(max)} = \frac{P_{Z(max)}}{V_Z} = \frac{1}{5} = 0.2 \text{ A}$$

$$I_{L(min)} = \frac{V_Z}{R_{L(max)}} = \frac{5}{\infty} = 0 \text{ A}$$

$$I_1(max) = I_{Z(max)} + I_{L(min)} = I_{Z(max)} = 0.2 \text{ A}$$

$$R_{1(min)} = \frac{V_{s(max)} - V_Z}{I_1(max)} = \frac{7 - 5}{0.2} = \underline{10\Omega}.$$

2.4.2 Other Zener Diode Regulators

- A single Zener diode can limit one side of a sinusoidal waveform to the Zener voltage while clamping the other side to near zero as shown in Figure 2.30 below

 


Figure 2.30: Single Zener diode clipper.

- With two opposing Zeners, the waveform can be limited to the Zener voltage on both polarities as shown in Figure 2.31 below.

 


Figure 2.31: Dual Zener diode clipper.

2.4.3 Zener Diode Parameters

The basic parameters of a Zener diode are:

- a) Obviously, the Zener voltage must be specified. The most common range of Zener voltage is 3.3 volts to 75 volts, however voltages out of this range are available.
- b) A tolerance of the specified voltage must be stated. While the most popular tolerances are 5% and 10%, more precision tolerances as low as 0.05% are available. A test current ($I_{Z(test)}$) must be specified with the voltage and tolerance.
- c) The power handling capability must be specified for the Zener diode. Popular power ranges are: 0.25, 0.5, 1, 5, 10, and 50 Watts.

2.5 Practical Applications of Diode Circuits

- **Rectifier Circuits**

- Conversions of AC to DC for DC operated circuits
- Battery Charging Circuits

- **Simple Diode Circuits**

- Protective Circuits against
 - Overcurrent
 - Polarity Reversal
 - Currents caused by an inductive kick in a relay circuit

- **Zener Circuits**

- Overvoltage Protection
- Setting Reference Voltages

Chapter 3

Rectifiers and Voltage Regulating Filters

3.1 Properties of Electrical Signals

3.1.1 DC Component (Average Value) and AC Component

- Every (periodic) signal has a DC component and an AC component, i.e.,

$$v(t) = V_{DC} + v_{ac}(t) \quad (3.1.1)$$

where V_{DC} is the DC component and $v_{ac}(t)$ is the AC component.

- **DC component** V_{DC} is defined as the **time-average** or **mean** of the signal within one period, i.e.,

$$V_{DC} = V_{\text{avg}} = \frac{1}{T} \int_0^T v(t) dt \quad (3.1.2)$$

where T is the period of the signal.

V_{DC} is the voltage value displayed for $v(t)$ on a DC voltmeter.

- **AC component** $v_{ac}(t)$ is the **zero-mean time-varying** component of the signal given by

$$v_{ac}(t) = v(t) - V_{DC} \quad (3.1.3)$$

IMPORTANT: In this course, we are going to use

1. **capital** letters for both quantity symbols and subscripts of **DC** components, e.g., I_{DQ} ,
2. **small** letters for both quantity symbols and subscripts of **AC** components, e.g., i_d ,
3. small letters for quantity symbols and capital letters for subscripts of **AC+DC** signals, e.g., i_D where $i_D = I_{DQ} + i_d$.

Example 3.1: Let us calculate the DC component of the half-wave rectifier output shown in Figure 3.1 below.

 


Figure 3.1: Ideal half-wave rectifier output of a sinusoidal input $v_i(t) = V_m \sin(2\pi t/T)$.

Solution: DC component of the signal given by its time-average in one period. However in the case of the half-wave rectifier output shown in Figure 3.1 above, second half-cycle of the signal is zero. So, we only need to integrate first half-cycle of the signal.

$$\begin{aligned}
 V_{DC} &= \frac{1}{T} \int_0^{T/2} V_m \sin(2\pi t/T) dt \\
 &= \frac{1}{2\pi} V_m \int_0^\pi \sin \theta d\theta && \dots \text{using change of variables with } \theta = \frac{2\pi t}{T} \\
 &= \frac{V_m}{2\pi} [-\cos \theta]_0^\pi && \dots \text{and } dt = \frac{T}{2\pi} d\theta. \\
 &= \frac{V_m}{\pi} && (3.1.4) \\
 &\cong 0.318 V_m && (3.1.5)
 \end{aligned}$$

Example 3.2: Let us calculate the DC component of the full-wave rectifier output shown in Figure 3.2 below.

 


Figure 3.2: Ideal full-wave rectifier output of a sinusoidal input $v_i(t) = V_m \sin(2\pi t/T)$.

Solution: DC component of the signal given by its time-average in one period. However in the case of the full-wave rectifier output shown in Figure 3.2 above, the period of the output signal

is $\frac{T}{2}$.

$$\begin{aligned}
 V_{DC} &= \frac{2}{T} \int_0^{T/2} V_m \sin(2\pi t/T) dt \\
 &= \frac{1}{\pi} V_m \int_0^\pi \sin \theta d\theta && \dots \text{ using change of variables with } \theta = \frac{2\pi t}{T} \\
 &= \frac{V_m}{\pi} [-\cos \theta]_0^\pi && \dots \text{ and } dt = \frac{T}{2\pi} d\theta. \\
 &= \frac{2V_m}{\pi} && (3.1.6)
 \end{aligned}$$

$$\cong 0.636 V_m \quad (3.1.7)$$

Example 3.3: Let us calculate the DC component of the triangular waveform shown in Figure 3.3 below.

 


Figure 3.3: Triangular waveform.

Solution: DC component of the signal given by its time-average in one period. In this case the integral of the waveform in one period is the area of the triangle present ($V_m T/2$) in one period as seen in Figure 3.2 above.

$$\begin{aligned}
 V_{DC} &= \frac{1}{T} \int_0^T v(t) dt \\
 &= \frac{1}{T} \left(\frac{V_m T}{2} \right) && (3.1.8)
 \end{aligned}$$

$$= \frac{V_m}{2} \quad (3.1.9)$$

Example 3.4: Let us find the AC component of the triangular waveform shown in Figure 3.3.

Solution: AC component of the signal is obtained by subtracting the DC component, i.e.,

$$v_{ac}(t) = v(t) - V_{DC} = v(t) - \frac{V_m}{2}. \quad (3.1.10)$$

Thus, the AC component of the triangular waveform is plotted as shown in Figure 3.4 below.

 


Figure 3.4: AC component of the triangular waveform in Figure 3.3.

3.1.2 Effective Value (RMS Value)

- **Average power** or **mean power** is defined as the time-average of the instantaneous power over a period, i.e.,

$$P_{\text{avg}} = \frac{1}{T} \int_0^T p(t) dt \quad (3.1.11)$$

where $p(t)$ is the instantaneous power and T is the period of $p(t)$.

- The idea of effective current and voltage values comes from the need for writing the average power as a multiple of voltage and current values just like the Watt's law, i.e.,

$$P_{\text{avg}} = V_{\text{effective}} I_{\text{effective}} \quad (3.1.12)$$

where $V_{\text{effective}}$ and $I_{\text{effective}}$ are the effective voltage and current values, respectively.

Effective Voltage Value

- Let us obtain the effective voltage value $V_{\text{effective}}$ by defining average power over a resistor R

$$\begin{aligned} P_{\text{avg}} &= \frac{1}{T} \int_0^T \frac{v^2(t)}{R} dt \\ &= \frac{1}{R} \underbrace{\left(\frac{1}{T} \int_0^T v^2(t) dt \right)}_{V_{\text{effective}}^2} \end{aligned} \quad (3.1.13)$$

$$= \frac{V_{\text{effective}}^2}{R} \quad (3.1.14)$$

- Thus, effective voltage value $V_{\text{effective}}$ is given as the **root-mean-square** (RMS) of the voltage signal, i.e.,

$$\boxed{V_{\text{effective}} = V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}} \quad (3.1.15)$$

V_{rms} is the voltage value displayed for $v(t)$ on an AC voltmeter.

Effective Current Value

- Let us obtain the effective current value $I_{\text{effective}}$ by defining average power over a resistor R

$$\begin{aligned} P_{\text{avg}} &= \frac{1}{T} \int_0^T i^2(t) R dt \\ &= \left(\frac{1}{T} \int_0^T i^2(t) dt \right) R \end{aligned} \quad (3.1.16)$$

$$= \underbrace{\left(\frac{1}{T} \int_0^T i^2(t) dt \right)}_{I_{\text{effective}}^2} R \quad (3.1.17)$$

- Thus, effective current value $I_{\text{effective}}$ is given as the **root-mean-square** (RMS) of the current signal, i.e.,

$$I_{\text{effective}} = I_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt} \quad (3.1.18)$$

I_{rms} is the voltage value displayed for $i(t)$ on an AC ammeter.

Example 3.5: Calculate the RMS value V_{rms} of the mixed signal

$$v(t) = A + B \cos \omega t.$$

Solution: Let us find V_{rms}^2 first where $\omega = 2\pi f = 2\pi/T$

$$\begin{aligned} V_{\text{rms}}^2 &= \frac{1}{T} \int_0^T (A + B \cos \omega t)^2 dt \\ &= \frac{1}{T} \int_0^T (A^2 + \cancel{2AB \cos \omega t} + B^2 \cos^2 \omega t) dt \\ &= \frac{1}{T} \left([A^2 t]_0^T + \frac{B^2}{2} \int_0^T (1 + \cos 2\omega t) dt \right) \\ &= A^2 + \frac{B^2}{2} + \frac{B^2}{2T} \left[\frac{\sin 2\omega t}{T} \right]_0^T \\ &= A^2 + \frac{B^2}{2} \end{aligned}$$

So,

$$V_{\text{rms}} = \sqrt{A^2 + \frac{B^2}{2}}$$

- We can generalize the result of Example 3.5 for the RMS value V_{rms} of a general AC+DC signal $v(t)$ where

$$v(t) = V_{\text{DC}} + v_{\text{ac}}(t),$$

as the **combined RMS equation** given below

$$V_{\text{rms}} = \sqrt{V_{\text{DC}}^2 + V_{\text{ac(rms)}}^2} \quad (3.1.19)$$

Example 3.6: Calculate the RMS value of the triangular waveform shown in Figure 3.5 below.

 


Figure 3.5: Triangular waveform and its analytical expression.

Solution: Let us calculate V_{rms}^2 by using integration by parts

$$\begin{aligned} V_{\text{rms}}^2 &= \frac{1}{T} \left(\int_0^{T/2} \left(\frac{2V_m}{T}t \right)^2 dt + \int_{T/2}^T \left(2V_m - \frac{2V_m}{T}t \right)^2 dt \right) \\ &= \frac{1}{T} \left(\frac{4V_m^2}{T^2} \int_0^{T/2} t^2 dt + 4V_m^2 \int_{T/2}^T \left(1 - \frac{2}{T}t + \frac{1}{T^2}t^2 \right) dt \right) \\ &= \frac{4V_m^2}{T^3} \left[\frac{t^3}{3} \right]_0^{T/2} + \frac{4V_m^2}{T} \left[t - \frac{t^2}{T} + \frac{t^3}{3T^2} \right]_{T/2}^T \\ &= \frac{4V_m^2}{\cancel{T^3}} \frac{\cancel{T^3}}{24} + \frac{4V_m^2}{\cancel{T}} \left[\frac{\cancel{T}}{2} - \frac{3\cancel{T}}{4} + \frac{7\cancel{T}}{24} \right] \\ &= \frac{V_m^2}{3} \end{aligned}$$

So, the **RMS value** of the **triangular waveform** is given by

$$V_{\text{rms}} = \frac{V_m}{\sqrt{3}} \quad (3.1.20)$$

Example 3.7: Calculate the RMS value of the ideal half-wave rectifier output given in Figure 3.1.

Solution: Let us first calculate the V_{rms}^2

$$\begin{aligned}
 V_{\text{rms}}^2 &= \frac{1}{T} \int_0^{T/2} V_m^2 \sin^2(2\pi t/T) dt \\
 &= \frac{1}{2\pi} V_m^2 \int_0^\pi \sin^2 \theta d\theta && \dots \text{using change of variables } \theta = \frac{2\pi t}{T} \\
 &= \frac{V_m^2}{2\pi} \int_0^\pi \frac{1}{2}(1 - \cancel{\cos 2\theta}) d\theta && \dots \text{using trigonometric identities} \\
 &= \frac{V_m^2}{4}
 \end{aligned}$$

So, the **RMS value** of the **ideal half-wave rectifier output** is given by

$$V_{\text{rms}} = \frac{V_m}{2} \tag{3.1.21}$$

Example 3.8: Calculate the RMS value of the ideal full-wave rectifier output given in Figure 3.2.

Solution: Let us first calculate the V_{rms}^2

$$\begin{aligned}
 V_{\text{rms}}^2 &= \frac{2}{T} \int_0^{T/2} V_m^2 \sin^2(2\pi t/T) dt \\
 &= \frac{1}{\pi} V_m^2 \int_0^\pi \sin^2 \theta d\theta && \dots \text{using change of variables } \theta = \frac{2\pi t}{T} \\
 &= \frac{V_m^2}{\pi} \int_0^\pi \frac{1}{2}(1 - \cancel{\cos 2\theta}) d\theta && \dots \text{using trigonometric identities} \\
 &= \frac{V_m^2}{2}
 \end{aligned}$$

So, the **RMS value** of the **ideal full-wave rectifier output** is given by

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}} \cong 0.707 V_m \tag{3.1.22}$$

Example 3.9: Calculate the RMS value $V_{ac(\text{rms})}$ of the AC component of the triangular waveform shown in Figure 3.4.

Solution: We are going to use the combined RMS equation given in (3.1.19) with the already calculated DC and RMS values of the triangular waveform given in (3.1.9) and (3.1.20),

respectively as follows

$$\begin{aligned}
 V_{ac(rms)}^2 &= V_{rms}^2 - V_{DC}^2 \\
 &= \left(\frac{V_m}{\sqrt{3}}\right)^2 - \left(\frac{V_m}{2}\right)^2 \\
 &= \frac{V_m^2}{3} - \frac{V_m^2}{4} \\
 &= \frac{V_m^2}{12}.
 \end{aligned}$$

So, the **RMS value of the AC component of the triangular waveform** is given by

$$\boxed{V_{ac(rms)} = \frac{V_m}{2\sqrt{3}}} \quad (3.1.23)$$

Example 3.10: Calculate the RMS value $V_{ac(rms)}$ of the AC component of the ideal half-wave rectifier output.

Solution: We are going to use the combined RMS equation given in (3.1.19) with the already calculated DC and RMS values of the ideal half-wave rectifier output given in (3.1.4) and (3.1.21), respectively as follows

$$\begin{aligned}
 V_{ac(rms)}^2 &= V_{rms}^2 - V_{DC}^2 \\
 &= \left(\frac{V_m}{2}\right)^2 - \left(\frac{V_m}{\pi}\right)^2 \\
 &= \frac{V_m^2}{4} - \frac{V_m^2}{\pi^2}
 \end{aligned}$$

So, the **RMS value of the AC component of the half-wave rectifier output** is given by

$$V_{ac(rms)} = V_m \sqrt{\frac{1}{4} - \frac{1}{\pi^2}} \cong 0.386 V_m \quad (3.1.24)$$

Example 3.11: Calculate the RMS value $V_{ac(rms)}$ of the AC component of the ideal full-wave rectifier output.

Solution: We are going to use the combined RMS equation given in (3.1.19) with the already calculated DC and RMS values of the ideal full-wave rectifier output given in (3.1.6) and (3.1.22), respectively, as follows

$$\begin{aligned}
 V_{ac(rms)}^2 &= V_{rms}^2 - V_{DC}^2 \\
 &= \left(\frac{V_m}{\sqrt{2}}\right)^2 - \left(\frac{2V_m}{\pi}\right)^2 \\
 &= \frac{V_m^2}{2} - \frac{4V_m^2}{\pi^2}
 \end{aligned}$$

So, the **RMS value of the AC component of the full-wave rectifier output** is given by

$$V_{ac(rms)} = V_m \sqrt{\frac{1}{2} - \frac{4}{\pi^2}} \cong 0.308 V_m \quad (3.1.25)$$

3.2 Half-Wave Rectifier

- Generating a waveform with a **non-zero mean** value, i.e., **non-zero DC component**, from an AC waveform (i.e., a zero-mean time-varying signal) is called **rectification**. The circuits which perform rectification are called **rectifiers**. This is a crude AC to DC conversion.
- A **half-wave rectifier** rectifies only half-cycle of the waveform, i.e., circuit conducts only for one-half of the AC cycle, maintaining the average of the output signal non-zero.
- A **half-wave rectifier circuit** is the same as the **series clipper circuit** shown in Figure 3.6 below.

 


Figure 3.6: A half-wave rectifier circuit.

- Sample input and ideal output waveforms for an half-wave rectifier such as given in Figure 3.6 are given in Figure 3.7 below.

 


Figure 3.7: Input and ideal output waveforms for the half-wave rectifier given in Figure 3.6.

- The DC voltage output of the half-wave rectifier is the DC component of the output waveform and as calculated before in (3.1.4) it is given by

$$V_{DC(\text{half-wave})} = \frac{1}{\pi} V_m \cong 0.318 V_m \quad (3.2.26)$$

where V_m is the peak voltage of the input sinusoidal signal.

- The output of the half-wave rectifier for $V_{D(ON)} = 0.7 \text{ V}$ is shown in Figure 3.8 below

 


Figure 3.8: Input and output waveforms for the half-wave rectifier when $V_{D(ON)} = 0.7 \text{ V}$.

When $V_{D(ON)} \neq 0$, the DC voltage output of the half-wave rectifier is approximately equal to

$$V_{DC(\text{half-wave})} \cong \frac{1}{\pi} V_m - \frac{1}{2} V_{D(ON)} = 0.318 V_m - 0.5 V_{D(ON)} \quad (3.2.27)$$

- When the diode is **OFF**, **maximum negative voltage** between the terminals of the diode is the negative peak value $-V_m$. So, the peak-inverse-voltage for the half-wave rectifier is given by

$$\text{PIV}_{(\text{half-wave rectifier})} = V_m \quad (3.2.28)$$

Thus, we need to select a diode with a PIV rating greater than V_m , i.e., $\text{PIV}_{\text{diode}} > V_m$, to use in our half-wave rectifier circuit.

3.3 Full-Wave Rectifier

- A **full-wave rectifier** rectifies both cycles of the waveform producing a higher DC output as shown in Figure 3.9 below

 


Figure 3.9: Input and ideal output waveforms of the full-wave rectifier.

- The DC voltage output of the full-wave rectifier is the DC component of the output waveform and as calculated before in (3.1.6) it is given by

$$V_{DC(\text{full-wave})} = \frac{2}{\pi} V_m \cong 0.636 V_m \quad (3.3.29)$$

where V_m is the peak voltage of the input sinusoidal.

Full-Wave Rectifier Circuits

There are two types of full-wave rectifier circuits:

1. Center-Tapped Transformer Full-Wave Rectifier
2. Full-Wave Bridge Rectifier

3.3.1 Center-Tapped Transformer Full-Wave Rectifier

Center-tapped transformer full-wave rectifier shown in Figure 3.10 below requires a center-tapped (CT) transformer to establish the replica of the input signal across each section of the secondary of the transformer and then combining two half-wave rectifiers together where the two half-wave rectifiers operate on opposite cycles of the input signal.

 


Figure 3.10: Center-tapped transformer full-wave rectifier.

Here, D_1 operates on the positive half-cycle and D_2 operates on the negative half-cycle of input v_i .

- Using the ideal diode model, operation of the center-tapped transformer full-wave rectifier are shown for positive and negative cycles in Figure 3.11 and Figure 3.12 below, respectively.

 


Figure 3.11: Positive half-cycle operation of the center-tapped transformer full-wave rectifier in Figure 3.10.

 


Figure 3.12: Negative half-cycle operation of the center-tapped transformer full-wave rectifier in Figure 3.10.

- When the diodes are **OFF**, **maximum negative voltage** between the terminals of the diodes are twice the negative peak value. So, the peak-inverse-voltage for the center-tapped transformer full-wave rectifier is given by

$$\boxed{\text{PIV}_{(\text{center-tapped})} = 2V_m} \quad (3.3.30)$$

- When the diodes are not ideal, i.e., $V_{D(ON)} \neq 0$, the DC voltage output of the center-tapped transformer full-wave rectifier is approximately equal to

$$\boxed{V_{DC(\text{center-tapped})} \cong \frac{2}{\pi} V_m - V_{D(ON)} = 0.636 V_m - V_{D(ON)}} \quad (3.3.31)$$

where V_m is the peak voltage of the input sinusoidal signal.

3.3.2 Full-Wave Bridge Rectifier

The most popular circuit to achieve full-wave rectification is four diodes in a bridge configuration as shown in Figure 3.13 below. The popularity of the rectifier comes from the fact that it eliminates the need for a transformer.

 


Figure 3.13: Full-wave bridge rectifier.

Here, D_2 and D_3 operate on the positive half-cycle, and D_4 and D_1 operate on the negative half-cycle of input v_i .

- Using the ideal diode model, operation of the full-wave bridge rectifier are shown for positive and negative cycles in Figure 3.14 and Figure 3.15 below, respectively.

 


Figure 3.14: Positive half-cycle operation of the full-wave bridge rectifier in Figure 3.13.

 


Figure 3.15: Negative half-cycle operation of the full-wave bridge rectifier in Figure 3.13.

- When the diodes are **OFF**, **maximum negative voltage** between the terminals of the diodes are equal to the negative peak value. So, the peak-inverse-voltage for the full-wave bridge rectifier is given by

$$\boxed{\text{PIV}_{(\text{bridge})} = V_m} \quad (3.3.32)$$

- The positive half-cycle operation and full output of the full-wave bridge rectifier for $V_{D(\text{ON})} = 0.7 \text{ V}$ is shown in Figure 3.16 below

 


Figure 3.16: Positive-half cycle operation and full output of the full-wave bridge rectifier when $V_{D(ON)} = 0.7 \text{ V}$.

When the diodes are not ideal, i.e., $V_{D(ON)} \neq 0$, the DC voltage output of the full-wave bridge rectifier is approximately equal to

$$V_{DC(\text{bridge})} \cong \frac{2}{\pi} V_m - 2V_{D(ON)} = 0.636 V_m - 2V_{D(ON)} \quad (3.3.33)$$

where V_m is the peak voltage of the input sinusoidal signal.

3.4 Rectifier Summary

Summary of the rectifier circuits is given in Table 3.1 below.

Table 3.1: Rectifier Summary

Rectifier	Ideal Output	Realistic Output	PIV
Half-Wave Rectifier	$V_{DC} = 0.318 V_m$	$V_{DC} = 0.318 V_m - 0.5 V_{D(ON)}$	V_m
Center-Tapped Transformer Full-Wave Rectifier	$V_{DC} = 0.636 V_m$	$V_{DC} = 0.636 V_m - V_{D(ON)}$	$2V_m$
Full-Wave Bridge Rectifier	$V_{DC} = 0.636 V_m$	$V_{DC} = 0.636 V_m - 2V_{D(ON)}$	V_m
Note: V_m is the peak value of the sinusoidal input voltage.			

Homework 3.1: Compare the center-tapped transformer rectifier and bridge rectifier listing their advantages and disadvantages. Which one is more preferable and why?

3.5 Voltage Regulation and Ripple Factor

 


Figure 3.17: Block diagram showing parts of a power supply.

A block diagram containing the parts of a typical power supply and the voltages at various points in the unit is shown in shown in Figure 3.17 above.

1. The mains AC voltage (120 Vrms 60 Hz in USA, and 230 Vrms 50 Hz in Europe), is connected to a transformer, which steps that AC voltage down to the level for the desired DC output.
2. A diode rectifier then provides a full-wave rectified voltage.
3. Full-wave rectified voltage is then filtered by a simple capacitor filter to produce a DC voltage. This resulting DC voltage usually has some **ripple** or AC voltage variation.
4. Finally, obtained DC voltage is regulated to obtain a desired fixed DC voltage. The regulation circuit takes a DC voltage and provides a somewhat lower DC voltage, which remains the same even if the input DC voltage varies or the output load changes. Although one of the simplest regulators is a Zener regulator, usually an integrated circuit (IC) voltage regulator unit is used for voltage regulation.

3.5.1 Voltage Regulation

- An important factor in a power supply is the amount the DC output voltage changes over a range of loads. The voltage provided at the output under no-load condition (no current drawn from the supply) is reduced when load current is drawn from the supply (under load). The amount the DC voltage changes between the no-load (NL) and full-load (FL) conditions is described by a factor called **voltage regulation** (VR) given by

$$\%VR = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100 \quad (3.5.34)$$

Example 3.12: A DC voltage supply provides 60 V when the output is unloaded. When connected to a load, the output drops to 56 V. Calculate the value of voltage regulation.

Solution:

$$\%VR = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100 = \frac{60 - 56}{56} \times 100 = 7.1\%.$$

- The smaller the voltage regulation, the better the operation of the voltage supply circuit.

3.5.2 Ripple Factor

 


Figure 3.18: Filter voltage waveform showing DC and ripple voltages.

- The filtered output shown in Figure 3.18 above has a DC value and some AC variation (ripple). The smaller the AC variation with respect to the DC level, the better the filter circuit's operation (or the better the power supply). This ratio is called the **ripple factor** (r) expressed by

$$\boxed{\%r = \frac{V_{r(\text{rms})}}{V_{DC}} \times 100} \quad (3.5.35)$$

where $V_{r(\text{rms})}$ the RMS value of the AC ripple voltage $v_r(t)$ fluctuating around the DC value V_{DC} at the output.

Example 3.13: Calculate the ripple factor of the ideal half-wave rectifier output shown in Figure 3.1.

Solution: From (3.1.5) and (3.1.24), we can obtain the ripple factor as

$$\%r_{(\text{half-wave})} = \frac{V_{ac(\text{rms})(\text{half-wave})}}{V_{DC(\text{half-wave})}} \times 100 = \frac{0.386 V_m}{0.318 V_m} \times 100 = 121\%.$$

Example 3.14: Calculate the ripple factor of the ideal full-wave rectifier output shown in Figure 3.2.

Solution: From (3.1.7) and (3.1.25), we can obtain the ripple factor as

$$\%r_{(\text{full-wave})} = \frac{V_{ac(\text{rms})(\text{full-wave})}}{V_{DC(\text{full-wave})}} \times 100 = \frac{0.308 V_m}{0.636 V_m} \times 100 = 48\%.$$

3.6 Capacitor Filter

 


Figure 3.19: Simple capacitor filter.

- A very popular filter circuit is the capacitor-filter circuit shown in Figure 3.19 above. A capacitor is connected at the rectifier output, and a DC voltage is obtained across the capacitor.

 


Figure 3.20: Capacitor filter after a center-tapped transformer full-wave rectifier.

- So, a full-wave rectifier integrated with a capacitor filter is shown in Figure 3.20 above.

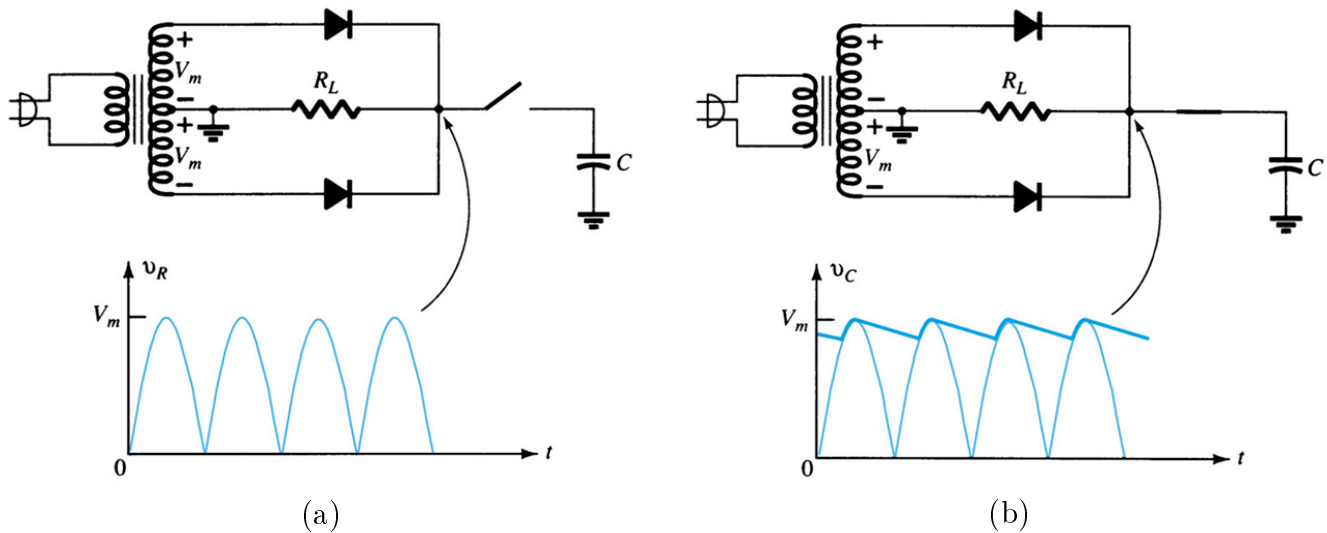


Figure 3.21: Capacitor filter operation: (a) ideal full-wave rectifier output, (b) filtered output voltage.

Figure 3.21(a) above shows the output voltage of the ideal full-wave rectifier before the signal is filtered,

while Figure 3.21(b) above shows the resulting waveform after the filter capacitor is connected at the rectifier output.

Notice that the filtered waveform is essentially a DC voltage with some ripple (or AC variation).

 


Figure 3.22: Capacitor filter output after a full-wave rectifier: (a) actual output, (b) approximate output where ripple waveform is approximated by a triangular waveform.

- When we analyse the capacitor filter output shown in Figure 3.22(a) above,
 - Time T_1 is the time during which diodes of the full-wave rectifier conduct, charging the capacitor up to the peak rectifier voltage, V_m .
 - Time T_2 is the time interval during which the rectifier voltage drops below the peak voltage, and the capacitor discharges through the load.
- Since the charge-discharge cycle occurs for each half-cycle for a full-wave rectifier, the period of the rectified waveform is $T/2$ (one-half the input signal frequency).
- The **ripples** of the filtered voltage can be approximated by a **triangular waveform** as shown in Figure 3.22(b) above, where the output waveform has a DC level V_{DC} and a triangular ripple voltage $V_{r(rms)}$ as the capacitor charges and discharges.

3.6.1 Ripple Factor of Capacitor Filter

 


Figure 3.23: Capacitor filter output (after a full-wave rectifier) with charging and discharging timings.

Let us derive the expression for the ripple factor of the capacitor filter output shown in Figure 3.23 above

1. Charging period T_1 and discharging period T_2 together constitute the whole period $T/2$. Thus,

$$T_2 = \frac{T}{2} - T_1 \quad (3.6.36)$$

2. Peak-to-peak ripple voltage $V_{r(p-p)}$ is given by

$$V_{r(p-p)} = 2(V_m - V_{DC}) \quad (3.6.37)$$

3. We can express discharge current (i.e., load current) I_{DC} as follows

$$I_{DC} = C \frac{\Delta V}{\Delta t} = C \frac{V_{r(p-p)}}{T_2} \quad (3.6.38)$$

4. Using similar triangles we can obtain an expression for T_1

$$\frac{V_{r(p-p)}}{T_1} \cong \frac{V_m}{T/4} \quad (3.6.39)$$

$$T_1 \cong \frac{V_{r(p-p)} T}{V_m} \frac{1}{4} \quad (3.6.40)$$

$$\cong \frac{2(V_m - V_{DC}) T}{V_m} \frac{1}{4} \quad \dots \text{from (3.6.37), (3.6.41)}$$

$$\cong \frac{T}{2} - \frac{V_{DC} T}{2V_m} \quad (3.6.42)$$

5. We can obtain T_2 from Step 1 and Step 3, i.e., from (3.6.37) and (3.6.42)

$$T_2 = \frac{V_{DC} T}{2V_m} \quad (3.6.43)$$

6. We can obtain $V_{r(p-p)}$ from Step 3 and Step 5, i.e., from (3.6.38) and (3.6.43)

$$\boxed{V_{r(p-p)} = \frac{I_{DC} V_{DC}}{2fC V_m} = \frac{I_{DC} V_{DC}}{f_{\text{ripple}}C V_m}} \quad (3.6.44)$$

where $f_{\text{ripple}} = 2f$ and $f = 1/T$ is the frequency of the input AC voltage.

7. Similarly, we can obtain $V_{r(\text{rms})}$ from Step 6 by using the RMS value of an AC triangular waveform given in (3.1.23)

$$V_{r(\text{rms})} = \frac{V_{r(p-p)}}{2\sqrt{3}} \quad \dots \text{i.e., } V_{r(p)} = \sqrt{3}V_{r(\text{rms})} \quad (3.6.45)$$

$$= \frac{I_{DC} V_{DC}}{2\sqrt{3}f_{\text{ripple}}C V_m} \quad (3.6.46)$$

8. Thus, ripple factor r is given by

$$r = \frac{V_{r(\text{rms})}}{V_{DC}} \quad (3.6.47)$$

$$= \frac{1}{2\sqrt{3}f_{\text{ripple}}C R_L} \frac{V_{DC}}{V_m} \quad \dots \text{as } V_{DC} = I_{DC}R_L \quad (3.6.48)$$

Due to $V_{r(p)} = \sqrt{3}V_{r(\text{rms})}$ and $V_m = V_{DC} + V_{r(p)}$, we obtain $\frac{V_{DC}}{V_m}$ as

$$\boxed{\frac{V_{DC}}{V_m} = \frac{V_{DC}}{V_{DC} + V_{r(p)}} = \frac{1}{1 + \frac{V_{r(p)}}{V_{DC}}} = \frac{1}{1 + \frac{\sqrt{3}V_{r(\text{rms})}}{V_{DC}}} = \frac{1}{1 + \sqrt{3}r}} \quad (3.6.49)$$

9. For light load (i.e., $r < 6.5\%$), $\frac{V_{DC}}{V_m} = \frac{1}{1 + \sqrt{3}r}$ ratio approaches to one, i.e.,

$$\frac{V_{DC}}{V_m} \cong 1.$$

So, expression for the ripple factor r reduces to

$$\boxed{r \cong \frac{1}{2\sqrt{3}f_{\text{ripple}}C R_L}} \quad (3.6.50)$$

10. Hence when $\frac{V_{DC}}{V_m} \cong 1$, peak-to-peak ripple voltage $V_{r(p-p)}$ becomes

$$\boxed{V_{r(p-p)} \cong \frac{I_{DC}}{f_{\text{ripple}}C}} \quad (3.6.51)$$

Thus, the **larger** the **capacitor** the **smaller** the **ripple voltage** and ripple factor.

3.6.2 Diode Conduction Period and Peak Diode Current

Larger values of capacitance provide less ripple and higher average voltage, thereby providing better filter action. From this, one might conclude that to improve the performance of a capacitor filter it is only necessary to increase the size of the filter capacitor. The capacitor, however, also affects the peak current drawn through the rectifying diodes, and as will be shown next, the larger the value of the capacitor, the larger the peak current drawn through the rectifying diodes.

Recall that the diodes conduct during period T_1 , during which time the diode must provide the necessary average current to charge the capacitor. The shorter this time interval, the larger the amount of the charging current. Figure 3.24 shows this relation for a half-wave rectified signal (it would be the same basic operation for full-wave). Notice that for smaller values of capacitor, with T_1 larger, the peak diode current is less than for larger values of filter capacitor.

 


Figure 3.24: Capacitor filter output voltage and diode current waveforms for a half-wave rectifier: (a) small C , (b) large C .

Since the total discharge must equal to total charge, the following relation can be used (assuming constant diode current during charging period):

$$I_{DC}T_2 = I_{\text{peak}}T_1 \quad (3.6.52)$$

$$I_{\text{peak}} = \frac{T_2}{T_1} I_{DC} \quad (3.6.53)$$

where $T_2 \cong T$ for a half-wave rectifier as shown in Figure 3.24 above. Similarly, $T_2 \cong \frac{T}{2}$ for a full-wave rectifier.

- Note that $f_{\text{ripple}} = f$ for a half-wave rectifier as seen from Figure 3.24, and $f_{\text{ripple}} = 2f$ for a full-wave rectifier as seen from Figure 3.22.

Example 3.15: (2004-2005 MI) A power-supply circuit is needed to deliver 0.1 A and an average of 15 V to a load. The AC source available is 230 V_{rms} with a frequency of 50 Hz. Assume that a **full-wave rectifier** circuit is to be used with a smoothing capacitor in parallel with the load as shown in the figure below. The **peak-to-peak** ripple voltage is to be 0.4 V. Allow $V_{D(ON)} = 0.7\text{ V}$ for the forward diode voltage drop.

Find

- The turns-ratio $n = N_1/N_2$ that is needed,
- The load resistor R_L , and
- The approximate value of the smoothing capacitor C .

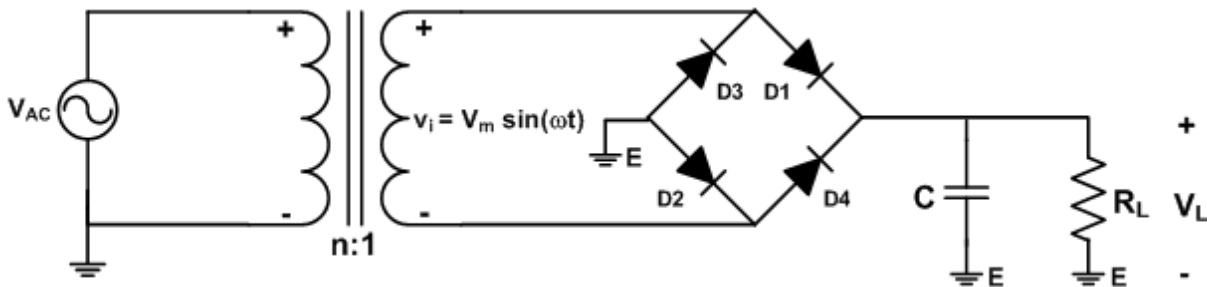
 


Figure 3.25: Capacitor filter circuit for Example 3.15.

Solution: For a full-wave bridge rectifier, DC voltage drop due to the diodes is $2V_{D(ON)}$.

- As $V_{DC} = 15\text{ V}$ and $V_{r(p-p)} = 0.4\text{ V}$, peak value V_m of the AC voltage at the secondary terminal of the transformer is given by

$$V_m = V_{DC} + V_{r(p-p)}/2 + 2V_{D(ON)} = 15 + 0.4/2 + 2(0.7) = 16.6\text{ V}.$$

Thus the turns ratio n is given by

$$n = \frac{V_{AC(p)}}{V_m} = \frac{\sqrt{2}V_{AC(rms)}}{V_m} = \frac{\sqrt{2}(230)}{16.6} = 19.6.$$

- As $V_{DC} = 15\text{ V}$ and $I_{DC} = 0.1\text{ A}$, R_L is given by

$$R_L = \frac{V_{DC}}{I_{DC}} = \frac{15}{0.1} = 150\ \Omega.$$

- As $\frac{V_{DC}}{V_{DC} + V_{r(p)}} = \frac{15}{15.2} \cong 1$, then $V_{r(p-p)} \cong \frac{I_{DC}}{f_{ripple}C}$. So, capacitor C is given by

$$C = \frac{I_{DC}}{f_{ripple}V_{r(p-p)}} = \frac{I_{DC}}{2fV_{r(p-p)}} = \frac{0.1}{2(50)(0.4)} = 2.5\text{ mF}.$$

3.7 Additional RC Filter

 


Figure 3.26: Additional RC filter stage.

It is possible to further reduce the amount of ripple across a filter capacitor by using an additional RC filter section as shown in Figure 3.26 above.

The purpose of the added RC section is to pass most of the DC component while attenuating (reducing) as much of the AC component as possible. Figure 3.27 shows a full-wave rectifier with capacitor filter followed by an RC filter section.

Thus, adding an RC section will further reduce the ripple voltage and decrease the surge current through the diodes.

 


Figure 3.27: Center-tapped transformer full-wave rectifier and RC filter circuit.

As ripple component of the capacitor filter is much smaller than the DC component, the operation of the filter circuit can be analysed using **superposition** for the DC and AC components of signal.

- So, we are going to first use the DC equivalent circuit (i.e., DC analysis) in order to obtain V'_{DC} .
- Then, we are going to use the AC equivalent circuit (i.e., AC analysis) in order to obtain $V'_{r(rms)}$.

3.7.1 DC Operation

 


Figure 3.28: DC equivalent circuit of the additional RC filter stage in Figure 3.26.

DC equivalent circuit, where both capacitors are open-circuit for DC operation, of the additional RC filter stage is shown in Figure 3.28 above.

Thus, DC output of the RC filter stage is given by

$$V'_{DC} = \frac{R_L}{R + R_L} V_{DC} \quad (3.7.54)$$

where V_{DC} is the DC output of the capacitor filter.

3.7.2 AC Operation

 


Figure 3.29: AC equivalent circuit of the additional RC filter stage in Figure 3.26.

AC equivalent circuit of the additional RC filter stage is shown in Figure 3.29 above.

So, AC output of the RC filter stage is given by

$$V'_{r(\text{rms})} = \left| \frac{1}{1 + \frac{R}{Z'}} \right| V_{r(\text{rms})} \quad (3.7.55)$$

where Z' is the parallel impedance of the capacitor C_2 and the load R_L , i.e.,

$$Z' = Z_C || R_L \quad (3.7.56)$$

$$|Z'| = \frac{R_L X_C}{\sqrt{R_L^2 + X_C^2}} \quad (3.7.57)$$

and $Z_C = -jX_C$ with $X_C = \frac{1}{\omega C_2}$ and $\omega = 2\pi f_{\text{ripple}}$.

Simplification

- If $R_L \gg X_C$, e.g., $R_L \geq 5X_C$, then $|Z'| \cong X_C$.

Consequently, $V'_{r(\text{rms})}$ could be written as

$$V'_{r(\text{rms})} \cong \frac{1}{\sqrt{1 + \frac{R^2}{X_C^2}}} V_{r(\text{rms})} = \frac{X_C}{\sqrt{R^2 + X_C^2}} V_{r(\text{rms})} \quad (3.7.58)$$

- Additionally if $\frac{R^2}{X_C^2} \gg 1$, then the above expression further reduces to

$$V'_{r(\text{rms})} \approx \frac{X_C}{R} V_{r(\text{rms})} \quad (3.7.59)$$

Example 3.16: Consider the circuit below with $f_{\text{ripple}} = 50 \text{ Hz}$, $C_2 = 10 \mu\text{F}$ and $R_L = 2 \text{ k}\Omega$, and calculate X_{C_2} and $|Z_{C_2} || R_L|$.

 


Figure 3.30: Capacitor filter circuit for Example 3.16.

Solution: Let us calculate X_C and $|Z'|$ where $X_C = X_{C_2}$ and $Z' = Z_{C_2} || R_L$

$$X_C = \frac{1}{2\pi f_{\text{ripple}} C_2} = \frac{1}{2\pi(50)(10\mu)} = 318 \Omega,$$

$$|Z'| = \frac{R_L X_C}{\sqrt{R_L^2 + X_C^2}} = \frac{(2k)(318)}{\sqrt{(2k)^2 + (318)^2}} = 314 \Omega.$$

Thus, the assumption $|Z'| \cong X_C$ holds when $R_L \geq 5X_C$.

Example 3.17: Consider the circuit in Figure 3.31 below with $f_{\text{mains}} = 50 \text{ Hz}$.

- Find the DC and AC voltages over the load,
- Find the ripple factors, $\%r$ and $\%r'$ values,
- Find the voltage regulation factor $\%VR$.

 


Figure 3.31: Capacitor filter circuit for Example 3.17.

Solution: As a full-wave rectifier is used $f_{\text{ripple}} = 2f_{\text{mains}} = 100 \text{ Hz}$.

- Let us find V'_{DC} first

$$V'_{DC} = \frac{R_L}{R + R_L} V_{DC} = \frac{5k}{0.5k + 5k} 150 = 136.4 \text{ V}.$$

We see that DC voltage value dropped by 13.6 V.

Now, let us find X_C

$$X_C = \frac{1}{2\pi f_{\text{ripple}} C_2} = \frac{1}{2\pi(100)(10\mu)} = 159 \Omega$$

As $R_L \gg X_C$,

$$V'_{r(\text{rms})} = \frac{X_C}{\sqrt{R^2 + X_C^2}} V_{r(\text{rms})} = \frac{159}{\sqrt{500^2 + 159^2}} 15 = 4.55 \text{ V}$$

We see that ripple voltage reduced by a factor of 3.3 times.

- Ripple factors before $\%r$ and after $\%r'$ are given by

$$\begin{aligned} \%r &= \frac{V_{r(\text{rms})}}{V_{DC}} \times 100 = \frac{15}{150} \times 100 = 10\% \\ \%r' &= \frac{V'_{r(\text{rms})}}{V'_{DC}} \times 100 = \frac{4.55}{136.4} \times 100 = 3.34\% \end{aligned}$$

We see that ripple factor reduced by a factor of 3 times.

c) Voltage regulation %VR is given by

$$\%VR = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100 = \frac{150 - 136.4}{136.4} \times 100 = 9.97\%.$$

- If we want the DC voltage drop to be smaller but AC ripple drop to be higher, we can achieve it by replacing the resistor R with a component such that its DC resistance is small while its AC resistance is high. Such a component is an **inductor**.

3.8 π -Filter

 


Figure 3.32: π -filter stage.

By replacing resistor R in the RC filter with inductor L , we obtain a π -filter as shown in Figure 3.32 above.

While DC resistance R_ℓ of the coil is small and its AC reactance X_L is high.

Example 3.18: For the π -filter shown in Figure 3.32, the output DC voltage and current are given as 200 V and 50 mA. Also $V_{DC(C_1)} = 210$ V, $V_{r(C_1)} = 12$ Vrms and the frequency of the ripple voltage $f_{\text{ripple}} = 100$ Hz. In order to satisfy $r' \leq 2\%$, determine the values of R_L , R_ℓ , L and C_2 . Explain any assumptions you make. NOTE: R_ℓ denotes the DC resistance of the coil.

Solution: As $V'_{DC} = 200$ V and $I'_{DC} = 50$ mA, the load R_L is given by

$$R_L = V'_{DC}/I'_{DC} = 200/50m = 4 \text{ k}\Omega.$$

We know that $V'_{DC} = \frac{R_L}{R_\ell + R_L} V_{DC}$, so R_ℓ is given by

$$R_\ell = (V_{DC} - V'_{DC})R_L/V'_{DC} = (210 - 200)/200 = 200 \Omega.$$

Let us find the ripple voltage requirement as $V'_{r(\text{rms})} \leq (2\%)V'_{DC} = (2\%)(200) = 4$ Vrms

$$V'_{r(\text{rms})} \leq 4 \text{ Vrms}.$$

Let us select $X_C \ll R_L$ as $X_C = R_L/10 = 4k/10 = 400 \Omega$.

Note that $Z_L = R_\ell + jX_L$, and assuming $X_L \gg R_\ell$ we will take $Z_L \cong jX_L$.

We know that $\frac{X_L - X_C}{X_C} \geq \frac{V_{r(\text{rms})}}{V'_{r(\text{rms})}} = \frac{12}{4} = 3$, so X_L is given by

$$X_L \geq 4X_C = (4)(400) = 1.6 \text{ k}\Omega$$

So, let us select $X_L = 1.7 \text{ k}\Omega$ and find the value of inductance L as follows

$$L = \frac{X_L}{\omega} = \frac{X_L}{2\pi f_{\text{ripple}}} = \frac{1.7 \text{ k}}{2\pi(100)} = 2.7 \text{ H.}$$

As $X_C = 400 \Omega$, we can find the value of capacitance C as follows

$$C = \frac{1}{\omega X_C} = \frac{1}{2\pi f_{\text{ripple}} X_C} = \frac{1}{2\pi(100)(400)} = 4 \mu\text{F.}$$

Chapter 4

Bipolar Junction Transistor (BJT)

4.1 Bipolar Junction Transistor

Bipolar junction transistor (BJT) is a three-layer semiconductor device consisting of either two *n*- and one *p*-type layers of material or two *p*- and one *n*-type layers of material. The former is called an *npn* transistor, and the latter is called a *pnp* transistor. Both are shown in Figure 4.1 below with the proper DC biasing.

The terminals have been indicated by the capital letters *E* for **emitter**, *C* for **collector**, and *B* for **base**. Emitter is the source of the majority carriers (electrons in an *npn* transistor and holes in a *pnp* transistor). In simple wording, majority carriers are emitted from the emitter and collected by the collector.

The term **bipolar** reflects the fact that holes and electrons participate in the current conduction process.

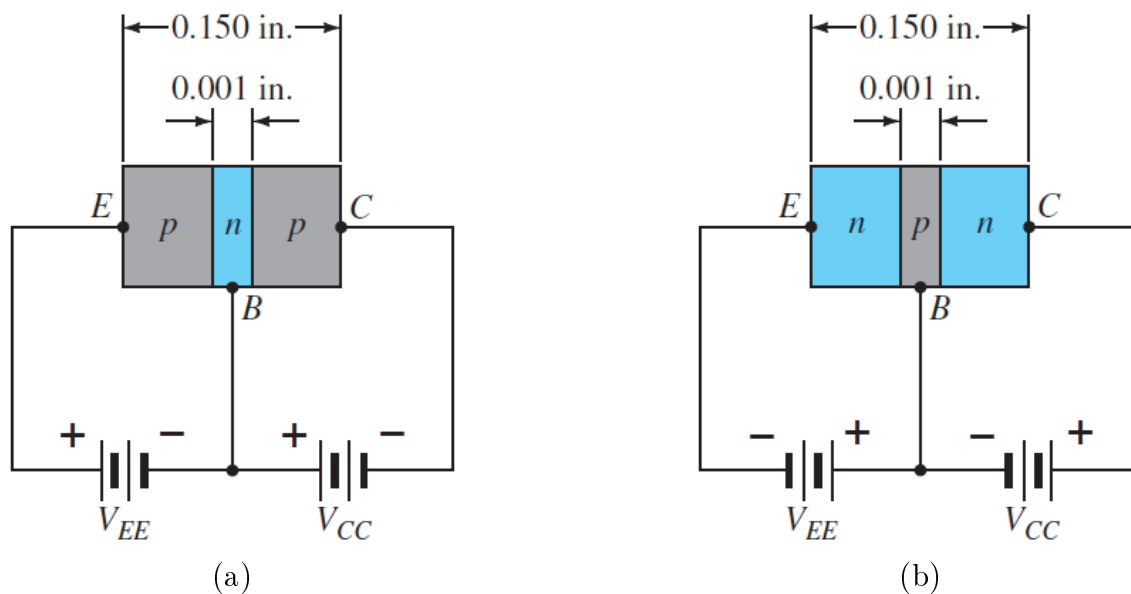


Figure 4.1: Types of transistors: (a) *pnp*, (b) *npn*.

The basic operation of the transistor will now be described using the *pn*p transistor. The operation of the *npn* transistor is exactly the same if the roles played by the electron and hole are interchanged. In Figure 4.2(a) below *pn*p transistor has been redrawn by removing the bias of base-collector junction (keeping base-emitter junction forward-biased). The depletion region has been reduced in width due to the applied bias, resulting in a heavy flow of **majority carriers** from emitter to base (i.e., **holes** from **emitter** to **base**).

Let us now remove the bias of base-emitter junction (keeping base-collector junction reverse-biased) as shown in Figure 4.2(b) below. Recall that the flow of majority carriers (electrons from base to collector) is zero, resulting in only a **minority-carrier** flow (i.e., **holes** from **base** to **collector**).

 


Figure 4.2: Biasing a transistor: (a) base-emitter forward-biased, (b) base-collector reverse-biased.

Once the **base-emitter** junction is **forward-biased**, and **base-collector** junction **reverse-biased** at the same time.

Then, most of the **holes** (majority carriers of the emitter region) coming from emitter region to the base region are **swept away** to the collector region as holes are the minority carriers for the base region and base-collector junction is reverse biased.

This basic transistor operation is shown in Figure 4.3 below as

$$\boxed{I_E = I_C + I_B} \tag{4.1.1}$$

where collector current I_C is comprised of two components

$$I_C = I_{C(\text{majority})} + I_{CO(\text{minority})} \cong I_{C(\text{majority})} \tag{4.1.2}$$

Here, the minority-current component is called the **leakage current** with the symbol I_{CO} (reverse-bias I_C current with emitter terminal open). Generally I_C is measured in milliamperes and I_{CO} is measured in microamperes or nanoamperes. I_{CO} , like I_s for a reverse-biased diode, is temperature sensitive and must be examined carefully when applications of wide temperature ranges are considered.

 


Figure 4.3: Current flow in a properly biased *pnp* transistor.

4.2 Common-Base Configuration

The common-base terminology is derived from the fact that the **base** is **common** to both the input and output sides of the configuration. In addition, the base is usually the terminal closest to, or at, ground potential.

On the BJT **circuit symbol**, an **arrow** is always drawn at the **emitter** leg of the transistor as shown in Figures 4.4(a) and 4.4(b) below in the **forward direction** of the base-emitter *pn* junction like the diode symbol. Hence, from the direction of the arrow we can determine type of the transistor, i.e., *npn* or *pnp*.

 


Figure 4.4: Notation and symbols used with the common-base configuration: (a) *nnp* transistor, (b) *pnp* transistor.

4.2.1 Input and Output Characteristics

To fully describe the behavior of a three-terminal device requires two sets of characteristics—one for the input parameters and the other for the output side.

The input set for the common-base amplifier relates an input current (I_E) to an input voltage (V_{BE}) for various levels of output voltage (V_{CB}) as shown in Figure 4.5(a) below.

The output set relates an output current (I_C) to an output voltage (V_{CB}) for various levels of input current (I_E) as shown in Figure 4.5(b) below. The output set of characteristics has three basic regions of interest, the **active**, **cutoff**, and **saturation** regions. The active region is the region normally employed for linear amplifiers.

 


Figure 4.5: Characteristics of an *npn* common-base amplifier: a) Input characteristics, b) Output characteristics.

4.2.2 Three Modes of Operation

 


Figure 4.6: Output characteristics of a common-base amplifier.

- **Cut-Off:** The amplifier is basically off: $I_E = 0$ A, $I_C = I_{CBO} \cong 0$ A and $I_B \cong 0$ A.
 - Base-Emitter junction: **reverse-biased**, i.e., OFF.
 - Base-Collector junction: **reverse-biased**, i.e., OFF.
- **Active:** *Operating region of the amplifier:* $I_C \cong I_E$ and $V_{BE} \cong V_{BE(ON)}$.

- Base-Emitter junction: **forward-biased**, i.e., ON.
- Base-Collector junction: **reverse-biased**, i.e., OFF.
- **Saturation:** The amplifier is saturated: $I_C = I_{C(sat)}$ and $V_{CE} = V_{CE(sat)} \cong 0\text{ V}$.
 - Base-Emitter junction: **forward-biased**, i.e., ON.
 - Base-Collector junction: **forward-biased**, i.e., ON.

4.2.3 Currents

- For any mode (or state) of the transistor and for any configuration, emitter current is **always** the **sum** of the base and collector currents, i.e.,

$$\boxed{I_E = I_C + I_B} \quad (4.2.3)$$

- Note that, collector current I_C is comprised of majority and minority carrier current components

$$I_C = I_{C(\text{majority})} + I_{C(\text{minority})} = I_{C(\text{majority})} + I_{CO} \cong I_{C(\text{majority})} \quad (4.2.4)$$

where I_{CO} is called the reverse saturation current (or leakage current). The notation most frequently used for I_{CO} in data and specification sheets is I_{CBO} (the collector-to-base current with the emitter leg open) as shown in Figure 4.7 below.

 


Figure 4.7: Common-base cutoff current (or reverse saturation current), I_{CBO} .

4.2.4 Alpha (α)

- In the active mode the DC levels of I_C and I_E due to the majority carriers are related by a quantity called alpha (α_{DC}), i.e., $I_{C(\text{majority})} = \alpha_{DC} I_E$. However, as I_{CBO} is very small we define α_{DC} as

$$\boxed{\alpha_{DC} = \frac{I_C}{I_E}} \quad (4.2.5)$$

In the specification sheets, α_{DC} is expressed as h_{FB} which is the static forward current transfer ratio.

- For AC situations where the point of operation moves on the characteristic curve, an AC alpha (α_{ac}) is defined by

$$\alpha_{ac} = \left. \frac{\Delta I_C}{\Delta I_E} \right|_{V_{CB} = \text{constant}} = \left. \frac{\partial I_C}{\partial I_E} \right|_{Q\text{-point}} \quad (4.2.6)$$

In the specification sheets, α_{ac} is expressed as h_{fb} which is the small signal forward current transfer ratio.

- For most situations the magnitudes of α_{ac} and α_{DC} are quite close, permitting the use of the magnitude of one for the other, i.e.,

$$\alpha = \alpha_{ac} = \alpha_{DC} \cong 1. \quad (4.2.7)$$

Ideally $\alpha = 1$, but in reality it lies between 0.9 and 0.998.

4.2.5 Simplification (Active Mode)

 


Figure 4.8: Simplified output characteristics of a common-base amplifier.

- As we see from Figure 4.8 above,

$$I_C \cong I_E \quad (4.2.8)$$

i.e., $\alpha \cong 1$

 


Figure 4.9: Simplified input characteristics of a common-base amplifier.

- As we see from Figure 4.9 above,

$$V_{BE} \cong V_{BE(ON)} = 0.7 \text{ V}. \quad (4.2.9)$$

4.2.6 AC Amplification

 


Figure 4.10: AC equivalent circuit of a common-base amplifier.

Example 4.1: For Figure 4.10 above, find output v_o and voltage gain A_v .

Solution: Let us first find $i_i = i_e$ as,

$$i_i = i_e = \frac{v_i}{R_i} = \frac{200 \text{ mV}}{20 \Omega} = 10 \text{ mA}.$$

As $\alpha_{ac} \cong 1$, $i_c \cong i_e = 10 \text{ mA}$. Thus, $i_o = \frac{R_o}{R_o + R} i_c = \frac{100k}{100k + 5k} i_c \cong i_c = 10 \text{ mA}$.

Consequently, output voltage v_o and voltage gain A_v are given by

$$v_o = i_o R = (10 \text{ mA})(5 \text{ k}\Omega) = 50 \text{ V},$$

$$A_v = \frac{v_o}{v_i} = \frac{50 \text{ V}}{200 \text{ mV}} = 250.$$

4.3 Common-Emitter Configuration

The common-emitter terminology is derived from the fact that the **emitter** is **common** to both the input and output sides of the configuration. In addition, the emitter is usually the terminal closest to, or at, ground potential.

On the BJT **circuit symbol**, an **arrow** is always drawn at the **emitter** leg of the transistor as shown in Figures 4.11(a) and 4.11(b) below in the **forward direction** of the base-emitter pn junction like the diode symbol. Hence, from the direction of the arrow we can determine type of the transistor, i.e., nnp or pnp .

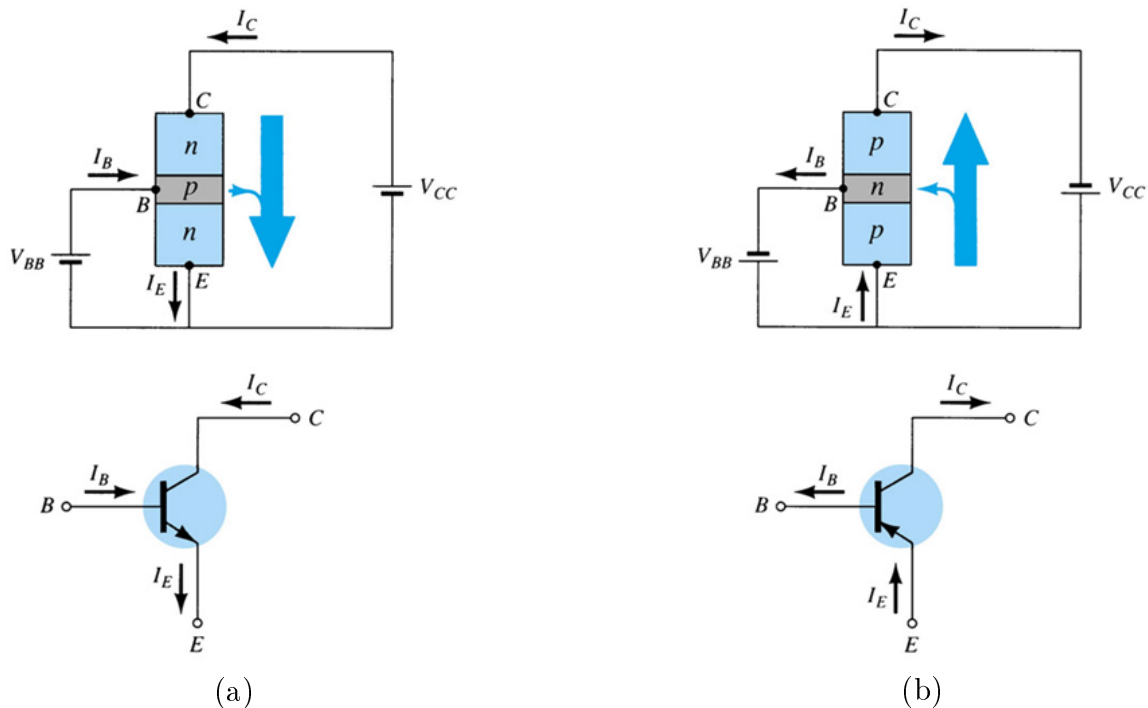


Figure 4.11: Notation and symbols used with the common-emitter configuration: (a) nnp transistor, (b) pnp transistor.

4.3.1 Input and Output Characteristics

The input set for the common-emitter amplifier relates an input current (I_B) to an input voltage (V_{BE}) for various levels of output voltage (V_{BC}) as shown in Figure 4.12(a) below.

The output set relates an output current (I_C) to an output voltage (V_{CE}) for various levels of input current (I_B) as shown in Figure 4.12(b) below. The output set of characteristics has three basic regions of interest, the **active**, **cutoff**, and **saturation** regions. The active region is the region normally employed for linear amplifiers.

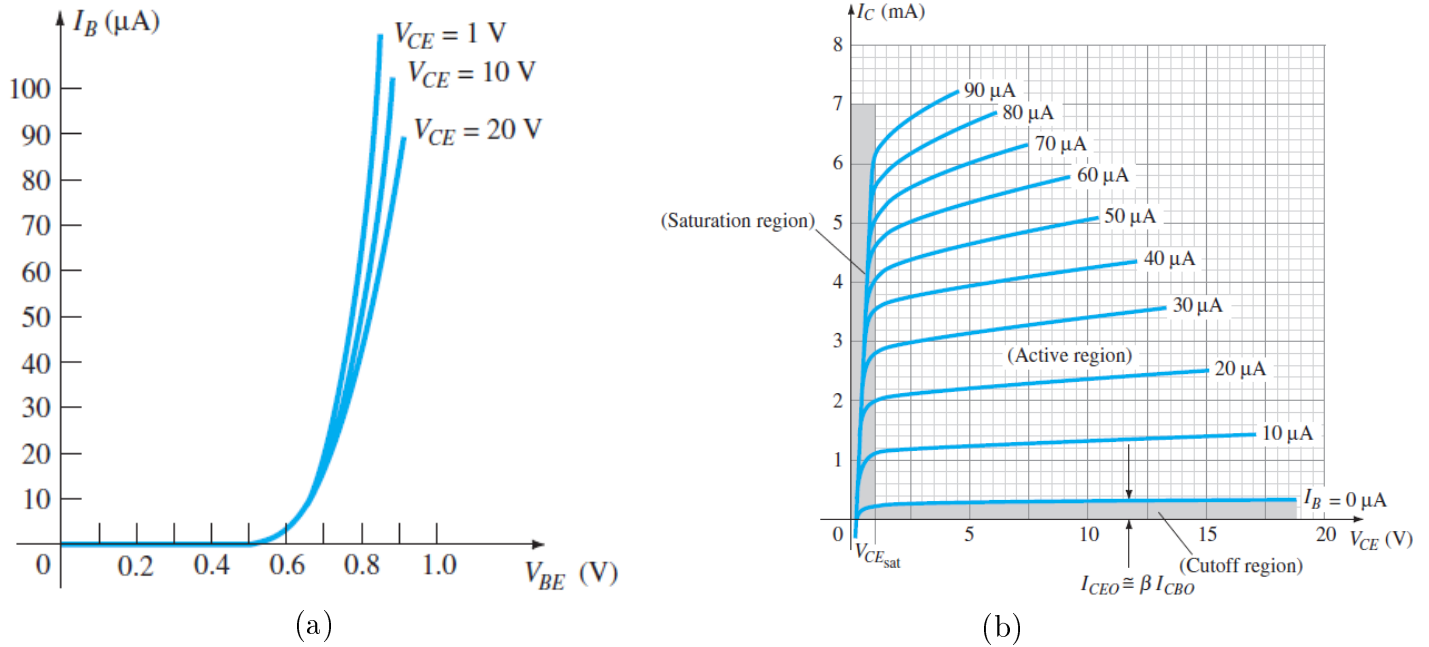


Figure 4.12: Characteristics of an *n*pn common-emitter amplifier: a) Input characteristics, b) Output characteristics.

4.3.2 Currents

Collector current I_C is given by $I_C = \alpha I_E + I_{CBO}$ where $I_E = I_C + I_B$. So,

$$I_C = \alpha I_E + I_{CBO} \quad (4.3.10)$$

$$= \alpha (I_C + I_B) + I_{CBO} \quad (4.3.11)$$

$$= \frac{\alpha}{1 - \alpha} I_B + \frac{1}{1 - \alpha} I_{CBO} \quad (4.3.12)$$

$$= \beta I_B + I_{CEO} \quad (4.3.13)$$

$$\cong \beta I_B \quad (4.3.14)$$

where I_{CEO} is the common-emitter cutoff current (or the collector-to-emitter current with the base leg open) as shown in Figure 4.13 below and defined by

$$I_{CEO} = \left. \frac{I_{CBO}}{1 - \alpha} \right|_{I_B = 0 \text{ A}} = (\beta + 1) I_{CBO} \quad (4.3.15)$$

 


Figure 4.13: Common-emitter cutoff current, I_{CEO} .

4.3.3 Beta (β)

- In the active mode, the DC levels of I_C and I_B are related by a quantity called beta (β_{DC}). However, as I_{CEO} is very small, we define β_{DC} as

$$\boxed{\beta_{DC} = \frac{I_C}{I_B}} \quad (4.3.16)$$

In the specification sheets, β_{DC} is expressed as h_{FE} which is the static forward current gain.

- For AC situations where the point of operation moves on the characteristic curve, an AC beta (β_{ac}) is defined by

$$\beta_{ac} = \left. \frac{\Delta I_C}{\Delta I_B} \right|_{V_{CE}=\text{constant}} = \left. \frac{\partial I_C}{\partial I_B} \right|_{Q\text{-point}} \quad (4.3.17)$$

In the specification sheets, β_{ac} is expressed as h_{fe} which is the small signal forward current gain.

- For most situations the magnitudes of β_{ac} and β_{DC} are quite close, permitting the use of the magnitude of one for the other, i.e.,

$$\boxed{\beta = \beta_{ac} = \beta_{DC}} \quad (4.3.18)$$

4.3.3.1 Determining β from a graph

 


Figure 4.14: Determining β_{DC} and β_{ac} from the output characteristics.

Example 4.2: From Figure 4.14 above, determine β_{DC} and β_{ac} .

Solution: Reading the values at Q -point, i.e., at $V_{CEQ} = 7.5\text{ V}$, from the figure above, β_{DC} and β_{ac} are given by

$$\beta_{DC} = \frac{I_{CQ}}{I_{BQ}} = \frac{2.7\text{ mA}}{25\text{ }\mu\text{A}} = 108$$

$$\beta_{ac} = \left. \frac{\Delta I_C}{\Delta I_B} \right|_{Q\text{-point}} = \frac{3.2\text{ mA} - 2.2\text{ mA}}{30\text{ }\mu\text{A} - 20\text{ }\mu\text{A}} = 100$$

We see that $\beta_{ac} \cong \beta_{DC}$.

4.3.4 Relationship between β and α

- As we derived before, β is given by

$$\boxed{\beta = \frac{\alpha}{1 - \alpha}} \quad (4.3.19)$$

- Similarly, α is given by

$$\boxed{\alpha = \frac{\beta}{\beta + 1}} \quad (4.3.20)$$

4.3.5 Simplification (Active Mode)

Simplification (Active Mode)

- In the active mode, collector and emitter currents I_C and I_E are given by

$$I_C = \beta I_B \quad (4.3.21)$$

$$I_E = (\beta + 1) I_B \quad \dots \text{ as } I_E = I_C + I_B \quad (4.3.22)$$

- Base-emitter junction is also ON. So,

$$V_{BE} \cong V_{BE(ON)} = 0.7\text{ V}. \quad (4.3.23)$$

4.4 Common-Collector Configuration

The common-collector terminology is derived from the fact that the **collector** is **common** to both the input and output sides of the configuration. In addition, the collector is usually the terminal closest to, or at, ground potential.

Input and output characteristics are similar to those of the common-emitter amplifier, except the output current is the emitter current I_E instead of the collector current I_C .

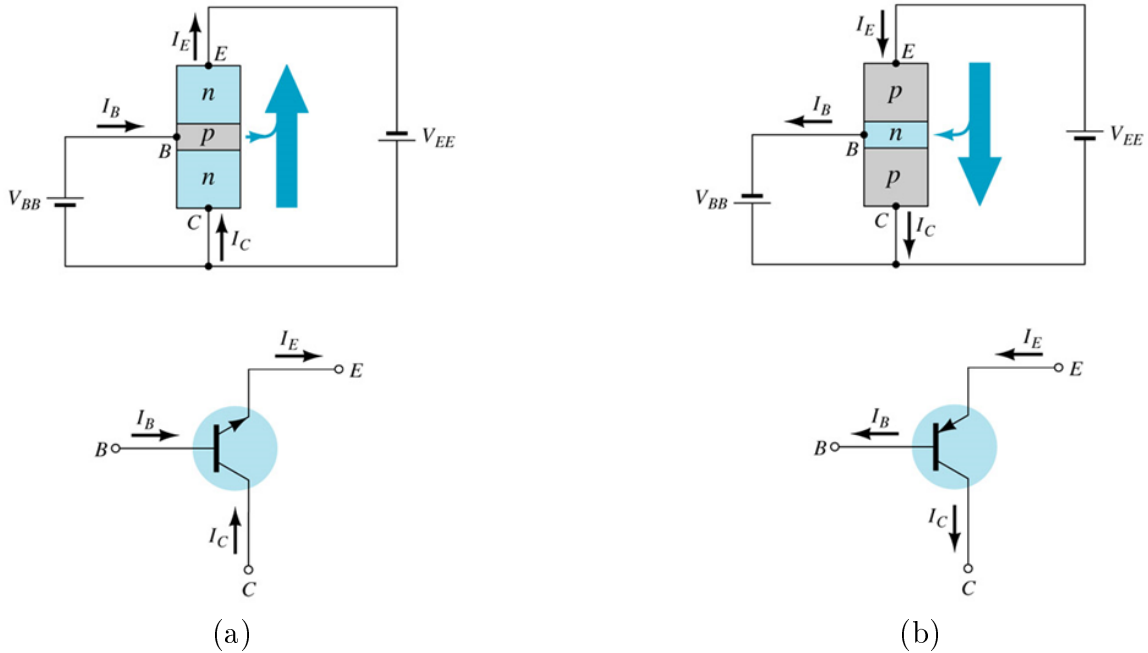


Figure 4.15: Notation and symbols used with the common-collector configuration: (a) *npn* transistor, (b) *pnp* transistor.

4.5 Operating Limits

 


Figure 4.16: Defining the region of operation for a transistor.

The figure above shows the limitations for the linear region of a common-emitter configuration:

1. Maximum and minimum CE voltages: BV_{CEO} and $V_{CE(sat)}$. Maximum collector-to-emitter voltage is often abbreviated as BV_{CEO} or $V_{(BR)CEO}$ in the specification sheets.
 2. Maximum and minimum collector current: $I_{C(max)}$ and I_{CEO} .
 3. Maximum power curve: $P_{C(max)}$.
- Design operating point (Q -point) to be in the middle of the linear region (white region).

Note that maximum power curves in different configurations are given below

- a) Common-Base: $V_{CB}I_C = P_{C(max)}$.
 - b) Common-Emitter: $V_{CE}I_C = P_{C(max)}$.
 - c) Common-Collector: $V_{CE}I_E = P_{C(max)}$.
- An example BJT packaging is shown in Figure 4.17 below.

 


Figure 4.17: An example BJT packaging.

4.6 Simplified BJT Model

We can summarize the simplified npn BJT model with its state and circuit behaviour with the table below and in Figure 4.18.

Simplified npn BJT Model		
State	Circuit Behaviour	Test Condition
CUTOFF	$I_B = 0,$ $I_C = 0, I_E = 0$	$V_{BE} < V_{BE(ON)},$ $V_{BC} < V_{BC(ON)}$
ACTIVE	$V_{BE} = V_{BE(ON)},$ $I_C = \beta I_B$	$I_B \geq 0,$ $V_{CE} > V_{CE(sat)}$
SATURATION	$V_{BE} = V_{BE(ON)},$ $V_{CE} = V_{CE(sat)}$	$I_B \geq 0,$ $I_C < \beta I_B$

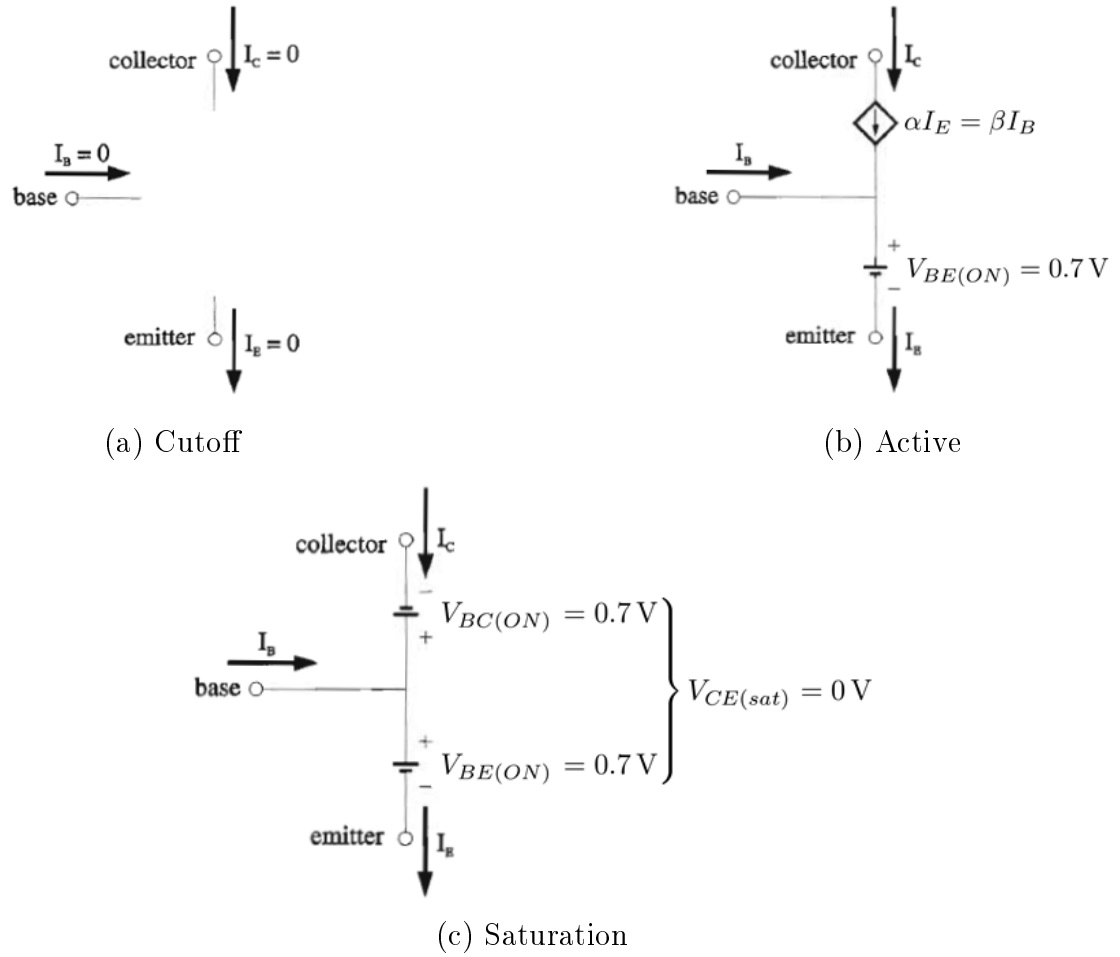


Figure 4.18: States of the simplified *npn* BJT model: (a) Cutoff, (b) Active, (c) Saturation

- For a *pnp* BJT transistor, the **polarities** and **directions** are simply **reversed**.

For example, the device will be ON (e.g., in ACTIVE mode) when $V_{EB} \geq V_{BE(ON)}$.

Chapter 5

DC Biasing of BJTs

5.1 DC Biasing

Biasing refers to the DC voltages applied to the transistor to put it into **active mode**, so that it can amplify the AC signal.

The DC input establishes an **operating point** or quiescent point called the **Q-point**.

Proper DC biasing should try to set the Q-point towards the middle of active region, e.g., Point *B* in Figure 5.1 below.

 


Figure 5.1: Various operating points within the limits of operation of a BJT transistor.

5.2 Three States of Operation

Proper DC biasing sets the BJT transistor into the **active state**, so that it can amplify the AC signal. Let us remember the states of the transistor:

- **Active:** Operating state of the amplifier: $I_C = \beta I_B$.
 - Base-Emitter (BE) junction: **forward-biased** (ON).
 - Base-Collector (BC) junction: **reverse-biased** (OFF).
- **Cut-Off:** The amplifier is basically off. There is **no current**, i.e., $I_C = I_B = I_E = 0$ A.
 - Base-Emitter (BE) junction: **reverse-biased** (OFF).
 - Base-Collector (BC) junction: **reverse-biased** (OFF).
- **Saturation:** The amplifier is saturated. Voltages are fixed, e.g., $V_{CE} = V_{CE(sat)} \cong 0$ V. **Output is distorted**, i.e., not the same shape as the input waveform.
 - Base-Emitter (BE) junction: **forward-biased** (ON).
 - Base-Collector (BC) junction: **forward-biased** (ON).

5.3 BJT DC Analysis

1. Draw the DC equivalent circuit (signal frequency is zero, i.e., $f = 0$)
 - a) Capacitors are open circuit, i.e., $X_C \rightarrow \infty$.
 - b) Kill the AC power sources (short-circuit AC voltage sources and open-circuit AC current sources).
 - c) Inductors are short circuit or replaced by their DC resistance (winding resistance) if given, i.e., $X_L \rightarrow 0$.
2. Write KVL for the loop which contains BE junction
 - a) Take $V_{BE} = V_{BE(ON)}$ to ensure the transistor is ON (or not in the cut-off state). Note: For a pnp transistor, $V_{EB} = V_{BE(ON)}$.
 - b) Determine the base current I_{BQ} (or emitter current I_{EQ}).
3. Write KVL for the loop which contains CE terminals
 - a) Assume the transistor is in the active state and take $I_{CQ} = \beta I_{BQ}$ (or $I_{CQ} = \alpha I_{EQ}$).
 - b) Calculate V_{CEQ} .
 - c) If $V_{CEQ} \leq V_{CE(sat)}$ then the transistor is in the saturation (SAT) state (i.e., $I_{CQ} \neq \beta I_{BQ}$), so take $V_{CEQ} = V_{CE(sat)}$ and recalculate I_{CQ} .

NOTE: Normally, a BJT should not be in the saturation state if it is used as an amplifier.

5.4 DC Biasing Circuits

Most common four common-emitter biasing circuits are given below

1. Fixed-Bias Circuit
2. Emitter-Stabilized Bias Circuit
3. Voltage Divider Bias Circuit
4. Collector Feedback Bias Circuit

5.4.1 Fixed-Bias Circuit

Fixed-bias circuit is given in Figure 5.2 below

 


Figure 5.2: Fixed-bias BJT circuit.

Let us start DC analysis by drawing the DC equivalent circuit as shown in Figure 5.3 below

 


Figure 5.3: DC equivalent circuit of the fixed-bias circuit in Figure 5.2.

5.4.1.1 Base-Emitter Loop

Let us continue with the BE loop shown in Figure 5.4 below

 


Figure 5.4: Base-emitter loop of the fixed-bias circuit in Figure 5.2.

Writing KVL on the BE loop

$$V_{CC} - I_B R_B - V_{BE} = 0 \quad (5.4.1)$$

and given $V_{BE} = V_{BE(ON)}$, we obtain I_{BQ} as

$$I_{BQ} = \frac{V_{CC} - V_{BE(ON)}}{R_B} \quad (5.4.2)$$

5.4.1.2 Collector-Emitter Loop

Let us continue with the CE loop shown in Figure 5.5 below

 


Figure 5.5: Collector-emitter loop of the fixed-bias circuit in Figure 5.2.

Writing KVL on the CE loop (i.e., DC load-line equation)

$$V_{CC} - I_C R_C - V_{CE} = 0 \quad (5.4.3)$$

and given (assuming BJT is in active state)

$$\boxed{I_{CQ} = \beta I_{BQ}} \quad (5.4.4)$$

we obtain V_{CEQ} as

$$\boxed{V_{CEQ} = V_{CC} - I_{CQ}R_C} \quad (5.4.5)$$

Thus, we obtained the Q -point (I_{CQ}, V_{CEQ}) , i.e., the operating point.

5.4.1.3 Saturation

The term **saturation** is applied to any system where levels have reached their maximum values. A saturated sponge is one that cannot hold another drop of water. For a transistor operating in the saturation region, the **current** is a **maximum** value for the particular design.

Note that it is in a region where the characteristic curves join and the collector-to-emitter voltage is at or below $V_{CE(sat)}$. If we approximate the curves of Figure 5.6(a) by those appearing in Figure 5.6(b), then the saturation voltage $V_{CE(sat)}$ is assumed to be 0 V, i.e.,

$$\boxed{V_{CE(sat)} \cong 0 \text{ V}} \quad (5.4.6)$$

 


Figure 5.6: Saturation regions: (a) actual, (b) approximate.

For the fixed-bias configuration shown in Figure 5.7 below, the resulting saturation current (i.e., maximum current) $I_{C(sat)}$ is given by

$$I_{C(sat)} = I_{C(max)} = \frac{V_{CC} - V_{CE(sat)}}{R_C} \cong \frac{V_{CC}}{R_C} \quad (5.4.7)$$

 


Figure 5.7: Determining $I_{C(sat)}$ for the fixed-bias configuration. Example 5.0.

Example 5.1: For the figure below, calculate all DC currents and voltages.

 


Figure 5.8: Fixed-bias circuit for Example 5.1.

Solution: Let us find I_{BQ} , I_{CQ} and V_{CEQ} as follows

$$I_{BQ} = \frac{V_{CC} - V_{BE(ON)}}{R_B} = \frac{12 - 0.7}{240k} = 47.08 \mu A,$$

$$I_{CQ} = \beta I_{BQ} = (50)(47.08 \mu) = 2.35 \text{ mA},$$

$$V_{CEQ} = V_{CC} - I_{CQ} R_C = 12 - (2.35m)(2.2k) = 6.83 \text{ V}.$$

As $V_{CEQ} > V_{CE(sat)} = 0 \text{ V}$, transistor is in the active state. Let us also prove it by showing $V_{BCQ} < V_{BC(ON)} = 0.7 \text{ V}$ as follows

$$V_{BCQ} = V_{BQ} - V_{CQ} = V_{BEQ} - V_{CEQ} = 0.7 - 6.83 = -6.13 \text{ V} < 0.7 \text{ V}.$$

5.4.1.4 DC Load Line

DC load line equation comes from KVL equation in the CE loop (i.e., output loop). For the fixed-bias circuit of Figure 5.2 DC load line equation is given by

$$\boxed{V_{CE} = V_{CC} - I_C R_C} \quad (5.4.8)$$

Let us draw the load line over output characteristics curve as shown in Figure 5.9 below. The **intersection** of the load-line with the output characteristics curve (determined by the base current I_{BQ}) is the **operating point**, i.e., **Q-point**.

 


Figure 5.9: Load line of the fixed-bias circuit in Figure 5.2.

- The Q -point is the operating point where the value of R_B sets the value of I_{BQ} that controls the values of V_{CEQ} and I_{CQ} .

Fixed-bias load line equation: $V_{CE} = V_{CC} - I_C R_C$

The load line end points are the SATURATION and CUTOFF points, i.e.,

- $I_{C(sat)}$ end point (on the current axis):

$$I_C = V_{CC}/R_C$$

$$V_{CE} = 0\text{ V}$$

- $V_{CE(cutoff)}$ end point (on the voltage axis):

$$V_{CE} = V_{CC}$$

$$I_C = 0\text{ mA}$$

The Effect of I_B on the Q -Point

Movement of the Q -point with increasing level of I_B (or decreasing level of R_B) is shown in Figure 5.10 below.

 


Figure 5.10: Movement of the Q -point with increasing level of I_B .

The Effect of R_C on the Q -Point

Effect of an increasing level of R_C on the load line (slope decreases with increasing R_C) and the Q -point is shown in Figure 5.11 below.

 


Figure 5.11: Effect of an increasing level of R_C on the load line and the Q -point.

The Effect of V_{CC} on the Q-Point

Effect of an decreasing level of V_{CC} on the load line (end points gets smaller with decreasing V_{CC}) and the Q-point is shown in Figure 5.12 below.

 


Figure 5.12: Effect of lower values of V_{CC} on the load line and the Q-point.

Example 5.2: For the fixed-bias load line below, calculate V_{CC} , R_C and R_B .

 


Figure 5.13: Fixed-bias load line for Example 5.2.

Solution: From the figure, $I_{BQ} = 25 \mu\text{A}$. So, let us find V_{CC} , R_C and R_B as follows

$$V_{CC} = V_{CE(\text{cutoff})} = 20 \text{ V},$$

$$R_C = \frac{V_{CC}}{I_{C(\text{sat})}} = \frac{20}{10\text{m}} = 2 \text{ k}\Omega,$$

$$R_B = \frac{V_{CC} - V_{BE(\text{ON})}}{I_{BQ}} = \frac{20 - 0.7}{25\mu} = 772 \text{ k}\Omega.$$

5.4.2 Emitter-Stabilized Bias Circuit

Adding a resistor to the emitter circuit stabilizes the bias circuit, as shown in Figure 5.14 below.

 


Figure 5.14: Emitter-stabilized bias circuit.

Let us start DC analysis by drawing the DC equivalent circuit as shown in Figure 5.15 below

 


Figure 5.15: DC equivalent circuit of the emitter-stabilized bias circuit in Figure 5.14.

5.4.2.1 Base-Emitter Loop

Let us continue with the BE loop shown in Figure 5.16 below

 


Figure 5.16: Base-emitter loop of the emitter-stabilized bias circuit in Figure 5.14: (a) normal circuit, (b) equivalent circuit for common base current.

Writing KVL on the BE loop

$$V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0 \quad (5.4.9)$$

$$V_{CC} - I_B R_B - V_{BE(ON)} - (\beta + 1)I_B R_E = 0, \quad \dots \text{as } V_{BE} = V_{BE(ON)} \text{ and } I_E = (\beta + 1)I_B \text{ in active mode} \quad (5.4.10)$$

we obtain I_{BQ} as

$$I_{BQ} = \frac{V_{CC} - V_{BE(ON)}}{R_B + (\beta + 1)R_E} \quad (5.4.11)$$

Similarly, we can obtain I_{EQ} directly from Figure 5.17, or dividing the denominator of the I_{BQ} in (5.4.12) by $(\beta + 1)$

 


Figure 5.17: Equivalent circuit for common emitter current for the base-emitter loop of the emitter-stabilized bias circuit in Figure 5.14.

as follows

$$I_{EQ} = \frac{V_{CC} - V_{BE(ON)}}{\frac{R_B}{\beta + 1} + R_E} \quad (5.4.12)$$

- It is generally better to calculate I_{EQ} directly to reduce the number of calculations, especially when there is an emitter resistor R_E is connected.

5.4.2.2 Collector-Emitter Loop

Let us continue with the CE loop shown in Figure 5.18 below

 


Figure 5.18: Collector-emitter loop of the emitter-stabilized bias circuit in Figure 5.14.

Let us write down the KVL equation on the CE loop

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0 \quad (5.4.13)$$

$$V_{CC} - I_C R_C - V_{CE} - I_C R_E = 0 \quad \dots \text{as } I_C = \alpha I_E \cong I_E \text{ in active mode} \quad (5.4.14)$$

$$V_{CC} - I_C (R_C + R_E) - V_{CE} = 0 \quad \dots \text{DC load line equation} \quad (5.4.15)$$

As $I_{CQ} = \beta I_{BQ} \cong I_{EQ}$ in active mode, we obtain V_{CEQ} as

$$\boxed{V_{CEQ} = V_{CC} - I_{CQ}(R_C + R_E)} \quad (5.4.16)$$

Thus, we obtained the Q -point (I_{CQ}, V_{CEQ}) , i.e., the operating point.

5.4.2.3 DC Load Line

DC load line equation comes from KVL equation in the CE loop (i.e., output loop). For the emitter-stabilized bias circuit of Figure 5.14 DC load line equation is given by

$$\boxed{V_{CE} = V_{CC} - I_C(R_C + R_E)} \quad (5.4.17)$$

Let us draw the load line over output characteristics curve as shown in Figure 5.19 below.

 


Figure 5.19: Load line of the emitter-stabilized bias circuit in Figure 5.14.

Here, $V_{CE(cutoff)} = V_{CC}$ and $I_{C(sat)}$ is given by

$$I_{C(sat)} = \frac{V_{CC}}{R_C + R_E} \quad (5.4.18)$$

- The Q -point is the operating point where the value of R_B and R_E sets the value of I_{BQ} that controls the values of V_{CEQ} and I_{CQ} .

5.4.2.4 Improved Biased Stability

Stability refers to a condition in which the currents and voltages remain fairly constant over a wide range of temperatures and transistor beta (β) values.

- Adding R_E resistor to the emitter improves the stability of a transistor.

Example 5.3: For the figure below, calculate all DC currents and voltages.

 


Figure 5.20: Emitter-stabilized bias circuit for Example 5.3.

Solution: Let us find I_{BQ} , I_{CQ} and V_{CEQ} as follows

$$I_{BQ} = \frac{V_{CC} - V_{BE(ON)}}{R_B + (\beta + 1)R_E} = \frac{20 - 0.7}{430k + (50 + 1)(1k)} = 40.13 \mu\text{A},$$

$$I_{CQ} = \beta I_{BQ} = (50)(40.13 \mu) = 2.01 \text{ mA},$$

$$V_{CEQ} \cong V_{CC} - I_{CQ}(R_C + R_E) = 20 - (2.01 \text{ m})(2k + 1k) = 13.97 \text{ V}.$$

As $V_{CEQ} > 0 \text{ V}$ ($V_{CE(sat)}$), transistor is in the active state. Let us also prove it by showing $V_{BCQ} < V_{BC(ON)} = 0.7 \text{ V}$ as follows

$$V_{BCQ} = V_{BQ} - V_{CQ} = V_{BEQ} - V_{CEQ} = 0.7 - 13.97 = -13.27 \text{ V} < 0.7 \text{ V}.$$

5.4.3 Voltage Divider Bias Circuit

Voltage divider bias circuit is given in Figure 5.21 below

 


Figure 5.21: Voltage divider bias BJT circuit.

Let us start DC analysis by drawing the DC equivalent circuit as shown in Figure 5.22 below

 


Figure 5.22: DC equivalent circuit of the voltage divider bias circuit in Figure 5.21.

5.4.3.1 Base-Emitter Loop (Exact Analysis)

Let us transform the BE loop circuit shown in Figure 5.23(a) below to the Thévenin simplified circuit in Figure 5.23(b) below

 


Figure 5.23: Base-emitter loop of the voltage divider bias circuit in Figure 5.21: (a) normal circuit, (b) Thévenin equivalent circuit.

where the Thévenin voltage V_{BB} and Thévenin resistance R_{BB} are calculated as follows

$$V_{BB} = \frac{R_2}{R_1 + R_2} V_{CC} \quad \dots \text{from Figure 5.24(a) below (5.4.19)}$$

$$R_{BB} = R_1 || R_2 \quad \dots \text{from Figure 5.24(b) below (5.4.20)}$$

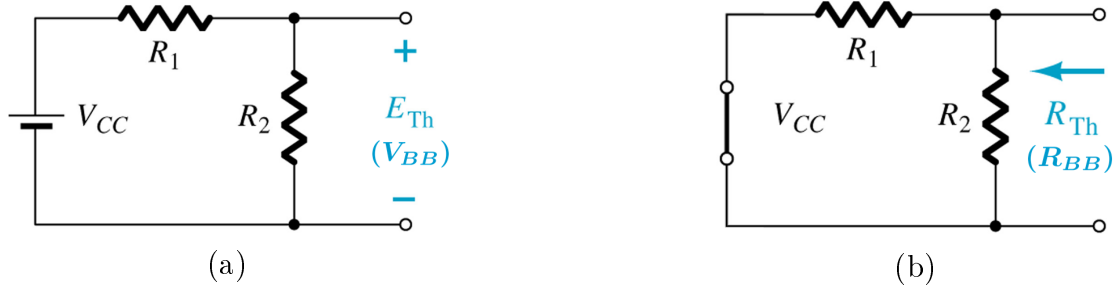


Figure 5.24: Thévenin analysis circuits for the circuit in Figure 5.23(a): (a) Open-circuit voltage calculation, (b) Test-voltage method for Thévenin resistance calculation.

Writing KVL on the Thévenin equivalent BE loop shown in Figure 5.23(b)

$$V_{BB} - I_B R_{BB} - V_{BE} - I_E R_E = 0 \quad (5.4.21)$$

$$V_{BB} - I_B R_{BB} - V_{BE(ON)} - (\beta + 1)I_B R_E = 0, \quad \dots \text{as } V_{BE} = V_{BE(ON)} \text{ and} \\ I_E = (\beta + 1)I_B \text{ in active mode} \quad (5.4.22)$$

we obtain I_{BQ} as

$$I_{BQ} = \frac{V_{BB} - V_{BE(ON)}}{R_{BB} + (\beta + 1)R_E} \quad (5.4.23)$$

Similarly, we obtain I_{EQ} as

$$I_{EQ} = \frac{V_{BB} - V_{BE(ON)}}{\frac{R_{BB}}{\beta + 1} + R_E} \quad (5.4.24)$$

5.4.3.2 Base-Emitter Loop (Approximate Analysis)

If we look at the I_{EQ} equation in (5.4.24), we see that if $R_E \gg \frac{R_{BB}}{\beta + 1}$, equation simplifies to

$$I_{EQ} = \frac{V_{BB} - V_{BE(ON)}}{R_E} \quad (5.4.25)$$

where $V_{BB} = \frac{R_2}{R_1 + R_2} V_{CC}$.

- Approximate approach can be used when $(\beta + 1)R_E \gg R_{BB}$. Approximate analysis condition can be rewritten as

$$(\beta + 1)R_E \geq 10(R_1 || R_2). \quad (5.4.26)$$

Assuming $R_1 > R_2$, we know that $(R_1 || R_2) \leq R_2$. So, the condition above can be further simplified to

$$\beta R_E \geq 10R_2. \quad (5.4.27)$$

- Satisfying this condition means that we can safely ignore the base current I_B in the DC equivalent circuit shown in Figure 5.22 and apply the voltage divider rule between R_2 and R_1 .
- Finally, if β times the value of R_E is at least 10 times the value of R_2 , the approximate approach can be applied with a high degree of accuracy.

5.4.3.3 Collector-Emitter Loop and DC Load line

- Analysis on the CE loop (i.e., output loop), is the same as the CE loop analysis of the emitter-stabilized circuit given in Section 5.4.2.2. So, V_{CEQ} is given by

$$V_{CEQ} = V_{CC} - I_{CQ}(R_C + R_E)$$

where $I_{CQ} \cong I_{EQ}$.

- Similarly, DC load line analysis is also the same as the DC load line of the emitter-stabilized circuit given in Section 5.4.2.3. So, DC load line equation is given by

$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

Example 5.4: For the figure below, calculate all DC currents and voltages using both exact and approximate analysis.

 


Figure 5.25: Voltage-divider bias circuit for Example 5.4.

Solution: Let us first find the Thévenin voltage V_{BB} and resistance R_{BB} as follows

$$V_{BB} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{3.9k}{39k + 3.9k} 22 = 2 \text{ V},$$

$$R_{BB} = R_1 || R_2 = 3.9k || 39k = 3.55 \text{ k}\Omega.$$

Now, let us calculate I_{BQ} , I_{CQ} and V_{CEQ} as follows

$$I_{EQ} = \frac{V_{BB} - V_{BE(ON)}}{R_{BB}/(\beta + 1) + R_E} = \frac{2 - 0.7}{3.55k/(140 + 1) + 1.5k} = 0.85 \text{ mA},$$

$$I_{CQ} \cong I_{EQ} = 0.85 \text{ mA},$$

$$V_{CEQ} \cong V_{CC} - I_{CQ}(R_C + R_E) = 22 - (0.85m)(10k + 1.5k) = 12.23 \text{ V}.$$

As $\beta R_E \geq 10R_2$ (i.e., $210 \text{ k}\Omega \geq 39 \text{ k}\Omega$), we can use the approximate analysis and ignore R_{BB} and voltage drop across R_{BB} as follows

$$I_{EQ} = \frac{V_{BB} - V_{BE(ON)}}{R_E} = \frac{2 - 0.7}{1.5k} = 0.87 \text{ mA},$$

$$I_{CQ} \cong I_{EQ} = 0.87 \text{ mA},$$

$$V_{CEQ} \cong V_{CC} - I_{CQ}(R_C + R_E) = 22 - (0.87m)(10k + 1.5k) = 12 \text{ V}.$$

We see that approximate analysis provides close values to the exact analysis. The differences in I_{CQ} and V_{CEQ} are only 0.02 mA and 0.23 V, respectively.

5.4.4 Collector Feedback Bias Circuit

Another way to improve the stability of a bias circuit is to add a feedback path from collector to base as shown in Figure 5.26 below

 


Figure 5.26: Collector feedback bias circuit.

Let us start DC analysis by drawing the DC equivalent circuit as shown in Figure 5.27 below

 


Figure 5.27: DC equivalent circuit of the collector feedback circuit in Figure 5.26.

5.4.4.1 Base-Emitter Loop

Let us continue with the *BE* loop shown in Figure 5.28 below

 


Figure 5.28: Base-emitter loop of the collector feedback circuit in Figure 5.26.

We can write KVL equation on the BE loop noting that $I'_C = I_C + I_B = I_E$

$$V_{CC} - I'_C R_C - I_B R_F - V_{BE} - I_E R_E = 0 \quad (5.4.28)$$

$$V_{CC} - I_E R_C - \frac{I_E}{\beta + 1} R_F - V_{BE(ON)} - I_E R_E = 0, \quad \dots \text{ as } V_{BE} = V_{BE(ON)} \text{ and}$$

$$I_B = \frac{I_E}{\beta + 1} \text{ in active mode} \quad (5.4.29)$$

and we obtain I_{EQ} as

$$I_{EQ} = \frac{V_{CC} - V_{BE(ON)}}{\frac{R_F}{\beta + 1} + (R_C + R_E)} \quad (5.4.30)$$

5.4.4.2 Collector-Emitter Loop

Let us continue with the CE loop shown in Figure 5.29 below

 


Figure 5.29: Collector-emitter loop of the collector feedback circuit in Figure 5.26.

Let us write down the KVL equation on the CE loop noting that $I'_C = I_C + I_B$

$$V_{CC} - I'_C R_C - V_{CE} - I_E R_E = 0 \quad (5.4.31)$$

$$V_{CC} - I_C R_C - V_{CE} - I_C R_E = 0 \quad \dots \text{as } I_C \cong I_E \text{ and } I_C \cong I'_C \text{ in active mode} \quad (5.4.32)$$

$$V_{CC} - I_C(R_C + R_E) - V_{CE} = 0 \quad \dots \text{DC load line equation} \quad (5.4.33)$$

As $I_{CQ} \cong I_{EQ}$ in active mode, we obtain V_{CEQ} as

$$\boxed{V_{CEQ} = V_{CC} - I_{CQ}(R_C + R_E)} \quad (5.4.34)$$

Thus, we obtained the Q -point (I_{CQ}, V_{CEQ}) , i.e., the operating point.

5.4.4.3 DC Load line

- Note that $I'_C = I_E$, and

$$I_C \cong I_E$$

in active mode (and β is high).

- So, DC load line analysis is the same as the DC load line of the emitter-stabilized circuit given in Section 5.4.2.3. So, DC load line equation is given by

$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

5.4.5 Various Different Bias Circuits

Example 5.5: For the figure below, calculate all DC currents and voltages.

 


Figure 5.30: Common-collector bias circuit for Example 5.5.

Solution: Let us find I_{EQ} , I_{CQ} and V_{CEQ} as follows

$$I_{EQ} = \frac{0 - V_{BE(ON)} - V_{EE}}{R_B/(\beta + 1) + R_E} = \frac{20 - 0.7}{240k/(90 + 1) + 2k} = 4.16 \text{ mA},$$

$$I_{CQ} \cong I_{EQ} = 4.16 \text{ mA},$$

$$V_{CEQ} = 0 - I_{EQ}R_E - V_{EE} = 20 - (4.16m)(2k) = 11.68 \text{ V}.$$

As $V_{CEQ} > V_{CE(sat)} = 0 \text{ V}$, transistor is in the active state.

5.4.6 *pn*p Transistors

The analysis for *pn*p bias transistor circuits is the same as that for *n*p*n* transistor circuits.

The only differences are that

1. Currents are flowing in the opposite direction.
2. Voltages have opposite polarity, e.g., $V_{EB} = V_{BE(ON)} = 0.7\text{ V}$ in the active mode.

Example 5.6: For the figure below, calculate all DC currents and voltages.

 


Figure 5.31: *pn*p transistor in a voltage-divider bias configuration Example 5.6.

Solution: As $\beta R_E \geq 10R_2$, i.e., $132\text{ k}\Omega \geq 100\text{ k}\Omega$, we can ignore R_{BB} and use the approximate approach. Thus, we can find V_B , I_{EQ} , I_{CQ} and V_{ECQ} as follows

$$V_B \cong \frac{R_2}{R_1 + R_2} V_{CC} = \frac{10\text{k}}{47\text{k} + 10\text{k}} (-18) = -3.16\text{ V}$$

$$I_{EQ} \cong \frac{0 - V_{EB} - V_B}{R_E} = \frac{0 - 0.7 - (-3.16)}{1.1\text{k}} = \frac{2.46}{1.1\text{k}} = 2.24\text{ mA},$$

$$I_{CQ} \cong I_{EQ} = 2.24\text{ mA},$$

$$V_{ECQ} = 0 - I_{CQ}(R_C + R_E) - V_{CC} = -(2.24\text{m})(2.4\text{k} + 1.1\text{k}) - (-18) = 10.16\text{ V}.$$

As $V_{ECQ} > V_{CE(sat)} = 0\text{ V}$, transistor is in the active state.

5.5 Bias Stabilization

Variation of three BJT (Si) parameters (I_{CO} , β and $V_{BE(ON)}$) with temperature are summarized below

$$\boxed{T \uparrow \quad I_{CO} \uparrow \quad \beta \uparrow \quad V_{BE(ON)} \downarrow} \quad (5.5.35)$$

- I_{CO} (reverse saturation current)

- doubles in value for every 10°C
- β (transistor current gain)
 - increases with increasing temperature
- $V_{BE(ON)}$ (forward bias potential of the base-emitter junction)
 - decreases about 2.5 mV per 1°C increase in temperature

Variation of the transistor parameters with temperature causes a shift in the operating point (i.e., Q -point).

Figures below (at 25°C on the left and at 100°C on the right) show the shift of the Q -point (or DC bias point) due to temperature change for a fixed-bias circuit.

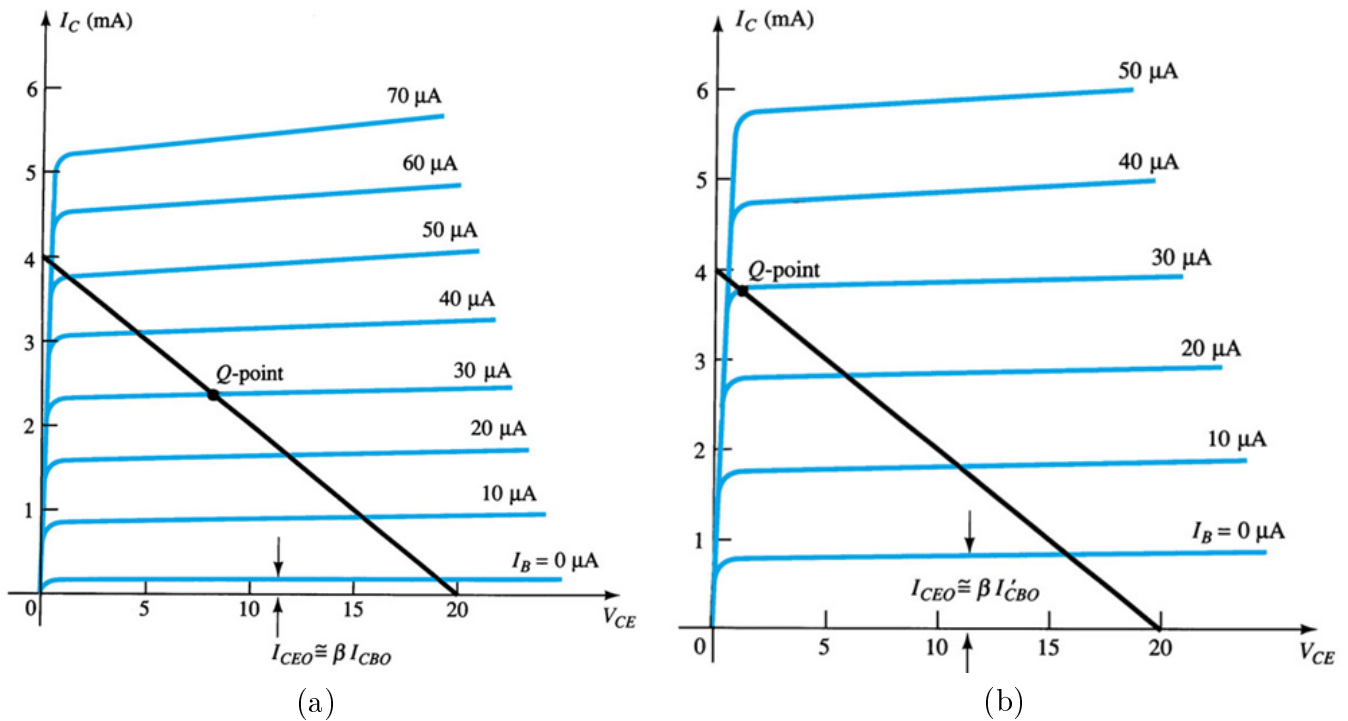


Figure 5.32: Shift in operating point (Q -point) due to change in temperature: (a) 25°C, (b) 100°C.

5.5.1 Stability Factors

Stability of the collector current I_C depends on the stability of several parameters like I_{CO} , β , $V_{BE(ON)}$, V_{CC} , R_B , R_C , etc.

A stability factor S is defined for **each** of the parameters affecting bias stability as follows:

$$S_{I_{CO}} = \frac{\partial I_C}{\partial I_{CO}} = \left. \frac{\Delta I_C}{\Delta I_{CO}} \right|_{\beta, V_{BE(ON)}, \dots \text{ constant}} \quad (5.5.36)$$

$$S_{\beta} = \frac{\partial I_C}{\partial \beta} = \left. \frac{\Delta I_C}{\Delta \beta} \right|_{I_{CO}, V_{BE(ON)}, \dots \text{ constant}} \quad (5.5.37)$$

$$S_{V_{BE(ON)}} = \frac{\partial I_C}{\partial V_{BE(ON)}} = \left. \frac{\Delta I_C}{\Delta V_{BE(ON)}} \right|_{I_{CO}, \beta, \dots \text{ constant}} \quad (5.5.38)$$

We know that differential dI_C is given by the linear map of parameter differentials as follows

$$dI_C = \frac{\partial I_C}{\partial I_{CO}} dI_{CO} + \frac{\partial I_C}{\partial \beta} d\beta + \frac{\partial I_C}{\partial V_{BE(ON)}} dV_{BE(ON)} + \dots \quad (5.5.39)$$

- Thus, we obtain the collector-current change ΔI_C using the stability factors as follows

$$\boxed{\Delta I_C \cong S_{I_{CO}} \Delta I_{CO} + S_{\beta} \Delta \beta + S_{V_{BE(ON)}} \Delta V_{BE(ON)}} \quad (5.5.40)$$

5.5.1.1 Derivation of Stability Factors (Voltage-Divider Bias Circuit)

 


Figure 5.33: Equivalent circuit for the voltage-divider configuration.

Let us write down the active mode collector current and BE -loop KVL equations for the circuit shown in Figure 5.33 above,

$$I_C = \beta I_B + (\beta + 1) I_{CO} \quad (5.5.41)$$

$$V_{BB} = I_B R_{BB} + V_{BE(ON)} + (I_B + I_C) R_E \quad (5.5.42)$$

Combining the two equations (5.5.41) and (5.5.42) above, we obtain the expression for I_C as

$$\boxed{I_C = \frac{\beta}{R_{BB} + (\beta + 1) R_E} (V_{BB} - V_{BE(ON)}) + \frac{(\beta + 1) (R_{BB} + R_E)}{R_{BB} + (\beta + 1) R_E} I_{CO}} \quad (5.5.43)$$

1. From equation (5.5.43), let us derive $S_{I_{CO}} = \frac{\partial I_C}{\partial I_{CO}}$ as

$$\boxed{S_{I_{CO}} = (\beta + 1) \frac{R_{BB} + R_E}{R_{BB} + (\beta + 1) R_E}} \quad (5.5.44)$$

2. From equation (5.5.43), let us derive $S_{V_{BE(ON)}} = \frac{\partial I_C}{\partial V_{BE(ON)}}$ as

$$\boxed{S_{V_{BE(ON)}} = \frac{-\beta}{R_{BB} + (\beta + 1) R_E}} \quad (5.5.45)$$

3. In order to derive $S_\beta = \frac{\partial I_C}{\partial \beta}$, let us first simplify (5.5.43) by letting $I_{CO} \cong 0$

$$I_C \cong \frac{\beta}{R_{BB} + (\beta + 1) R_E} (V_{BB} - V_{BE(ON)}) \quad (5.5.46)$$

Using the simplified I_C equation (5.5.46) we can express I_{C1} and I_{C2} as follows

$$I_{C1} \cong \frac{\beta_1}{R_{BB} + (\beta_1 + 1) R_E} (V_{BB} - V_{BE(ON)}) \quad (5.5.47)$$

$$I_{C2} \cong \frac{\beta_2}{R_{BB} + (\beta_2 + 1) R_E} (V_{BB} - V_{BE(ON)}) \quad (5.5.48)$$

Thus, using (5.5.47) and (5.5.48), let us obtain the ratio $\frac{I_{C2} - I_{C1}}{I_{C1}}$ as

$$\frac{I_{C2} - I_{C1}}{I_{C1}} = \frac{\beta_2 - \beta_1}{\beta_1} \frac{R_{BB} + R_E}{R_{BB} + (\beta_2 + 1) R_E} \quad (5.5.49)$$

From equation (5.5.50), we can obtain the ratio $\frac{\Delta I_C}{\Delta \beta}$ by using $\Delta I_C = I_{C2} - I_{C1}$ and $\Delta \beta = \beta_2 - \beta_1$ as

$$\frac{\Delta I_C}{\Delta \beta} = \frac{I_{C1}}{\beta_1} \frac{R_{BB} + R_E}{R_{BB} + (\beta_2 + 1) R_E} \quad (5.5.50)$$

Thus, as $S_\beta = \frac{\partial I_C}{\partial \beta} \cong \frac{\Delta I_C}{\Delta \beta}$

$$\boxed{S_\beta = \frac{I_{C1}}{\beta_1} \frac{R_{BB} + R_E}{R_{BB} + (\beta_2 + 1) R_E}} \quad (5.5.51)$$

5.5.1.2 Stability Factors for Other Bias Circuits

A. For the **fixed-bias** circuit, i.e., by substituting $R_E = 0$ and $R_{BB} = R_B$ into (5.5.44), (5.5.45) and (5.5.51), the stability factors are given by

$$S_{ICO} = \beta + 1 \quad (5.5.52)$$

$$S_{V_{BE(ON)}} = \frac{-\beta}{R_B} \quad (5.5.53)$$

$$S_\beta = \frac{I_{C1}}{\beta_1} \quad (5.5.54)$$

B. For the **emitter-stabilized bias** circuit, i.e., $R_{BB} = R_B$ and $R_B \gg R_E$, the stability factors are given by

$$S_{ICO} = (\beta + 1) \frac{R_B + R_E}{R_B + (\beta + 1) R_E} \cong \frac{\beta + 1}{1 + \frac{(\beta + 1) R_E}{R_B}} \quad (5.5.55)$$

$$S_{V_{BE(ON)}} = \frac{-\beta}{R_B + (\beta + 1) R_E} \quad (5.5.56)$$

$$S_\beta = \frac{I_{C1}}{\beta_1} \frac{R_B + R_E}{R_B + (\beta_2 + 1) R_E} \cong \frac{I_{C1}}{\beta_1} \frac{1}{1 + \frac{(\beta_2 + 1) R_E}{R_B}} \quad (5.5.57)$$

C. For the **voltage-divider bias** circuit with $(\beta + 1)R_E \geq 10R_{BB}$, the stability factors are given by

$$S_{I_{CO}} = (\beta + 1) \frac{R_{BB} + R_E}{R_{BB} + (\beta + 1) R_E} \cong 1 + \frac{R_{BB}}{R_E} \quad (5.5.58)$$

$$S_{V_{BE(ON)}} = \frac{-\beta}{R_{BB} + (\beta + 1) R_E} \cong \frac{-1}{R_E} \quad (5.5.59)$$

$$S_\beta = \frac{I_{C1}}{\beta_1} \frac{R_{BB} + R_E}{R_{BB} + (\beta_2 + 1) R_E} \cong \frac{I_{C1}}{\beta_1 \beta_2} \left(1 + \frac{R_{BB}}{R_E} \right) \quad (5.5.60)$$

D. For the **collector feedback bias** circuit, i.e., $R_{BB} = R_F$, replacing R_E with $R_{CE} = R_C + R_E$ and $R_F \gg R_{CE}$, the stability factors are given by

$$S_{I_{CO}} = (\beta + 1) \frac{R_F + R_{CE}}{R_F + (\beta + 1) R_{CE}} \cong \frac{\beta + 1}{1 + \frac{(\beta + 1) R_{CE}}{R_F}} \quad (5.5.61)$$

$$S_{V_{BE(ON)}} = \frac{-\beta}{R_F + (\beta + 1) R_{CE}} \quad (5.5.62)$$

$$S_\beta = \frac{I_{C1}}{\beta_1} \frac{R_F + R_{CE}}{R_F + (\beta_2 + 1) R_{CE}} \cong \frac{I_{C1}}{\beta_1} \frac{1}{1 + \frac{(\beta_2 + 1) R_{CE}}{R_F}} \quad (5.5.63)$$

Example 5.7: Find and compare the collector current change ΔI_C when the temperature rises from 25°C to 100°C for the transistor defined by the table below for the following bias arrangements.

- Fixed-bias with $R_B = 240 \text{ k}\Omega$ and $I_{C1} = 2 \text{ mA}$,
- Voltage-divider bias with $R_E = 4.7 \text{ k}\Omega$, $R_{BB}/R_E = 2$ and $I_{C1} = 2 \text{ mA}$.

Temperature	I_{CO}	β	$V_{BE(ON)}$
-65°C	0.02 nA	20	0.85 V
25°C	0.1 nA	50	0.65 V
100°C	20 nA	80	0.48 V
175°C	3.3 μA	120	0.30 V

Solution: From the table above, let us first calculate ΔI_{CO} , $\Delta\beta$ and $\Delta V_{BE(ON)}$

$$\Delta I_{CO} = I_{CO_2} - I_{CO_1} = 20 \text{ n} - 0.1 \text{ n} = 19.9 \text{ nA}$$

$$\Delta\beta = \beta_2 - \beta_1 = 80 - 50 = 30$$

$$\Delta V_{BE(ON)} = V_{BE(ON)_2} - V_{BE(ON)_1} = 0.48 - 0.65 = -0.17 \text{ V}$$

We are going to calculate ΔI_C using

$$\Delta I_C \cong S_{I_{CO}} \Delta I_{CO} + S_\beta \Delta\beta + S_{V_{BE(ON)}} \Delta V_{BE(ON)}$$

- a. Let us calculate the stability factors for the fixed-bias circuit using (5.5.52), (5.5.54) and (5.5.53)

$$\begin{aligned}
 S_{I_{CO}} &= \beta + 1 = 51 \\
 S_{\beta} &= \frac{I_{C1}}{\beta_1} = \frac{2m}{50} = 0.04 \text{ mA} \\
 S_{V_{BE(ON)}} &= \frac{-\beta}{R_B} = \frac{-50}{240k} = -0.21 \text{ m}\Omega^{-1}
 \end{aligned}$$

Thus, ΔI_C is given by

$$\begin{aligned}
 \Delta I_C &\cong (51)(19.9n) + (0.04m)(30) + (-0.21m)(-0.17) \\
 &= 1.02\mu + 1.2m + 0.036m \\
 &= 1.236 \text{ mA}
 \end{aligned}$$

That means, for the fixed-bias circuit I_C increases to 3.236 mA at 100°C from 2 mA.

- b. Let us calculate the stability factors for the voltage-divider bias circuit using (5.5.58), (5.5.60) and (5.5.59)

$$\begin{aligned}
 S_{I_{CO}} &\cong 1 + \frac{R_{BB}}{R_E} = 1 + 2 = 3 \\
 S_{\beta} &\cong \frac{I_{C1}}{\beta_1\beta_2} \left(1 + \frac{R_{BB}}{R_E} \right) = \frac{2m}{(50)(80)} (1 + 2) = 1.5 \mu\text{A} \\
 S_{V_{BE(ON)}} &= \frac{-1}{R_E} = \frac{-1}{4.7k} = -0.21 \text{ m}\Omega^{-1}
 \end{aligned}$$

Thus, ΔI_C is given by

$$\begin{aligned}
 \Delta I_C &\cong (3)(19.9n) + (1.5\mu)(30) + (-0.21m)(-0.17) \\
 &= 0.060\mu + 0.045m + 0.036m \\
 &= 0.081 \text{ mA}
 \end{aligned}$$

That means, for the voltage-divider bias circuit I_C increases to 2.08 mA at 100°C from 2 mA. Most of the improvement comes from the reduction in S_{β} .

- These two results show that voltage-divider bias circuit is much more stable than the fixed-bias circuit. In other words, adding R_E resistor to the emitter leg of the transistor stabilizes the bias circuit.

5.5.2 Stability of Transistor Circuits with Active Components

- V_{BE} compensation
 - by using a reverse-biased diode at the emitter

 


Figure 5.34: Active V_{BE} compensation using a reverse-biased diode at the emitter.

- I_{CO} compensation
 - by replacing R_2 with a reverse-biased diode

 


Figure 5.35: Active I_{CO} compensation replacing R_2 with a reverse-biased diode.

- I_C compensation (without R_E)
 - by using a current mirror

 


Figure 5.36: Active I_C compensation using a current mirror.

5.6 Practical Applications

5.6.1 Relay Driver

 


Figure 5.37: Relay driver in the absence of protective device.

When the transistor turns OFF, a high voltage (given by $v_L = L(di_L/dt)$) is induced across the coil as shown in Figure 5.38 above. If its magnitude exceeds the maximum ratings of the transistor, then the semiconductor device will be permanently damaged.

This destructive action can be subdued by placing a diode across the coil as shown in Figure 5.38 below. During the ON state of the transistor, the diode is reverse-biased (i.e., open circuit) and doesn't affect a thing. However, when the transistor turns off, the voltage across the coil will reverse and will forward-bias the diode, placing the diode in its ON state (hence protecting the transistor).

 


Figure 5.38: Relay driver protected with a diode across the relay coil.

5.6.2 Transistor Switch

A transistor can be used as a switch to control the ON and OFF states of the light-bulb in the collector branch of the circuit as shown in Figure 5.39 below.

 


Figure 5.39: Using the BJT as a switch to control the on/off states of a bulb with a limiting resistor.

5.6.3 Transistor Switching Networks

 


Figure 5.40: A BJT inverter circuit and its operation.

The application of transistors is not limited solely to the amplification of signals. Through proper design, transistors can also be used as switches for computer and control applications. The circuit shown in Figure 5.40 above can be employed as an inverter in computer logic circuitry.

Inversion process requires that the Q -point switch from **cutoff** ($V_o = V_{CE(cutoff)} = 5\text{ V}$) to **saturation** ($V_o = V_{CE(sat)} = 0\text{ V}$) along the load line depicted in Figure 5.41 below.

 


Figure 5.41: Load-line of the inverter circuit in Figure 5.40.

The total time required for the transistor to switch from the OFF to the ON state is designated as t_{on} , and the total time required for a transistor to switch from the ON to the OFF state is referred to as t_{off} as shown in Figure 5.42 below. t_{on} and t_{off} are defined by

$$t_{on} = t_r + t_d \tag{5.6.64}$$

$$t_{off} = t_s + t_f \tag{5.6.65}$$

where t_r is the rise time from 10% to 90% of the output, t_d is the delay time between the changing state of the input and the beginning of a response at the output, t_s is the storage time and t_f the fall time from 90% to 10% of the output.

 


Figure 5.42: Defining the time intervals of a pulse waveform.

5.6.4 Logic Gates

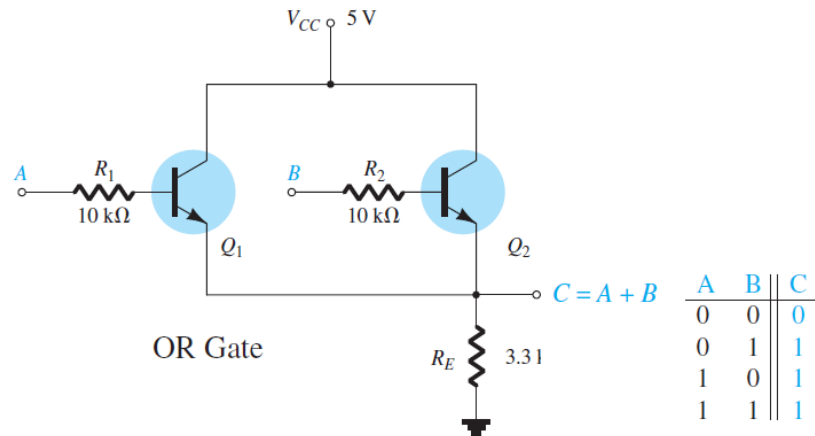


Figure 5.43: BJT logic OR gate.

Figure 5.43 above shows a BJT logic OR gate, and similarly Figure 5.44 below shows a BJT logic AND gate.

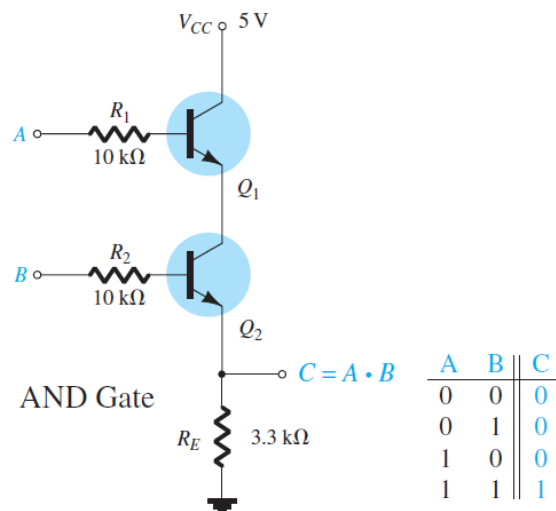


Figure 5.44: BJT logic AND gate.

5.6.5 Current Mirror

The **current mirror** shown in Figure 5.45 below is a DC circuit in which the current through a **load** is controlled by a current at another point in the circuit. That is, the current through the load is independent of the load.

 


Figure 5.45: BJT logic OR gate.

Homework 5.1: For Figure 5.45 above, show that the load current is equal to the load control current and given by

$$I_L \cong I_{control} = \frac{V_{CC} - V_{BE(ON)}}{R} \quad (5.6.66)$$

where the transistors are identical ($Q_1 \equiv Q_2$), i.e., $V_{BE_1(ON)} = V_{BE_2(ON)} = V_{BE(ON)}$ and $\beta_1 = \beta_2 = \beta$, and current gain β is high, e.g., $\beta \geq 100$.

5.6.6 Voltage Level Indicator

The voltage level indicator circuit uses a green LED to indicate when the source voltage is close to its monitoring level of 9 V. The potentiometer is set to establish 5.4 V at the point indicated in Figure 5.46 below. The result is sufficient voltage to turn on both the 4.7 V Zener and the transistor and establish a collector current through the LED sufficient in magnitude to turn on the green LED. The LED will immediately turn off, revealing that the supply voltage has dropped below 9 V or that the power source has been disconnected (i.e., when the voltage set up by the voltage divider circuit drops below 5.4 V).

 


Figure 5.46: Voltage level indicator.

Chapter 6

AC-DC Load Lines of BJT Circuits

6.1 BJT AC Analysis

1. Draw the AC equivalent circuit (signal frequency is infinity, i.e., $f = \infty$)
 - a) Capacitors are short circuit, i.e., $X_C \rightarrow 0$.
 - b) Kill the DC power sources (short-circuit DC voltage sources and open-circuit DC current sources).
2. Write KVL for the loop which contains CE terminals
 - a) Develop AC load-line equation.
3. Draw AC-DC load lines
 - a) Find available swings for a given input or find maximum undistorted swings.

 


Figure 6.1: A voltage-divider common-emitter BJT circuit.

Consider the common-emitter BJT circuit shown in Figure 6.1 above where $v_i = V_m \sin(\omega t)$. Its DC and AC equivalent circuits are shown in Figure 6.2 below.

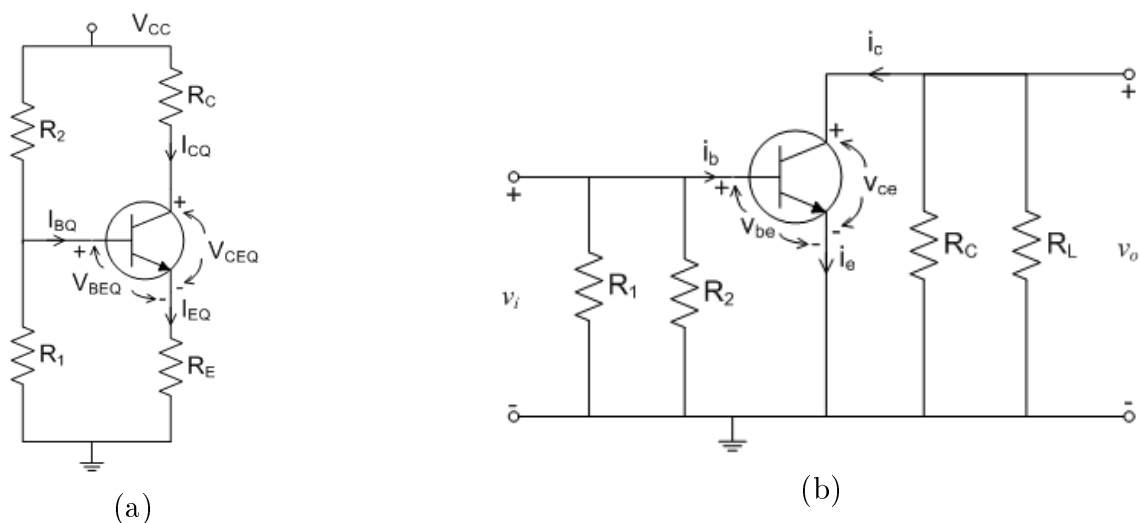


Figure 6.2: DC and AC equivalent circuits of the common-emitter circuit in Figure 6.1: (a) DC equivalent circuit (b) AC equivalent circuit.

6.1.1 DC Load Line

 


Figure 6.3: DC equivalent circuit of Figure 6.1.

DC equivalent circuit shown in Figure 6.3 above, let us first define the equivalent output-loop (CE -loop) DC resistance R_{DC} and V_{CE} as follows

$$R_{DC} = R_C + R_E \quad (6.1.1)$$

$$V_{CE} = V_{CC} - I_C R_{DC} \quad (6.1.2)$$

Thus, the rearranged **DC load line equation** (DC output equation) is given by

$$I_C = \frac{-1}{R_{DC}} V_{CE} + \frac{V_{CC}}{R_{DC}} \quad (6.1.3)$$

Note that, AC swings are around the Q -points. Here, input swing $v_{be} = v_i$ in Figure 6.4(a) below is around the input Q -point (I_{BQ}, V_{BEQ}), and output swing $v_o = v_{ce}$ in Figure 6.4(b) below is around the output Q -point (I_{CQ}, V_{CEQ}).

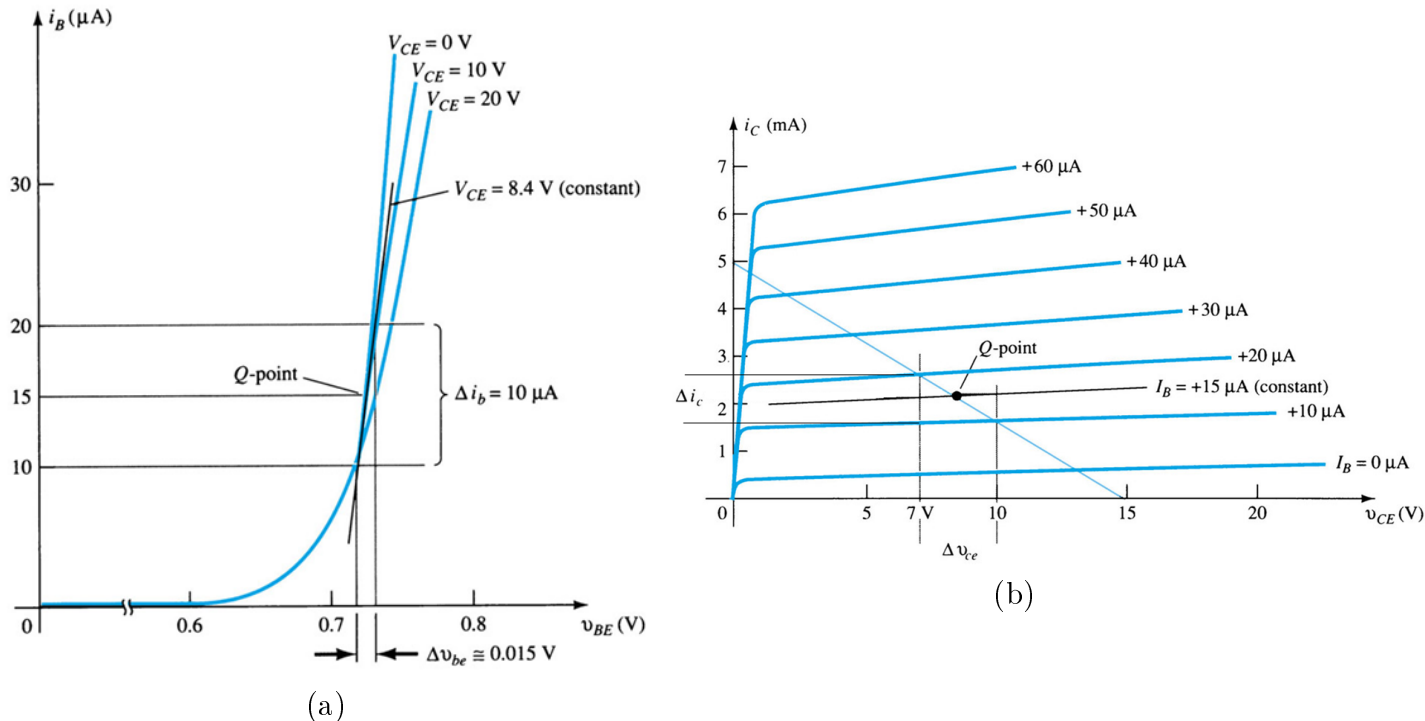


Figure 6.4: Input and output swings around the Q -points: (a) input swing (b) output swing.

6.1.2 Distortion

If the Q -point is incorrect as shown in Figure 6.5(a) below, or if the input is too high as shown in Figure 6.5(b) below, then the output swings (for a sinusoidal input) as shown in the figures below will be **distorted**, i.e., not the same shape as the input waveform.

NOTE: Load-lines shown in the figures below are the AC load-lines which we will derive in the next section.

 


Figure 6.5: Distorted output swings: (a) incorrect Q -point (b) incorrect input (i.e., high input).

6.1.3 AC Load Line

 


Figure 6.6: AC-equivalent circuit of Figure 6.1.

AC equivalent circuit shown in Figure 6.6 above, let us first define the equivalent output-loop (CE -loop) AC resistance R_{ac} and output v_o as follows

$$R_{ac} = R_C || R_L \quad (6.1.4)$$

$$v_o = v_{ce} = -i_c R_{ac} \quad (6.1.5)$$

Let us now define the AC+DC output signals i_C and v_{CE} as follows

$$i_C = i_c + I_{CQ} \quad (6.1.6)$$

$$v_{CE} = v_{ce} + V_{CEQ} \quad (6.1.7)$$

Now let us express the AC output equation $v_{ce} = -i_c R_{ac}$ in terms of v_{CE} and i_C so that we can draw this equation over the output characteristics curve as the AC load line equation.

$$v_{ce} = -i_c R_{ac} \quad (6.1.8)$$

$$v_{CE} - V_{CEQ} = -(i_C - I_{CQ}) R_{ac} \quad (6.1.9)$$

$$v_{CE} = -i_C R_{ac} + V_{CEQ} + I_{CQ} R_{ac} \quad (6.1.10)$$

Thus, the rearranged **AC load line equation** (AC output equation) is given by

$$i_C = \frac{-1}{R_{ac}} v_{CE} + I_{CQ} + \frac{V_{CEQ}}{R_{ac}} \quad (6.1.11)$$

6.1.4 AC-DC Load Lines

Let us draw DC ($V_{CE} = v_{ce} + V_{CEQ}$) and AC ($v_{CE} = -i_C R_{ac} + V_{CEQ} + I_{CQ} R_{ac}$) load lines together as shown in Figure 6.7 below.

 


Figure 6.7: AC-DC load lines.

Output swings are defined with respect to the **Q-point** (I_{CQ}, V_{CEQ}) and the **AC load line end points** on the axes.

Homework 6.1: Show that AC and DC load lines are the **same** if $R_{DC} = R_{ac}$.

Once the **Q-point** is known, i.e., the resistor values are given, **peak** values of the **maximum undistorted** voltage and current **swings** $v_{ce(p)(\max)}$ and $i_{c(p)(\max)}$ are given by

$$v_{ce(p)(\max)} = \min(V_{CEQ}, I_{CQ} R_{ac}) \quad (6.1.12)$$

and

$$i_{c(p)(\max)} = \min\left(I_{CQ}, \frac{V_{CEQ}}{R_{ac}}\right) \quad (6.1.13)$$

respectively

6.1.4.1 Maximum Symmetric Undistorted Swing Design

If we want design our circuit (i.e., select appropriate values for the resistors) in order to obtain the maximum available undistorted swing, i.e., to obtain $\max(\min(V_{CEQ}, I_{CQ}R_{ac}))$, then we obtain the following condition

$$\boxed{V_{CEQ} = I_{CQ}R_{ac}} \quad (6.1.14)$$

Thus, **Q-point** must be in the **middle** of the **AC load line**. In other words, maximum available negative and positive swings are symmetric.

Combining this AC load line requirement in (6.1.14) with the DC load-line equation given in (6.1.2), we find that we have to select the Q-point collector current as

$$\boxed{I_{CQ} = \frac{V_{CC}}{R_{DC} + R_{ac}}} \quad (6.1.15)$$

In order to attain this Q-point, we need to select appropriate values for the resistors in the *BE* loop to obtain $I_{BQ} = \frac{I_{CQ}}{\beta}$.

Once we obtained the desired Q-point in the middle of the AC load line, then the maximum available undistorted output swings will be obtained as shown in Figure 6.8 below.

 


Figure 6.8: Maximum undistorted swing design with Q-point in the middle of the AC load line.

6.1.4.2 Other Amplifier Configurations

We developed and plotted AC-DC load lines for the common-emitter configuration. Now, let us look at other configurations.

- Common-base (CB) configuration

1. Obtain R_{ac} from the CB loop.
2. Obtain R_{DC} from the CE loop.
3. Draw the AC-DC load lines i_C vs. v_{CE} as before.

NOTE: You can also draw the AC-DC load lines as i_C vs. v_{CB} by shifting the voltage axis by $V_{BE(ON)}$ volts to the left as $V_{CBQ} = V_{CEQ} - V_{BE(ON)}$. Thus, current axis will be drawn at $V_{CB(sat)} = V_{CE(sat)} - V_{BE(ON)} = 0 - V_{BE(ON)} = -V_{BE(ON)}$ volts not at 0 V.

- Common-collector (CC) configuration (also known as emitter-follower)

1. Obtain R_{ac} and R_{DC} from the CE loop as before.
2. Draw the AC-DC load lines i_E vs. v_{CE} .

NOTE: As $i_E \cong i_C$, it will be the same as drawing i_C vs. v_{CE} .

- For npn transistors, we express the currents in the reverse direction (i.e., having positive current values) and reverse the polarity of the terminal voltages (i.e., having positive voltage values), and then draw the AC-DC load lines, e.g., i_C vs. v_{EC} .

Example 6.1: Consider the circuit below with $I_{BQ} = 50 \mu\text{A}$, $I_{CQ} = 13 \text{ mA}$ and $\alpha \cong 1$.

- If $i_i = 50 \mu\text{A} \sin(\omega t)$, find i_C and v_{CE} .
- Plot AC and DC load lines together with the output voltage and current swings.

 


Figure 6.9: BJT amplifier circuit for Example 6.1.

Solution: Here $\beta_{ac} = \beta_{DC} = \beta = \frac{I_{CQ}}{I_{BQ}} = \frac{13\text{m}}{50\mu} = 260$, $R_{DC} = R_C + R_E = 1\text{k} + 0.47\text{k} = 1.47\text{k}\Omega$ and $R_{ac} = R_C || R_L = 1\text{k} || 1\text{k} = 0.5\text{k}\Omega$. So, we can find V_{CEQ} as

$$V_{CEQ} = V_{CC} - I_{CQ}R_{DC} = 30 - (13\text{m})(1.47\text{k}) = 10.89 \text{ V}$$

As $i_b \cong i_i$, we can find i_c and v_{ce} as

$$\begin{aligned} i_c &= \beta_{ac}i_b \cong \beta i_i = (260)(50\mu) = 13 \text{ mA} \sin(\omega t) \\ v_{ce} &= -i_c R_{ac} = -(13\text{m})(0.5\text{k}) = -6.5 \text{ V} \sin(\omega t). \end{aligned}$$

We find i_C and v_{CE} as

$$\begin{aligned} i_C &= I_{CQ} + i_c = 13 \text{ mA} + 13 \text{ mA} \sin(\omega t) \\ v_{CE} &= V_{CEQ} + v_{ce} = 10.89 \text{ V} - 6.5 \text{ V} \sin(\omega t) \end{aligned}$$

Thus, the AC-DC load-lines are shown in Figure 6.10 below

 


Figure 6.10: AC-DC load-lines for Example 6.1.

Example 6.2: Consider the circuit below with $\alpha \cong 1$.

- Determine the Q -point in order to obtain maximum undistorted current swing.
- Draw AC and DC load lines.

 


Figure 6.11: BJT amplifier circuit for Example 6.2.

Solution: We can design this circuit to have maximum symmetric undistorted output swing and select R_1 and R_2 values accordingly. So, from the figure $R_{DC} = R_C + R_E = 1k + 0.5k = 1.5k\Omega$ and $R_{ac} = R_C = 1k\Omega$. Thus,

$$I_{CQ} = \frac{V_{CC}}{R_{DC} + R_{ac}} = \frac{15}{1.5k + 1k} = 6 \text{ mA}$$

$$V_{CEQ} = V_{CC} - I_{CQ}R_{DC} = 15 - (6m)(1.5k) = 6 \text{ V}$$

Maximum available swings i_c and v_{ce} are given as

$$i_c = 6 \text{ mA} \sin(\omega t)$$

$$v_{ce} = -6 \text{ V} \sin(\omega t)$$

Consequently, the AC-DC load-lines are shown in Figure 6.12 below

 


Figure 6.12: AC-DC load-lines for Example 6.2.

Example 6.3: (2004-2005 MI) Consider the common-emitter BJT amplifier in the figure below.

- Explain briefly the effects of the capacitors C_1 , C_2 and C_3 on DC biasing and AC operation.
- Design the DC bias (I_{CQ} and V_{CEQ}) for the **maximum undistorted output swing** and then find the values of R_1 and R_2 which satisfies this condition. Take $\beta R_E \geq 10(R_1 || R_2)$, $V_{BE(ON)} = 0.7\text{ V}$ and $\beta = 100$.
- Draw the DC and AC load lines for this circuit and show the maximum voltage and current swings on the graph. Also, express these current and voltage swings in written form with their AC and DC components.

 


Figure 6.13: BJT amplifier circuit for Example 6.3.

Solution: a. Capacitors are open-circuit in DC operation. Thus, C_1 and C_2 are called the coupling capacitors for the protection of the Q -point of the amplifier from the input and output circuitries by preventing the circulation/leakage of DC signals and enabling only AC signals in and out. C_3 is called the emitter bypass capacitor ensuring the stability of the Q -point by enabling the emitter resistor to be in effect in DC operation and increasing the AC gain by bypassing the emitter resistor in AC operation.

b. We can design this circuit to have maximum symmetric undistorted output swing and select R_1 and R_2 values accordingly. So, from the figure $R_{DC} = R_C + R_E = 1k + 0.5k = 1.5\text{ k}\Omega$ and $R_{ac} = R_C || R_L = 1k || 1k = 0.5\text{ k}\Omega$. Thus,

$$I_{CQ} = \frac{V_{CC}}{R_{DC} + R_{ac}} = \frac{18}{1.5k + 0.5k} = 9\text{ mA}$$

$$V_{CEQ} = V_{CC} - I_{CQ}R_{DC} = 18 - (9m)(1.5k) = 4.5\text{ V}$$

As $I_{EQ} \cong I_{CQ} = 9\text{ mA}$, base voltage V_{BQ} is given by

$$V_{BQ} = V_{BE(ON)} + I_{EQ}R_E = 0.7 + (9m)(0.5k) = 5.2\text{ V}.$$

By making the assumption $\beta R_E \geq 10(R_1 || R_2)$, we can ignore the base current I_{BQ} and directly apply the voltage divider rule as

$$\begin{aligned} \frac{R_2}{R_1 + R_2} V_{CC} &\cong V_{BQ} \\ \frac{R_1 + R_2}{R_2} &= \frac{V_{CC}}{V_{BQ}} \\ \frac{R_1}{R_2} &= \frac{V_{CC}}{V_{BQ}} - 1 = \frac{18}{5.2} - 1 = 2.46. \end{aligned}$$

Let us take the highest value of $R_{BB} = R_1 || R_2$ in order to reduce the currents through R_1 and R_2 as

$$R_{BB} = R_1 || R_2 = \beta R_E / 10 = 100 \times 0.5k / 10 = 5 \text{ k}\Omega$$

If we take $a = \frac{R_1}{R_2} = 2.46$, then $R_{BB} = \frac{a}{a+1} R_2$. So, R_2 is given by

$$R_2 = \frac{a+1}{a} R_{BB} = \frac{2.46+1}{2.46} 5k = 7.03 \text{ k}\Omega$$

Thus, R_1 is given by

$$R_1 = a R_2 = (2.46)(7.03k) = 17.29 \text{ k}\Omega$$

c. AC+DC output current i_C and output voltage v_{CE} are given by

$$\begin{aligned} i_C &= I_{CQ} + i_c = 9 \text{ mA} + 9 \text{ mA} \sin(\omega t) \\ v_{CE} &= V_{CEQ} + v_{ce} = 4.5 \text{ V} - 4.5 \text{ V} \sin(\omega t) \end{aligned}$$

Consequently, the AC-DC load-lines are shown in Figure 6.14 below

 


Figure 6.14: AC-DC load-lines for Example 6.3.

Chapter 7

Field Effect Transistors (FETs)

7.1 Similarities and Differences with BJTs

Field-effect transistors (FETs) are three-terminal devices used for a variety of applications that match, to a large extent, those of the BJTs.

Similarities:

- Amplifiers
- Switching devices
- Impedance matching circuits

Differences:

- FETs are voltage controlled devices whereas BJTs are current controlled devices
- FETs also have a higher input impedance, but BJTs have higher gains
- FETs are less sensitive to temperature variations and because of their construction they are more easily integrated on ICs
- FETs are also generally more static sensitive than BJTs
- FETs have a poorer frequency response (i.e., lower gain-bandwidth product) than BJTs
- FETs have a higher output impedance than BJTs

BJT is a current-controlled device as depicted in Figure 7.1(a) below, whereas FET is a voltage-controlled device as shown in Figure 7.1(b) below.

 


Figure 7.1: BJT (*npn*) and FET (*n*-channel) comparison: (a) current-controlled device (BJT), (b) voltage-controlled device (FET).

7.2 FET Types

We are going to cover three types (JFET, DMOSFET and EMOSFET) of field effect transistors (FETs)

- **JFET:** Junction Field-Effect Transistor
- **MOSFET:** Metal-Oxide-Semiconductor Field-Effect Transistor
 - **DMOSFET:** Depletion-type MOSFET
 - **EMOSFET:** Enhancement-type MOSFET

7.3 FET Operation

FET operation can be compared to a water spigot shown in Figure 7.2 below. Water flow signifies the charge flow. In *n*-channel FETs charge flow is the electron flow, and in *p*-channel FETs charge flow is the hole flow.

 


Figure 7.2: Water analogy for the FET control mechanism.

- The source of water pressure can be likened to the applied voltage from drain to source, which establishes a flow of water (charge) from the spigot (source) to the drain.
- The valve (gate), controls the flow of water (charge) to the drain by adjusting the width of the pipe (channel). In a FET, gate adjusts the width of the channel via the applied potential between gate and the source terminals.

7.4 Junction Field-Effect Transistor (JFET)

7.4.1 Construction

There are two types of JFETs: n -channel and p -channel. The n -channel whose construction is shown in Figure 7.3 below is more widely used. There are three terminals: Drain, Source and Gate.

 


Figure 7.3: n -channel junction field-effect transistor (JFET) construction.

Here,

- Drain (D) and Source (S) are connected to n -channel.
- Gate (G) is connected to the p -type material.
- For correct operation, gate-channel pn junction must be **reverse-biased**, i.e., $V_{GS} \leq 0$.

7.4.2 Operating Characteristics

There are three basic operating conditions for a JFET:

- $V_{GS} = 0$ and $V_{DS} > 0$
- $V_{GS} < 0$ and $V_{DS} > 0$
- Voltage-controlled resistor

7.4.2.1 $V_{GS} = 0$ and $V_{DS} > 0$

A positive voltage V_{DS} is applied across the channel and the gate is connected directly to the source to establish the condition $V_{GS} = 0$ V as shown in Figure 7.4(a) below. Under these conditions the flow of charge is relatively uninhibited and is limited solely by the resistance of the n -channel between drain and source.

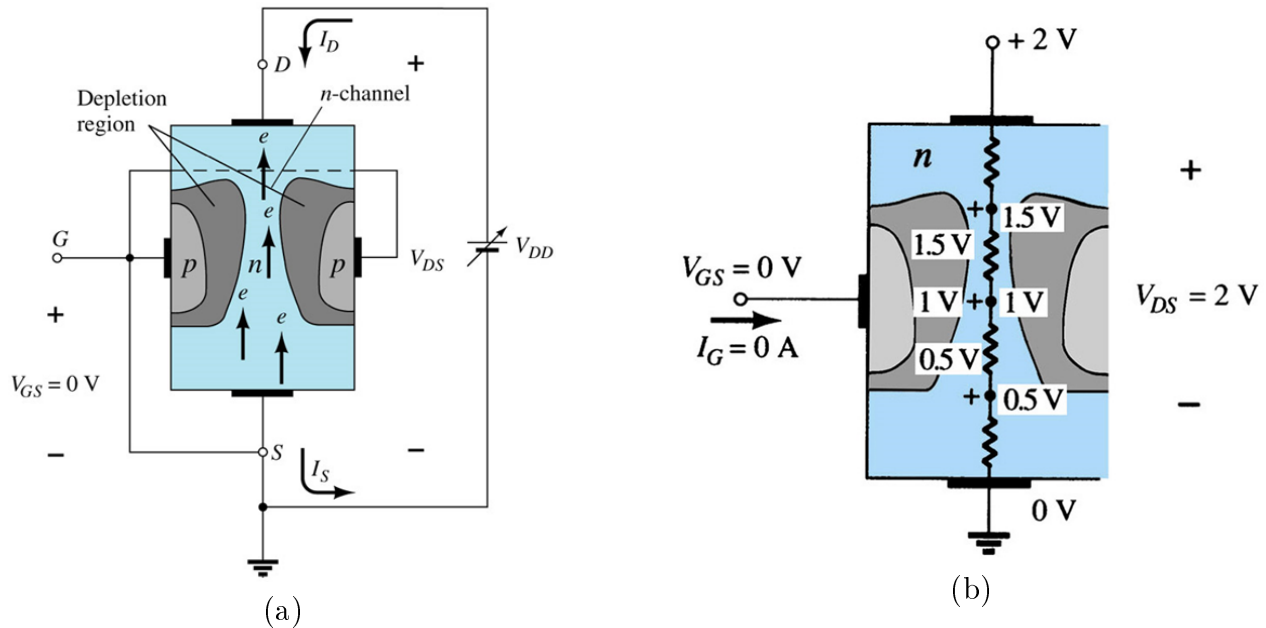


Figure 7.4: JFET at $V_{GS} = 0$ V and $V_{DS} > 0$ V: (a) DC biasing, (b) variation of the gate-channel junction reverse-bias voltages through the channel.

It is important to note that the depletion region is wider near the top of both p -type materials. The reason for the change in width of the region is best described through the help of Figure 7.4(b) above. The result is that the upper region of the p -type material will be reverse-biased by around 1.5 V, with the lower region only reverse-biased by 0.5 V.

Pinch-off

 


Figure 7.5: Pinch-off ($V_{GS} = 0$ V, $V_{DS} = -V_P$).

If $V_{GS} = 0$ and V_{DS} is further increased to a more positive voltage, then the depletion zone gets so large that it **pinches off** the n -channel as shown in Figure 7.5 above.

The level of V_{DS} that establishes this condition is referred to as the **pinch-off voltage** and is denoted by $-V_P$.

At pinch-off, I_D maintains a **saturation level** defined as I_{DSS} .

As V_{DS} is increased beyond $-V_P$, the region of close encounter between the two depletion regions increases in length along the channel, but the level of I_D remains essentially the same.

Output characteristics for $V_{GS} = 0$

The resultant output characteristics curve for $V_{GS} = 0$ V is shown in Figure 7.6 below.

 


Figure 7.6: Output characteristics, i.e., I_D versus V_{DS} , for $V_{GS} = 0$ V.

7.4.2.2 $V_{GS} < 0$ and $V_{DS} > 0$

As V_{GS} is negative the depletion regions are larger from the beginning, thus channel is narrower from the beginning. So, the pinch-off will occur at lower voltage of $V_{DS(sat)} = V_{GS} - V_P$, and the saturation current will be smaller than I_{DSS} . Once $V_{GS} = V_P$, the channel is blocked from the start, and no current flows, i.e., $I_D = 0$.

Consequently, when we draw the corresponding IV curves for each V_{GS} , we obtain the complete **output characteristics** shown in Figure 7.7 below.

 


Figure 7.7: Output characteristics of an n -Channel JFET with $I_{DSS} = 8 \text{ mA}$ and $V_P = -4 \text{ V}$.

The region to the **right** of the pinch-off point of Figure 7.7 is the region employed in amplifiers and is commonly referred to as the **constant-current**, **saturation**, or linear amplification region.

The region to the **left** of the locus (curve) of pinch-off values of Figure 7.7 is called the **ohmic** or **linear** region.

On most specification sheets the pinch-off voltage is specified as $V_{GS(off)}$ rather than V_P .

The saturation current values (constant current values after pinch-off) Figure 7.7 can be expressed in terms of the control voltage V_{GS} as

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 \quad (7.4.1)$$

This equation is called the **transfer characteristics** equation and will be investigated in detail later in the transfer characteristics section.

7.4.2.3 Voltage-Controlled Resistor (Ohmic Region)

The region to the **left** of the locus (curve) of pinch-off values of Figure 7.7 is called the **ohmic** or **linear** region.

In this region, JFET can be used as a variable resistor, where V_{GS} controls the drain-source resistance (r_d)

As V_{GS} becomes more negative, the resistance (r_d) increases.

$$r_d = \frac{r_0}{\left(1 - \frac{V_{GS}}{V_P}\right)^2} \quad (7.4.2)$$

where r_0 is the resistance with $V_{GS} = 0\text{ V}$ given in the specification sheets.

7.4.3 *p*-channel JFET

p-channel JFET acts the same as the *n*-channel JFET, except the polarities and currents are reversed as shown in Figure 7.8 below.

 


Figure 7.8: *p*-Channel JFET biasing.

7.4.3.1 Characteristics

Output characteristics of a *p*-channel JFET is shown in Figure 7.9 below. Note that Also at high levels of V_{DS} the JFET reaches a breakdown situation where I_D increases uncontrollably if $V_{DS} > V_{DS(\max)}$. Although we have not shown before breakdown region also exists in *n*-channel JFETs.

 


Figure 7.9: Output characteristics of an p -Channel JFET with $I_{DSS} = 6 \text{ mA}$ and $V_P = +6 \text{ V}$.

7.4.4 Circuit Symbol

The graphic symbols for the n -channel and p -channel JFETs are provided in Figure 7.10 below.

Note that the **arrow** at the **gate** terminal is pointing **in** for the n -channel device in Figure 7.10(a) to represent the direction in which I_G would flow if the pn junction was forward-biased.

For the p -channel device in Figure 7.10(b) the **arrow** at the **gate** terminal is pointing **out**.

 


Figure 7.10: JFET circuit symbols: (a) n -channel, (b) p -channel.

7.4.5 Transfer Characteristics

The saturation current is determined by the control voltage V_{GS} as follows

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 \quad (7.4.3)$$

This equation is called the **transfer characteristics** (transfer from input to output, i.e., from V_{GS} to I_D) and can be plotted on a graph as shown in Figure 7.11 below

 


Figure 7.11: Transfer and output characteristics curves together for an n -channel JFET.

We can also plot this transfer characteristics as the ratios of $a_D = \frac{I_D}{I_{DSS}}$ and $a_G = \frac{V_{GS}}{V_P}$ without needing the actual values of I_{DSS} and V_P as shown in Figure 7.12 below. The scaled transfer characteristics is obtained as

$$a_D = (1 - a_G)^2 \quad (7.4.4)$$

where $0 \leq a_G \leq 1$ (note that also $0 \leq a_D \leq 1$). For $a_D = 0.5$, we obtain $a_G \cong 0.3$. So, (0.3, 0.5)-point can be also used in plot generation. With the values of I_{DSS} and V_P , we know that

$$V_{GS} = a_G V_P \quad (7.4.5)$$

$$I_D = a_D I_{DSS} \quad (7.4.6)$$

 


Figure 7.12: Scaled transfer characteristics curve.

7.5 Metal-Oxide-Semiconductor Field-Effect Transistors (MOSFETs)

MOSFETs have characteristics similar to JFETs and additional characteristics that make them very useful.

There are two types of MOSFETs:

- Depletion-type MOSFET (DMOSFET)
- Enhancement-type MOSFET (EMOSFET)

The terms *depletion* and *enhancement* define their basic mode of operation.

7.5.1 Depletion-Type MOSFET (DMOSFET)

7.5.1.1 Construction

There are two types of DMOSFETs: *n*-channel and *p*-channel. The *n*-channel whose construction is shown in Figure 7.13 below is more widely used.

 


Figure 7.13: *n*-channel depletion-type MOSFET construction.

- A slab of *p*-type material is formed from a silicon base and is referred to as the **substrate**.
- For correct operation, substrate-channel *pn* junction must be **reverse-biased**.

In this course, we will only consider the cases where the **substrate** (*SS*) terminal is **connected** (shorted) to the **source** (*S*) terminal.

- Drain (*D*) and Source (*S*) are connected to *n*-channel via metal contacts.
- **Gate** (*G*) is connected to a metal contact surface but remains **insulated** from the *n*-channel by a very thin silicon dioxide (SiO_2) layer.

7.5.1.2 Operating Characteristics

In a DMOSFET, the **channel is already present** under no-bias conditions or $V_{GS} = 0\text{ V}$.

Here, V_{GS} controls the **initial channel width** (and value of the saturation current).

When V_{GS} is fixed, for a positive value of V_{DS} the width of the channel gets narrower towards the top of the channel as the voltage across the channel increases towards the top as shown in Figure 7.14 below.

Eventually, when we increase the value of V_{DS} , the channel will be pinched-off at some value of V_{DS} and the device will go into the saturation mode.

 


Figure 7.14: Change in channel width (and depletion region) for a fixed value of V_{GS} (V_{GS} determines the initial channel width) with $V_{DS} > 0$.

- V_{GS} controls the **initial channel width** by attracting or repelling electrons.

A **negative** value of V_{GS} repels electrons (and attracts holes), so the channel gets narrower. This mode is exactly like a JFET, and it is called the **depletion mode**.

A **positive** value of V_{GS} attracts electrons (and repels holes), so the channel gets wider as shown in Figure 7.15 below. Thus unlike JFETs, the channel width can be increased in DMOSFETs. This mode is called the **enhancement mode**.

 


Figure 7.15: Increase (or enhancement) in initial channel width when $V_{GS} > 0$.

7.5.1.3 Transfer Characteristics

Similar to JFET, DMOSFET transfer characteristics equation is given by

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 \quad (7.5.7)$$

where V_{GS} is allowed to be opposite polarity of V_P (i.e., $V_{GS} > 0$ allowed for n -channel DMOSFETs) as shown in Figure 7.16

 


Figure 7.16: Transfer and output characteristics curves together for an n -channel DMOSFET.

7.5.1.4 *p*-channel DMOSFET

The *p*-channel DMOSFET is similar to the *n*-channel, except that the voltage polarities and current directions are reversed. Its construction (a), transfer characteristics (b) and output characteristics (c) are shown in Figure 7.17 below.

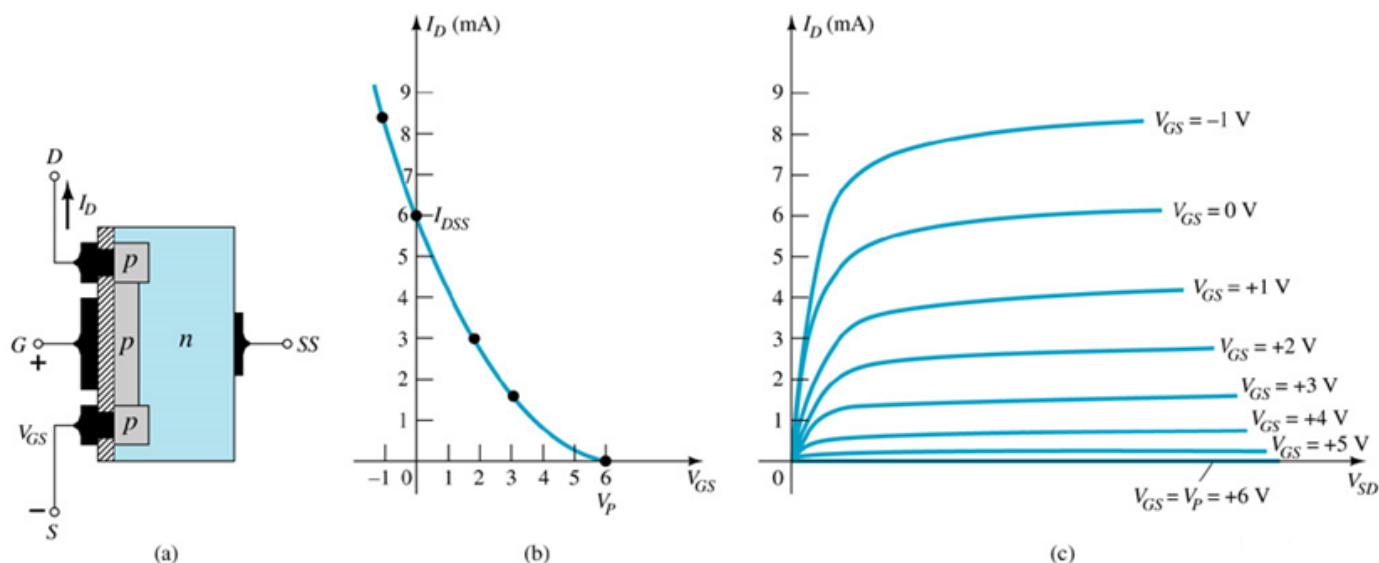


Figure 7.17: *p*-channel DMOSFET with $I_{DSS} = 6$ mA and $V_P = +6$ V: (a) construction, (b) transfer characteristics, (c) output characteristics.

7.5.2 Circuit Symbol

The graphic symbols for the *n*-channel and *p*-channel DMOSFETs are provided in Figure 7.18 below. Notice that there is a gap between the gate and the channel representing the insulation (SiO_2) layer between the gate and the channel.

Note that the **arrow** at the **substrate** (SS) terminal is pointing **in** for the *n*-channel device in Figure 7.18(a) to represent the direction of substrate-channel *pn* junction.

For the *p*-channel device in Figure 7.18(b) the **arrow** at the **substrate** terminal is pointing **out**.

 


Figure 7.18: DDMOSFET circuit symbols: (a) n -channel, (b) p -channel.

7.5.3 Enhancement-Type MOSFET (EMOSFET)

7.5.3.1 Construction

There are two types of EMOSFETs: n -channel and p -channel. The n -channel whose construction is shown in Figure 7.19 below is more widely used.

 


Figure 7.19: n -channel enhancement-type MOSFET construction.

- In an EMOSFET, **no channel** is present under no-bias conditions. We need to provide a positive gate-to-source voltage **greater** than a **threshold voltage** to initially form a channel between drain and source terminals, i.e., $V_{GS} \geq V_{GS(Th)}$.
- Thus, EMOSFET always works in the **enhancement** mode.

- Once V_{GS} is fixed and a channel is formed, it operates like a normal FET.

7.5.3.2 Transfer Characteristics

EMOSFET transfer characteristics equation plotted in shown in Figure 7.20 below is given by

$$I_D = k (V_{GS} - V_{GS(Th)})^2 \quad (7.5.8)$$

where k and $V_{GS(Th)}$ are device constants given in the specifications sheets.

If k is not given, it can also be determined from a particular point (V_{GS_0}, I_{D_0}) on the transfer characteristics curve of the device as follows

$$k = \frac{I_{D_0}}{(V_{GS_0} - V_{GS(Th)})^2} \quad (7.5.9)$$

 


Figure 7.20: Transfer and output characteristics curves together for an n -channel EMOSFET.

Drain-to-source pinch-off (saturation) voltage $V_{DS(sat)}$ is also given by

$$V_{DS(sat)} = V_{GS} - V_{GS(Th)} \quad (7.5.10)$$

- EMOSFET transfer characteristics equation below can also be **used** for **DMOSFETS**

$$I_D = k (V_{GS} - V_{GS(Th)})^2$$

where

$$V_{GS(Th)} = V_P \quad (7.5.11)$$

$$k = \frac{I_{DSS}}{V_P^2} \quad (7.5.12)$$

Homework 7.1: Show that results (7.5.11) and (7.5.12) above are correct.

7.5.3.3 *p*-channel EMOSFET

The *p*-channel DMOSFET is similar to the *n*-channel, except that the voltage polarities and current directions are reversed. Its construction (a), transfer characteristics (b) and output characteristics (c) are shown in Figure 7.21 below.

 


Figure 7.21: *p*-channel EMOSFET with $V_{GS(th)} = 2$ V and $k = 0.5$ mA/V²: (a) construction, (b) transfer characteristics, (c) output characteristics.

7.5.4 Circuit Symbol

The graphic symbols for the *n*-channel and *p*-channel EMOSFETs are provided in Figure 7.22 below. Notice that channel is represented as **dashed line** to reflect the fact that a channel does not exist under no-bias conditions.

Note that the **arrow** at the **substrate** (*SS*) terminal is pointing **in** for the *n*-channel device in Figure 7.22(a) to represent the direction of substrate-channel *pn* junction.

For the *p*-channel device in Figure 7.22(b) the **arrow** at the **substrate** terminal is pointing **out**.

 


Figure 7.22: EMOFET circuit symbols: (a) n -channel, (b) p -channel.

7.5.5 MOSFET Handling

MOSFETs are very static sensitive. Because of the very thin SiO_2 layer between the external terminals and the layers of the device, any small electrical discharge can establish an unwanted conduction.

Protection:

- Always transport in a static sensitive bag
- Always wear a static strap when handling MOSFETs
- Apply voltage limiting devices between the Gate and Source, such as back-to-back Zeners to limit any transient voltage.

7.6 Summary

The transfer curves and some important characteristics of the n -channel FETs are displayed in Figure 7.23 below. A clear understanding of all the curves and parameters of the table will provide a sufficient background for the DC and AC analyses.

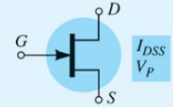
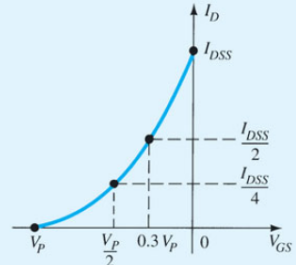
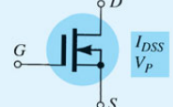
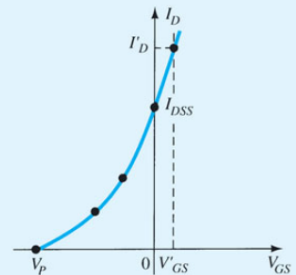
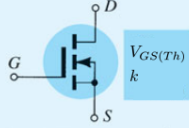
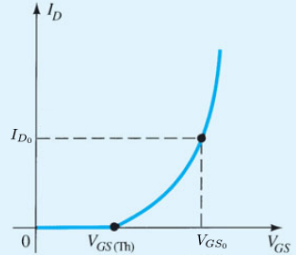
Type	Symbol and Basic Relationships	Transfer Curve	Input Resistance and Capacitance
JFET (<i>n</i> -channel)	$I_G = 0 \text{ A}, I_D = I_S$  $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$		$R_i > 100 \text{ M}\Omega$ $C_i: (1 - 10) \text{ pF}$
MOSFET depletion type (<i>n</i> -channel)	$I_G = 0 \text{ A}, I_D = I_S$  $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$		$R_i > 10^{10} \Omega$ $C_i: (1 - 10) \text{ pF}$
MOSFET enhancement type (<i>n</i> -channel)	$I_G = 0 \text{ A}, I_D = I_S$  $I_D = k (V_{GS} - V_{GS(Th)})^2$ $k = \frac{I_{D0}}{(V_{GS0} - V_{GS(Th)})^2}$		$R_i > 10^{10} \Omega$ $C_i: (1 - 10) \text{ pF}$

Figure 7.23: *n*-channel FET summary.

We can summarize the *n*-channel FET model with its state and circuit behaviour with the table below.

<i>n</i> -channel FET Model		
State	Circuit Behaviour	Test Condition
CUTOFF	$I_D = 0,$ $I_S = 0, I_G = 0$	$V_{GS} < V_{GS(Th)}$
SATURATION	$I_D = k (V_{GS} - V_{GS(Th)})^2,$ $I_S = I_D, I_G = 0$	$V_{GS} \geq V_{GS(Th)},$ $V_{DS} \geq V_{DS(sat)}$
OHMIC (LINEAR)	$I_D = \text{not covered in this course},$ $I_S = I_D, I_G = 0$	$V_{GS} \geq V_{GS(Th)},$ $V_{DS} < V_{DS(sat)}, I_D < I_{D(sat)}$

- **NOTE 1:** For JFET and DMOSFETs, take $V_{GS(Th)} = V_P$ and $k = \frac{I_{DSS}}{V_P^2}$
- **NOTE 2:** For JFETs, make sure $V_P \leq V_{GS} \leq 0$.

- **NOTE 3:** V_{Th} , V_T and V_{TN} (or V_{TP}) notations are also used in place of $V_{GS(Th)}$.

We can show the circuit behaviour for the CUTOFF and SATURATION modes of the n -channel FETs in Figure 7.24 below.

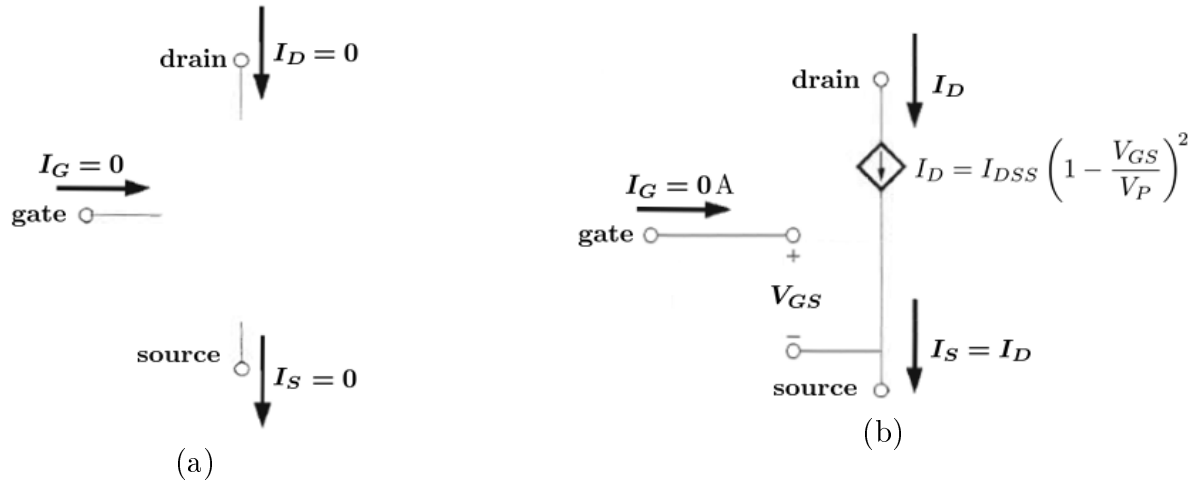


Figure 7.24: Circuit behaviour of the n -channel FET model: (a) Cutoff state, (b) Saturation state

- For a p -channel FET transistor, the **polarities** and **directions** are simply **reversed**.

For example, the a p -channel FET will be ON (i.e., in SATURATION mode) when $V_{SG} \geq V_{SG(Th)}$ (i.e., when $V_{GS} \leq V_{GS(Th)}$).

Chapter 8

DC Biasing of FETs

8.1 DC Biasing

8.2 FET DC Analysis

1. Draw the DC equivalent circuit (signal frequency is zero, i.e., $f = 0$)
 - a) Capacitors are open circuit, i.e., $X_C \rightarrow \infty$.
 - b) Kill the AC power sources (short-circuit AC voltage sources and open-circuit AC current sources).
2. Write KVL for the GS -loop (i.e., GS -loop load line (or transfer load line) equation)
 - a) Draw the transfer characteristics curve using the appropriate transfer characteristics equation.
 - b) Draw the GS -loop load line over the transfer characteristics curve
 - c) The intersection gives us I_{DQ} and V_{GSQ} .

NOTE: You can also solve two equations simultaneously and obtain the result analytically by solving the resultant quadratic equation. However, graphical way is less error-prone if the graph has a fine resolution.
3. Write KVL for the DS -loop (i.e., DS -loop load line (or output load line) load line equation)
 - a) Calculate V_{DSQ} using I_{DQ} value from Step 2c.

8.3 DC Biasing Circuits

Most common four common-source biasing circuits are given below

JFET Biasing Circuits

- Fixed-Bias
- Self-Bias
- Voltage-Divider

DMOSFET Biasing Circuits

- Self-Bias
- Voltage-Divider

EMOSFET Biasing Circuits

- Voltage-Feedback
- Voltage-Divider

8.3.1 Fixed-Bias Configuration

A fixed-bias JFET circuit is given in Figure 8.1 below

 


Figure 8.1: Fixed-bias JFET circuit.

Let us start DC analysis by drawing the DC equivalent circuit as shown in Figure 8.2 below

 


Figure 8.2: DC equivalent circuit (with $I_G = 0$) of the fixed-bias configuration in Figure 8.1.

Note that R_G is ignored as $I_G = 0$.

8.3.1.1 Gate-Source Loop

We can write KVL equation on the GS -loop

$$V_{GS} = -V_{GG}. \quad (8.3.1)$$

Then, we obtain V_{GSQ} and I_{DSQ} by solving the following two equations simultaneously

$$V_{GS} = -V_{GG} \quad \dots \text{transfer load-line} \quad (8.3.2)$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 \quad \dots \text{transfer characteristics} \quad (8.3.3)$$

The solution is trivial in this case and we obtain the result as

$$V_{GSQ} = -V_{GG} \quad (8.3.4)$$

$$I_{DQ} = I_{DSS} \left(1 - \frac{V_{GSQ}}{V_P}\right)^2 \quad (8.3.5)$$

We can also obtain the result graphically by plotting equations (8.3.2) and (8.3.3) on the same graph as shown in Figure 8.3 below.

 


Figure 8.3: Graphical solution (for transfer load-line and transfer characteristics equations) for the fixed-bias configuration in Figure 8.1.

8.3.1.2 Drain-Source Loop

Let us write down the KVL equation on the DS -loop

$$V_{DD} - I_D R_D - V_{DS} = 0 \quad (8.3.6)$$

$$V_{DS} = V_{DD} - I_D R_D \quad \dots \text{DC load-line equation} \quad (8.3.7)$$

As we already obtained I_{DQ} in Figure 8.3 we find V_{DSQ} as

$$\boxed{V_{DSQ} = V_{DD} - I_{DQ} R_D} \quad (8.3.8)$$

Thus, we obtained the Q -point (I_{DQ}, V_{DSQ}) , i.e., the operating point.

8.3.2 Self-Bias Configuration

A fixed-bias JFET circuit is given in Figure 8.4 below

 


Figure 8.4: Self-bias JFET circuit.

Let us start DC analysis by drawing the DC equivalent circuit as shown in Figure 8.5 below

 


Figure 8.5: DC equivalent circuit (with $I_G = 0$) of the self-bias configuration in Figure 8.4.

Note that R_G is ignored as $I_G = 0$.

8.3.2.1 Gate-Source Loop

We can write KVL equation on the GS -loop

$$-V_{GS} - I_S R_S = 0 \quad (8.3.9)$$

$$V_{GS} = -I_D R_S \quad \dots \text{ as } I_S = I_D. \quad (8.3.10)$$

Then, we obtain V_{GSQ} and I_{DSQ} by solving the following two equations simultaneously

$$V_{GS} = -I_D R_S \quad \dots \text{transfer load-line} \quad (8.3.11)$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 \quad \dots \text{transfer characteristics} \quad (8.3.12)$$

It is better to obtain the result graphically by plotting equations (8.3.11) and (8.3.12) on the same graph as shown in Figure 8.6 below.

 


Figure 8.6: Graphical solution (for transfer load-line and transfer characteristics equations) for the self-bias configuration in Figure 8.4.

The graphically obtained current value I_{DQ} may be refined using equations (8.3.11) and (8.3.12) in an iteration loop as follows

1. Insert graphically obtained I_D into (8.3.11) and obtain a V_{GS} value
2. Insert V_{GS} obtained in Step 1 into (8.3.12) and obtain a new I_D value to be used in Step 1.
3. Repeat Step 1 and Step 2 until ΔI_D , the difference between the old I_D used in Step 1 and new I_D obtained in Step 2, is small enough.

8.3.2.2 Drain-Source Loop

Let us write down the KVL equation on the DS -loop

$$V_{DD} - I_D R_D - V_{DS} - I_S R_S = 0 \quad (8.3.13)$$

$$V_{DD} - I_D R_D - V_{DS} - I_D R_S = 0 \quad \dots \text{as } I_S = I_D \quad (8.3.14)$$

$$V_{DD} - I_D (R_D + R_S) - V_{DS} = 0 \quad \dots \text{DC load-line equation} \quad (8.3.15)$$

As we already obtained I_{DQ} in Figure 8.6 we find V_{DSQ} as

$$\boxed{V_{DSQ} = V_{DD} - I_{DQ}(R_D + R_S)} \quad (8.3.16)$$

Thus, we obtained the Q -point (I_{DQ}, V_{DSQ}) , i.e., the operating point.

Example 8.1: For the figure below, calculate all DC currents and voltages.

 


Figure 8.7: Self-bias JFET circuit for Example 8.1.

Solution: Let us express V_{GS} using the KVL equation of GS -loop and I_D from the transfer characteristics equation

$$V_{GS} = -I_D R_S = -1k I_D$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 = (8m) \left(1 + \frac{V_{GS}}{6}\right)^2$$

where $-6 \leq V_{GS} \leq 0$.

We obtain I_{DQ} and V_{GSQ} by drawing these two equations on the same graph as shown in Figure 8.8 below

 


Figure 8.8: Obtaining I_{DQ} graphically for the circuit in Figure 8.7.

Finally, we obtain V_{DSQ} from the DS -loop as

$$V_{DSQ} = V_{DD} - I_{DQ}(R_D + R_S) = 20 - (2.6m)(3.3k + 1k) = 8.82 \text{ V}.$$

8.3.3 Voltage-Divider Bias Configuration

A voltage-divider bias JFET circuit is given in Figure 8.9 below

 


Figure 8.9: Voltage-divider bias JFET circuit.

Let us start DC analysis by drawing the DC equivalent circuit as shown in Figure 8.10 below

 


Figure 8.10: DC equivalent circuit of the voltage-divider configuration in Figure 8.9.

8.3.3.1 Gate-Source Loop

We can write KVL equation on the GS -loop

$$V_G - V_{GS} - I_S R_S = 0 \quad \dots \text{ where } V_G = \frac{R_2}{R_1 + R_2} V_{DD} \quad (8.3.17)$$

$$V_{GS} = V_G - I_D R_S \quad \dots \text{ as } I_S = I_D. \quad (8.3.18)$$

Then, we obtain V_{GSQ} and I_{DSSQ} by solving the following two equations simultaneously

$$V_{GS} = V_G - I_D R_S \quad \dots \text{ transfer load-line} \quad (8.3.19)$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 \quad \dots \text{ transfer characteristics} \quad (8.3.20)$$

It is better to obtain the result graphically by plotting equations (8.3.19) and (8.3.20) on the same graph as shown in Figure 8.11 below.

 


Figure 8.11: Graphical solution (for transfer load-line and transfer characteristics equations) for the voltage-divider configuration in Figure 8.9.

The graphically obtained current value I_{DQ} may be refined using equations (8.3.19) and (8.3.20) in an iteration loop as follows

1. Insert graphically obtained I_D into (8.3.19) and obtain a V_{GS} value
2. Insert V_{GS} obtained in Step 1 into (8.3.20) and obtain a new I_D value to be used in Step 1.
3. Repeat Step 1 and Step 2 until ΔI_D , the difference between the old I_D used in Step 1 and new I_D obtained in Step 2, is small enough.

8.3.3.2 Drain-Source Loop

Let us write down the KVL equation on the DS -loop

$$V_{DD} - I_D R_D - V_{DS} - I_S R_S = 0 \quad (8.3.21)$$

$$V_{DD} - I_D R_D - V_{DS} - I_D R_S = 0 \quad \dots \text{ as } I_S = I_D \quad (8.3.22)$$

$$V_{DD} - I_D (R_D + R_S) - V_{DS} = 0 \quad \dots \text{ DC load-line equation } (8.3.23)$$

As we already obtained I_{DQ} in Figure 8.11 we find V_{DSQ} as

$$\boxed{V_{DSQ} = V_{DD} - I_{DQ} (R_D + R_S)} \quad (8.3.24)$$

Thus, we obtained the Q -point (I_{DQ}, V_{DSQ}) , i.e., the operating point.

Example 8.2: For the figure below, calculate all DC currents and voltages.

 


Figure 8.12: Voltage-divider bias JFET circuit for Example 8.2.

Solution: Let us find V_G , and express V_{GS} using the KVL equation of GS -loop and I_D from the transfer characteristics equation

$$V_G = \frac{R_2}{R_1 + R_2} V_{DD} = \frac{0.27M}{2.1M + 0.27M} 16 = 1.82 \text{ V.}$$

$$V_{GS} = V_G - I_D R_S = 1.82 - 1.5k I_D$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 = (8m) \left(1 + \frac{V_{GS}}{4} \right)^2$$

where $-4 \leq V_{GS} \leq 0$.

We obtain I_{DQ} and V_{GSQ} by drawing these two equations on the same graph as shown in Figure 8.13 below

 


Figure 8.13: Obtaining I_{DQ} graphically for the circuit in Figure 8.12.

Finally, we obtain V_{DSQ} from the DS -loop as

$$V_{DSQ} = V_{DD} - I_{DQ} (R_D + R_S) = 16 - (2.4m)(2.4k + 1.5k) = 6.64 \text{ V}.$$

Example 8.3: For the figure below, calculate Q -point. Repeat for $R_S = 150 \Omega$.

 


Figure 8.14: Voltage-divider bias DMOSFET circuit for Example 8.3.

Solution: Let us find V_G , and express V_{GS} using the KVL equation of GS -loop and I_D from

the transfer characteristics equation

$$V_G = \frac{R_2}{R_1 + R_2} V_{DD} = \frac{10M}{110M + 10M} 18 = 1.5 \text{ V.}$$

$$V_{GS} = V_G - I_D R_S = 1.5 - 0.75k I_D$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 = (6m) \left(1 + \frac{V_{GS}}{3} \right)^2$$

where $V_{GS} \geq -3 \text{ V}$.

We obtain I_{DQ} and V_{GSQ} by drawing these two equations on the same graph as shown in Figure 8.15 below

 


Figure 8.15: Obtaining I_{DQ} graphically for the circuit in Figure 8.14 with $R_S = 750 \Omega$.

Finally, we obtain V_{DSQ} from the DS -loop as

$$V_{DSQ} = V_{DD} - I_{DQ} (R_D + R_S) = 18 - (3.1m) (1.8k + 0.75k) = 10.1 \text{ V.}$$

Let us repeat the calculations for $R_S = 150 \Omega$. Transfer load-line equation (GS -loop equation) changes as below

$$V_{GS} = V_G - I_D R_S = 1.5 - 0.15k I_D$$

We reobtain I_{DQ} and V_{GSQ} by redrawing the transfer load-line and transfer characteristics equations on the same graph as shown in Figure 8.16 below

 


Figure 8.16: Obtaining I_{DQ} graphically for the circuit in Figure 8.14 with $R_S = 150\ \Omega$.

Finally, V_{DSQ} is recalculated from the DS -loop as

$$V_{DSQ} = V_{DD} - I_{DQ}(R_D + R_S) = 18 - (7.6\text{m})(1.8\text{k} + 0.15\text{k}) = 3.18\text{ V}.$$

Example 8.4: For the figure below, calculate all DC currents and voltages.

 


Figure 8.17: Voltage-divider bias EMOSFET circuit for Example 8.4.

Solution: Let us find V_G , and express V_{GS} using the KVL equation of GS -loop and I_D from

the transfer characteristics equation

$$V_G = \frac{R_2}{R_1 + R_2} V_{DD} = \frac{18M}{22M + 18M} 40 = 18 \text{ V.}$$

$$V_{GS} = V_G - I_D R_S = 18 - 0.82k I_D$$

$$I_D = k (V_{GS} - V_{GS(Th)})^2 = (0.12m) (V_{GS} - 5)^2$$

where $V_{GS} \geq 5 \text{ V}$.

We obtain I_{DQ} and V_{GSQ} by drawing these two equations on the same graph as shown in Figure 8.18 below

 


Figure 8.18: Obtaining I_{DQ} graphically for the circuit in Figure 8.17.

Finally, we obtain V_{DSQ} from the DS -loop as

$$V_{DSQ} = V_{DD} - I_{DQ} (R_D + R_S) = 40 - (6.7m) (3k + 0.82k) = 14.4 \text{ V.}$$

8.3.4 Voltage-Feedback Bias Configuration

A voltage-feedback bias EMOSFET circuit is given in Figure 8.19 below

 


Figure 8.19: Voltage-feedback bias EMOSFET circuit.

Let us start DC analysis by drawing the DC equivalent circuit as shown in Figure 8.20 below

 


Figure 8.20: DC equivalent circuit (with $I_G = 0$) of the voltage-feedback configuration in Figure 8.19.

Note that R_G is ignored as $I_G = 0$.

8.3.4.1 Gate-Source Loop

We can write KVL equation on the GS -loop

$$V_{DD} - V_{GS} - I_D R_D = 0 \quad (8.3.25)$$

$$V_{GS} = V_G - I_D R_D \quad (8.3.26)$$

Then, we obtain V_{GSQ} and I_{DSQ} by solving the following two equations simultaneously

$$V_{GS} = V_{DD} - I_D R_D \quad \dots \text{transfer load-line} \quad (8.3.27)$$

$$I_D = k (V_{GS} - V_{GS(Th)})^2 \quad \dots \text{transfer characteristics} \quad (8.3.28)$$

It is better to obtain the result graphically by plotting equations (8.3.27) and (8.3.28) on the same graph as shown in Figure 8.21 below.

 


Figure 8.21: Graphical solution (for transfer load-line and transfer characteristics equations) for the voltage-feedback configuration in Figure 8.19.

The graphically obtained current value I_{DQ} may be refined using equations (8.3.27) and (8.3.28) in an iteration loop as follows

1. Insert graphically obtained I_D into (8.3.27) and obtain a V_{GS} value
2. Insert V_{GS} obtained in Step 1 into (8.3.28) and obtain a new I_D value to be used in Step 1.
3. Repeat Step 1 and Step 2 until ΔI_D , the difference between the old I_D used in Step 1 and new I_D obtained in Step 2, is small enough.

8.3.4.2 Drain-Source Loop

Let us write down the KVL equation on the DS -loop

$$V_{DD} - I_D R_D - V_{DS} = 0 \quad \dots \text{DC load-line equation (8.3.29)}$$

As we already obtained I_{DQ} in Figure 8.21 we find V_{DSQ} as

$$\boxed{V_{DSQ} = V_{DD} - I_{DQ} R_D} \quad (8.3.30)$$

Note that, here $V_{DSQ} = V_{GSQ}$.

Thus, we obtained the Q -point (I_{DQ}, V_{DSQ}) , i.e., the operating point.

Example 8.5: For the figure below, calculate all DC currents and voltages.

 


Figure 8.22: Voltage-feedback bias EMOSFET circuit for Example 8.5.

Solution: Let us find V_G , and express V_{GS} using the KVL equation of GS -loop and I_D from the transfer characteristics equation

$$V_{GS} = V_{DD} - I_D R_D = 12 - 2k I_D$$

$$I_D = k (V_{GS} - V_{GS(Th)})^2 = (0.24\text{m}) (V_{GS} - 3)^2$$

where $V_{GS} \geq 3 \text{ V}$.

We obtain I_{DQ} and V_{GSQ} by drawing these two equations on the same graph as shown in Figure 8.23 below

 


Figure 8.23: Obtaining I_{DQ} graphically for the circuit in Figure 8.22.

Finally, we obtain V_{DSQ} from the DS -loop as

$$V_{DSQ} = V_{DD} - I_{DQ}R_D = 12 - (2.75\text{m})(2k) = 6.4 \text{ V}.$$

8.3.5 p -channel FETs

The analysis for p -channel FET circuits is the same as that for n -channel FET circuits.

The only differences are that

1. Currents are flowing in the opposite direction.
2. Voltages have opposite polarity, e.g., $V_{SG} \geq V_{SG(Th)}$ (i.e., $V_{GS} \leq V_{GS(Th)}$) is needed to turn on a p -channel FET.
3. If properly biased, then $V_S > V_D$, i.e., $V_{SD} > 0$.

Example 8.6: For the figure below, calculate all DC currents and voltages.

 


Figure 8.24: Voltage-divider bias JFET circuit for Example 8.6.

Solution: Let us find V_G , and express V_{GS} using the KVL equation of GS -loop and I_D from the transfer characteristics equation

$$V_G = \frac{R_2}{R_1 + R_2} V_{DD} = \frac{20k}{68k + 20k} (-20) = -4.55 \text{ V.}$$

$$V_{GS} = V_G + I_D R_S = -4.55 + 1.8k I_D$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 = (8m) \left(1 - \frac{V_{GS}}{4}\right)^2$$

where $-4 \leq V_{GS} \leq 0$.

We obtain I_{DQ} and V_{GSQ} by drawing these two equations on the same graph as shown in Figure 8.25 below

 


Figure 8.25: Obtaining I_{DQ} graphically for the circuit in Figure 8.24.

Finally, we obtain V_{DSQ} from the DS -loop as

$$V_{DSQ} = V_{DD} + I_{DQ} (R_D + R_S) = (-20) + (3.4m) (2.7k + 1.8k) = -4.7V.$$

Thus, $V_{SDQ} = 4.7V$.

8.4 Practical Applications

Some practical FET applications are listed below:

- Voltage-controlled resistor
- JFET voltmeter
- Timer network
- Fiber optic circuitry
- MOSFET relay driver

8.5 Summary

Summary of n -channel JFET and MOSFET bias circuits are given in Figure 8.26 and Figure 8.27, respectively.

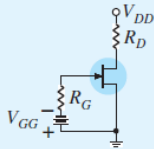
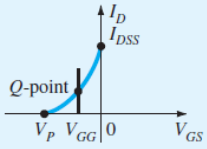
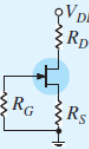
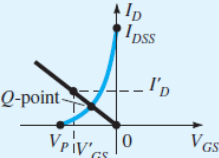
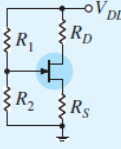
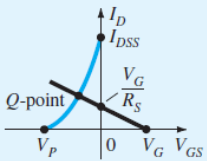
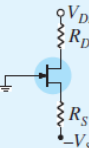
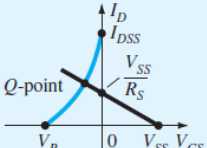
Type	Configuration	Pertinent Equations	Graphical Solution
JFET Fixed-bias		$V_{GSQ} = -V_{GG}$ $V_{DS} = V_{DD} - I_D R_D$	
JFET Self-bias		$V_{GS} = -I_D R_S$ $V_{DS} = V_{DD} - I_D (R_D + R_S)$	
JFET Voltage-divider bias		$V_G = \frac{R_2}{R_1 + R_2} V_{DD}$ $V_{GS} = V_G - I_D R_S$ $V_{DS} = V_{DD} - I_D (R_D + R_S)$	
JFET Common-gate		$V_{GS} = V_{SS} - I_D R_S$ $V_{DS} = V_{DD} + V_{SS} - I_D (R_D + R_S)$	

Figure 8.26: n -channel JFET bias circuits.

Type	Configuration	Pertinent Equations	Graphical Solution
Depletion-type MOSFET Fixed-bias		$V_{GS_Q} = +V_{GG}$ $V_{DS} = V_{DD} - I_D R_D$	
Depletion-type MOSFET Voltage-divider bias		$V_G = \frac{R_2}{R_1 + R_2} V_{DD}$ $V_{GS} = V_G - I_S R_S$ $V_{DS} = V_{DD} - I_D (R_D + R_S)$	
Enhancement type MOSFET Feedback configuration		$V_{GS} = V_{DS}$ $V_{GS} = V_{DD} - I_D R_D$	
Enhancement type MOSFET Voltage-divider bias		$V_G = \frac{R_2}{R_1 + R_2} V_{DD}$ $V_{GS} = V_G - I_D R_S$	

Figure 8.27: *n*-channel MOSFET bias circuits.

Chapter 9

AC-DC Load Lines of FET Circuits

9.1 FET AC Analysis

1. Draw the AC equivalent circuit (signal frequency is infinity, i.e., $f = \infty$)
 - a) Capacitors are short circuit, i.e., $X_C \rightarrow 0$.
 - b) Kill the DC power sources (short-circuit DC voltage sources and open-circuit DC current sources).
2. Write KVL for the loop which contains DS terminals
 - a) Develop AC load-line equation.
3. Draw AC-DC load lines
 - a) Find available swings for a given input or find maximum undistorted swings.

9.1.1 AC and DC Load Lines

- AC and DC load line equations of FETs are similar to the AC and DC load line equations of BJTs where gate (G), drain (D) and source (S) replace base (B), collector (C) and emitter (E), respectively, in the subscripts of the equations.
- Thus, FET DC load line equation is given by

$$V_{DS} = V_{DD} - I_D R_{DC} \quad (9.1.1)$$

where R_{DC} is the equivalent output-loop (DS -loop) DC resistance. Hence, the rearranged **DC load line equation** (DC output equation) is given by

$$I_D = \frac{-1}{R_{DC}} V_{DS} + \frac{V_{DD}}{R_{DC}} \quad (9.1.2)$$

- Similarly, FET AC load line equation is given by

$$v_{DS} = -i_D R_{ac} + V_{DSQ} + I_{DQ} R_{ac} \quad (9.1.3)$$

where R_{ac} is the equivalent output-loop (DS -loop) AC resistance, $v_{DS} = V_{DSQ} + v_{ds}$ and $i_D = I_{DQ} + i_d$. Hence, the rearranged **AC load line equation** (AC output equation) is given by

$$i_D = \frac{-1}{R_{ac}} v_{DS} + I_{DQ} + \frac{V_{DSQ}}{R_{ac}} \quad (9.1.4)$$

Let us draw DC and AC load lines together as shown in Figure 9.1 below.

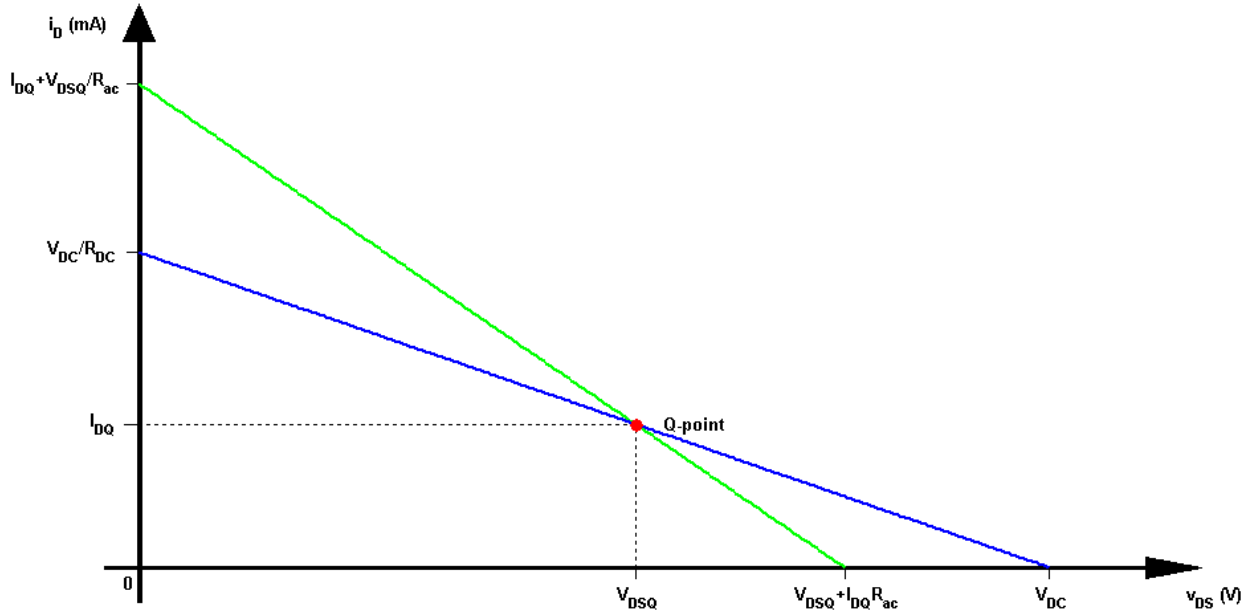


Figure 9.1: AC-DC load lines for FETs.

Once the Q -point is known, **peak** values of the **maximum undistorted** voltage and current **swings** $v_{ds(p)(max)}$ and $i_{d(p)(max)}$ are given by

$$v_{ds(p)(max)} = \min(V_{DSQ}, I_{DQ} R_{ac}) \quad (9.1.5)$$

and

$$i_{d(p)(max)} = \min\left(I_{DQ}, \frac{V_{DSQ}}{R_{ac}}\right) \quad (9.1.6)$$

respectively

9.1.2 Maximum Symmetric Undistorted Swing Design

Once we obtained the desired Q -point in the middle of the AC load line, i.e.,

$$I_{DQ} = \frac{V_{DD}}{R_{DC} + R_{ac}} \quad (9.1.7)$$

then the maximum available undistorted output swings will be obtained as shown in Figure 9.2 below.

 


Figure 9.2: Maximum undistorted swing design for FETs with Q -point in the middle of the AC load line.

9.1.3 Other Amplifier Configurations

We developed and plotted AC-DC load lines for the common-source configuration. Now, let us look at other configurations.

- Common-gate (CG) configuration

1. Obtain R_{ac} from the DG loop.
2. Obtain R_{DC} from the DS loop.
3. Draw the AC-DC load lines i_D vs. v_{DS} as before.

NOTE: You can also draw the AC-DC load lines as i_D vs. v_{DG} by shifting the voltage axis by V_{GSQ} volts to the left as $V_{DGQ} = V_{DSQ} - V_{GSQ}$. Thus, current axis will be drawn at $V_{DG}|_{I_D=0} = -V_{GSQ}$ volts not at 0 V.

- Common-drain (CD) configuration (also known as source-follower)

1. Obtain R_{ac} and R_{DC} from the DS loop as before.
2. Draw the AC-DC load lines i_S vs. v_{DS} where $i_S = i_D$.

- For p -channel FETs, we express the currents in the reverse direction (i.e., having positive current values) and reverse the polarity of the terminal voltages (i.e., having positive voltage values), and then draw the AC-DC load lines, e.g., i_D vs. v_{SD} .

Chapter 10

BJT Small-Signal Analysis

10.1 Purpose of SSAC Analysis

The purpose of small-signal AC (SSAC) analysis is to determine the **three** parameters of an amplifier: **input resistance**, **output resistance** and **gain**. In this course, we are mostly interested in the two-port voltage-gain amplifier model shown in Figure 10.1 below.

 


Figure 10.1: Two-port voltage-gain amplifier model.

- Input resistance R_i is defined by the no-load input voltage of the amplifier divided by the no-load input current to the amplifier, i.e.,

$$R_i = \left. \frac{v_i}{i_i} \right|_{R_L = \infty} \quad (10.1.1)$$

NOTE: Input resistance **cannot** include the source resistance R_s .

- Output resistance R_o is obtained by the test-voltage method, i.e., by dividing the test voltage value with the measured test current value. In the test-voltage method, load is replaced with a test voltage $v_{t\text{est}}$ and the independent power sources (v_s or i_s) are killed, i.e., $v_s = 0$ or $i_s = 0$. Thus, output resistance R_o is given by

$$R_o = \left. \frac{v_{t\text{est}}}{i_{t\text{est}}} \right|_{v_s = 0, R_L = v_{t\text{est}}} \quad (10.1.2)$$

NOTE: Output resistance **cannot** include the load resistance R_L .

- No-load voltage gain A_v (or $A_{V_{NL}}$) is defined by

$$A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} \quad (10.1.3)$$

- When load is connected, the voltage gain will decrease due to the voltage-divider consisting of R_L and R_o . So, voltage gain with load, A_V , is given by

$$A_V = \frac{v_o}{v_i} = \left(\frac{v_o}{A_v v_i} \right) \left(\frac{A_v v_i}{v_i} \right) = \frac{R_L}{R_o + R_L} A_v \quad (10.1.4)$$

- Current gain A_i is defined by the output current versus the input current, i.e.,

$$A_i = \frac{i_o}{i_i} = \frac{v_o/R_L}{v_i/R_i} = \frac{R_i}{R_L} A_V = \frac{R_i}{R_o + R_L} A_v \quad (10.1.5)$$

- Finally, overall voltage gain A_{V_s} is given by

$$A_{V_s} = \frac{v_o}{v_s} = \frac{R_L}{R_o + R_L} A_v \frac{R_i}{R_s + R_i} \quad (10.1.6)$$

10.1.1 BJT SSAC Analysis Steps

1. Draw the SSAC equivalent circuit
 - a) Draw the AC equivalent circuit (signal frequency is infinity, i.e., $f = \infty$)
 - i. Capacitors are short circuit, i.e., $X_C \rightarrow 0$.
 - ii. Kill the DC power sources (i.e., AC value of DC sources is zero).
 - b) Replace BJT with its small-signal equivalent model (e.g., hybrid equivalent model or r_e model).
2. Calculate the three amplifier parameters: R_i , R_o and A_v
 - a) Calculate no-load input resistance, $R_i = \left. \frac{v_i}{i_i} \right|_{R_L=\infty}$.
 - b) Calculate output resistance, R_o .
 - c) Calculate no-load voltage gain, $A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty}$.

10.2 BJT Small-Signal Models

A small-signal model is an equivalent circuit that represents the SSAC characteristics of the transistor. It uses circuit elements that approximate the behavior of the transistor.

Two commonly used models used in SSAC analysis of BJTs are given below:

- hybrid equivalent model
- r_e model

Mostly, we are going to use the **hybrid equivalent model**. But, we are going to introduce and provide results for the r_e model as well.

NOTE: Small-signal equivalent model and its analysis are the same for both *npn* and *pnp* transistors.

10.2.1 Hybrid Equivalent Model

Parameters of the hybrid equivalent circuit provide the entire set on the specification sheet of a BJT and cover all operating conditions. Generalized hybrid equivalent circuit for any transistor configuration is provided in Figure 10.2 below.

 


Figure 10.2: Complete hybrid equivalent circuit.

Here,

- h_i : input resistance
- h_r : reverse transfer voltage ratio (v_i/v_o)
- h_f : forward transfer current ratio (i_o/i_i)
- h_o : output conductance

For a specific configuration, the model parameters modified with the label of the common-mode terminal in their subscript. So, common-emitter and common-base configurations and their hybrid equivalent models are shown in Figure 10.3 and Figure 10.4 below, respectively.

 


Figure 10.3: Common-emitter configuration and its complete hybrid equivalent circuit.

 


Figure 10.4: Common-base configuration and its complete hybrid equivalent circuit.

- For the common-collector configuration, we always use the common-emitter hybrid equivalent model.

10.2.1.1 Simplified Hybrid Equivalent Model

Because h_r is normally a relatively small quantity, its removal is approximated by $h_r \approx 0$ and $h_r v_o = 0$, resulting in the simplified hybrid equivalent circuit shown in Figure 10.5 below. In this course, we are going to use the **simplified hybrid equivalent model**.

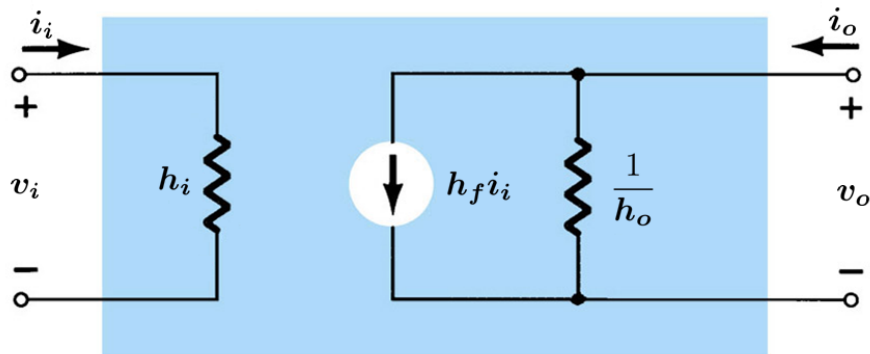


Figure 10.5: Simplified hybrid equivalent circuit.

This circuit, can be further simplified if a value for the parameter h_o or $1/h_o$ is not provided. In that case, we can safely assume that $h_o = 0$ or $1/h_o = \infty$ resulting in the approximate hybrid equivalent circuit shown in Figure 10.6 below.

 


Figure 10.6: Approximate hybrid equivalent circuit.

10.2.1.2 Common-Emitter Hybrid Equivalent Model

Common-emitter simplified hybrid equivalent circuit is shown in Figure 10.7 below.

 


Figure 10.7: Common-emitter simplified hybrid equivalent circuit.

Here, the h -parameters are defined as below

$$h_{ie} = \left. \frac{\partial V_{BE}}{\partial I_B} \right|_{Q\text{-point}} = \frac{\gamma}{I_{BQ}} \quad \dots \text{see diode dynamic resistance in Section 1.3.11} \quad (10.2.7)$$

$$h_{fe} = \left. \frac{\partial I_C}{\partial I_B} \right|_{Q\text{-point}} = \beta_{ac} \quad (10.2.8)$$

$$1/h_{oe} = \left. \frac{\partial V_{CE}}{\partial I_C} \right|_{Q\text{-point}} = \frac{V_A + V_{CEQ}}{I_{CQ}} \quad \dots V_A \text{ is the early voltage and } V_A \gg V_{CEQ} \quad (10.2.9)$$

Typical values of h_{fe} run from 50 to 200, h_{ie} run from $500\ \Omega$ to $7\ \text{k}\Omega$, and $1/h_{oe}$ run from $40\ \text{k}\Omega$ to $100\ \text{k}\Omega$.

Note that, as $I_{CQ} = \beta I_{BQ}$ and $I_{EQ} = (\beta + 1) I_{BQ}$, we can also express h_{ie} in terms of I_{CQ} or I_{EQ} as follows

$$h_{ie} = \frac{\gamma}{I_{BQ}} \quad (10.2.10)$$

$$= h_{fe} \frac{\gamma}{I_{CQ}} \quad (10.2.11)$$

$$= (h_{fe} + 1) \frac{\gamma}{I_{EQ}} \quad (10.2.12)$$

where $\gamma = kT/q$ is the thermal voltage and have fixed values for a given temperature, e.g., $\gamma = 26$ mV at room temperature $T = 300$ K.

10.2.1.3 Common-Emitter r_e Model

Common-emitter r_e model is shown in Figure 10.8 below.

 


Figure 10.8: Common-emitter r_e model.

One-to-one correspondence with the h -parameters are given below,

$$h_{fe} = \beta \quad (10.2.13)$$

$$h_{ie} = (\beta + 1) r_e \cong \beta r_e \quad (10.2.14)$$

$$1/h_{oe} = r_o. \quad (10.2.15)$$

Thus, $\beta = h_{fe}$, $\beta r_e = h_{ie}$ and $r_o = 1/h_{oe}$.

10.2.1.4 Common-Base Hybrid Equivalent Model

Common-base simplified hybrid equivalent circuit is shown in Figure 10.9 below.

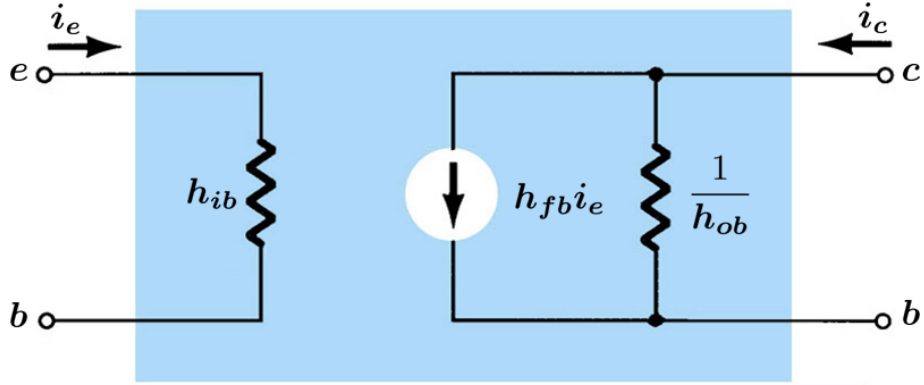


Figure 10.9: Common-base simplified hybrid equivalent circuit.

Here, the h -parameters are defined as below,

$$h_{ib} = \left. \frac{\partial V_{BE}}{\partial I_E} \right|_{Q\text{-point}} = \frac{\gamma}{I_{EQ}} \quad \dots \text{see diode dynamic resistance in Section 1.3.11} \quad (10.2.16)$$

$$h_{fb} = - \left. \frac{\partial I_C}{\partial I_E} \right|_{Q\text{-point}} = -\alpha_{ac} \cong -1 \quad (10.2.17)$$

$$1/h_{ob} = \left. \frac{\partial V_{CB}}{\partial I_C} \right|_{Q\text{-point}} \approx \infty \quad (10.2.18)$$

Typically, $h_{fb} = -1$, and h_{ib} run from 5Ω to 50Ω , and $1/h_{ob}$ is in the megohm range. Thus, $1/h_{ob} \gg 1/h_{oe}$.

Note that, the relationship between h_{ib} and h_{ie} is given below

$$h_{ie} = (h_{fe} + 1) h_{ib} \quad (10.2.19)$$

$$\text{or } h_{ib} = \frac{h_{ie}}{h_{fe} + 1}.$$

10.2.1.5 Common-Base r_e Model

Common-base r_e model is shown in Figure 10.10 below.

 


Figure 10.10: Common-base r_e model.

One-to-one correspondence with the h -parameters are given below

$$h_{fb} = -\alpha \quad (10.2.20)$$

$$h_{ib} = r_e \quad (10.2.21)$$

$$1/h_{ob} = r_o. \quad (10.2.22)$$

Thus, $\alpha = -h_{fb} \cong 1$, $r_e = h_{ib}$ and $r_o = 1/h_{ob} \cong \infty$. Note that, minus sign is due to the direction of the current source.

10.2.1.6 Phase Relationship

The phase relationship between input and output depends on the amplifier configuration circuit as listed below.

- Common-Emitter: 180 degrees
- Common-Base: 0 degrees
- Common-Collector: 0 degrees (Emitter-Follower)

10.3 Common-Emitter Fixed-Bias Configuration

Common-emitter fixed-bias configuration is given in Figure 10.11 below

 


Figure 10.11: Common-emitter fixed-bias configuration.

Let us start SSAC analysis by drawing the AC equivalent circuit as shown in Figure 10.12 below

 


Figure 10.12: AC equivalent circuit of the fixed-bias circuit in Figure 10.11.

Then, we are going to replace BJT with its common-emitter hybrid equivalent model as shown in Figure 10.13 below

 


Figure 10.13: Small-signal equivalent circuit of the fixed-bias circuit in Figure 10.11.

- Obtain h_{fe} and $1/h_{oe}$ from the specification sheet of the transistor or by testing the transistor using a curve tracer. Calculate h_{ie} using the DC analysis values as $h_{ie} = \frac{26 \text{ mV}}{I_{BQ}} = h_{fe} \frac{26 \text{ mV}}{I_{CQ}}$.

10.3.1 Input Resistance

Input resistance R_i is given as

$$R_i = \left. \frac{v_i}{i_i} \right|_{R_L=\infty} = R_B || h_{ie} \quad (10.3.23)$$

- If $R_B \geq 10h_{ie}$, then R_i simplifies to $R_i = h_{ie}$.
- Input resistance R_i according to the r_e model is given by

$$R_i = R_B || \beta r_e \quad (10.3.24)$$

10.3.2 Voltage Gain

No-load voltage gain A_v is given by

$$\begin{aligned} A_v &= \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = \left(\frac{v_o}{h_{fe} i_b} \right) \left(\frac{h_{fe} i_b}{i_b} \right) \left(\frac{i_b}{v_i} \right) \\ &= (-R_C || 1/h_{oe}) (h_{fe}) \left(\frac{1}{h_{ie}} \right) \\ &= -\frac{h_{fe} (R_C || 1/h_{oe})}{h_{ie}} \end{aligned}$$

As a result, A_v is given by

$$A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = -\frac{h_{fe} (R_C || 1/h_{oe})}{h_{ie}} \quad (10.3.25)$$

- No-load voltage gain A_v according to the r_e model is given by

$$A_v = -\frac{R_C || r_o}{r_e} \quad (10.3.26)$$

- If $1/h_{oe} \geq 10R_C$, no-load voltage gain A_v reduces to

$$A_v = -\frac{h_{fe} R_C}{h_{ie}} \quad \dots r_e \text{ model: } A_v = -\frac{R_C}{r_e} \quad (10.3.27)$$

- For the circuit in Figure 10.13, we can obtain the current gain A_i as follows

$$\begin{aligned} A_i &= \frac{i_o}{i_i} = \frac{v_o/R_C}{v_i/R_i} = \frac{R_i}{R_C} \frac{v_o}{v_i} \\ &= \frac{R_i}{R_C} A_v \end{aligned} \quad (10.3.28)$$

- If $1/h_{oe} \geq 10R_C$ and $R_B \geq 10h_{ie}$, current gain A_i reduces to

$$A_i = -h_{fe} \quad \dots r_e \text{ model: } A_i = -\beta \quad (10.3.29)$$

10.3.3 Output Resistance

 


Figure 10.14: Test voltage circuit of Figure 10.13 in order to calculate the output resistance R_o .

Output resistance, i.e., Thévenin equivalent resistance, R_o is calculated using the test voltage circuit in Figure 10.14 above. Note that in the circuit $i_b = 0$, so $h_{fe}i_b = 0$ as well.

$$R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}} = R_C || 1/h_{oe} \quad (10.3.30)$$

- If $1/h_{oe} \geq 10R_C$, then R_o simplifies to $R_o = R_C$.
- Output resistance R_o according to the r_e model is given by

$$R_o = R_C || r_o \quad (10.3.31)$$

10.3.4 Phase Relationship

 


Figure 10.15: Demonstrating the 180° phase shift between input and output waveforms.

- The phase relationship between input and output is 180 degrees as shown in Figure 10.15 above.
- The negative sign used in the voltage gain formulas indicates the inversion.

10.4 Common-Emitter Voltage-Divider Bias Configuration

Common-emitter voltage-divider bias configuration is given in Figure 10.16 below

 


Figure 10.16: Common-emitter voltage-divider bias configuration.

Corresponding SSAC equivalent circuit is shown in Figure 10.17 below

 


Figure 10.17: Small-signal equivalent circuit of the voltage-divider bias circuit in Figure 10.16.

10.4.1 Input Resistance

Input resistance R_i is given as

$$R_i = \left. \frac{v_i}{i_i} \right|_{R_L=\infty} = R_1 || R_2 || h_{ie} \quad (10.4.32)$$

- Input resistance R_i according to the r_e model is given by

$$R_i = R_1 || R_2 || \beta r_e \quad (10.4.33)$$

10.4.2 Voltage Gain

No-load voltage gain A_v is given by

$$\begin{aligned} A_v &= \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = \left(\frac{v_o}{h_{fe}i_b} \right) \left(\frac{h_{fe}i_b}{i_b} \right) \left(\frac{i_b}{v_i} \right) \\ &= (-R_C || 1/h_{oe}) (h_{fe}) \left(\frac{1}{h_{ie}} \right) \\ &= -\frac{h_{fe}(R_C || 1/h_{oe})}{h_{ie}} \end{aligned}$$

As a result, A_v is given by

$$\boxed{A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = -\frac{h_{fe}(R_C || 1/h_{oe})}{h_{ie}}} \quad (10.4.34)$$

- No-load voltage gain A_v according to the r_e model is given by

$$A_v = -\frac{R_C || r_o}{r_e} \quad (10.4.35)$$

- If $1/h_{oe} \geq 10R_C$, no-load voltage gain A_v reduces to

$$A_v = -\frac{h_{fe}R_C}{h_{ie}} \quad \dots r_e \text{ model: } A_v = -\frac{R_C}{r_e} \quad (10.4.36)$$

- For the circuit in Figure 10.17, we can obtain the current gain A_i as follows

$$\begin{aligned} A_i &= \frac{i_o}{i_i} = \frac{v_o/R_C}{v_i/R_i} = \frac{R_i}{R_C} \frac{v_o}{v_i} \\ &= \frac{R_i}{R_C} A_v \end{aligned} \quad (10.4.37)$$

- If $1/h_{oe} \geq 10$, and given $R' = R_1 || R_2$, current gain A_i reduces to

$$A_i = -h_{fe} \frac{R'}{R' + h_{ie}} \quad \dots r_e \text{ model: } A_i = -\frac{R'}{R'/\beta + r_e} \quad (10.4.38)$$

10.4.3 Output Resistance

 


Figure 10.18: Test voltage circuit of Figure 10.17 in order to calculate the output resistance R_o .

Output resistance, i.e., Thévenin equivalent resistance, R_o is calculated using the test voltage circuit in Figure 10.18 above. Note that in the circuit $i_b = 0$, so $h_{fe}i_b = 0$ as well.

$$R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}} = R_C || 1/h_{oe} \quad (10.4.39)$$

- If $1/h_{oe} \geq 10R_C$, then R_o simplifies to $R_o = R_C$.
- Output resistance R_o according to the r_e model is given by

$$R_o = R_C || r_o \quad (10.4.40)$$

10.4.4 Phase Relationship

- Phase relationship between input and output of a common-emitter amplifier configuration is always 180 degrees. This is independent of the type of the bias-configuration.

10.5 Common-Emitter Unbypassed-Emitter Bias Configuration

Common-emitter unbypassed-emitter bias configuration is given in Figure 10.19 below

 


Figure 10.19: Common-emitter unbypassed-emitter bias configuration.

Corresponding SSAC equivalent circuit is shown in Figure 10.20 below

 


Figure 10.20: Small-signal equivalent circuit of the unbypassed-emitter bias circuit in Figure 10.19.

- When R_E is not bypassed, we normally assume $1/h_{oe} = \infty$ in order to reduce the calculation complexity. Because of the feedback, even $1/h_{oe} \neq \infty$ the results do not really change at all.

10.5.1 Input Resistance

Input resistance R_i is given as

$$\begin{aligned}
 R_i = \left. \frac{v_i}{i_i} \right|_{R_L=\infty} &= R_B \parallel R_b & \dots R_b &= h_{ie} + (h_{fe} + 1) R_E \\
 &= R_B \parallel [h_{ie} + (h_{fe} + 1) R_E]
 \end{aligned}$$

As a result, R_i is given by

$$\boxed{R_i = \left. \frac{v_i}{i_i} \right|_{R_L=\infty} = R_B \parallel [h_{ie} + (h_{fe} + 1) R_E]} \quad (10.5.41)$$

- Input resistance R_i according to the r_e model is given by

$$R_i = R_B \parallel (\beta + 1) (r_e + R_E) \cong R_B \parallel \beta (r_e + R_E) \quad (10.5.42)$$

10.5.2 Voltage Gain

No-load voltage gain A_v is given by

$$\begin{aligned}
 A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} &= \left(\frac{v_o}{h_{fe} i_b} \right) \left(\frac{h_{fe} i_b}{i_b} \right) \left(\frac{i_b}{v_i} \right) \\
 &= (-R_C) (h_{fe}) \left(\frac{1}{R_b} \right) \\
 &= -\frac{h_{fe} R_C}{h_{ie} + (h_{fe} + 1) R_E}
 \end{aligned}$$

As a result, A_v is given by

$$A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = -\frac{h_{fe}R_C}{h_{ie} + (h_{fe} + 1)R_E} \quad (10.5.43)$$

- No-load voltage gain A_v according to the r_e model is given by

$$A_v = -\frac{R_C}{r_e + R_E} \quad (10.5.44)$$

- If $(h_{fe} + 1)R_E \geq 10h_{ie}$, no-load voltage gain A_v reduces to

$$A_v = -\frac{R_C}{R_E} \quad \dots r_e \text{ model: } A_v = -\frac{R_C}{R_E} \quad (10.5.45)$$

- For the circuit in Figure 10.20, we can obtain the current gain A_i as follows

$$\begin{aligned} A_i &= \frac{i_o}{i_i} = \frac{v_o/R_C}{v_i/R_i} = \frac{R_i}{R_C} \frac{v_o}{v_i} \\ &= \frac{R_i}{R_C} A_v \end{aligned} \quad (10.5.46)$$

- Resultant current gain A_i is given by

$$A_i = -h_{fe} \frac{R_B}{R_B + R_b} \quad \dots r_e \text{ model: } A_i = -\frac{R_B}{R_B/\beta + r_e + R_E} \quad (10.5.47)$$

10.5.3 Output Resistance

 


Figure 10.21: Test voltage circuit of Figure 10.20 in order to calculate the output resistance R_o .

Output resistance, i.e., Thévenin equivalent resistance, R_o is calculated using the test voltage circuit in Figure 10.21 above. Note that in the circuit $i_b = 0$, so $h_{fe}i_b = 0$ as well.

$$R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}} = R_C \quad (10.5.48)$$

- Output resistance R_o according to the r_e **model** is given by

$$R_o = R_C \quad (10.5.49)$$

10.5.4 Phase Relationship

- Phase relationship between input and output of a common-emitter amplifier configuration is always 180 degrees. This is independent of the type of the bias-configuration.

10.6 Emitter-Follower Configuration

Emitter-follower (common-collector) configuration is given in Figure 10.22 below

 


Figure 10.22: Emitter-follower configuration.

Corresponding SSAC equivalent circuit is shown in Figure 10.23 below

 


Figure 10.23: Small-signal equivalent circuit of the emitter-follower circuit in Figure 10.22.

- When R_E is not bypassed, we normally assume $1/h_{oe} = \infty$ in order to reduce the calculation complexity.

10.6.1 Input Resistance

Input resistance R_i is given as

$$\begin{aligned} R_i = \left. \frac{v_i}{i_i} \right|_{R_L=\infty} &= R_B \parallel R_b & \dots R_b = h_{ie} + (h_{fe} + 1) R_E \\ &= R_B \parallel [h_{ie} + (h_{fe} + 1) R_E] \end{aligned}$$

As a result, R_i is given by

$$\boxed{R_i = \left. \frac{v_i}{i_i} \right|_{R_L=\infty} = R_B \parallel [h_{ie} + (h_{fe} + 1) R_E]} \quad (10.6.50)$$

- Input resistance R_i according to the r_e model is given by

$$R_i = R_B \parallel (\beta + 1) (r_e + R_E) \cong R_B \parallel \beta (r_e + R_E) \quad (10.6.51)$$

10.6.2 Voltage Gain

No-load voltage gain A_v is given by

$$\begin{aligned} A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} &= \left(\frac{v_o}{i_b} \right) \left(\frac{i_b}{v_i} \right) \\ &= [(h_{fe} + 1) R_E] \left(\frac{1}{R_b} \right) & \dots R_b = h_{ie} + (h_{fe} + 1) R_E \\ &= \frac{(h_{fe} + 1) R_E}{h_{ie} + (h_{fe} + 1) R_E} \cong 1 \end{aligned}$$

As a result, A_v is given by

$$A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = \frac{(h_{fe} + 1) R_E}{h_{ie} + (h_{fe} + 1) R_E} \cong 1 \quad (10.6.52)$$

- No-load voltage gain A_v according to the r_e model is given by

$$A_v = \frac{R_E}{r_e + R_E} \cong 1 \quad (10.6.53)$$

- For the circuit in Figure 10.23, we can obtain the current gain A_i as follows

$$\begin{aligned} A_i &= \frac{i_o}{i_i} = \frac{v_o/R_E}{v_i/R_i} = \frac{R_i v_o}{R_E v_i} \\ &= \frac{R_i}{R_E} A_v \end{aligned} \quad (10.6.54)$$

- Resultant current gain A_i is given by,

$$A_i = (h_{fe} + 1) \frac{R_B}{R_B + R_b} \quad \dots r_e \text{ model: } A_i = \frac{R_B}{R_B/(\beta + 1) + r_e + R_E} \quad (10.6.55)$$

10.6.3 Output Resistance

 


Figure 10.24: Test voltage circuit of Figure 10.23 in order to calculate the output resistance R_o .

Output resistance, i.e., Thévenin equivalent resistance, R_o is calculated using the test voltage circuit in Figure 10.24 above.

$$R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}} = R_E \parallel \frac{h_{ie}}{h_{fe} + 1} \quad (10.6.56)$$

- Output resistance R_o according to the r_e **model** is given by

$$R_o = R_E || r_e \quad (10.6.57)$$

- If $1/h_{oe} \neq \infty$, then replace R_E with $(R_E || 1/h_{oe})$ in R_i , A_v and R_o calculations.
- If a voltage source with source resistance R_s is connected to the input, replace h_{ie} with $(h_{ie} + R_B || R_s)$ in R_o calculations.

10.6.4 Phase Relationship

- Emitter-follower (common-collector) configuration has **no phase shift** between input and output.

10.7 Common-Emitter Collector Feedback Configuration

Common-emitter collector feedback bias configuration is given in Figure 10.25 below

 


Figure 10.25: Common-emitter collector feedback bias configuration.

Corresponding SSAC equivalent circuit is shown in Figure 10.26 below

 


Figure 10.26: Small-signal equivalent circuit of the collector feedback bias circuit in Figure 10.25.

10.7.1 Input Resistance

Input resistance R_i is given as

$$R_i = \left. \frac{v_i}{i_i} \right|_{R_L=\infty} = \frac{h_{ie}}{1 + \frac{h_{ie} + h_{fe}R_C}{R_F + R_C}} \quad \dots i_f = -\frac{h_{ie} + h_{fe}R_C}{R_F + R_C} i_b$$

$$\cong \frac{h_{ie}}{1 + \frac{h_{fe}R_C}{R_F + R_C}} \quad \dots h_{fe}R_C \gg h_{ie}$$

As a result, R_i is given by

$$R_i = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} \cong \frac{h_{ie}}{1 + \frac{h_{fe}R_C}{R_F + R_C}} \quad (10.7.58)$$

- Input resistance R_i according to the r_e model is given by

$$R_i \cong \frac{\beta r_e}{1 + \frac{\beta R_C}{R_F + R_C}} \quad (10.7.59)$$

10.7.2 Voltage Gain

No-load voltage gain A_v is given by

$$A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = \left(\frac{h_{fe}R_F - h_{ie}}{R_F + R_C} \right) \left(\frac{-R_C}{h_{ie}} \right) \quad \dots i_f = -\frac{h_{ie} + h_{fe}R_C}{R_F + R_C} i_b$$

$$\cong \left(\frac{h_{fe}R_F}{R_F + R_C} \right) \left(\frac{-R_C}{h_{ie}} \right) \quad \dots h_{fe}R_F \gg h_{ie}$$

$$\approx -\frac{h_{fe}R_C}{h_{ie}} \quad \dots R_F \gg R_C$$

As a result, A_v is given by

$$A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} \approx -\frac{h_{fe}R_C}{h_{ie}} \quad (10.7.60)$$

- No-load voltage gain A_v according to the r_e model is given by

$$A_v \approx -\frac{R_C}{r_e} \quad (10.7.61)$$

- For the circuit in Figure 10.26, we can obtain the current gain A_i as follows

$$A_i = \frac{i_o}{i_i} = \frac{v_o/R_C}{v_i/R_i} = \frac{R_i}{R_C} \frac{v_o}{v_i}$$

$$= \frac{R_i}{R_C} A_v \quad (10.7.62)$$

- Resultant current gain A_i is given by,

$$A_i \cong -\frac{h_{fe}(R_F + R_C)}{R_F + (h_{fe} + 1)R_C} \quad \dots r_e \text{ model: } A_i = -\frac{R_F + R_C}{R_F/\beta + R_C} \quad (10.7.63)$$

10.7.3 Output Resistance

 


Figure 10.27: Test voltage circuit of Figure 10.26 in order to calculate the output resistance R_o .

Output resistance, i.e., Thévenin equivalent resistance, R_o is calculated using the test voltage circuit in Figure 10.27 above. Note that in the circuit $i_b = 0$, so $h_{fe}i_b = 0$ as well.

$$R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}} = R_C || R_F \quad (10.7.64)$$

- Output resistance R_o according to the r_e model is given by

$$R_o = R_C || R_F \quad (10.7.65)$$

- If $1/h_{oe} \neq \infty$, then replace R_C with $(R_C || 1/h_{oe})$ in R_i , A_v and R_o calculations.
- If a voltage source with source resistance R_s is connected to the input, replace R_F with $[R_F(R_s + h_{ie}) / (h_{fe}R_s + h_{ie})]$ in R_o calculations.

10.7.4 Phase Relationship

- Phase relationship between input and output of a common-emitter amplifier configuration is always 180 degrees. This is independent of the type of the bias-configuration.

10.8 Common-Base Configuration

Common-base configuration is given in Figure 10.28 below

 


Figure 10.28: Common-base configuration.

Corresponding SSAC equivalent circuit is shown in Figure 10.29 below

 


Figure 10.29: Small-signal equivalent circuit of the common-base circuit in Figure 10.28.

- Here, $h_{ib} = \frac{h_{ie}}{h_{fe} + 1} = \frac{26 \text{ mV}}{I_{EQ}}$ and $h_{fb} = -\alpha_{ac} = -1$.

10.8.1 Input Resistance

Input resistance R_i is given as

$$R_i = \left. \frac{v_i}{i_i} \right|_{R_L = \infty} = R_E || h_{ib} \quad (10.8.66)$$

- If $R_E \geq 10h_{ib}$, then R_i simplifies to $R_i = h_{ib}$.
- Input resistance R_i according to the **r_e model** is given by

$$R_i = R_E || r_e \quad (10.8.67)$$

10.8.2 Voltage Gain

No-load voltage gain A_v is given by

$$\begin{aligned} A_v &= \left. \frac{v_o}{v_i} \right|_{R_L = \infty} = \left(\frac{v_o}{h_{fb} i_e} \right) \left(\frac{h_{fb} i_e}{i_e} \right) \left(\frac{i_e}{v_i} \right) \\ &= (-R_C) (h_{fb}) \left(\frac{1}{h_{ib}} \right) \\ &= \frac{R_C}{h_{ib}} \quad \dots h_{fb} = -1 \end{aligned}$$

As a result, A_v is given by

$$A_v = \left. \frac{v_o}{v_i} \right|_{R_L = \infty} = \frac{R_C}{h_{ib}} \quad (10.8.68)$$

- No-load voltage gain A_v according to the **r_e model** is given by

$$A_v = \frac{R_C}{r_e} \quad (10.8.69)$$

- For the circuit in Figure 10.29, we can obtain the current gain A_i as follows

$$\begin{aligned} A_i &= \frac{i_o}{i_i} = \frac{v_o/R_C}{v_i/R_i} = \frac{R_i}{R_C} \frac{v_o}{v_i} \\ &= \frac{R_i}{R_C} A_v \end{aligned} \quad (10.8.70)$$

- Resultant current gain A_i is given by,

$$A_i = \frac{R_E || h_{ib}}{h_{ib}} \approx 1 \quad \dots r_e \text{ model: } A_i = \frac{R_E || r_e}{r_e} \approx 1 \quad (10.8.71)$$

10.8.3 Output Resistance

 


Figure 10.30: Test voltage circuit of Figure 10.29 in order to calculate the output resistance R_o .

Output resistance, i.e., Thévenin equivalent resistance, R_o is calculated using the test voltage circuit in Figure 10.30 above. Note that in the circuit $i_e = 0$, so $h_{fb}i_e = 0$ as well.

$$\boxed{R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}}} = R_C \quad (10.8.72)$$

- Output resistance R_o according to the r_e **model** is given by

$$R_o = R_C \quad (10.8.73)$$

- If $1/h_{ob} \neq \infty$, then replace R_C with $(R_C || 1/h_{ob})$ in R_i , A_v and R_o calculations.

10.8.4 Phase Relationship

- A common-base amplifier configuration has **no phase shift** between input and output

Example 10.1: Consider the common-base BJT amplifier in the figure below.

- a) Perform DC analysis and find the Q -point.
- b) Evaluate the overall voltage gain A_{V_s} and the current gain A_i .
- c) Sketch v_o on the AC+DC load line graph when
 - i. $v_s = 100 \sin(\omega t)$ mV,
 - ii. $v_s = 900 \sin(\omega t)$ mV.

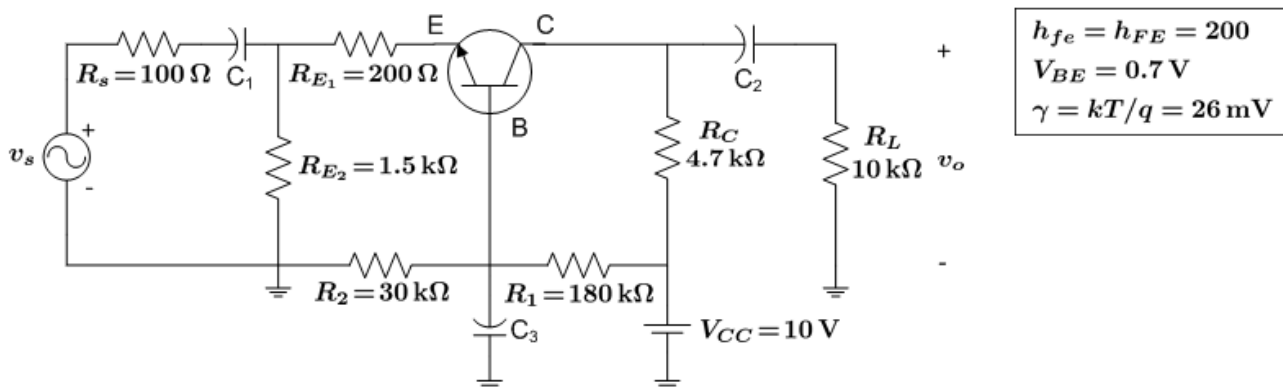


Figure 10.31: BJT amplifier circuit for Example 10.1.

Solution: a) Let us first draw the DC equivalent circuit first as shown in Figure 10.32 below,

 


Figure 10.32: DC equivalent circuit of Figure 10.31: (a) as it is (b) Thévenin applied.

Here, $R_E = R_{E_1} + R_{E_2} = 0.2k + 1.5k = 1.7k\Omega$.

Now, let us calculate V_{BB} , R_{BB} , I_{CQ} , V_{CEQ} and V_{CBQ}

$$V_{BB} = \left(\frac{30k}{30k + 180k} \right) (10) = 1.43 \text{ V},$$

$$R_{BB} = 30k || 180k = 25.71 \text{ k}\Omega,$$

$$I_{CQ} \cong I_{EQ} = \frac{1.43 - 0.7}{25.71k/201 + 1.7k} = 0.4 \text{ mA},$$

$$V_{CEQ} = 10 - (0.4m)(4.7k + 1.7k) = 7.44 \text{ V},$$

$$V_{CBQ} = 7.44 - 0.7 = 6.74 \text{ V}.$$

b) In order to calculate the voltage gain, we need to draw the common-base SSAC equivalent circuit. As it is not given $1/h_{ob} = \infty$. Let us now calculate h_{ib} as

$$h_{ib} = \frac{26m}{0.4m} = 65 \Omega.$$

So, the small-signal equivalent circuit is given in Figure 10.32 below

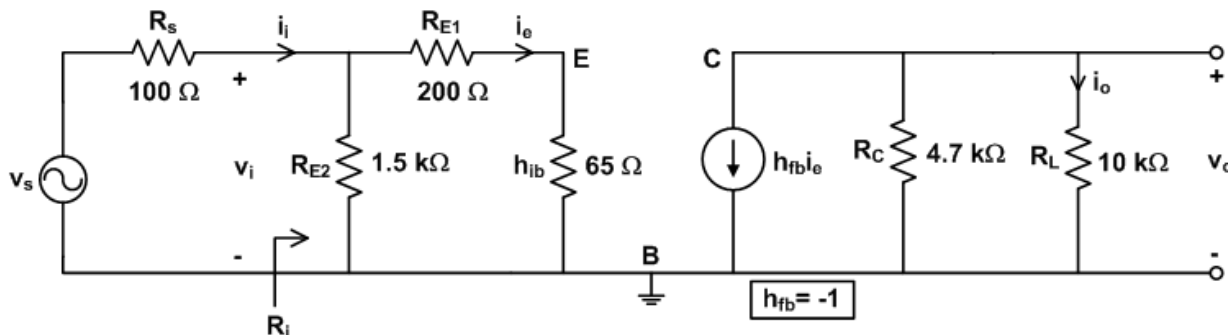


Figure 10.33: Small-signal equivalent circuit of Figure 10.31.

Now, let us calculate input resistance R_i and voltage gain with load A_V as follows

$$R_i = R_{E2} || (R_{E1} + h_{ib}) = 1.5k || (200 + 65) \cong 225 \Omega$$

$$A_V = \frac{v_o}{v_i} = \left(\frac{v_o}{h_{fb} i_e} \right) \left(\frac{h_{fb} i_e}{i_e} \right) \left(\frac{i_e}{v_i} \right)$$

$$= (-R_C || R_L) (h_{fb}) \left(\frac{1}{R_{E1} + h_{ib}} \right) = \frac{R_C || R_L}{R_{E1} + h_{ib}}$$

$$= \frac{4.7k || 10k}{200 + 65} = \frac{3.2k}{0.265k} = 12.08.$$

Thus, overall voltage gain A_{V_s} and current gain A_i are given by

$$A_{V_s} = \frac{v_o}{v_s} = \left(\frac{v_o}{v_i} \right) \left(\frac{v_i}{v_s} \right) = A_V \frac{R_i}{R_s + R_i} = (12.08) \left(\frac{225}{100 + 225} \right)$$

$$= 8.36,$$

$$A_i = \frac{i_o}{i_i} = \frac{v_o/R_L}{v_i/R_i} = A_V \frac{R_i}{R_L} = (12.08) \left(\frac{0.225k}{10k} \right)$$

$$= 0.27.$$

c) Let us write down the AC load line equation for this common-base amplifier, noting that $v_o = v_{cb} = -i_c(R_C || R_L) = -i_c R_{ac}$ and $v_{cb} = v_{ce} - v_{be} = v_{ce} - \frac{h_{ib}}{R_{E1} + h_{ib}} v_i \approx v_{ce}$)

$$\begin{aligned} v_{CB} &= -i_c R_{ac} + V_{CBQ} + I_{CQ} R_{ac} & \dots V_{CBQ} &= V_{CEQ} - V_{BEQ} \\ v_{CE} - V_{BEQ} &= -i_c R_{ac} + V_{CEQ} - V_{BEQ} + I_{CQ} R_{ac} & \dots v_{CB} &\approx v_{CE} - V_{BEQ} \\ v_{CE} &= -i_c R_{ac} + V_{CEQ} + I_{CQ} R_{ac} \end{aligned}$$

So, we calculate R_{ac} from the C-B loop and R_{DC} from the C-E loop as follows

$$\begin{aligned} R_{ac} &= R_C || R_L = 4.7k || 10k = 3.2 \text{ k}\Omega, \\ R_{DC} &= R_C + R_E = 4.7k + 1.7k = 6.4 \text{ k}\Omega. \end{aligned}$$

Note that, maximum available undistorted swing amplitude is

$$\min(V_{CEQ}, I_{CQ} R_{ac}) = \min(7.44, (0.4 \text{ mA})(3.2 \text{ k}\Omega)) = \min(7.44, 1.28) = 1.28 \text{ V}.$$

Thus, as $A_{Vs} = 8.36$, maximum input source amplitude which gives an undistorted output is

$$\max(v_{s(p)}) = 1.28 / 8.36 = 153.1 \text{ mV}.$$

If the input source amplitude exceeds this value, we will observe distortion at the output.

i. For $v_s = 100 \sin(\omega t)$ mV, we are going to observe an undistorted sinusoidal output with an amplitude of 0.836 V around $V_{CBQ} = 6.74$ V as shown in Figure 10.34 below.

 


Figure 10.34: AC-DC load-lines for Example 10.1 with input $v_s = 100 \sin(\omega t)$ mV.

ii. For $v_s = 900 \sin(\omega t)$ mV, we are going to observe a distorted output as shown in Figure 10.35 below.

 


Figure 10.35: AC-DC load-lines for Example 10.1 with input $v_s = 900 \sin(\omega t)$ mV.

Chapter 11

FET Small-Signal Analysis

11.0.1 FET SSAC Analysis Steps

1. Draw the SSAC equivalent circuit
 - a) Draw the AC equivalent circuit (signal frequency is infinity, i.e., $f = \infty$)
 - i. Capacitors are short circuit, i.e., $X_C \rightarrow 0$.
 - ii. Kill the DC power sources (i.e., AC value of DC sources is zero).
 - b) Replace FET with its small-signal equivalent model.
2. Calculate the three amplifier parameters: R_i , R_o and A_v
 - a) Calculate no-load input resistance, $R_i = \left. \frac{v_i}{i_i} \right|_{R_L = \infty}$.
 - b) Calculate output resistance, R_o .
 - c) Calculate no-load voltage gain, $A_v = \left. \frac{v_o}{v_i} \right|_{R_L = \infty}$.

11.1 FET Small-Signal Model

Small-signal equivalent model for a FET transistor is provided in Figure 11.1 below. This model and its analysis is the same for all FET types, i.e., JFET, DMOSFET, EMOSFET, n -channel and p -channel.

 


Figure 11.1: FET small-signal equivalent circuit.

Here,

- $g_m = g_{fs} = y_{fs} = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{Q\text{-point}}$ is the forward transfer conductance,
- $r_{ds} = \frac{1}{g_{os}} = \frac{1}{y_{os}} = \left. \frac{\partial V_{DS}}{\partial I_D} \right|_{Q\text{-point}}$ is the output resistance.

Forward transfer conductance g_m is mostly called as the **transconductance** parameter.

When $r_{ds} \neq \infty$, we can also use the voltage-controlled voltage source model (via Norton-to-Thévenin transformation, a.k.a source transformation) as shown in Figure 11.2 below. We mostly use this model for the common-gate and unbypassed self-bias configurations.

 


Figure 11.2: FET small-signal equivalent circuit with the voltage-controlled voltage source.

Here $\mu = g_m r_{ds}$ is the forward transfer-voltage gain.

- Typical values of g_m run from 1 mS to 5 mS,
- Typical values of r_{ds} run from 20 k Ω to 100 k Ω ,
- Consequently, typical values of μ run from 20 to 500.

11.1.0.1 Transconductance Parameter (g_m)

Transconductance parameter g_m is given by

$$g_m = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{Q\text{-point}} \cong \left. \frac{\Delta I_D}{\Delta V_{GS}} \right|_{Q\text{-point}} \quad (11.1.1)$$

In other words, g_m is the slope of the characteristics at the point of operation as shown in Figure 11.3 below.

 


Figure 11.3: Graphical definition of the transconductance g_m .

- Let us derive g_m for the JFET equation, $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$

$$\begin{aligned} g_m &= \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{Q\text{-point}} = \left. \frac{2I_{DSS}}{|V_P|} \left(1 - \frac{V_{GS}}{V_P}\right) \right|_{Q\text{-point}} \\ &= \frac{2I_{DSS}}{|V_P|} \left(1 - \frac{V_{GSQ}}{V_P}\right) \end{aligned} \quad (11.1.2)$$

$$\begin{aligned} &= \frac{2I_{DSS}}{|V_P|} \sqrt{\frac{I_{DQ}}{I_{DSS}}} \quad \dots I_{DQ} = I_{DSS} \left(1 - \frac{V_{GSQ}}{V_P}\right)^2 \\ &= g_{m0} \sqrt{\frac{I_{DQ}}{I_{DSS}}} \quad \dots g_{m0} = \frac{2I_{DSS}}{|V_P|} \end{aligned} \quad (11.1.3)$$

- Let us derive g_m for the MOSFET equation, $I_D = k (V_{GS} - V_{GS(Th)})^2$

$$\begin{aligned} g_m &= \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{Q\text{-point}} = 2k (V_{GS} - V_{GS(Th)}) \Big|_{Q\text{-point}} \\ &= 2k (V_{GSQ} - V_{GS(Th)}) \end{aligned} \quad (11.1.4)$$

$$= 2\sqrt{k} \sqrt{I_{DQ}} \quad \dots I_{DQ} = k (V_{GS} - V_{GS(Th)})^2 \quad (11.1.5)$$

11.1.0.2 Phase Relationship

The phase relationship between input and output depends on the amplifier configuration circuit as listed below.

- Common-Source: 180 degrees
- Common-Gate: 0 degrees
- Common-Drain: 0 degrees (Source-Follower)

11.2 Common-Source Fixed-Bias Configuration

Common-source fixed-bias configuration is given in Figure 11.4 below

 


Figure 11.4: Common-source fixed-bias configuration.

Corresponding SSAC equivalent circuit is shown in Figure 11.5 below

 


Figure 11.5: Small-signal equivalent circuit of the fixed-bias circuit in Figure 11.4.

11.2.1 Input Resistance

Input resistance R_i is given as

$$R_i = \left. \frac{v_i}{i_i} \right|_{R_L=\infty} = R_G \quad (11.2.6)$$

11.2.2 Voltage Gain

No-load voltage gain A_v is given by

$$\begin{aligned} A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} &= \left(\frac{v_o}{g_m v_{gs}} \right) \left(\frac{g_m v_{gs}}{v_{gs}} \right) \left(\frac{v_{gs}}{v_i} \right) \\ &= (-R_D || r_{ds}) (g_m) (1) \\ &= -g_m (R_D || r_{ds}) \end{aligned}$$

As a result, A_v is given by

$$A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = -g_m (R_D || r_{ds}) \quad (11.2.7)$$

- If $r_{ds} \geq 10R_D$, voltage gain A_v reduces to

$$A_v = -g_m R_D \quad (11.2.8)$$

- For the circuit in Figure 11.5, we can obtain the current gain A_i as follows

$$\begin{aligned} A_i = \frac{i_o}{i_i} &= \frac{v_o/R_D}{v_i/R_i} = \frac{R_i}{R_D} \frac{v_o}{v_i} \\ &= \frac{R_i}{R_D} A_v \end{aligned} \quad (11.2.9)$$

- If $r_{ds} \geq 10R_D$, current gain A_i reduces to

$$A_i = -g_m R_G \quad (11.2.10)$$

11.2.3 Output Resistance

 


Figure 11.6: Test voltage circuit of Figure 11.5 in order to calculate the output resistance R_o .

Output resistance, i.e., Thévenin equivalent resistance, R_o is calculated using the test voltage circuit in Figure 11.6 above. Note that in the circuit $v_{gs} = 0$, so $g_m v_{gs} = 0$ as well.

$$R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}} = R_D || r_{ds} \quad (11.2.11)$$

- If $r_{ds} \geq 10R_D$, then R_o simplifies to $R_o = R_D$.

11.3 Common-Source Self-Bias Configuration

Common-source self-bias configuration is given in Figure 11.7 below

 


Figure 11.7: Common-source self-bias configuration.

Corresponding SSAC equivalent circuit is shown in Figure 11.8 below

 


Figure 11.8: Small-signal equivalent circuit of the self-bias circuit in Figure 11.7.

11.3.1 Input Resistance

Input resistance R_i is given as

$$R_i = \left. \frac{v_i}{i_i} \right|_{R_L=\infty} = R_G \quad (11.3.12)$$

11.3.2 Voltage Gain

No-load voltage gain A_v is given by

$$\begin{aligned} A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} &= \left(\frac{v_o}{g_m v_{gs}} \right) \left(\frac{g_m v_{gs}}{v_{gs}} \right) \left(\frac{v_{gs}}{v_i} \right) \\ &= (-R_D || r_{ds}) (g_m) (1) \\ &= -g_m (R_D || r_{ds}) \end{aligned}$$

As a result, A_v is given by

$$A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = -g_m (R_D || r_{ds}) \quad (11.3.13)$$

- If $r_{ds} \geq 10R_D$, no-load voltage gain A_v reduces to

$$A_v = -g_m R_D \quad (11.3.14)$$

- For the circuit in Figure 11.8, we can obtain the current gain A_i as follows

$$\begin{aligned} A_i = \frac{i_o}{i_i} &= \frac{v_o/R_D}{v_i/R_i} = \frac{R_i}{R_D} \frac{v_o}{v_i} \\ &= \frac{R_i}{R_D} A_v \end{aligned} \quad (11.3.15)$$

- If $r_{ds} \geq 10R_D$, current gain A_i reduces to

$$A_i = -g_m R_G \quad (11.3.16)$$

11.3.3 Output Resistance

 


Figure 11.9: Test voltage circuit of Figure 11.8 in order to calculate the output resistance R_o .

Output resistance, i.e., Thévenin equivalent resistance, R_o is calculated using the test voltage circuit in Figure 11.9 above. Note that in the circuit $v_{gs} = 0$, so $g_m v_{gs} = 0$ as well.

$$R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}} = R_D || r_{ds} \quad (11.3.17)$$

- If $r_{ds} \geq 10R_D$, then R_o simplifies to $R_o = R_D$.

11.4 Common-Source Voltage-Divider Bias Configuration

Common-source voltage-divider bias configuration is given in Figure 11.10 below

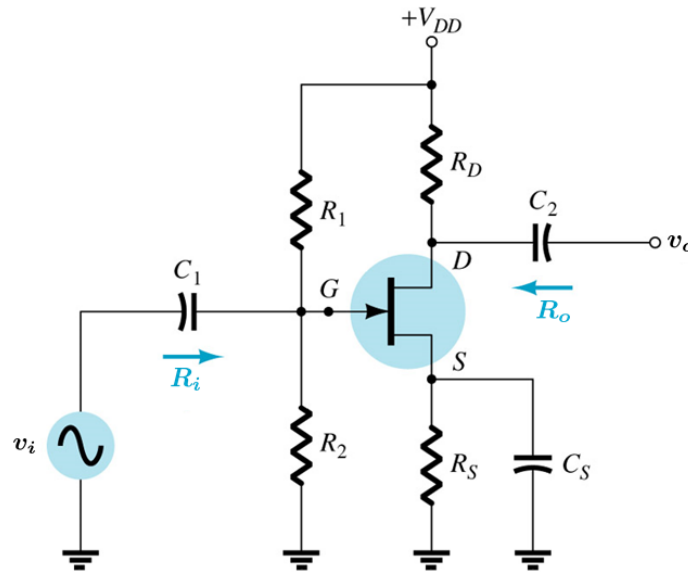


Figure 11.10: Common-source voltage-divider bias configuration.

Corresponding SSAC equivalent circuit is shown in Figure 11.11 below

 


Figure 11.11: Small-signal equivalent circuit of the voltage-divider bias circuit in Figure 11.10.

11.4.1 Input Resistance

Input resistance R_i is given as

$$R_i = \left. \frac{v_i}{i_i} \right|_{R_L=\infty} = R_1 || R_2 \quad (11.4.18)$$

11.4.2 Voltage Gain

No-load voltage gain A_v is given by

$$\begin{aligned} A_v &= \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = \left(\frac{v_o}{g_m v_{gs}} \right) \left(\frac{g_m v_{gs}}{v_{gs}} \right) \left(\frac{v_{gs}}{v_i} \right) \\ &= (-R_D || r_{ds}) (g_m) (1) \\ &= -g_m (R_D || r_{ds}) \end{aligned}$$

As a result, A_v is given by

$$A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = -g_m (R_D || r_{ds}) \quad (11.4.19)$$

- If $r_{ds} \geq 10R_D$, no-load voltage gain A_v reduces to

$$A_v = -g_m R_D \quad (11.4.20)$$

- For the circuit in Figure 11.11, we can obtain the current gain A_i as follows

$$\begin{aligned} A_i &= \frac{i_o}{i_i} = \frac{v_o/R_D}{v_i/R_i} = \frac{R_i}{R_D} \frac{v_o}{v_i} \\ &= \frac{R_i}{R_D} A_v \end{aligned} \quad (11.4.21)$$

- If $r_{ds} \geq 10R_D$, current gain A_i reduces to

$$A_i = -g_m (R_1 || R_2) \quad (11.4.22)$$

11.4.3 Output Resistance

 


Figure 11.12: Test voltage circuit of Figure 11.11 in order to calculate the output resistance R_o .

Output resistance, i.e., Thévenin equivalent resistance, R_o is calculated using the test voltage circuit in Figure 11.12 above. Note that in the circuit $v_{gs} = 0$, so $g_m v_{gs} = 0$ as well.

$$R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}} = R_D || r_{ds} \quad (11.4.23)$$

- If $r_{ds} \geq 10R_D$, then R_o simplifies to $R_o = R_D$.

11.5 Common-Source Unbypassed Self-Bias Configuration

Common-source unbypassed self-bias (unbypassed R_S) configuration is given in Figure 11.13 below

 


Figure 11.13: Common-source unbypassed self-bias configuration.

Corresponding SSAC equivalent circuit is shown in Figure 11.14 below

 


Figure 11.14: Small-signal equivalent circuit of the unbypassed self-bias circuit in Figure 11.13.

- When R_S is not bypassed, we normally use the voltage-controlled voltage source model in the small-signal equivalent circuit as shown in Figure 11.14 above.

11.5.1 Input Resistance

Input resistance R_i is given as

$$R_i = \left. \frac{v_i}{i_i} \right|_{R_L=\infty} = R_G \quad (11.5.24)$$

11.5.2 Voltage Gain

No-load voltage gain A_v is given by

$$\begin{aligned} A_v &= \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = \left(\frac{v_o}{i_d} \right) \left(\frac{i_d}{v_{gs}} \right) \left(\frac{v_{gs}}{v_i} \right) & \dots i_d &= \frac{\mu v_{gs}}{R_S + R_D + r_{ds}} \\ &= (-R_D) \left(\frac{\mu}{R_S + R_D + r_{ds}} \right) \left(\frac{v_{gs}}{v_{gs} + i_d R_S} \right) & \dots \mu &= g_m r_{ds} \\ &= (-R_D) \left(\frac{\mu}{R_S + R_D + r_{ds}} \right) \left(\frac{1}{1 + \frac{\mu R_S}{R_S + R_D + r_{ds}}} \right) \\ &= -\frac{\mu R_D}{(\mu + 1) R_S + R_D + r_{ds}} \\ &= -\frac{g_m R_D}{1 + g_m R_S + \frac{R_S + R_D}{r_{ds}}} \end{aligned}$$

As a result, A_v is given by

$$A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = -\frac{g_m R_D}{1 + g_m R_S + \frac{R_S + R_D}{r_{ds}}} \quad (11.5.25)$$

- If $r_{ds} \geq 10(R_D + R_S)$, no-load voltage gain A_v reduces to

$$A_v = -\frac{g_m R_D}{1 + g_m R_S} \quad (11.5.26)$$

- If $r_{ds} \geq 10(R_D + R_S)$ and $g_m R_S \gg 1$, no-load voltage gain A_v reduces to

$$A_v \approx -\frac{R_D}{R_S} \quad (11.5.27)$$

- For the circuit in Figure 11.14, we can obtain the current gain A_i as follows

$$\begin{aligned} A_i &= \frac{i_o}{i_i} = \frac{v_o/R_D}{v_i/R_i} = \frac{R_i}{R_D} \frac{v_o}{v_i} \\ &= \frac{R_i}{R_D} A_v \end{aligned} \quad (11.5.28)$$

11.5.3 Output Resistance

 


Figure 11.15: Test voltage circuit of Figure 11.14 in order to calculate the output resistance R_o .

Output resistance, i.e., Thévenin equivalent resistance, R_o is calculated using the test voltage circuit in Figure 11.15 above.

$$\begin{aligned}
 R_o &= \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}} = \frac{v_{test}}{\frac{v_{test}}{R_D} + i_d} & \dots i_{test} &= i_{R_D} + i_d \\
 &= \frac{v_{test}}{\frac{v_{test}}{R_D} - \frac{v_{gs}}{R_S}} & \dots v_s &= -v_{gs}, i_d = \frac{-v_{gs}}{R_S} \\
 &= \frac{v_{test}}{\frac{v_{test}}{R_D} + \frac{v_{test}}{(\mu+1)R_S + r_{ds}}} & \dots v_{gs} &= -\frac{v_{test}}{(\mu+1) + r_{ds}/R_S} \\
 &= R_D || [(\mu+1)R_S + r_{ds}] & \dots \mu &= g_m r_{ds} \\
 &= R_D || [(g_m R_S + 1)r_{ds} + R_S] \\
 &\cong R_D
 \end{aligned}$$

As a result, R_o is given by

$$\boxed{R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}} \cong R_D} \quad (11.5.29)$$

11.6 Source-Follower Configuration

Source-follower (common-drain) configuration is given in Figure 11.16 below

 


Figure 11.16: Source-follower configuration.

Corresponding SSAC equivalent circuit is shown in Figure 11.17 below

 


Figure 11.17: Small-signal equivalent circuit of the source-follower circuit in Figure 11.16.

11.6.1 Input Resistance

Input resistance R_i is given as

$$R_i = \left. \frac{v_i}{i_i} \right|_{R_L=\infty} = R_G \quad (11.6.30)$$

11.6.2 Voltage Gain

No-load voltage gain A_v is given by

$$\begin{aligned} A_v &= \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = \left(\frac{v_o}{v_{gs}} \right) \left(\frac{v_{gs}}{v_i} \right) \\ &= [g_m (R_S || r_{ds})] \left(\frac{1}{1 + g_m (R_S || r_{ds})} \right) \quad \dots v_i = v_{gs} + v_o \\ &= \frac{g_m (R_S || r_{ds})}{1 + g_m (R_S || r_{ds})} \\ &\cong 1 \end{aligned}$$

As a result, A_v is given by

$$A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = \frac{g_m (R_S || r_{ds})}{1 + g_m (R_S || r_{ds})} \cong 1 \quad (11.6.31)$$

- For the circuit in Figure 11.17, we can obtain the current-gain A_i as follows

$$\begin{aligned} A_i &= \frac{i_o}{i_i} = \frac{v_o/R_S}{v_i/R_i} = \frac{R_i}{R_S} \frac{v_o}{v_i} \\ &= \frac{R_i}{R_S} A_v \end{aligned} \quad (11.6.32)$$

11.6.3 Output Resistance

 


Figure 11.18: Test voltage circuit of Figure 11.17 in order to calculate the output resistance R_o .

Output resistance, i.e., Thévenin equivalent resistance, R_o is calculated using the test voltage circuit in Figure 11.18 above.

$$\begin{aligned} R_o &= \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}} = \frac{v_{test}}{\frac{v_{test}}{R_S || r_{ds}} - g_m v_{gs}} && \dots i_{test} = i_{R_S || r_{ds}} - g_m v_{gs} \\ &= \frac{v_{test}}{\frac{v_{test}}{R_S || r_{ds}} + g_m v_{test}} && \dots v_{test} = -v_{gs} \\ &= \frac{v_{test}}{\frac{v_{test}}{R_S || r_{ds}} + \frac{v_{test}}{1/g_m}} \\ &= R_S || r_{ds} || \frac{1}{g_m} \end{aligned}$$

As a result, R_o is given by

$$R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}} = R_S || r_{ds} || \frac{1}{g_m} \quad (11.6.33)$$

- If $(R_S || r_{ds}) \geq 10/g_m$, output resistance R_o reduces to

$$R_o \cong \frac{1}{g_m} \quad (11.6.34)$$

11.7 Common-Source Drain Feedback Configuration

Common-source drain feedback bias configuration is given in Figure 11.19 below

 


Figure 11.19: Common-source drain feedback bias configuration.

Corresponding SSAC equivalent circuit is shown in Figure 11.20 below

 


Figure 11.20: Small-signal equivalent circuit of the drain feedback bias circuit in Figure 11.19.

11.7.1 Input Resistance

Input resistance R_i is given as

$$\begin{aligned}
 R_i &= \left. \frac{v_i}{i_i} \right|_{R_L=\infty} = \frac{v_{gs}}{g_m v_{gs} + v_o / (R_D || r_{ds})} & \dots v_i &= v_{gs} \\
 &= \frac{R_F + R_D || r_{ds}}{1 + g_m (R_D || r_{ds})} & \dots v_o &= \frac{(1 - g_m R_F) (R_D || r_{ds}) v_{gs}}{R_F + R_D || r_{ds}} \\
 &\cong \frac{R_F}{1 + g_m (R_D || r_{ds})} & \dots R_F &\gg R_D || r_{ds}
 \end{aligned}$$

As a result, R_i is given by

$$R_i = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} \cong \frac{R_F}{1 + g_m (R_D || r_{ds})} \quad (11.7.35)$$

11.7.2 Voltage Gain

No-load voltage gain A_v is given by

$$A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = \frac{(1 - g_m R_F) (R_D || r_{ds})}{R_F + R_D || r_{ds}} \quad \dots v_i = v_{gs}$$

$$\cong -g_m (R_D || r_{ds} || R_F) \quad \dots g_m R_F \gg 1$$

As a result, A_v is given by

$$A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} \cong -g_m (R_D || r_{ds} || R_F) \quad (11.7.36)$$

- For the circuit in Figure 11.20, we can obtain the current-gain A_i as follows

$$A_i = \frac{i_o}{i_i} = \frac{v_o/R_D}{v_i/R_i} = \frac{R_i}{R_D} \frac{v_o}{v_i}$$

$$= \frac{R_i}{R_D} A_v \quad (11.7.37)$$

11.7.3 Output Resistance

 


Figure 11.21: Test voltage circuit of Figure 11.20 in order to calculate the output resistance R_o .

Output resistance, i.e., Thévenin equivalent resistance, R_o is calculated using the test voltage circuit in Figure 11.21 above. Note that in the circuit $v_{gs} = 0$, so $g_m v_{gs} = 0$ as well.

$$R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}} = R_D || r_{ds} || R_F \quad (11.7.38)$$

- If a voltage source with source resistance R_s is connected to the input, replace R_F with $[(R_F + R_s) / (1 + g_m R_s)]$ in R_o calculations.

11.8 Common-Gate Configuration

Common-gate configuration is given in Figure 11.22 below

 


Figure 11.22: Common-gate configuration.

Corresponding SSAC equivalent circuit is shown in Figure 11.23 below

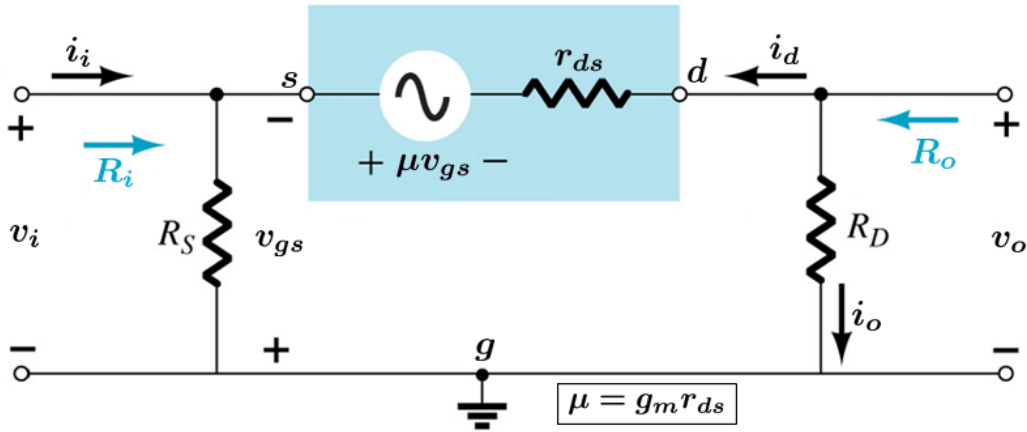


Figure 11.23: Small-signal equivalent circuit of the common-gate circuit in Figure 11.22.

11.8.1 Input Resistance

Input resistance R_i is given as

$$\begin{aligned}
 R_i &= \left. \frac{v_i}{i_i} \right|_{R_L=\infty} = \frac{v_i}{v_i/R_S - i_d} && \dots v_i = -v_{gs} \\
 &= \frac{v_i}{v_i/R_S + v_i/\left(\frac{R_D+r_{ds}}{\mu+1}\right)} && \dots i_d = \frac{(\mu+1)v_{gs}}{R_D+r_{ds}} \\
 &= R_S \parallel \frac{R_D+r_{ds}}{1+g_m r_{ds}} && \dots \mu = g_m r_{ds} \\
 &\cong R_S \parallel \frac{1}{g_m} && \dots r_{ds} \geq 10R_D \text{ and } g_m r_{ds} \gg 1
 \end{aligned}$$

As a result, R_i is given by

$$\boxed{R_i = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} \cong R_S \parallel \frac{1}{g_m}} \quad (11.8.39)$$

11.8.2 Voltage Gain

No-load voltage gain A_v is given by

$$\begin{aligned}
 A_v = \frac{v_o}{v_i} \Big|_{R_L=\infty} &= \frac{-i_d R_D}{-v_{gs}} && \dots v_i = -v_{gs} \\
 &= \frac{(\mu + 1) R_D}{R_D + r_{ds}} && \dots i_d = \frac{(\mu + 1) v_{gs}}{R_D + r_{ds}} \\
 &= \frac{(g_m r_{ds} + 1) R_D}{R_D + r_{ds}} && \dots \mu = g_m r_{ds} \\
 &\cong g_m R_D && \dots r_{ds} \geq 10 R_D \text{ and } g_m r_{ds} \gg 1
 \end{aligned} \tag{11.8.40}$$

As a result, A_v is given by

$$\boxed{A_v = \frac{v_o}{v_i} \Big|_{R_L=\infty} \cong g_m R_D} \tag{11.8.41}$$

- For the circuit in Figure 11.23, we can obtain the current-gain A_i as follows

$$\begin{aligned}
 A_i = \frac{i_o}{i_i} &= \frac{v_o/R_D}{v_i/R_i} = \frac{R_i}{R_D} \frac{v_o}{v_i} \\
 &= \frac{R_i}{R_D} A_v
 \end{aligned} \tag{11.8.42}$$

- If $r_{ds} \geq 10 R_D$ and $g_m r_{ds} \gg 1$, current-gain A_i reduces to

$$A_i = g_m \left(R_S \parallel \frac{1}{g_m} \right) \approx 1 \tag{11.8.43}$$

11.8.3 Output Resistance

 


Figure 11.24: Test voltage circuit of Figure 11.23 in order to calculate the output resistance R_o .

Output resistance, i.e., Thévenin equivalent resistance, R_o is calculated using the test voltage circuit in Figure 11.24 above. Note that in the circuit $v_{gs} = 0$, so $g_m v_{gs} = 0$ as well.

$$\boxed{R_o = \left. \frac{v_{test}}{i_{test}} \right|_{v_s=0, R_L=v_{test}}} = R_D || r_{ds} \quad (11.8.44)$$

- If $r_{ds} \geq 10R_D$, then R_o simplifies to $R_o = R_D$.
- If a voltage source with source resistance R_s is connected to the input, replace r_{ds} with $([1 + g_m (R_s || R_G)] r_{ds} + R_s || R_G)$ in R_o calculations. We can say that $R_o \approx R_D$ in most cases.

Chapter 12

Frequency Response of Amplifiers

12.1 First-Order RC Filters

12.1.1 First-Order Highpass RC Filter

Consider the first order highpass (HP) RC circuit given in Figure 12.1 below, let us calculate the voltage gain $A = v_o/v_i$. Note that, as the impedance of the capacitor changes with the frequency the gain will change with the frequency.

 


Figure 12.1: First order highpass RC filter.

$$\begin{aligned} A(\omega) &= \frac{v_o}{v_i} = \frac{R}{R + Z_C} && \dots Z_C = -jX_C = -j\frac{1}{\omega C} \\ &= \frac{1}{1 + \frac{Z_C}{R}} && \dots \omega = 2\pi f \\ &= \frac{1}{1 - j\frac{1}{\omega CR}} && \end{aligned} \tag{12.1.1}$$

$A(\omega)$ is called frequency response of the filter circuit above. As the frequency response $A(\omega)$ is complex, it has a magnitude and phase, i.e.,

$$A(\omega) = |A(\omega)| e^{j\angle A(\omega)} \tag{12.1.2}$$

Thus, $A(\omega)$ is called the **frequency response**, $|A(\omega)|$ is called the **magnitude response** and $\angle A(\omega)$ is called the **phase response**.

Given that we know the frequency response of the system. Then, for a sinusoidal input $v_i(t)$

$$v_i(t) = V_m \cos(\omega_0 t), \quad (12.1.3)$$

we obtain the output signal $v_o(t)$ as

$$v_o(t) = |A(\omega_0)| V_m \cos(\omega_0 t + \angle A(\omega_0)). \quad (12.1.4)$$

So, the magnitude and phase of the output determined by the frequency response of the system.

For this highpass system given in (12.1.1), magnitude response $|A(\omega)|$ and phase response $\angle A(\omega)$ are given by

$$|A(\omega)| = \frac{1}{\sqrt{1 + \frac{1}{\omega^2 R^2 C^2}}} \quad (12.1.5)$$

$$\angle A(\omega) = \arctan\left(\frac{1}{\omega RC}\right) \quad (12.1.6)$$

Note that $\omega \rightarrow \infty \Rightarrow |A(\omega)| \rightarrow 1$ and $\omega \rightarrow 0 \Rightarrow |A(\omega)| \rightarrow 0$.

12.1.1.1 Cutoff Frequency

The frequency where the output power drops to half (of the maximum output power) is called the **cutoff frequency** or corner frequency, ω_c . Thus, at the cutoff frequency, the output voltage gain magnitude square will drop to half. As, in this case the maximum gain is one, i.e. $\max |A(\omega)| = 1$,

$$\begin{aligned} |A(\omega_c)|^2 &= \frac{1}{2} & \dots \text{i.e., } |A(\omega_c)| &= \frac{1}{\sqrt{2}} \\ \frac{1}{1 + \frac{1}{\omega_c^2 R^2 C^2}} &= \frac{1}{2} \\ \omega_c &= \frac{1}{RC} & \dots f_c &= \frac{1}{2\pi RC} \end{aligned}$$

Thus, cutoff frequency ω_c for the first order highpass RC filter is given by

$$\boxed{\omega_c = \frac{1}{RC}} \quad (12.1.7)$$

Consequently, frequency response of the highpass filter $A(\omega)$ is given by

$$A(\omega) = \frac{1}{1 - j\frac{\omega_c}{\omega}} \quad (12.1.8)$$

$$|A(\omega)| = \frac{1}{\sqrt{1 + \frac{\omega_c^2}{\omega^2}}} \quad (12.1.9)$$

$$\angle A(\omega) = \arctan\left(\frac{\omega_c}{\omega}\right) \quad (12.1.10)$$

12.1.1.2 Bode Plot

Amplitude response in (12.1.9) above has two asymptotes as shown below

$$\frac{\omega_c^2}{\omega^2} \ll 1 \Rightarrow |A(\omega)| = 1 \quad (12.1.11)$$

$$\frac{\omega_c^2}{\omega^2} \gg 1 \Rightarrow |A(\omega)| = \frac{\omega}{\omega_c} \quad \dots |A(\omega_c)| = \frac{\omega_c}{\omega_c} = 1 \quad (12.1.12)$$

These two lines intersect at $\omega = \omega_c$ as shown in Figure 12.2 below.

 


Figure 12.2: Asymptotic Bode plot (scalar) of the first order highpass RC filter in Figure 12.1.

12.1.1.3 Decibels (dB)

The **decibel (dB)** is a logarithmic unit used to express the ratio of two values of a physical quantity, often power or intensity. One of these values is often a standard reference value, in which case the decibel is used to express the level of the other value relative to this reference. The term decibel has

its origin in the fact that power and audio levels are related on a logarithmic basis, i.e.,

$$G_{dB} = 10 \log_{10} \frac{P_o}{P_i} \quad (12.1.13)$$

$$= 20 \log_{10} \left| \frac{V_o}{V_i} \right| \quad \dots P = \frac{V^2}{R} \quad (12.1.14)$$

Thus, **magnitude response** in decibels is given by

$$\boxed{|A(\omega)|_{dB} = 20 \log_{10} |A(\omega)|} \quad (12.1.15)$$

Consequently, the **normalized magnitude response** (i.e., maximum value is 1) in decibels is given by

$$\boxed{|\tilde{A}(\omega)|_{dB} = 20 \log_{10} \frac{|A(\omega)|}{\max |A(\omega)|}} \quad (12.1.16)$$

The two asymptotes of the amplitude response in (12.1.9) are expressed in dB as follows

$$\frac{\omega_c^2}{\omega^2} \ll 1 \Rightarrow 20 \log_{10} 1 = 0 \text{ dB} \quad (12.1.17)$$

$$\frac{\omega_c^2}{\omega^2} \gg 1 \Rightarrow |A(\omega)| = 20 \log_{10} \frac{\omega}{\omega_c} = 20 \log_{10} \omega - 20 \log_{10} \omega_c \quad (12.1.18)$$

These two lines intersect at $\omega = \omega_c$ as shown in Figure 12.3 below.

 


Figure 12.3: Asymptotic Bode plot (dB) of the first order highpass RC filter in Figure 12.1.

As we see from the asymptotic magnitude response in Figure 12.3 above, a **highpass** filter attenuates the low frequencies and keeps the high frequencies intact.

Let us consider the second asymptote (i.e., $20 \log_{10} \frac{\omega}{\omega_c}$) and for a given $\omega = \omega_1$ consider the two cases where $\omega_2 = \omega_1/2$ and $\omega_3 = \omega_1/10$, then

$$20 \log_{10} \frac{\omega_2}{\omega_c} = 20 \log_{10} \frac{\omega_1}{\omega_c} - 20 \log_{10} 2 \cong 20 \log_{10} \frac{\omega_1}{\omega_c} - 6 \text{ dB} \quad \dots \text{one octave} \quad (12.1.19)$$

$$20 \log_{10} \frac{\omega_3}{\omega_c} = 20 \log_{10} \frac{\omega_1}{\omega_c} - 20 \log_{10} 10 = 20 \log_{10} \frac{\omega_1}{\omega_c} - 20 \text{ dB} \quad \dots \text{one decade} \quad (12.1.20)$$

A change in frequency by a factor of **two** is equivalent to one **octave**. Similarly, a change in frequency by a factor of **ten** is equivalent to one **decade**.

Thus, the slope of the second asymptote (i.e., $20 \log_{10} \frac{\omega}{\omega_c}$) is 6 dB/octave or 20 dB/decade.

So, actual magnitude of the normalized magnitude response at the **cutoff frequency** ω_c is $|\tilde{A}(\omega_c)| = 1/\sqrt{2}$. Thus, in dBs

$$20 \log_{10} |\tilde{A}(\omega_c)| = 20 \log_{10} \frac{1}{\sqrt{2}} \cong -3 \text{ dB} \quad (12.1.21)$$

Thus, **cutoff frequency** is **always** 3 dB below the maximum gain.

As a result if we plot (12.1.9) and (12.1.10) against ω , we obtain the **magnitude** and **phase** responses of the first order highpass RC filter as shown in Figure 12.4 below.

 


Figure 12.4: Magnitude (top) and phase (bottom) responses of the first order highpass RC filter in Figure 12.1.

12.1.2 First-Order Lowpass RC Filter

Consider the first order lowpass (LP) RC circuit given in Figure 12.5 below, let us calculate the voltage gain $A = v_o/v_i$. Note that, as the impedance of the capacitor changes with the frequency the gain

will change with the frequency.

 


Figure 12.5: First order lowpass RC filter.

$$\begin{aligned}
 A(\omega) &= \frac{v_o}{v_i} = \frac{Z_C}{Z_C + R} & \dots Z_C &= -jX_C = \frac{1}{j\omega C} \\
 &= \frac{1}{1 + \frac{R}{Z_C}} & \dots \omega &= 2\pi f \\
 &= \frac{1}{1 + j\omega CR} & &
 \end{aligned} \tag{12.1.22}$$

Thus, **magnitude response** $|A(\omega)|$ and **phase response** $\angle A(\omega)$ are given as

$$|A(\omega)| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} \tag{12.1.23}$$

$$\angle A(\omega) = -\arctan(\omega RC) \tag{12.1.24}$$

Note that $\omega \rightarrow \infty \Rightarrow |A(\omega)| \rightarrow 0$ and $\omega \rightarrow 0 \Rightarrow |A(\omega)| \rightarrow 1$.

12.1.2.1 Cutoff Frequency

Cutoff frequency ω_c can be found as,

$$\begin{aligned}
 |A(\omega_c)|^2 &= \frac{1}{2} & \dots \text{i.e., } |A(\omega_c)| &= \frac{1}{\sqrt{2}} \\
 \frac{1}{1 + \omega_c^2 R^2 C^2} &= \frac{1}{2} \\
 \omega_c &= \frac{1}{RC} & \dots f_c &= \frac{1}{2\pi RC}
 \end{aligned}$$

Thus, cutoff frequency ω_c for the first order lowpass RC filter is given by

$$\boxed{\omega_c = \frac{1}{RC}} \tag{12.1.25}$$

Consequently, frequency response of the lowpass filter $A(\omega)$ is given by

$$A(\omega) = \frac{1}{1 + j\frac{\omega}{\omega_c}} \quad (12.1.26)$$

$$|A(\omega)| = \frac{1}{\sqrt{1 + \frac{\omega^2}{\omega_c^2}}} \quad (12.1.27)$$

$$\angle A(\omega) = -\arctan\left(\frac{\omega}{\omega_c}\right) \quad (12.1.28)$$

12.1.2.2 Bode Plot

The two asymptotes of the amplitude response in (12.1.27) are expressed in dB as follows

$$\frac{\omega^2}{\omega_c^2} \ll 1 \Rightarrow 20 \log_{10} 1 = 0 \text{ dB} \quad (12.1.29)$$

$$\frac{\omega^2}{\omega_c^2} \gg 1 \Rightarrow |A(\omega)| = 20 \log_{10} \frac{\omega_c}{\omega} = 20 \log_{10} \omega_c - 20 \log_{10} \omega \quad (12.1.30)$$

These two lines intersect at $\omega = \omega_c$ as shown in Figure 12.6 below.

 


Figure 12.6: Asymptotic Bode plot (dB) of the first order lowpass RC filter in Figure 12.5.

As we see from the asymptotic magnitude response in Figure 12.6 above, a **lowpass** filter keeps the low frequencies intact and attenuates the high frequencies.

Let us consider the second asymptote (i.e., $20 \log_{10} \frac{\omega_c}{\omega}$) and for a given $\omega = \omega_1$ consider the two cases where $\omega_2 = 2\omega_1$ and $\omega_3 = 10\omega_1$, then

$$20 \log_{10} \frac{\omega_c}{\omega_2} = 20 \log_{10} \frac{\omega_c}{\omega_1} - 20 \log_{10} 2 \cong 20 \log_{10} \frac{\omega_c}{\omega_1} - 6 \text{ dB} \quad \dots \text{one octave} \quad (12.1.31)$$

$$20 \log_{10} \frac{\omega_c}{\omega_3} = 20 \log_{10} \frac{\omega_c}{\omega_1} - 20 \log_{10} 10 = 20 \log_{10} \frac{\omega_c}{\omega_1} - 20 \text{ dB} \quad \dots \text{one decade} \quad (12.1.32)$$

Thus, the slope of the second asymptote (i.e., $20 \log_{10} \frac{\omega}{\omega_c}$) is 6 dB/octave or 20 dB/decade.

So, actual magnitude of the normalized magnitude response at the **cutoff frequency** ω_c is $|\tilde{A}(\omega_c)| = 1/\sqrt{2}$. Thus, in dBs

$$\boxed{20 \log_{10} |\tilde{A}(\omega_c)| = 20 \log_{10} \frac{1}{\sqrt{2}} \cong -3 \text{ dB}} \quad (12.1.33)$$

Thus, **cutoff frequency** is **always** 3 dB below the maximum gain.

As a result if we plot (12.1.27) and (12.1.28) against ω , we obtain the **magnitude** and **phase** responses of the first order lowpass RC filter as shown in Figure 12.7 below.

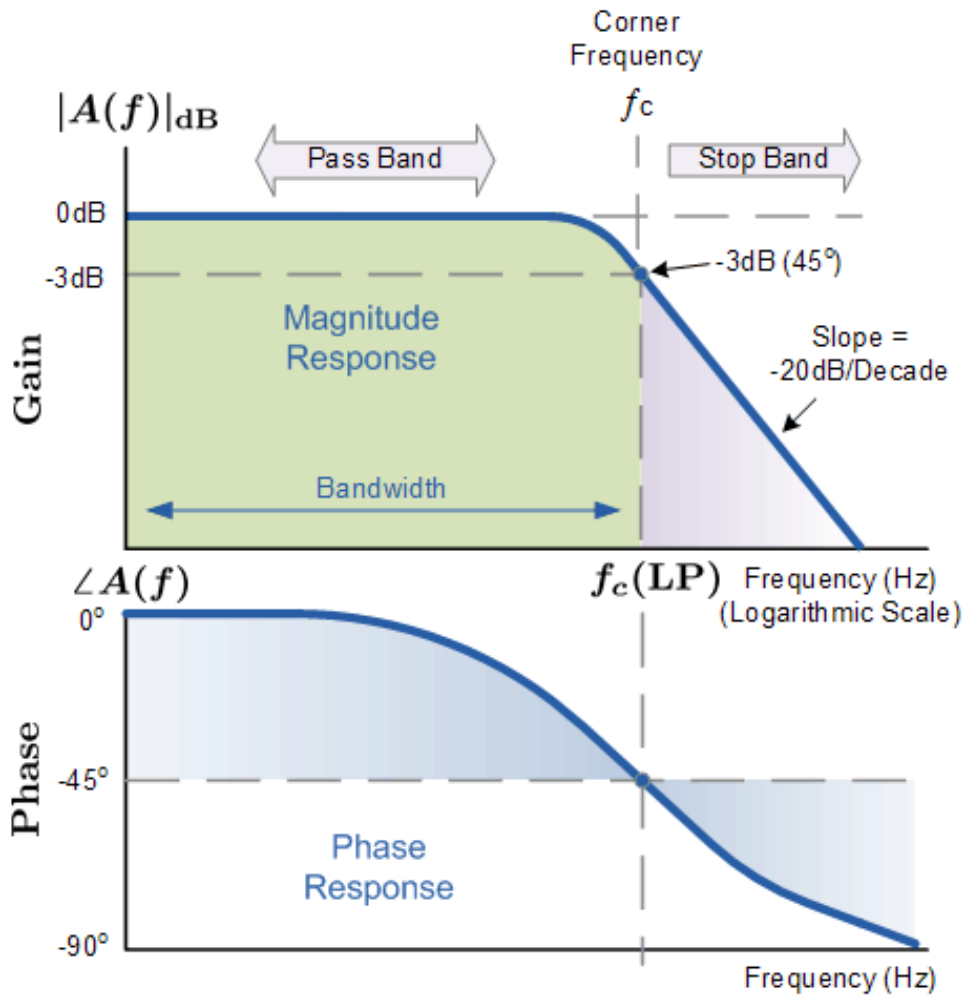


Figure 12.7: Magnitude (top) and phase (bottom) responses of the first order lowpass RC filter in Figure 12.5.

12.2 Typical Frequency Response

The magnitudes of the gain response curves of an RC-coupled amplifier system are given in Figure 12.8 below. In the plot low-, high-, and mid-frequency regions are defined. This magnitude response shown in Figure 12.8 below is the response of a **bandpass amplifier**. It amplifies a band of frequencies

(namely midband, or mid-frequency band) and attenuates the low or high frequencies. Note that, the low-frequency part of the amplifier looks like a highpass amplifier and the high-frequency part of the amplifier looks like a lowpass amplifier. Thus, we can obtain a bandpass amplifier by combining a highpass and a lowpass amplifier.

 


Figure 12.8: Typical magnitude response of a transistor amplifier.

The **purpose of frequency analysis** in this course is to determine the low-frequency cutoff f_L and the high-frequency cutoff f_H of the amplifier. Low-frequency cut-off f_L is determined by the capacitors in the circuit, i.e., C_1 , C_2 and C_3 , and high-frequency cutoff f_H is determined by the internal device capacitances, wiring capacitances or parasitic capacitances.

Typically, low-frequency capacitors C_1 , C_2 and C_3 are in the microFarad (μF) range, and high-frequency capacitances (wiring capacitances and parasitic capacitances) are in the picoFarad (pF) range.

Consequently, low-frequency capacitors are short-circuit for high-frequency, and high-frequency capacitances are open-circuit for low-frequency. So, low-frequency response and high-frequency response will be dealt with separately. The **bandwidth** (or passband, or midband) of the amplifier is determined as,

$$\boxed{\text{Bandwidth (BW)} = f_H - f_L} \quad (12.2.34)$$

Up to now, we have calculated the mid-frequency (midband) input resistance $R_i = Z_{i_{mid}}$, voltage gain $A_v = A_{v_{mid}}$ and output resistance input resistance $R_o = Z_{o_{mid}}$, where we ignored the low-frequency and high-frequency effects assuming the low-frequency capacitances were short-circuit and high-frequency capacitances were open-circuit.

Scalar and decibel plot of the normalized magnitude response is shown in Figure 12.9 and Figure 12.10 below, respectively.

 


Figure 12.9: Normalized scalar plot of the magnitude response given in Figure 12.8.

 


Figure 12.10: Normalized decibel plot of the magnitude response given in Figure 12.8.

12.3 Low Frequency Response

12.3.1 BJT Amplifiers

For the circuit shown in Figure 12.11 below, the capacitors C_1 , C_2 , and C_3 will determine the low-frequency response. Capacitors C_1 and C_2 at the input and output of the circuit are called the **coupling** capacitors, and C_3 is called the **bypass** capacitor. We will now examine the impact of each independently in the order listed as first order RC filters.

 


Figure 12.11: A common-emitter voltage-divider bias BJT circuit.

12.3.1.1 Effect of Coupling Capacitor C_1

For the BJT circuit shown in Figure 12.11 above, capacitor C_1 and the equivalent-resistance of R_s and R_i ($R_{eq1} = R_s + R_i$) form a first-order highpass filter structure given in Figure 12.1 with a cutoff frequency f_{L1} of

$$f_{L1} = \frac{1}{2\pi (R_s + R_i) C_1} \quad (12.3.35)$$

where R_s is the source (e.g., voltage source) resistance and R_i is the **input resistance** of the amplifier, value of which for this circuit is given by

$$R_i = R_1 || R_2 || h_{ie}.$$

12.3.1.2 Effect of Coupling Capacitor C_2

For the BJT circuit shown in Figure 12.11 above, capacitor C_2 and the equivalent-resistance of R_o and R_L ($R_{eq2} = R_o + R_L$) form a first-order highpass filter structure given in Figure 12.1 with a cutoff frequency f_{L2} of

$$f_{L2} = \frac{1}{2\pi (R_o + R_L) C_2} \quad (12.3.36)$$

where R_L is the load resistance and R_o is the **output resistance** of the amplifier, value of which for this circuit is given by

$$R_o = R_C || 1/h_{oe}.$$

12.3.1.3 Effect of Bypass Capacitor C_3

For the BJT circuit shown in Figure 12.11 above, capacitor C_3 and the equivalent Thévenin resistance R_{eq3} seen by C_3 form a first-order lowpass filter structure given in Figure 12.5 with a cutoff frequency f_{L3} of

$$f_{L3} = \frac{1}{2\pi R_{eq3} C_3} \quad (12.3.37)$$

where R_{eq3} is the Thévenin resistance seen by C_3 (i.e., like the output resistance of the emitter-follower), value of which for this circuit is given by

$$R_{eq3} = R_E \parallel \frac{R_s \parallel R_1 \parallel R_2 + h_{ie}}{h_{fe} + 1}.$$

12.3.1.4 Combined Effect of C_1 , C_2 and C_3

Each cutoff frequency f_{L1} , f_{L2} and f_{L3} adds an additional 6 dB/octave slope as shown in Figure 12.12 below. Overall cutoff frequency f_L is higher than the highest value of these three cutoff frequencies, i.e.,

$$f_L \geq \max(f_{L1}, f_{L2}, f_{L3}) \quad (12.3.38)$$

When the three cut-off frequencies (or the highest cutoff frequency) are a decade apart from each other, than the overall cutoff frequency is almost equal to the highest of these three frequencies as depicted in Figure 12.12 below, i.e.,

$$f_L \approx \max(f_{L1}, f_{L2}, f_{L3}) \quad (12.3.39)$$

 


Figure 12.12: Low-frequency plot for the circuit given in Figure 12.11.

As R_{eq3} normally has the lowest resistance value, generally f_{L3} holds the highest value. Also as generally $R_i > R_o$, mostly $f_{L2} > f_{L1}$. So, generally $f_{L3} > f_{L2} > f_{L1}$.

Even though these assumptions may not hold, we generally select the value of the capacitors C_1 , C_2 and C_3 properly to have the cutoff frequencies to be at least a decade apart, e.g., $f_{L3} > 10f_{L2} > 10f_{L1}$, in order to reduce the coupling effect of all three capacitors to the cutoff frequency f_L .

If the decade-apart condition do not hold, then the cutoff frequency f_L will move up towards the mid-frequency range and has to be calculated from the overall third-order highpass system by considering the effects of all three-capacitors.

12.3.2 FET Amplifiers

For the circuit shown in Figure 12.13 below, the capacitors C_1 , C_2 , and C_3 will determine the low-frequency response. Capacitors C_1 and C_2 at the input and output of the circuit are called the **coupling** capacitors, and C_3 is called the **bypass** capacitor. We will now examine the impact of each independently in the order listed as first order RC filters.

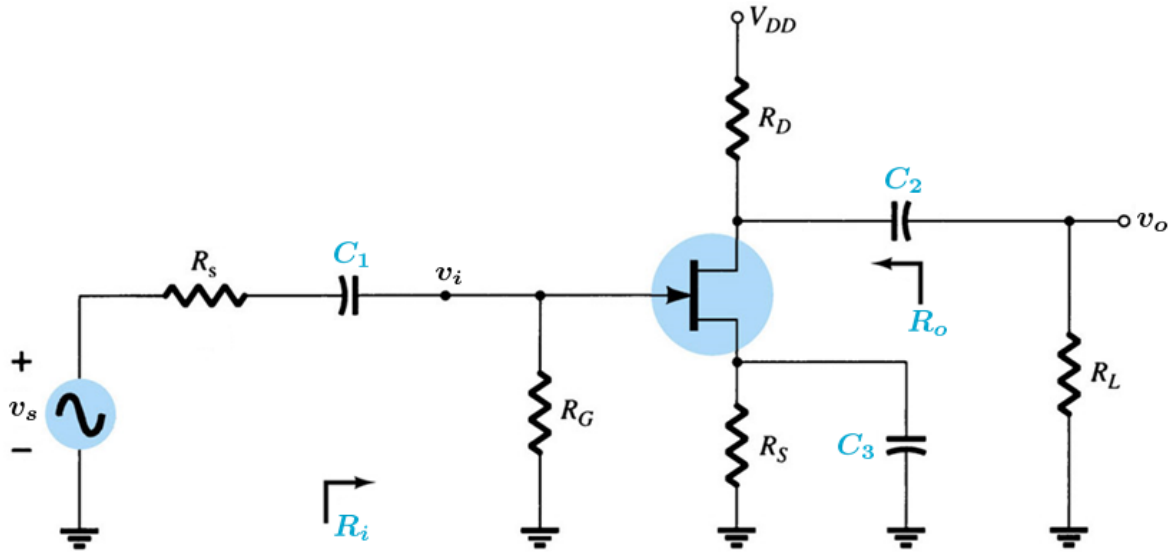


Figure 12.13: A common-source self-bias JFET circuit.

12.3.2.1 Effect of Coupling Capacitor C_1

For the JFET circuit shown in Figure 12.13 above, capacitor C_1 and the equivalent-resistance of R_s and R_i ($R_{eq1} = R_s + R_i$) form a first-order highpass filter structure given in Figure 12.1 with a cutoff frequency f_{L1} of

$$f_{L1} = \frac{1}{2\pi (R_s + R_i) C_1} \quad (12.3.40)$$

where R_s is the source (e.g., voltage source) resistance and R_i is the **input resistance** of the amplifier, value of which for this circuit is given by

$$R_i = R_G.$$

12.3.2.2 Effect of Coupling Capacitor C_2

For the JFET circuit shown in Figure 12.13 above, capacitor C_2 and the equivalent-resistance of R_o and R_L ($R_{eq2} = R_o + R_L$) form a first-order highpass filter structure given in Figure 12.1 with a cutoff frequency f_{L2} of

$$f_{L2} = \frac{1}{2\pi (R_o + R_L) C_2} \quad (12.3.41)$$

where R_L is the load resistance and R_o is the **output resistance** of the amplifier, value of which for this circuit is given by

$$R_o = R_D || r_{ds}.$$

12.3.2.3 Effect of Bypass Capacitor C_3

For the JFET circuit shown in Figure 12.13 above, capacitor C_3 and the equivalent Thévenin resistance R_{eq3} seen by C_3 form a first-order lowpass filter structure given in Figure 12.5 with a cutoff frequency f_{L3} of

$$f_{L3} = \frac{1}{2\pi R_{eq3} C_3} \quad (12.3.42)$$

where R_{eq3} is the Thévenin resistance seen by C_3 (i.e., like the output resistance of the source-follower), value of which for this circuit is given by

$$R_{eq3} = R_S || r_{ds} || \frac{1}{g_m}$$

12.3.2.4 Combined Effect of C_1 , C_2 and C_3

Each cutoff frequency f_{L1} , f_{L2} and f_{L3} adds an additional 6 dB/octave slope as shown in Figure 12.14 below. Overall cutoff frequency f_L is higher than the highest value of these three cutoff frequencies, i.e.,

$$f_L \geq \max(f_{L1}, f_{L2}, f_{L3}) \quad (12.3.43)$$

When the three cut-off frequencies (or the highest cutoff frequency) are a decade apart from each other, than the overall cutoff frequency is almost equal to the highest of these three frequencies as depicted in Figure 12.14 below, i.e.,

$$f_L \approx \max(f_{L1}, f_{L2}, f_{L3}) \quad (12.3.44)$$

 


Figure 12.14: Low-frequency plot for the circuit given in Figure 12.13.

As R_{eq3} has the lowest resistance value, f_{L3} holds the highest value. Also as $R_i \gg R_o$, $f_{L2} > f_{L1}$. So, almost always $f_{L3} > f_{L2} > f_{L1}$.

We generally select the value of the capacitors C_1 , C_2 and C_3 properly to have the cutoff frequencies to be at least a decade apart, e.g., $f_{L3} > 10f_{L2} > 10f_{L1}$, in order to reduce the coupling effect of all three capacitors to the cutoff frequency f_L .

12.4 Miller Effect

For **inverting amplifiers** (phase shift of 180° between input and output, resulting in a negative value for A_v), the input and output capacitance is increased by a capacitance level sensitive to the interelectrode capacitance between the input and output terminals of the device and the gain of the amplifier. Thus, Miller effect only occurs in common-emitter and common-source amplifiers.

Capacitance C_f between input and output will be represented by its equivalent Miller capacitance at the input C_{M_i} and at the output C_{M_o} .

For noninverting amplifiers such as the common-base and emitter-follower (or common-gate and source-follower) configurations, the Miller effect capacitance is not a contributing concern for high-frequency applications.

12.4.0.1 Miller Input Capacitance C_{M_i}

Consider the network shown in Figure 12.15 below, let us calculate the input impedance $Z_i = v_i/i_i$

$$\begin{aligned}
Z_i &= \frac{v_i}{i_i} = \frac{v_i}{i_1 + i_f} & \dots i_1 &= \frac{v_i}{R_i}, i_f = \frac{v_i - v_o}{Z_{C_f}} \\
&= \frac{v_i}{v_i/R_i + \frac{v_i - A_v v_i}{Z_{C_f}}} & \dots v_o &= A_v v_i, Z_{C_f} = \frac{1}{j\omega C_f} \\
&= R_i \parallel \frac{Z_{C_f}}{1 - A_v} & \dots Z_{M_i} &= \frac{Z_{C_f}}{1 - A_v} \\
&= Z_{M_i} \parallel R_i & \dots Z_{M_i} &= \frac{1}{j\omega C_{M_i}}, C_{M_i} = (1 - A_v) C_f
\end{aligned}$$

 


Figure 12.15: Circuit employed in the derivation of an equation for the Miller input capacitance C_{M_i} , where $A_v < 0$.

So, Miller input capacitance C_{M_i} is given by

$$\boxed{C_{M_i} = (1 - A_v) C_f} \tag{12.4.45}$$

Thus, the feedback capacitance C_f appears as a higher capacitance at the input, increased by a factor of $(1 - A_v)$. Note that, $A_v < 0$.

12.4.0.2 Miller Output Capacitance C_{M_o}

Consider the network shown in Figure 12.16 below, let us calculate the output impedance $Z_o = v_o/i_o$

$$\begin{aligned}
Z_o &= \frac{v_o}{i_o} = \frac{v_o}{i_1 + i_f} & \dots i_1 &= \frac{v_o}{R_o}, i_f = \frac{v_o - v_i}{Z_{C_f}} \\
&= \frac{v_o}{v_o/R_o + \frac{v_o - v_o/A_v}{Z_{C_f}}} & \dots v_o &= A_v v_i, Z_{C_f} = \frac{1}{j\omega C_f} \\
&= R_o \parallel \frac{Z_{C_f}}{1 - \frac{1}{A_v}} & \dots Z_{M_o} &= \frac{Z_{C_f}}{1 - \frac{1}{A_v}} \\
&= R_o \parallel Z_{M_o} & \dots Z_{M_o} &= \frac{1}{j\omega C_{M_o}}, C_{M_o} = \left(1 - \frac{1}{A_v}\right) C_f
\end{aligned}$$

 


Figure 12.16: Circuit employed in the derivation of an equation for the Miller output capacitance C_{M_o} , where $A_v < 0$.

So, Miller output capacitance C_{M_o} is given by

$$\boxed{C_{M_o} = \left(1 - \frac{1}{A_v}\right) C_f \cong C_f} \quad (12.4.46)$$

Thus, the feedback capacitance C_f appears as a similar capacitance at the output. Note that, $A_v < 0$ and $|A_v| \gg 1$.

12.4.0.3 Miller Representation

Miller input and output capacitances for the feedback capacitance (C_f) remove the feedback and simplify the representation as shown in Figure 12.17 below.

 


Figure 12.17: Miller representation of the feedback capacitance in negative gain amplifiers.

12.5 High Frequency Response

12.5.1 BJT Amplifiers

For the high-frequency circuit shown in Figure 12.18 below, there are two factors that define the -3 dB cutoff point: the network capacitance (parasitic (C_{be} , C_{bc} , C_{ce}) and wiring (C_{W_i} , C_{W_o}) capacitance) and the frequency dependence of h_{fe} (or β). Note that, low-frequency capacitors C_1 , C_2 and C_3 are short circuit and have **no effect** in high-frequency analysis.

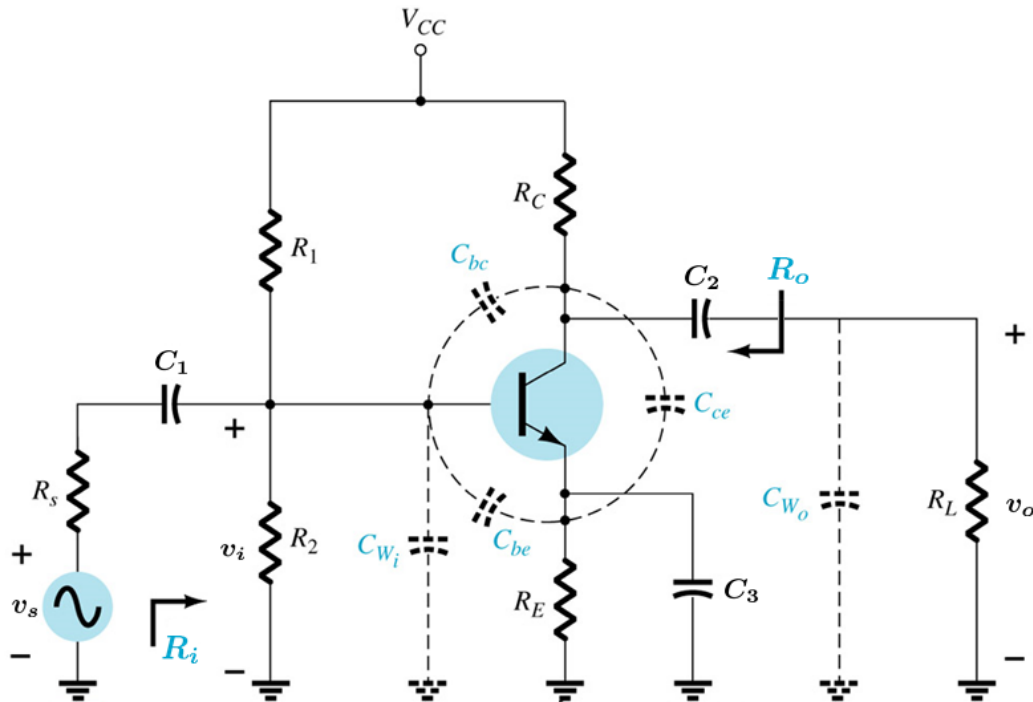


Figure 12.18: A common-emitter voltage-divider bias BJT circuit with the capacitors that affect the high-frequency response.

12.5.1.1 Input Circuit Cutoff Frequency f_{H_1}

For the BJT circuit shown in Figure 12.18 above, equivalent total input capacitance C_{eq_i} and the Thévenin equivalent input resistance of $R_{eq_i} = R_s || R_i$ form a first-order lowpass filter structure given

in Figure 12.5 with a cutoff frequency f_{H_1} of

$$f_{H_1} = \frac{1}{2\pi (R_s || R_i) C_{eq_i}} \quad (12.5.47)$$

with

$$C_{eq_i} = C_{W_i} + C_{M_i} + C_{be} \quad (12.5.48)$$

where R_s is the source (e.g., voltage source) resistance, R_i is the **input resistance** of the amplifier and C_{M_i} is the **Miller input capacitance** given by

$$R_i = R_1 || R_2 || h_{ie}, \quad (12.5.49)$$

$$C_{M_i} = (1 - A_V) C_{bc}. \quad (12.5.50)$$

12.5.1.2 Output Circuit Cutoff Frequency f_{H_2}

For the BJT circuit shown in Figure 12.18 above, equivalent total output capacitance C_{eq_o} and the Thévenin equivalent output resistance of $R_{eq_o} = R_o || R_L$ form a first-order lowpass filter structure given in Figure 12.5 with a cutoff frequency f_{H_2} of

$$f_{H_2} = \frac{1}{2\pi (R_o || R_L) C_{eq_o}} \quad (12.5.51)$$

with

$$C_{eq_o} = C_{ce} + C_{M_o} + C_{W_o} \quad (12.5.52)$$

where R_L is the load resistance, R_o is the **output resistance** of the amplifier and C_{M_o} is the **Miller output capacitance** given by

$$R_o = R_C || 1/h_{oe}, \quad (12.5.53)$$

$$C_{M_o} = (1 - 1/A_V) C_{bc} \cong C_{bc}. \quad (12.5.54)$$

12.5.1.3 h_{fe} (or β) Variation Cutoff Frequency f_β

The h_{fe} parameter (or β) of a transistor varies with frequency as shown in Figure 12.19 below and given by

$$h_{fe} = \frac{h_{fe_{mid}}}{1 + j \frac{f}{f_\beta}} \quad (12.5.55)$$

where f_β is given by

$$f_\beta = \frac{f_T}{h_{fe_{mid}}} \cong \frac{1}{2\pi h_{ie} (C_{be} + C_{bc})} \quad \dots \quad f_T \cong \frac{1}{2\pi r_e (C_{be} + C_{bc})} \quad (12.5.56)$$

 


Figure 12.19: h_{fe} and h_{fb} versus frequency in the high-frequency region.

12.5.1.4 Combined Effect of f_{H_1} , f_{H_2} and f_{β}

Each cutoff frequency f_{H_1} , f_{H_2} and f_{β} adds an additional 6 dB/octave slope as shown in Figure 12.20 below. Overall cutoff frequency f_H is lower than the lowest value of these three cutoff frequencies, i.e.,

$$f_H \leq \min(f_{H_1}, f_{H_2}, f_{\beta}) \quad (12.5.57)$$

When the three cut-off frequencies (or the lowest cutoff frequency) are a decade apart from each other, than the overall higher cutoff frequency f_H is almost equal to the lowest of these three frequencies as depicted in Figure 12.20 below, i.e.,

$$f_H \approx \min(f_{H_1}, f_{H_2}, f_{\beta}) \quad (12.5.58)$$

 


Figure 12.20: Normalized magnitude response (normalized gain vs. frequency) for the circuit given in Figure 12.18.

As Miller input capacitance C_{M_i} has the highest capacitance, almost always f_{H_1} holds the lowest value. Also not always, but generally $f_{\beta} < f_{H_2}$.

12.5.2 FET Amplifiers

For the high-frequency circuit shown in Figure 12.21 below, there are two factors that define the -3 dB cutoff point: the network capacitance (parasitic (C_{gs}, C_{gd}, C_{ds}) and wiring (C_{W_i}, C_{W_o}) capacitance). Note that, low-frequency capacitors C_1, C_2 and C_3 are short circuit and have **no effect** in high-frequency analysis.

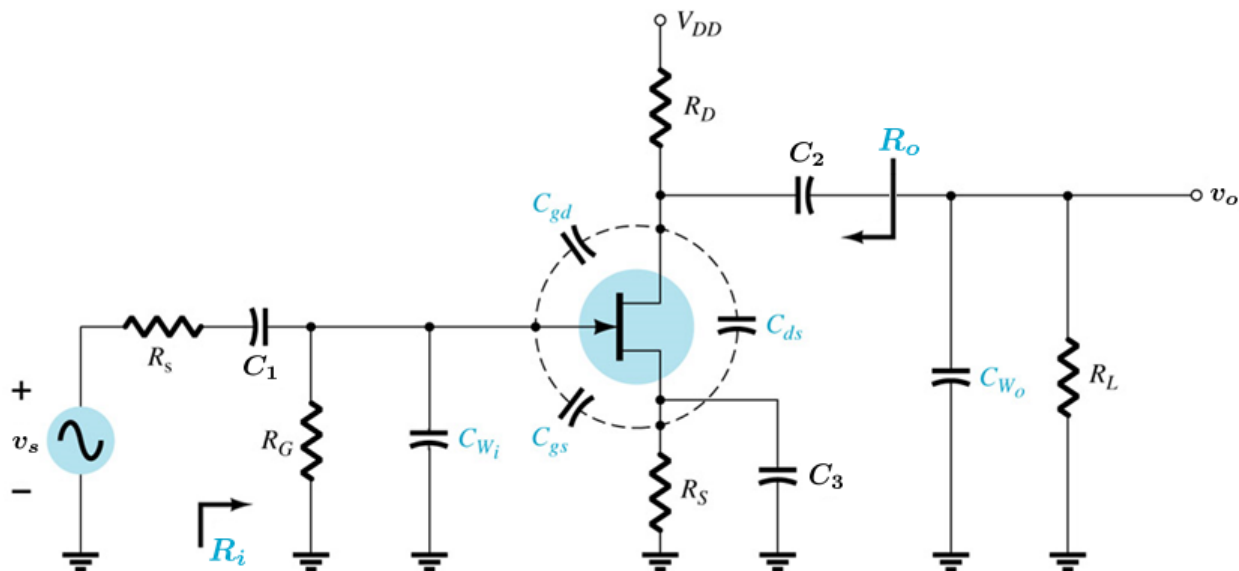


Figure 12.21: A common-source self-bias JFET circuit with the capacitors that affect the high-frequency response.

12.5.2.1 Input Circuit Cutoff Frequency f_{H_1}

For the JFET circuit shown in Figure 12.21 above, equivalent total input capacitance C_{eq_i} and the Thévenin equivalent input resistance of $R_{eq_i} = R_s || R_i$ form a first-order lowpass filter structure given in Figure 12.5 with a cutoff frequency f_{H_1} of

$$f_{H_1} = \frac{1}{2\pi (R_s || R_i) C_{eq_i}} \quad (12.5.59)$$

with

$$C_{eq_i} = C_{W_i} + C_{M_i} + C_{gs} \quad (12.5.60)$$

where R_s is the source (e.g., voltage source) resistance, R_i is the **input resistance** of the amplifier and C_{M_i} is the **Miller input capacitance** given by

$$R_i = R_G, \quad (12.5.61)$$

$$C_{M_i} = (1 - A_V) C_{gd}. \quad (12.5.62)$$

12.5.2.2 Output Circuit Cutoff Frequency f_{H_2}

For the JFET circuit shown in Figure 12.21 above, equivalent total output capacitance C_{eq_o} and the Thévenin equivalent output resistance of $R_{eq_o} = R_o || R_L$ form a first-order lowpass filter structure given in Figure 12.5 with a cutoff frequency f_{H_2} of

$$f_{H_2} = \frac{1}{2\pi (R_o || R_L) C_{eq_o}} \quad (12.5.63)$$

with

$$C_{eq_o} = C_{ds} + C_{M_o} + C_{W_o} \quad (12.5.64)$$

where R_L is the load resistance, R_o is the **output resistance** of the amplifier and C_{M_o} is the **Miller output capacitance** given by

$$R_o = R_D || r_{ds}, \quad (12.5.65)$$

$$C_{M_o} = (1 - 1/A_V) C_{gd} \cong C_{gd}. \quad (12.5.66)$$

12.5.2.3 Combined Effect of f_{H_1} and f_{H_2}

Each cutoff frequency f_{H_1} and f_{H_2} adds an additional 6dB/octave slope. Overall cutoff frequency f_H is lower than the lowest value of these three cutoff frequencies, i.e.,

$$\boxed{f_H \leq \min(f_{H_1}, f_{H_2})} \quad (12.5.67)$$

When the two cut-off frequencies are a decade apart from each other, than the overall higher cutoff frequency f_H is almost equal to the lowest of the two frequencies, i.e.,

$$f_H \approx \min(f_{H_1}, f_{H_2}) \quad (12.5.68)$$

As Miller input capacitance C_{M_i} has the highest capacitance, almost always $f_{H_1} > f_{H_2}$.

12.6 Gain-Bandwidth Product

There is a **Figure of Merit** applied to amplifiers called the **Gain-Bandwidth Product (GBP)** that is commonly used to initiate the design process of an amplifier. It provides important information about the relationship between the gain of the amplifier and the expected operating frequency range.

The gain-bandwidth product of an amplifier is **constant**. Thus, gain and bandwidth are inversely proportional, i.e., when we increase the gain, the bandwidth decreases. As a result, we can express the gain-bandwidth product (GBP) as follows

$$\text{GBP} = |A_{v_{mid}}| \times \text{BW} \quad \dots \text{BW} = f_H - f_L \quad (12.6.69)$$

$$\cong |A_{v_{mid}}| \times f_H \quad \dots f_H \gg f_L \quad (12.6.70)$$

For example, f_T is the gain-bandwidth product for f_β as it is the cutoff frequency for $h_{fe} = 1$, i.e., $f_\alpha \cong f_T$.

Chapter 13

Multistage (Cascaded) Amplifiers

13.1 Cascaded Systems

In cascaded (or multistage) systems output of one amplifier is connected to the input to the next amplifier as shown in Figure 13.1 below.

 


Figure 13.1: A cascaded (or multistage) system.

We would like to represent the overall system as a voltage-gain amplifier as shown in Figure 13.2 below.

 


Figure 13.2: Overall representation of the system as a single voltage-gain amplifier.

So, the input resistance $R_i = \frac{v_i}{i_i}$, the output resistance $R_o = \frac{v_{L(\text{open-circuit})}}{i_{L(\text{short-circuit})}}$ and the no-load voltage gain $A_v = \frac{v_o(\text{no-load})}{v_i}$ of the whole cascaded system is given by

$$R_i = R_{i_1} \quad (13.1.1)$$

$$R_o = R_{o_n} \quad (13.1.2)$$

$$A_v = A_{v_1} \times \frac{R_{i_2}}{R_{o_1} + R_{i_2}} \times A_{v_2} \times \dots \times \frac{R_{i_k}}{R_{o_{k-1}} + R_{i_k}} \times A_{v_k} \times \dots \times \frac{R_{i_n}}{R_{o_{n-1}} + R_{i_n}} \times A_{v_n} \quad (13.1.3)$$

where R_{i_k} , R_{o_k} and A_{v_k} are the input resistance, output resistance and no-load gain of the k -th stage, respectively, $1 \leq k \leq n$ and n is the maximum number of stages.

NOTE: Thus, the input resistance of the current stage acts as a load for the previous stage, or the output resistance of the previous stage acts as a source resistance for the current stage.

Consequently, we can represent the overall no-load voltage-gain A_v in terms of the load-included voltage gains of each stage except the last stage

$$A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = A_{V_1} \times A_{V_2} \times \cdots \times A_{V_k} \cdots \times A_{v_n} \quad (13.1.4)$$

where A_{V_k} is the load-included voltage gain of k -th stage given by

$$A_{V_k} = A_{v_k} \left(\frac{R_{i_{k+1}}}{R_{o_k} + R_{i_{k+1}}} \right). \quad (13.1.5)$$

Similarly, we can represent the overall no-load voltage-gain A_v in terms of the source-included voltage gains of each stage except the first stage

$$A_v = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = A_{v_1} \times A_{v_{s_2}} \times \cdots \times A_{v_{s_k}} \cdots \times A_{v_{s_n}} \quad (13.1.6)$$

where $A_{v_{s_k}}$ is the source-included voltage gain of k -th stage given by

$$A_{v_{s_k}} = \left(\frac{R_{i_k}}{R_{o_{k-1}} + R_{i_k}} \right) A_{v_k}. \quad (13.1.7)$$

Example 13.1: For the figure below, find the input resistance R_i , output resistance R_o and the overall voltage gain $A_{V_s} = v_o/v_s$ of the whole system.

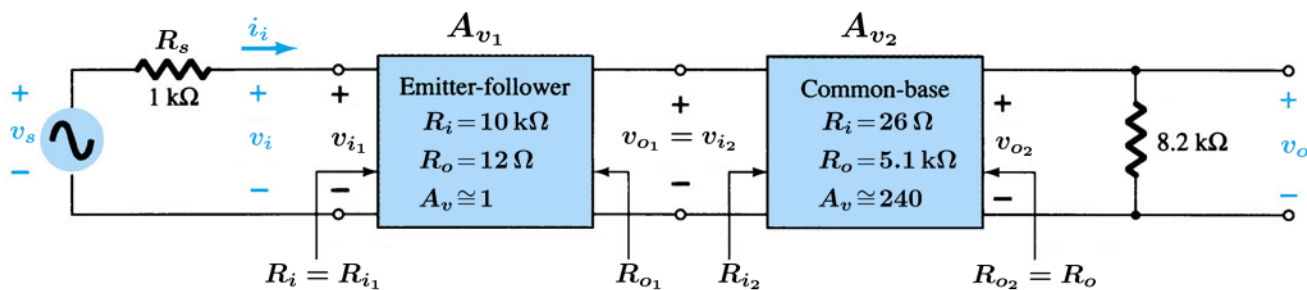


Figure 13.3: A two-stage cascaded system for Example 13.1.

Solution: The input resistance R_i , output resistance R_o and the total voltage gain A_{V_s} of the overall system are given as follows

$$R_i = R_{i_1} = 10 \text{ k}\Omega, \quad (13.1.8)$$

$$R_o = R_{o_2} = 5.1 \text{ k}\Omega, \quad (13.1.9)$$

$$A_v = A_{v_1} \left(\frac{R_{i_2}}{R_{o_1} + R_{i_2}} \right) A_{v_2} = (1) \left(\frac{26}{12 + 26} \right) (240) \cong 164.21, \quad (13.1.10)$$

$$A_{V_s} = \left(\frac{R_i}{R_s + R_i} \right) A_v \left(\frac{R_L}{R_o + R_L} \right) = \left(\frac{10k}{1k + 10k} \right) (164.21) \left(\frac{8.2k}{5.1k + 8.2k} \right) \cong 92. \quad (13.1.11)$$

Homework 13.1: Calculate the overall voltage gain A_{V_s} by removing the first stage in Figure 13.3, i.e., connecting R_s directly to the second stage. Thus, explain the purpose of the first stage.

13.2 AC-Coupled Multistage Amplifiers

In AC-coupled multistage amplifiers, the DC bias circuits are **isolated** from each other by the **coupling capacitors** at the input and output of **each stage**.

Thus,

- The **DC** calculations are **independent** of the cascading.
- The AC calculations for gain and impedance are interdependent.

Example 13.2: For the figure below, find the input resistance R_i , output resistance R_o and the no-load voltage gain $A_v = v_o/v_i$ of the whole system.

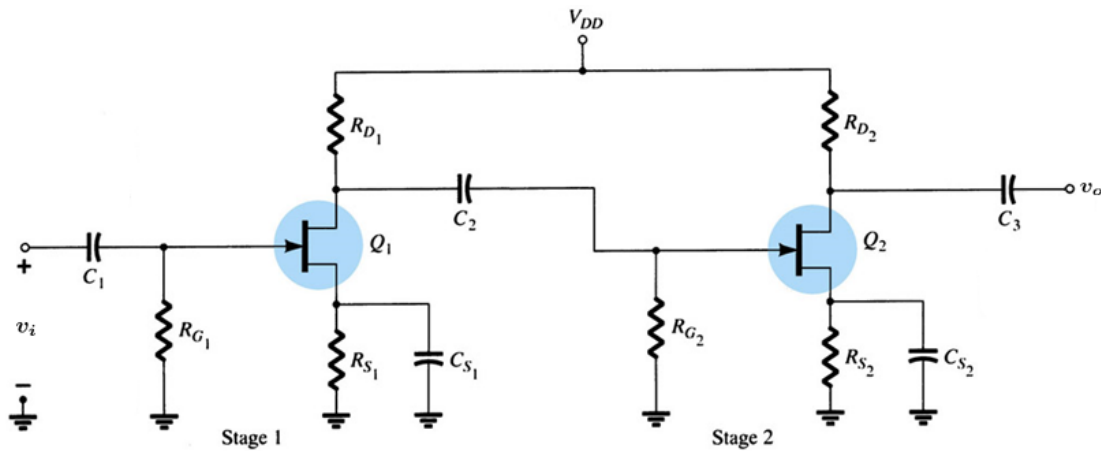


Figure 13.4: An AC-coupled two-stage FET amplifier for Example 13.2.

Solution: The input resistance R_i , output resistance R_o and the no-load voltage gain A_v of the overall system are given as follows

$$R_i = R_{G1} \quad (13.2.12)$$

$$R_o = R_{D2} \parallel r_{ds2} \quad (13.2.13)$$

$$A_v = [-g_{m2} (R_{D2} \parallel r_{ds2})] [-g_{m1} (R_{D1} \parallel r_{ds1} \parallel R_{i2})] \quad (13.2.14)$$

$$= g_{m2} g_{m1} (R_{D2} \parallel r_{ds2}) (R_{D1} \parallel r_{ds1} \parallel R_{G2}). \quad (13.2.15)$$

Example 13.3: For the figure below, find the input resistance R_i , output resistance R_o and the no-load voltage gain $A_v = v_o/v_i$ of the whole system.

 


Figure 13.5: An AC-coupled two-stage BJT amplifier for Example 13.3.

Solution: The input resistance R_i , output resistance R_o and the no-load voltage gain A_v of the overall system are given as follows

$$R_i = R_1 || R_2 || h_{ie1} \quad (13.2.16)$$

$$R_o = R_{C2} || 1/h_{oe2} \quad (13.2.17)$$

$$A_v = \left(-\frac{h_{fe2} (R_{C2} || 1/h_{oe2})}{h_{ie2}} \right) \left(-\frac{h_{fe1} (R_{C1} || 1/h_{oe1} || R_{i2})}{h_{ie1}} \right) \quad (13.2.18)$$

$$= \frac{h_{fe2} h_{fe1} (R_{C2} || 1/h_{oe2}) (R_{C1} || 1/h_{oe1} || R_3 || R_4 || h_{ie2})}{h_{ie2} h_{ie1}}. \quad (13.2.19)$$

- We can also represent these results in the r_e model as follows

$$R_i = R_1 || R_2 || \beta_1 r_{e1} \quad (13.2.20)$$

$$R_o = R_{C2} || r_{o2} \quad (13.2.21)$$

$$A_v = \left(\frac{-R_{C2} || r_{o2}}{r_{e2}} \right) \left(-\frac{R_{C1} || r_{o1} || R_{i2}}{r_{e1}} \right) \quad (13.2.22)$$

$$= \frac{(R_{C2} || r_{o2}) (R_{C1} || r_{o1} || R_3 || R_4 || \beta_2 r_{e2})}{r_{e2} r_{e1}}. \quad (13.2.23)$$

Example 13.4: For the figure below,

- Draw AC and DC load lines for both transistors.
- Calculate the overall voltage gain $A_{V_s} = v_o/v_s$.
- Find $v_{s(\max)}$ which produces maximum undistorted output voltage.

 


Figure 13.6: An AC-coupled two-stage BJT amplifier for Example 13.4.

Homework 13.2: Solve the question given in Example 13.4.

13.3 DC-Coupled Multistage Amplifiers

In DC-coupled multistage amplifiers, the DC bias circuits are **not isolated** from each other.

Thus,

- The **DC** calculations are **not independent** of the cascading.
- The AC calculations for gain and impedance are interdependent.

DC-coupled multistage amplifiers are used either to amplify very low frequency signals or to amplify DC signals.

Example 13.5: For the figure below,

- Draw AC and DC load lines for both transistors.
- Calculate the overall voltage gain $A_{V_s} = v_o/v_s$.
- Find $v_{s(\max)}$ which produces maximum undistorted output voltage.

 


Figure 13.7: A DC-coupled two-stage BJT amplifier for Example 13.5.

Solution: a) Let us first start with DC analysis and apply the Thévenin theorem at the base of the first transistor

$$V_{BB1} = \frac{30k}{30k + 60k} 30 = 10 \text{ V} \quad (13.3.24)$$

$$R_{BB1} = 30k || 60k = 20 \text{ k}\Omega \quad (13.3.25)$$

Note that, $I_{E1} = I_{RE1} + I_{B2} \cong I_{RE1}$ assuming $I_{E2} \sim I_{E1}$. So, we can find I_{RE1} as follows

$$I_{RE1} \cong \frac{V_{BB1} - V_{BE1(ON)}}{R_{E1} + R_{BB1}/(\beta + 1)} = \frac{10 - 0.6}{1k + 20k/21} \cong 4.82 \text{ mA} \quad (13.3.26)$$

Consequently, $I_{CQ1} \cong I_{RE1} = 4.82 \text{ mA}$ and $R_{DC1} \cong R_{E1} = 1 \text{ k}\Omega$. Also, as $V_{B2} = V_{E2} = 4.82 \text{ V}$, we can find I_{E2} as

$$I_{E2} = \frac{V_{E1} - V_{BE2(ON)}}{R_{E2}} = \frac{4.82 - 0.6}{1k} \cong 4.22 \text{ mA} \quad (13.3.27)$$

Thus, $I_{E2} \sim I_{E1}$ and our assumption holds. Here assuming $\alpha = 20/21 \approx 1$, we obtain $R_{DC2} \cong R_C + R_{E2} = 3 \text{ k}\Omega$.

As $R_{ac1} \cong R_{DC1} = 1\text{ k}\Omega$ and $R_{ac2} = R_{DC2} = 3\text{ k}\Omega$, AC and DC load-lines coincide for both transistors, i.e.,

$$v_{CE1} = V_{CC} - i_{C1}R_{ac1} \quad \dots \text{AC-DC load lines are the same} \quad (13.3.28)$$

$$v_{CE2} = V_{CC} - i_{C2}R_{ac2} \quad \dots \text{AC-DC load lines are the same} \quad (13.3.29)$$

Consequently, AC (and DC) load-line for the first transistor is shown in Figure 13.8 below

 


Figure 13.8: AC-DC load-line for the first transistor in Example 13.5.

We can see that maximum undistorted swing for the first transistor is given by

$$v_{CE1(\max)} = \min(V_{CEQ1}, I_{CQ1}R_{ac1}) = \min(25.18, 4.82) = 4.82\text{ V}. \quad (13.3.30)$$

Similarly, AC (and DC) load-line for the second transistor is shown in Figure 13.9 below

 


Figure 13.9: AC-DC load-line for the second transistor in Example 13.5.

We can see that maximum undistorted swing for the second transistor is given by

$$v_{CE_2(\max)} = \min(V_{CE_{Q_2}}, I_{C_{Q_2}} R_{ac_2}) = \min(17.34, 12.66) = 12.66 \text{ V.} \quad (13.3.31)$$

b) Let us first find h_{ie_1} , h_{ie_2} and R_{i_1}

$$h_{ie_1} = h_{fe_1} \frac{\gamma}{I_{C_{Q_1}}} = 20 \frac{26m}{4.82m} = (20)(5.39) \cong 108 \Omega \quad (13.3.32)$$

$$h_{ie_2} = (h_{fe_2} + 1) \frac{\gamma}{I_{C_{Q_2}}} = 21 \frac{26m}{4.22m} = (21)(6.16) \cong 129 \Omega \quad (13.3.33)$$

$$R_{i_1} \cong R_1 || R_2 || [h_{ie_1} + (h_{fe_1} + 1) R_{E_1}] = 30k || 60k || [108 + (21)(1k)] \cong 10.3 \text{ k}\Omega \quad (13.3.34)$$

Later, let us calculate the no-load gain $A_{v_2} = v_o/v_{i_2} = v_o/v_{o_1}$ of the second stage

$$A_{v_2} = \frac{v_o}{v_{o_1}} = \frac{-h_{fe_2} R_C}{h_{ie_2} + (h_{fe_2} + 1) R_{E_2}} = \frac{-(20)(2k)}{129 + (21)(1k)} = 1.89 \quad (13.3.35)$$

Now, let us calculate the overall gain $A_{V_{s_1}} = v_{o_1}/v_s$ of the first stage

$$\begin{aligned} A_{V_{s_1}} = \frac{v_{o_1}}{v_s} &= \left(\frac{R_{i_1}}{R_s + R_{i_1}} \right) \left(\frac{(h_{fe_1} + 1) R_{E_1}}{h_{ie_1} + (h_{fe_1} + 1) R_{E_1}} \right) \\ &= \left(\frac{10.3k}{1k + 10.3k} \right) \left(\frac{(21)(1k)}{108 + (21)(1k)} \right) \cong 0.91. \end{aligned} \quad (13.3.36)$$

So, the overall voltage gain A_{V_s} is given by

$$A_{V_s} = A_{V_{s_1}} \times A_{v_2} = (0.91)(1.89) = 1.72. \quad (13.3.37)$$

- c) From $v_{CE1(max)}$ and $v_{CE2(max)}$ calculated (13.3.30) and (13.3.31) in part (a), and from A_{v_2} and $A_{V_{s1}}$ calculated (13.3.35) and (13.3.36) in part (b), we see that the limiting factor comes from the first stage. Because

$$\left(v_{CE1(max)} < \frac{v_{CE2(max)}}{A_{v_2}} \right) \Rightarrow \left(4.82 < \frac{12.66}{1.89} \right) \Rightarrow (4.82 \text{ V} < 6.7 \text{ V}) \quad (13.3.38)$$

Consequently,

$$v_{s(max)} = \frac{v_{CE1(max)}}{A_{V_{s1}}} = \frac{4.82}{0.91} = 5.30 \text{ V}. \quad (13.3.39)$$

Example 13.6: For the figure below,

- Draw AC and DC load lines for both transistors.
- Calculate the overall voltage gain $A_{V_s} = v_o/v_s$.
- Find $v_{s(max)}$ which produces maximum undistorted output voltage.

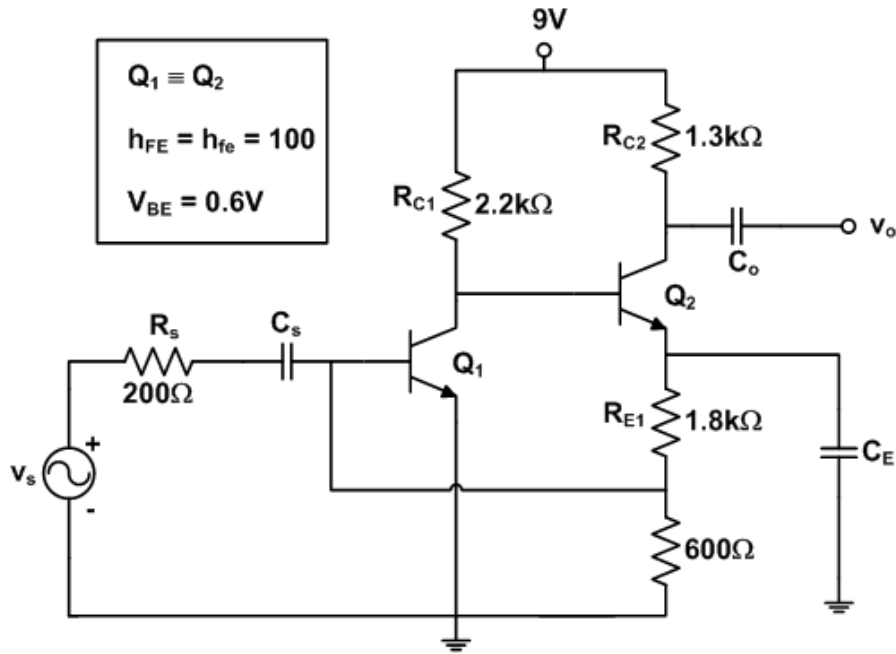


Figure 13.10: A DC-coupled two-stage BJT amplifier for Example 13.6.

Homework 13.3: Solve the question given in Example 13.6.

Example 13.7: For the figure below,

- a) Calculate the overall voltage gain $A_{V_s} = v_o/v_s$.
- b) Find the output resistance R_o .

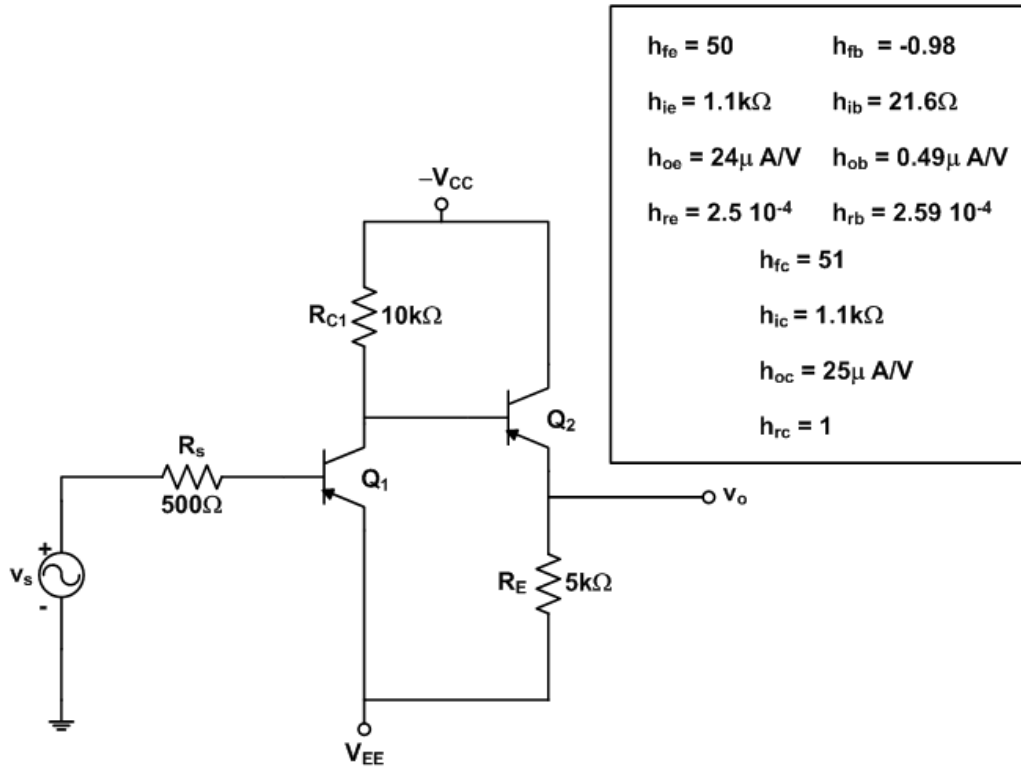


Figure 13.11: A DC-coupled two-stage BJT amplifier for Example 13.7.

Homework 13.4: Solve the question given in Example 13.7.

13.4 Cascode Amplifier

The cascode configuration is a CE-CB combination, where the collector of the first transistor is connected to the emitter of the second transistor as shown in Figure 13.12 below.

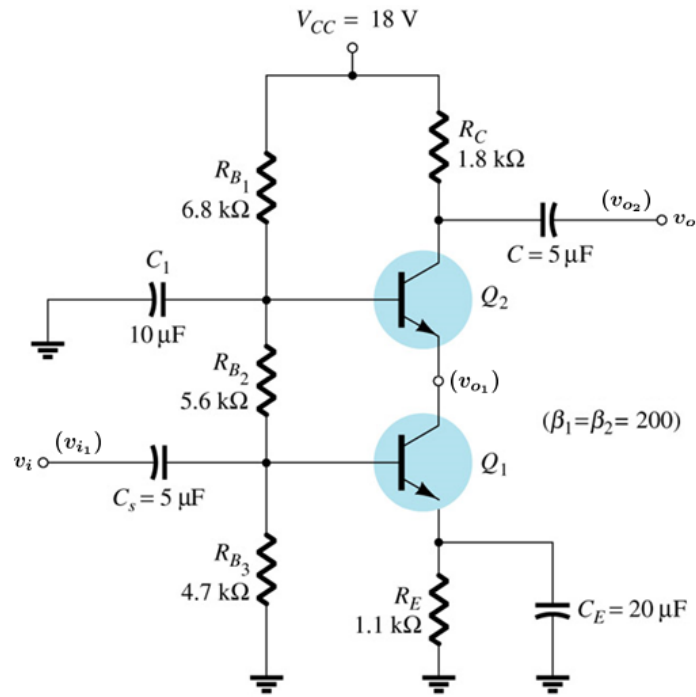


Figure 13.12: A cascode configuration.

The arrangements provide a relatively high-input impedance with low voltage gain for the first CE stage to ensure the input Miller capacitance is at a minimum, whereas the following CB stage provides the high gain.

Therefore, therefore this combination works well in **high frequency** applications.

Example 13.8: For the cascode amplifier below, find the input resistance R_i , output resistance R_o and the voltage gain $A_v = v_o/v_i$.

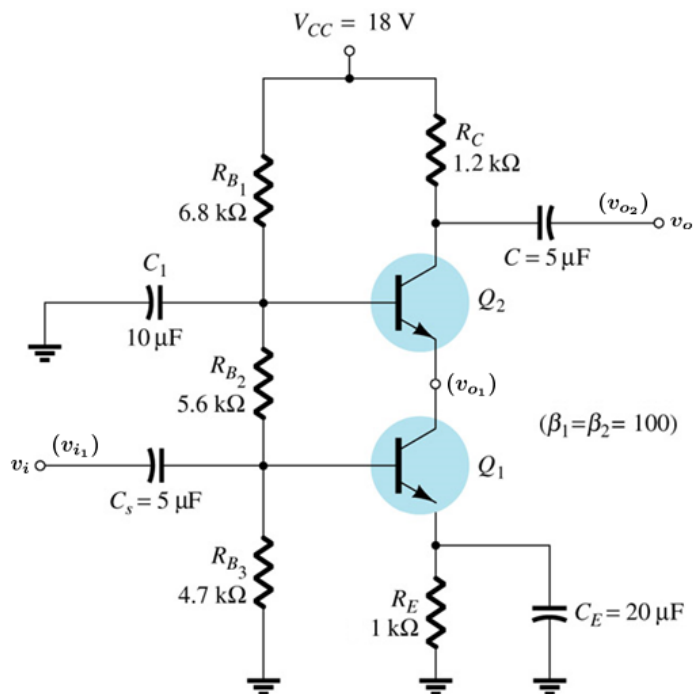


Figure 13.13: A cascode amplifier circuit for Example 13.8.

Solution: Let us perform DC analysis first and calculate I_{EQ_1}

$$I_{EQ_1} = \frac{V_{B_1} - V_{BE(ON)}}{R_E} \quad (13.4.40)$$

$$\cong \frac{\frac{R_{B_3}}{R_{B_1} + R_{B_2} + R_{B_3}} V_{CC} - V_{BE(ON)}}{R_E} \quad \dots \text{ignoring } I_{B_1} \text{ and } I_{B_2} \text{ as } \beta R_E \gg R_{B_3} \quad (13.4.41)$$

$$= \frac{\frac{4.7k}{6.8k + 5.6k + 4.7k} 18 - 0.7}{1k} = \frac{4.95 - 0.7}{1k} \quad (13.4.42)$$

$$= 4.25 \text{ mA} \quad (13.4.43)$$

$$(13.4.44)$$

As $\alpha = 100/101 \cong 1$, $I_{EQ_1} \cong I_{CQ_1} = I_{EQ_2} \cong I_{CQ_2}$. So, $h_{ie} = h_{ie_1} = h_{ie_2}$ given by

$$h_{ie} = (h_{fe} + 1) \frac{\gamma}{I_{EQ}} = (101) \left(\frac{26m}{4.25m} \right) \cong 618 \Omega \quad (13.4.45)$$

So, the SSAC equivalent circuit is given in Figure ?? below

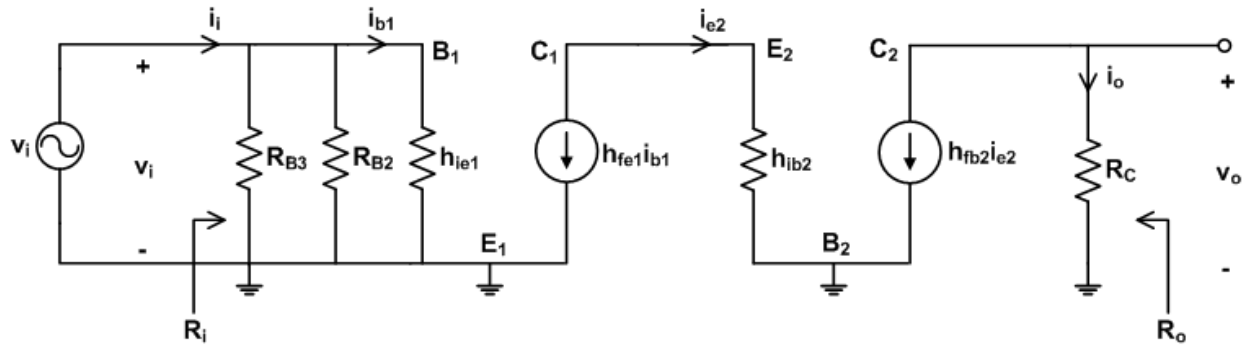


Figure 13.14: SSAC equivalent circuit for Example 13.8.

Thus, we can calculate R_i , R_o and A_v as follows

$$R_i = R_{B3} \parallel R_{B2} \parallel h_{ie1} = 4.7k \parallel 5.6k \parallel 618 \cong 498 \Omega \quad (13.4.46)$$

$$R_o = R_C = 1.2 \text{ k}\Omega \quad (13.4.47)$$

$$A_v = \left(\frac{v_o}{i_{e2}} \right) \left(\frac{i_{e2}}{i_{b1}} \right) \left(\frac{i_{b1}}{v_i} \right) \quad (13.4.48)$$

$$= (-h_{fb2}R_C)(-h_{fe1}) \left(\frac{1}{h_{ie1}} \right) \quad \dots h_{fb} = -1 \quad (13.4.49)$$

$$= -\frac{(100)(1.2k)}{0.618k} = -194. \quad (13.4.50)$$

Homework 13.5: Show that the voltage gain $A_{V1} = v_{o1}/v_i = -1$ for the first stage of the amplifier. Consequently, comment on the Miller effect.

13.5 Darlington Pair

A very popular connection of *npn* two bipolar junction transistors for operation as one **superbeta** *npn* transistor is the Darlington connection shown in Figure 13.15 below.

 


Figure 13.15: Darlington combination.

The main feature of the Darlington connection is that the composite transistor as shown in Figure 13.16 below acts as a single unit with a current gain that is the product of the current gains of the individual transistors.

 


Figure 13.16: Single *npn* transistor representation of the Darlington pair.

Consequently, current gain β_D and base-emitter turn-on voltage $V_{BE_D(ON)}$ are given as follows

$$\beta_D = \beta_1\beta_2 + \beta_1 + \beta_2 \approx \beta_1\beta_2 \quad (13.5.51)$$

$$V_{BE_D(ON)} = 2V_{BE(ON)} \quad (13.5.52)$$

Such that $I_C = \beta_D I_B$ and $I_E = (\beta_D + 1) I_B$ when both transistors are in the forward active mode.

Homework 13.6: Show that expressions (13.5.51) and (13.5.52) above for β_D and $V_{BE_D(ON)}$ are correct.

13.6 Feedback Pair

The feedback pair connection shown in Figure 13.17 below is a two-transistor circuit that operates like the Darlington circuit.

 


Figure 13.17: Feedback pair connection.

Notice that the feedback pair uses a *pnp* transistor driving an *npn* transistor, the two devices acting effectively much like one *pnp* transistor as shown in Figure 13.18 below. As with a Darlington connection, the feedback pair also provides a very high current gain.

 


Figure 13.18: Single *pnp* transistor representation of the feedback pair.

Consequently, current gain β_F and emitter-base turn-on voltage $V_{BE_F(ON)}$ are given as follows

$$\beta_F = \beta_1\beta_2 + \beta_1 \approx \beta_1\beta_2 \quad (13.6.53)$$

$$V_{BE_F(ON)} = V_{BE(ON)} \quad (13.6.54)$$

Such that $I_C = \beta_F I_B$ and $I_E = (\beta_F + 1) I_B$ when both transistors are in the forward active mode.

Homework 13.7: Show that expressions (13.6.53) and (13.6.54) above for β_F and $V_{BE_F(ON)}$ are correct.