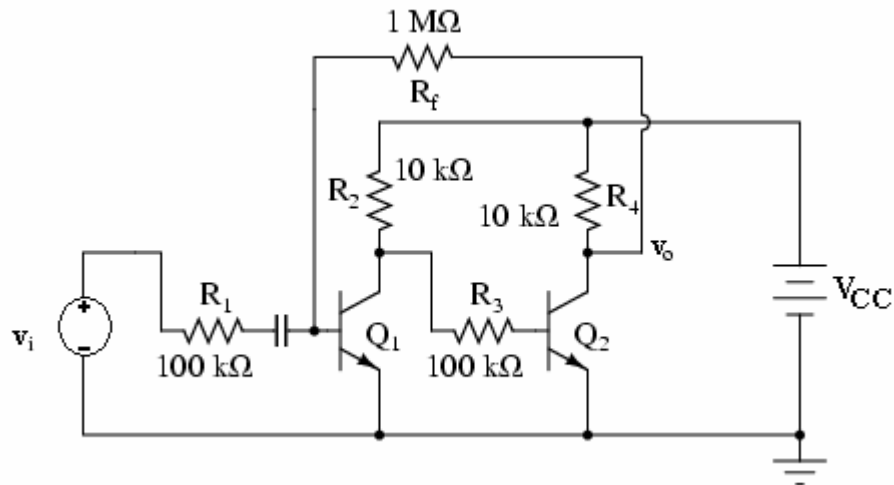


## EXERCISE – Direct-coupled feedback amplifier



$V_{CC} = 12 \text{ V}$
$h_{FE} = h_{fe} = 200$
$V_{BE} = 0.7 \text{ V}$
$I_{CO} \approx 0 \text{ A}$
$V_{CEsat} \approx 0 \text{ V}$
$1/h_{oe} = 120 \text{ k}\Omega$

- Describe the type of feedback and find  $\beta$  and  $A_f$ ?
- $A_{vf} = v_o / v_i$  ?
- $A_{v1} = v_{c1} / v_i$  ?
- Plot the DC and AC lines.
- $v_{imax} = ?$

ANSWER:

- Voltage-shunt (voltage-parallel) feedback

$$\beta = i_f / v_o \approx -1 / R_f = -1 \mu\Omega^{-1}$$

$$A_f = R_{Mf} = v_o / i_i \approx 1 / \beta = -R_f = -1 \text{ M}\Omega$$

Note:  $A = R_M \approx h_{fe1} R_2 / R_3 h_{fe2} R_4 = 40 \text{ M}\Omega$  and  $A_v = R_M / R_1 = 400$ .

- $A_{vf} = v_o / v_i = (v_o / i_i) (i_i / v_i) = R_{Mf} / R_1 \approx -10$

- Let's consider the following equalities

$$v_o = A_{vf} v_i$$

$$i_{c2} \approx -v_o / R_4$$

$$i_{c2} \approx h_{fe} i_{b2}$$

$$i_{b2} \approx v_{c1} / R_3$$

$$\begin{aligned}
A_{v1} &= \frac{v_{c1}}{v_i} \\
&= \frac{v_{c1}}{v_o} \frac{v_o}{v_i} = \frac{v_{c1}}{v_o} \frac{i_{b2}}{i_{b2}} \frac{v_o}{v_i} \\
&= \frac{v_{c1}}{v_o} \frac{i_{b2}}{i_{c2}} \frac{i_{c2}}{v_o} \frac{v_o}{v_i} \\
&= R_3 \frac{1}{h_{fe}} \frac{-1}{R_4} A_{vf} \\
&= 100K / 200 / -10K \times -10 = \underline{0.5}
\end{aligned}$$

#### d) DC equations

##### Base-emitter loop

$$V_{CC} - I_{BQ1} R_f - (I_{CQ2} + I_{BQ1})R_4 - V_{BE1} = 0$$

$$V_{CC} - I_{BQ2} R_3 - (I_{CQ1} + I_{BQ2}) R_2 - V_{BE2} = 0$$

$$V_{CC} - I_{BQ1} R_f - h_{FE} I_{BQ2} R_4 - V_{BE1} = 0$$

$$\dots R_f \gg R_4$$

$$V_{CC} - I_{BQ2} R_3 - h_{FE} I_{BQ1} R_2 - V_{BE2} = 0$$

$$\dots R_3 \gg R_2$$

$$1.00M I_{BQ1} + 2M I_{BQ2} = 11.3$$

$$100K I_{BQ2} + 2M I_{BQ1} = 11.3$$

Solving these three equations give us

$$I_{BQ1} = 5.51 \mu A \quad I_{BQ2} = 2.90 \mu A$$

Consequently the collector currents will be

$$I_{CQ1} = h_{FE} I_{BQ1} = 1.10 \text{ mA}$$

$$I_{CQ2} = h_{FE} I_{BQ2} = 0.58 \text{ mA}$$

##### Collector-emitter loop

$$V_{CC} - (I_{CQ1} + I_{BQ2})R_2 - V_{CEQ1} = 0$$

$$V_{CC} - (I_{CQ2} + I_{BQ1})R_4 - V_{CEQ2} = 0$$


$$12 - 11.0 - V_{CEQ1} = 0$$

$$12 - 5.8 - V_{CEQ2} = 0$$

Hence

$$V_{CEQ1} = 1 \text{ V}$$

$$V_{CEQ2} = 6.2 \text{ V}$$

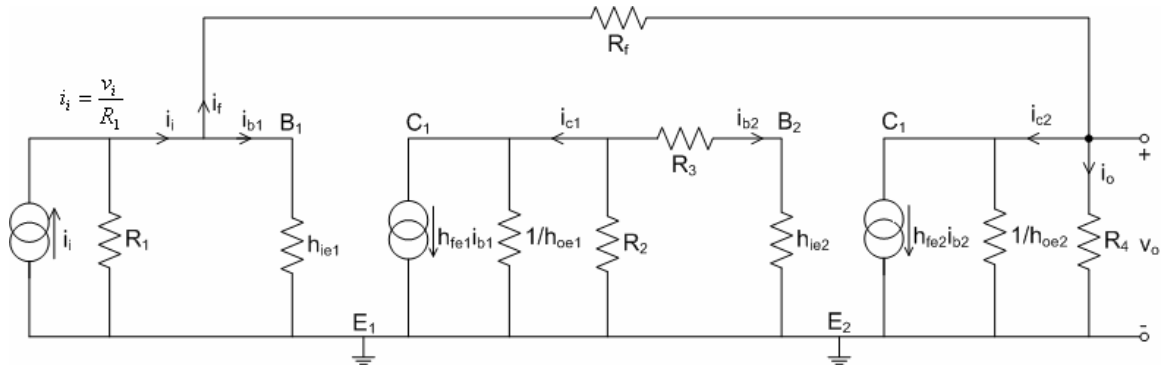

### AC equations

$$\dots h_{ie1} = h_{fe1} \cdot 26\text{mV} / I_{EQ1} = 4.73 \text{ k}\Omega$$

$$\dots h_{ie2} = h_{fe2} \cdot 26\text{mV} / I_{EQ2} = 8.96 \text{ k}\Omega$$

$$v_{CE} = v_{ce} + V_{CEQ}, \quad i_C = i_c + I_{CQ}$$

$$v_{ce1} = -i_{c1} (R_2 \parallel (R_3 + h_{ie2})) \approx -R_2 (i_{c1} - I_{CQ1})$$

$$v_{ce2} \approx -i_{c2} R_4 = -R_4 (i_{c2} - I_{CQ2})$$

$$v_{CE1} = V_{CEQ1} + R_2 (I_{CQ1} - i_{c1})$$

$$v_{CE2} = V_{CEQ2} + R_4 (I_{CQ2} - i_{c2})$$

As  $V_{CEQ1} = V_{CC} - I_{CQ1} R_2$

$V_{CEQ2} = V_{CC} - I_{CQ2} R_4$


Hence

$$v_{CE1} = V_{CC} - R_2 i_{c1}$$


$$v_{CE2} = V_{CC} - R_4 i_{c2}$$

So AC loadline is the same as the DC the load line

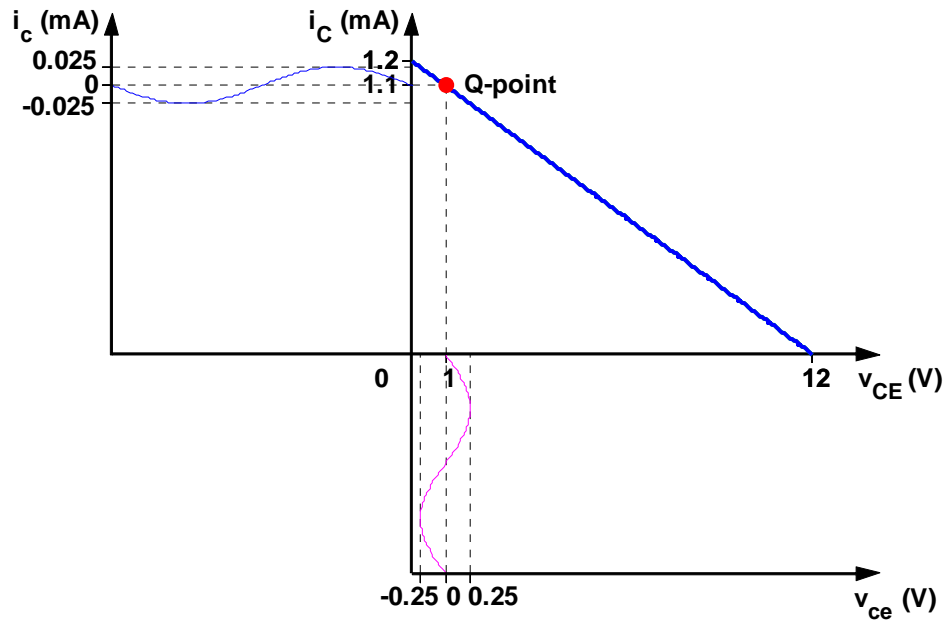For  $v_i = 0.5 \sin(\omega t)$  V, the AC-DC loadlines of Q1 and Q2 are given as



$v_{ce1} = 0.25 \sin(\omega t)$  V

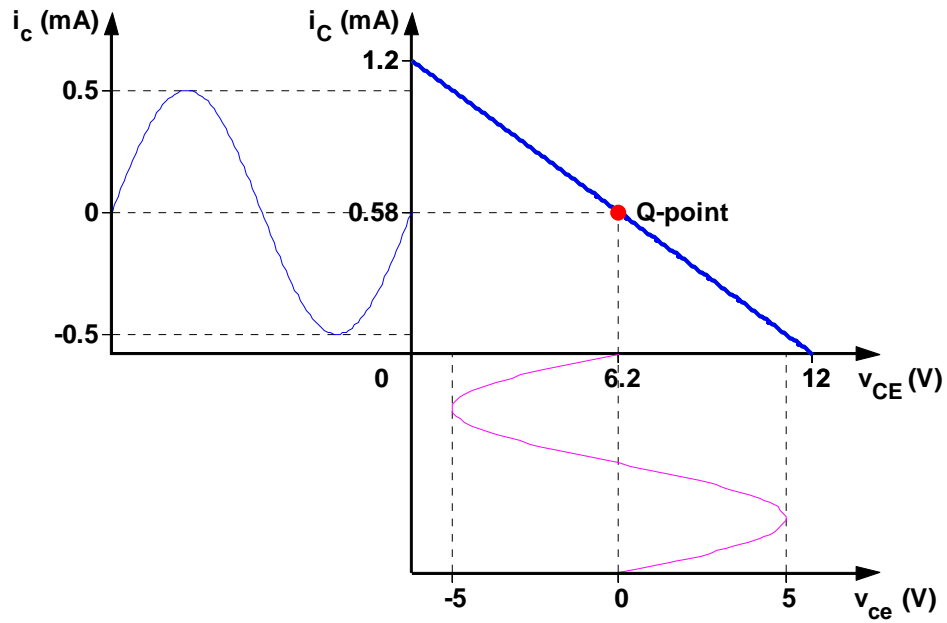

$v_{ce2} = -5 \sin(\omega t)$  V

e) Maximum voltage swing for Q1 is  $v_{ce1max} = V_{CEQ1} = 1V$   
Maximum voltage swing for Q2 is  $v_{ce2max} = V_{CC} - V_{CEQ2} = 5.8V$

For Q1,  $v_{imax} = v_{ce1max} / A_{v1} = 1 / 0.5 = 2 V$

For Q2,  $v_{imax} = v_{ce2max} / A_{vf} = 5.8 / 10 = 0.58 V$

So  $v_{imax} = \underline{0.58 \sin(\omega t)V}$