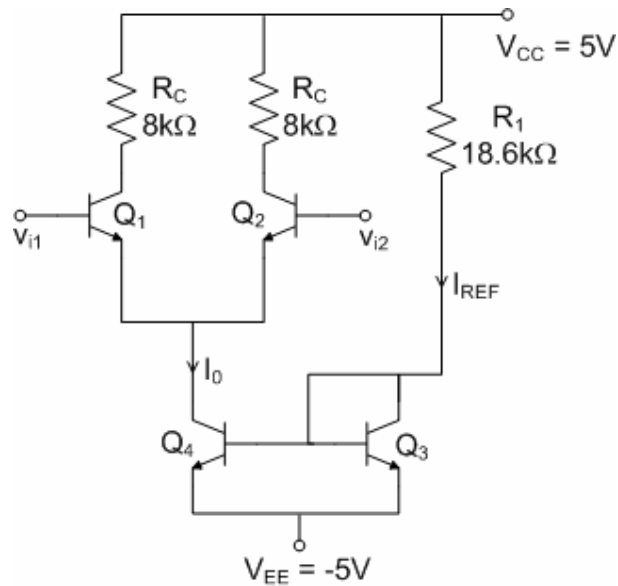


**ELE311  
EXAMPLES**

1. For the circuit shown below, determine the differential and common mode input resistances calculate  $R_{id}$  and  $R_{ic}$  respectively. (2002 Midterm I)



$Q_1 \equiv Q_2$ $h_{fe} = h_{FE} = 100$ $V_{BE} = 0.7V$ $1/h_{oe1} = 1/h_{oe2} = 400k\Omega$ $1/h_{oe4} = 200k\Omega$
--

**ANSWER:**

$$I_0 = I_{REF} = (V_{CC} - V_{BE} - V_{EE}) / R_1 = (5 - 0.7 + 5) / 18.6k = 0.5mA$$

$$I_{E1} = I_{E2} = I_0 / 2 = 0.25mA$$

$$h_{ie} \cong (h_{fe} + 1) V_T / I_{EQ} = 101 \times 26mV / 0.25mA = 10.8k\Omega$$

In the differential mode, i.e.  $v_{i2} = -v_{i1}$ .


$$R_{id} = 2h_{ie} = 2(10.4k) = \underline{21.6k\Omega}$$

In the differential mode, i.e.  $v_{i2} = v_{i1}$ .

Let us define  $r_{o1} = 1/h_{oe1}$ ,  $r_{o2} = 1/h_{oe2}$ ,  $r_{o4} = 1/h_{oe4}$

$$R_{ic} = (h_{fe} + 1)(r_{o4} \parallel r_{o1} \parallel r_{o2}) = (100 + 1)(200k \parallel 400k \parallel 400k) = \underline{10.1 M\Omega}$$

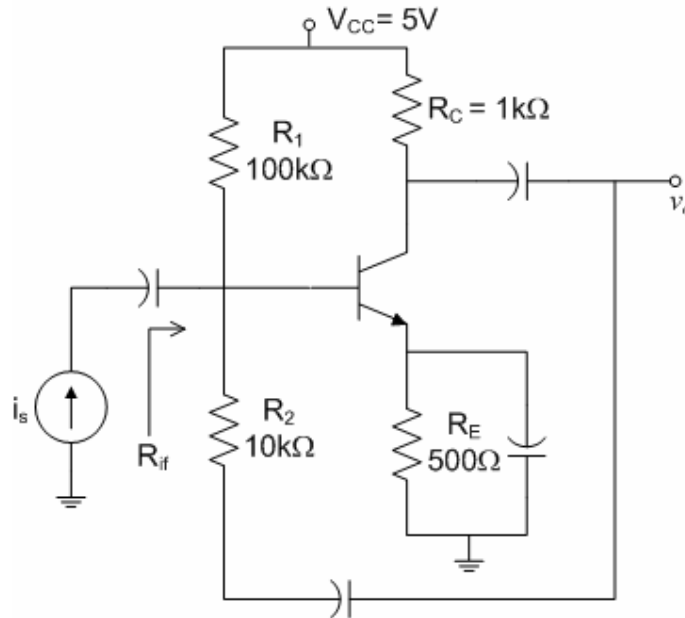2. For the circuit shown below,
- Identify the type of feedback
  - Find input resistance  $R_{if}$
  - Find the gain  $A_f = v_o / i_s$ . (2002 Midterm I)



$h_{fe} = h_{FE} = 100$ $V_{BE} = 0.7V$
---

ANSWER:

- Voltage-parallel feedback
- Let us find first  $I_{EQ}$   

$$V_{CC} - V_{BE} = I_{EQ}R_E + I_{BQ}R_B$$

$$I_{EQ} = (5 - 0.7) / (500 + 100k / (50 + 1)) = 1.75mA$$

$$h_{ie} \cong (h_{fe} + 1)V_T / I_{EQ} = 51 \times 26mV / 1.75mA = 758\Omega$$

Let write down, the open-loop (i.e. without feedback) input resistance  $R_i$

$$R_i = R_1 \parallel R_2 \parallel h_{ie} = 10k \parallel 100k \parallel 758 = 700 \Omega ,$$

the open-loop gain A

$$\begin{aligned}
 A &= v_o / i_s \text{ (open-loop)} \\
 &= -(R_C \parallel R_2) h_{fe} i_b / [h_{ie} i_b / R_i] \\
 &= -909 \times 50 / (758 / 700) \\
 &= -42 \text{ k}\Omega
 \end{aligned}$$

and the feedback gain  $\beta$

$$\beta = i_f / v_o = -1/R_2 = -100 \mu\Omega^{-1}$$

$$R_{if} = R_i / (1 + \beta A) = 700 / (1 + 100\mu \times 42k) = 700 / 5.2 = \underline{135\Omega}$$

$$c) A_f = A / (1 + \beta A) = -42k / (1 + 100\mu \times 42k) = 42k / 5.2 = \underline{-8.08k\Omega}$$