

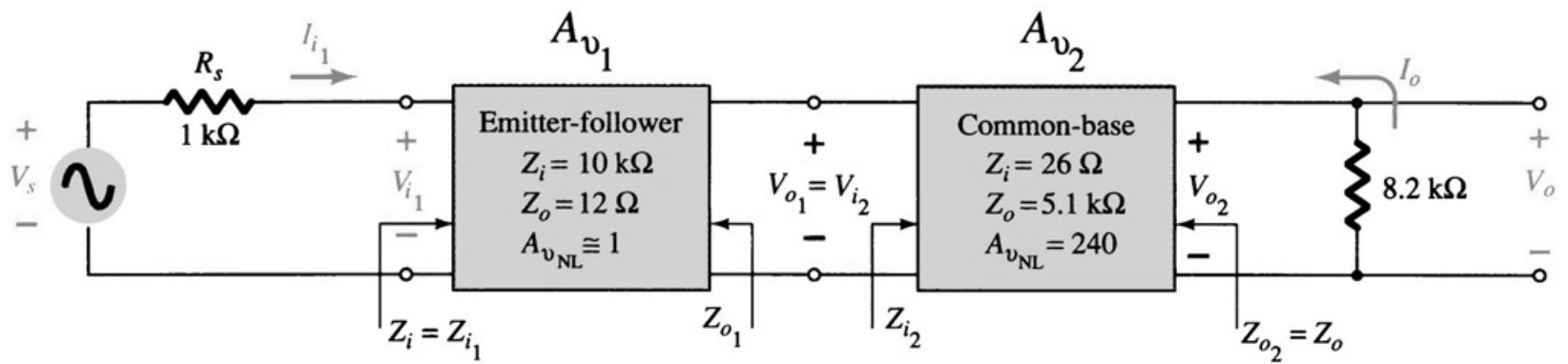



# **Multistage Amplifiers**

# Cascade Connection

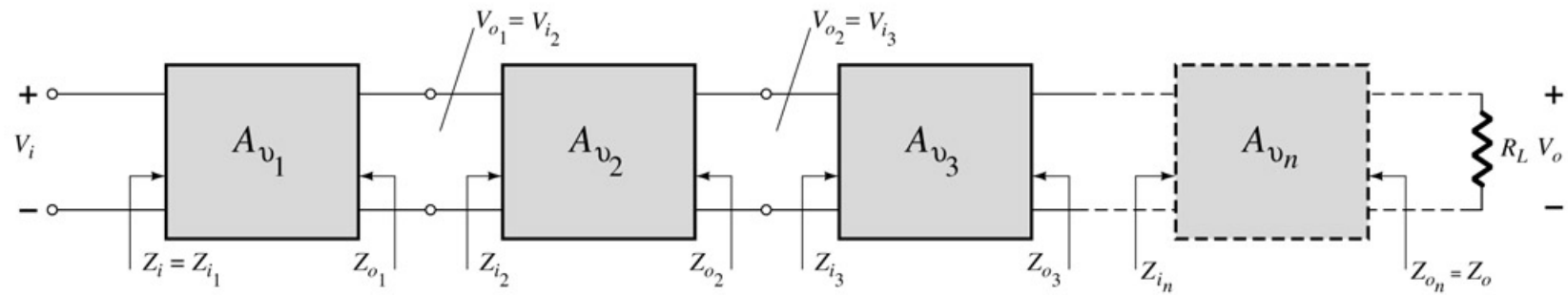


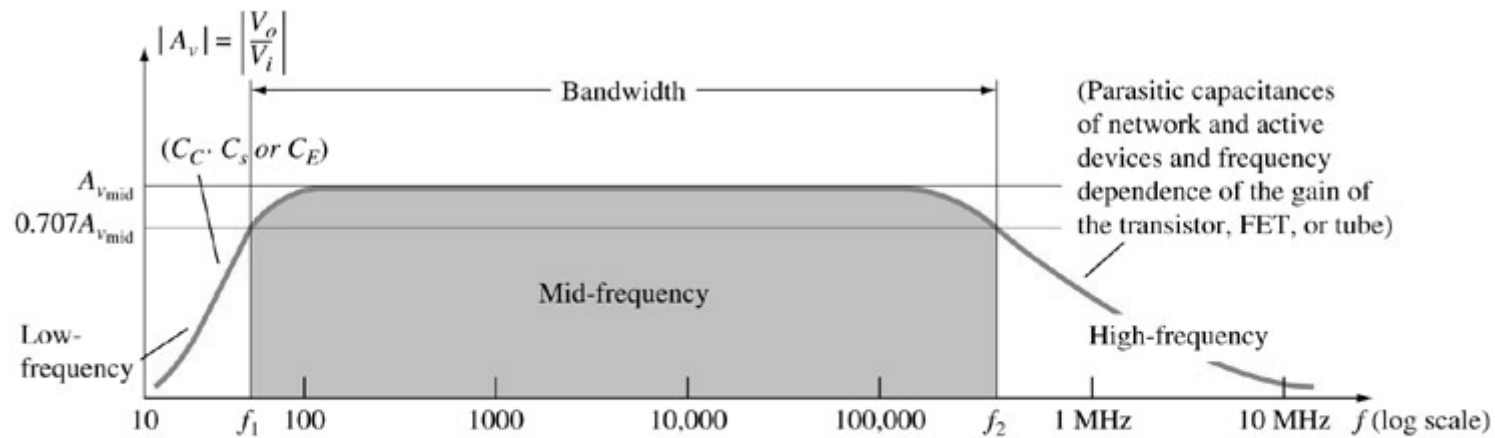

(a)

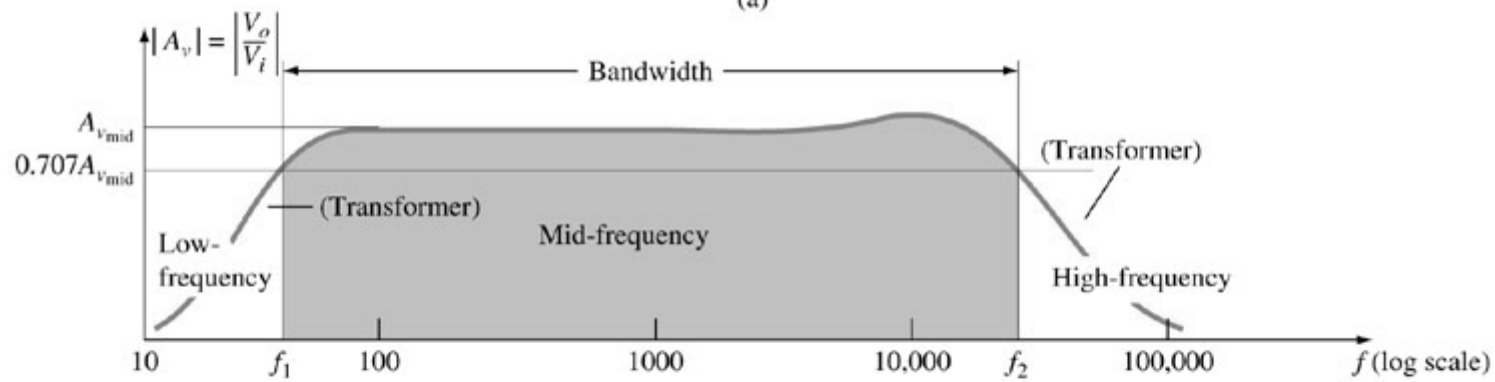


(b)

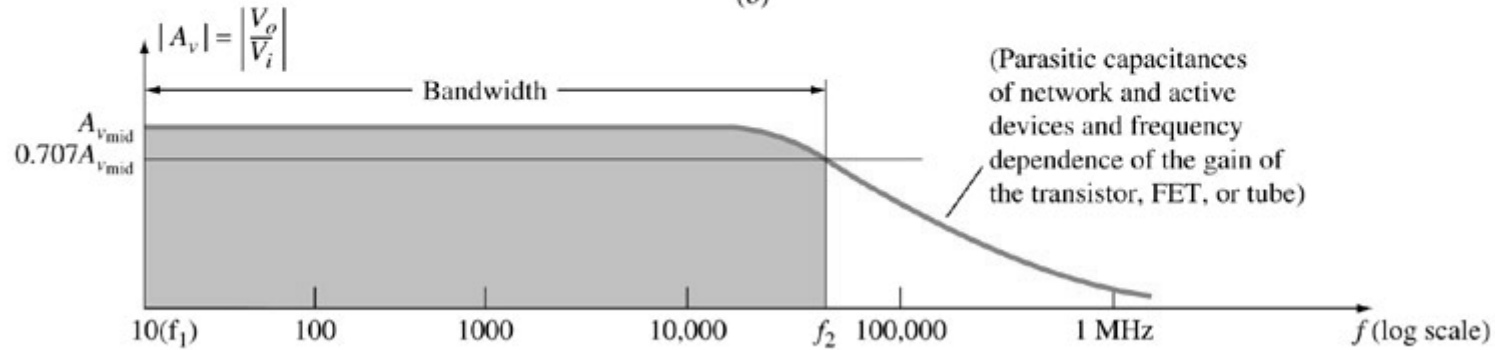

(c)

# AC Coupled Multistage Amplifiers

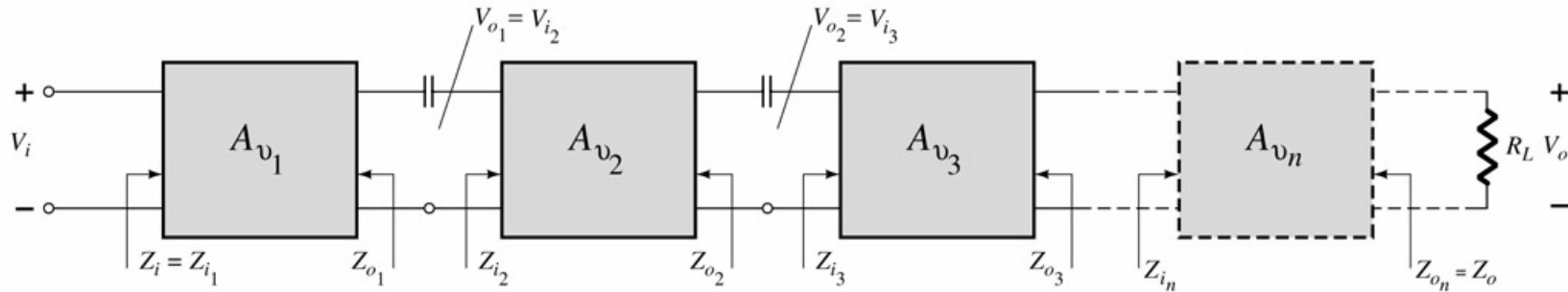

The output of one amplifier is the input to the next amplifier.

Note the DC bias circuits **are isolated** from each other by the coupling capacitors.

The DC calculations **are independent** of the cascading.


The AC calculations for gain and impedance are interdependent.

The overall gain:

$$A_v = A_{v1} \times \frac{Z_{i2}}{Z_{o1} + Z_{i2}} \times A_{v2} \times \dots \times \frac{Z_{ik}}{Z_{o_{k-1}} + Z_{ik}} \times A_{vk} \dots \times \frac{Z_{in}}{Z_{o_{n-1}} + Z_{in}} \times A_{vn}$$

with  $Z_i = Z_{i1}$  and  $Z_o = Z_{on}$

# AC Coupled Multistage Amplifiers

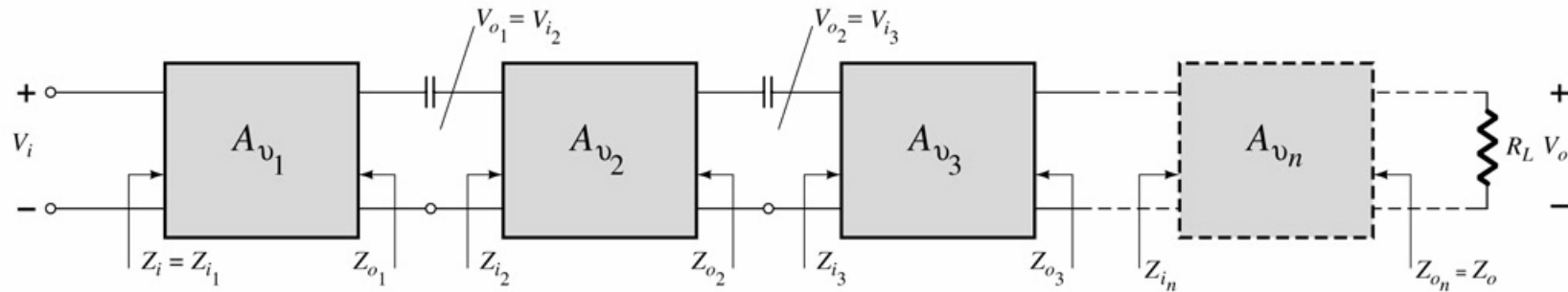


We can also express the overall gain as follows

$$A_v = A_{v1}^* \times A_{v2}^* \times \cdots \times A_{vk}^* \cdots \times A_{vn}$$

where

$$A_{vk}^* = A_{vk} \times \frac{Z_{i_{k+1}}}{Z_{o_k} + Z_{i_{k+1}}}$$

# FET Cascade Amplifier

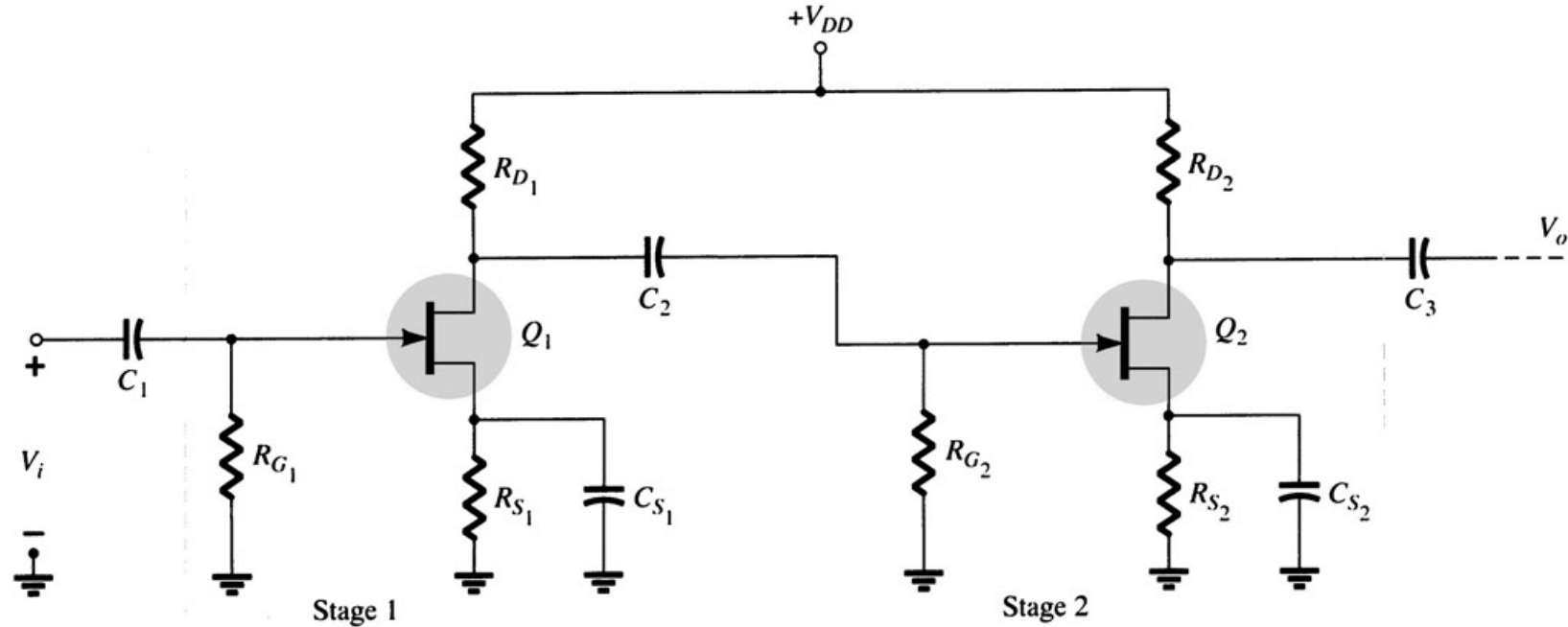


Voltage Gain: 
$$A_v = A_{v_2} A_{v_1}^* = (-g_{m_2} R_{D_2}) [-g_{m_1} (R_{D_1} \parallel R_{G_2})]$$

Input Impedance: 
$$Z_i = R_{G_1}$$

Output Impedance: 
$$Z_o = R_{D_2}$$

## BJT Cascade Amplifier

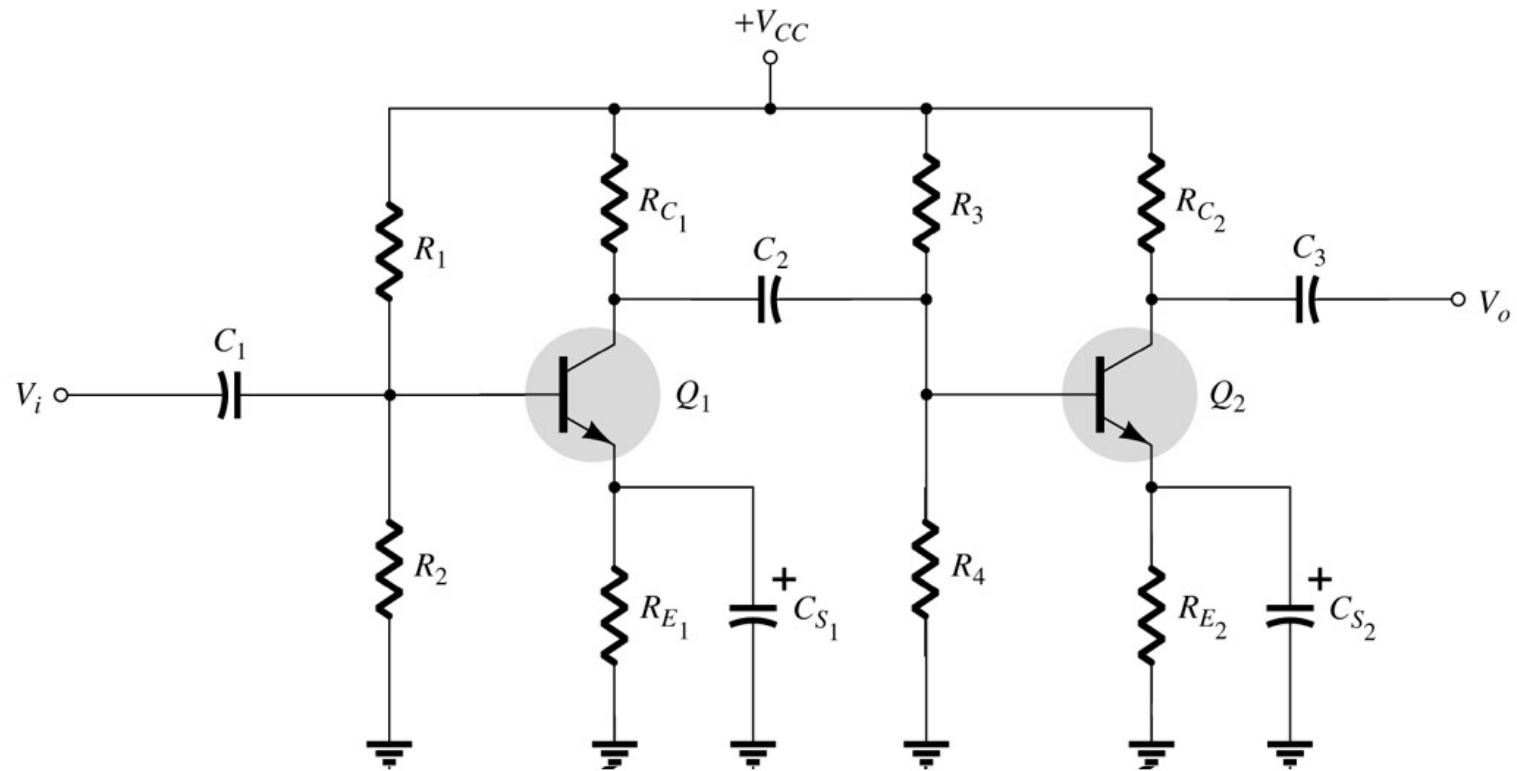

Voltage Gain: 
$$A_v = A_{v_2} A_{v_1}^* = \left( -\frac{h_{fe_2} R_{C_2}}{h_{ie_2}} \right) \left( -\frac{h_{fe_1} [R_{C_1} \parallel (R_3 \parallel R_4 \parallel h_{ie_2})]}{h_{ie_1}} \right)$$

Input Impedance: 
$$Z_i = R_1 \parallel R_2 \parallel h_{ie_1}$$

Output Impedance: 
$$Z_o = R_{C_2} \parallel \frac{1}{h_{oe_2}}$$


## **Combination of FET and BJT Cascade**

A FET-BJT cascade is calculated in a similar fashion as a FET-FET or a BJT-BJT cascade.

This combination provides a high gain from the BJT with the high input impedance from the FET.




**Ex1:**

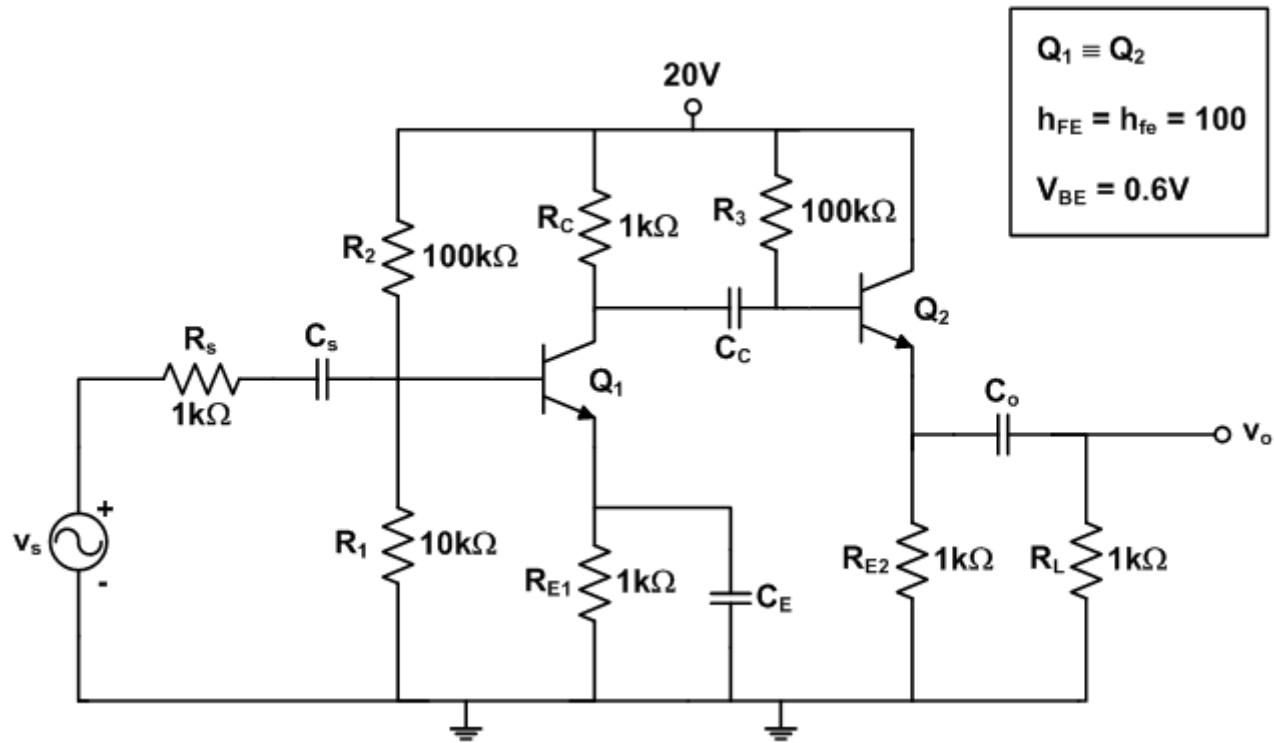

- a) Draw AC and DC load lines for both transistors.
- b) Calculate the overall voltage gain  $A_V = v_o / v_s$ .
- c) Find  $v_{s(max)}$  which produces maximum undistorted output voltage.

# DC Coupled Multistage Amplifiers

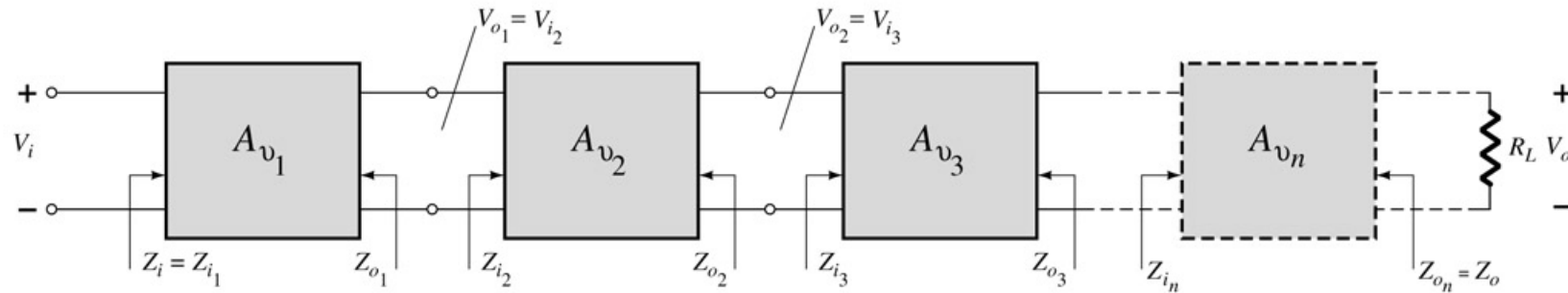

The output of one amplifier is the input to the next amplifier.

Note the DC bias circuits **are not isolated** from each other  
The DC calculations **are not independent** of the cascading.


Used either to amplify very low frequency signals or to amplify DC signals

The overall gain:

$$A_v = A_{v1} \times \frac{Z_{i2}}{Z_{o1} + Z_{i2}} \times A_{v2} \times \dots \times \frac{Z_{ik}}{Z_{o_{k-1}} + Z_{ik}} \times A_{vk} \times \dots \times \frac{Z_{in}}{Z_{o_{n-1}} + Z_{in}} \times A_{vn}$$


with  $Z_i = Z_{i1}$  and  $Z_o = Z_{on}$

## Ex2:

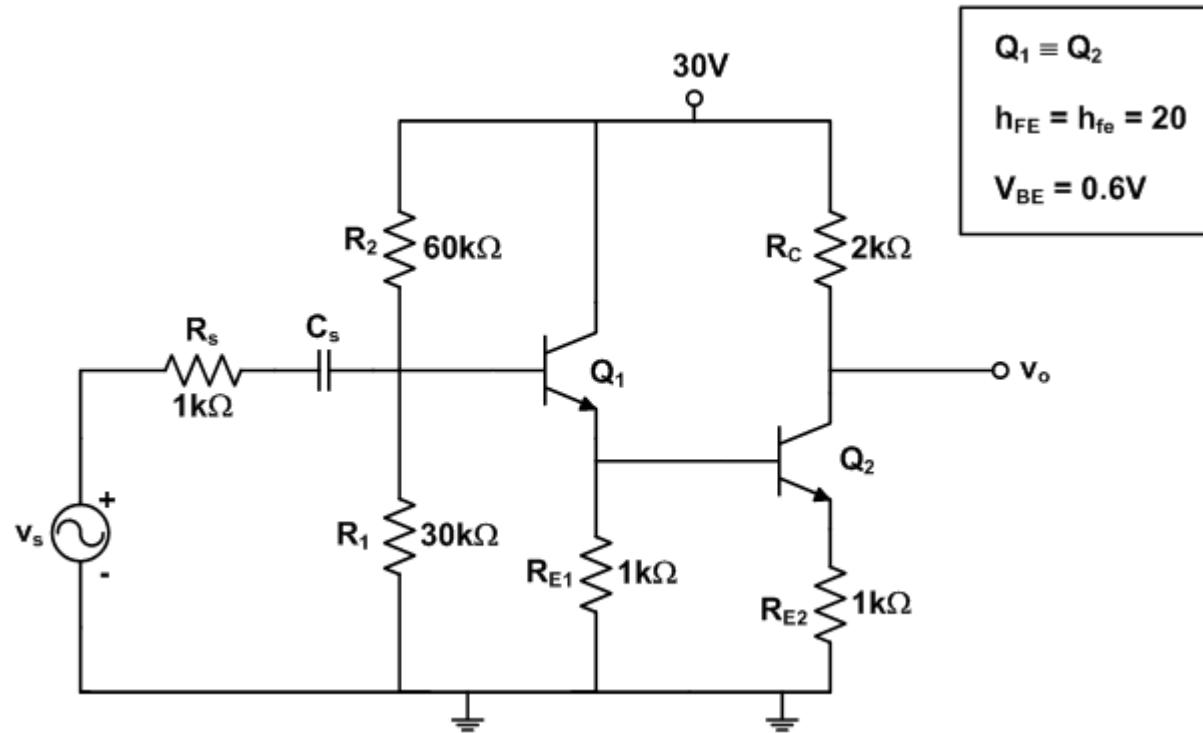


- Draw AC and DC load lines for both transistors.
- Calculate the overall voltage gain  $\mathbf{A}_V = \mathbf{v}_o / \mathbf{v}_s$ .
- Find  $\mathbf{v}_{s(\max)}$  which produces maximum undistorted output voltage.

**Ex3:**

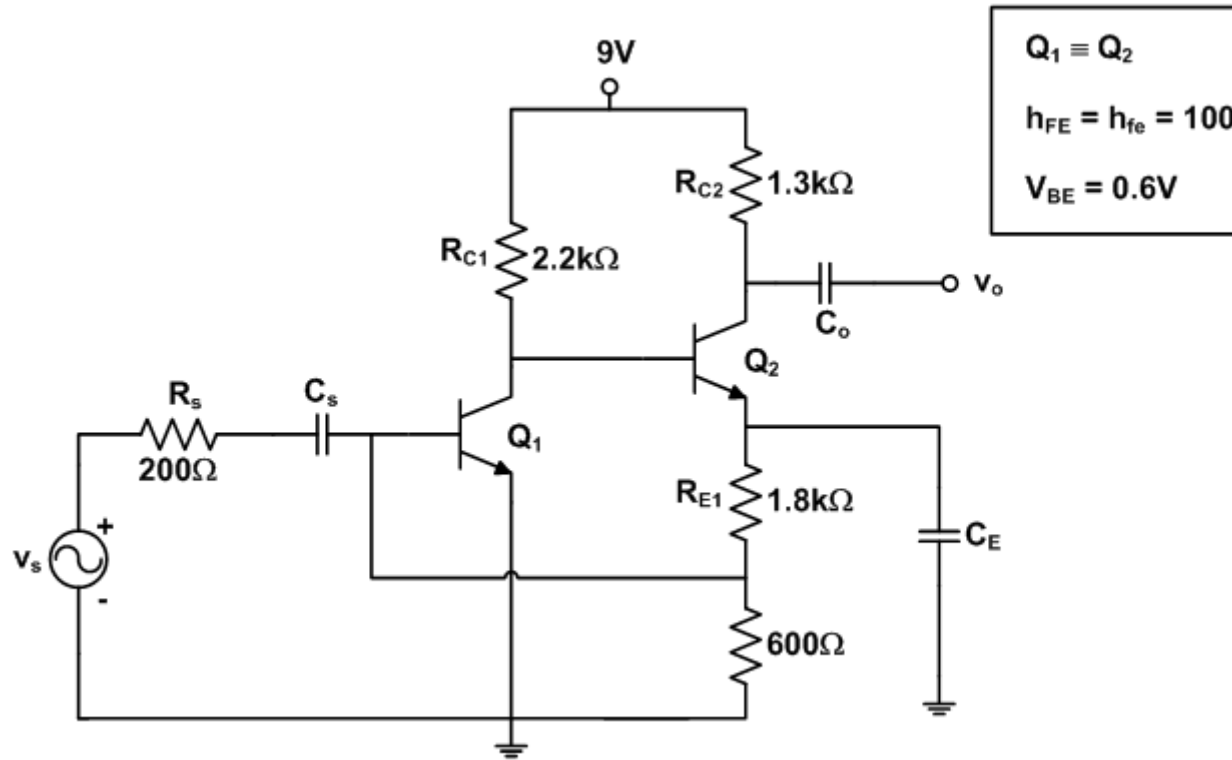

- Draw AC and DC load lines for both transistors.
- Calculate the overall voltage gain  $A_V = v_o / v_s$ .
- Find  $v_{s(max)}$  which produces maximum undistorted output voltage.


### Ex4:

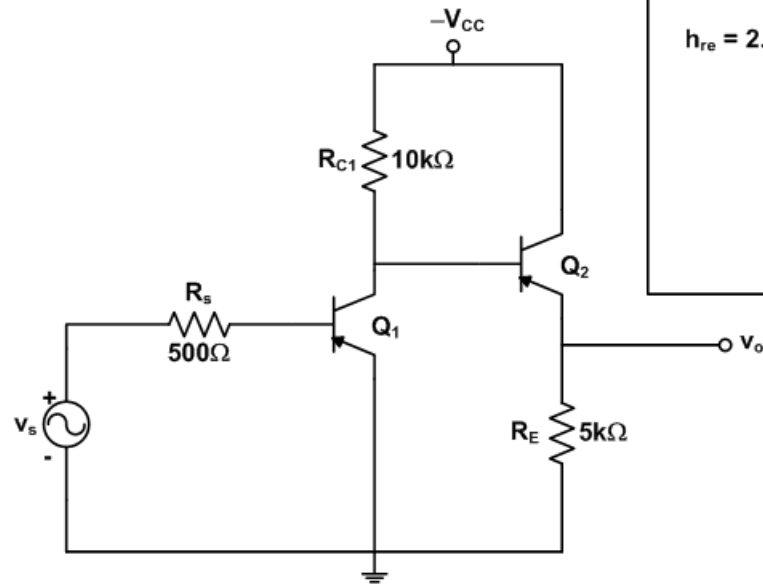

$h_{fe} = 50$	$h_{fb} = -0.98$
$h_{ie} = 1.1k\Omega$	$h_{ib} = 21.6\Omega$
$h_{oe} = 24\mu A/V$	$h_{ob} = 0.49\mu A/V$
$h_{re} = 2.5 \cdot 10^{-4}$	$h_{rb} = 2.59 \cdot 10^{-4}$
$h_{fc} = 51$	
$h_{ic} = 1.1k\Omega$	
$h_{oc} = 25\mu A/V$	
$h_{rc} = 1$	

- b) Calculate the overall voltage gain  $A_V = v_o / v_s$ .
- c) Find  $R_o$ .

# Cascode Connection

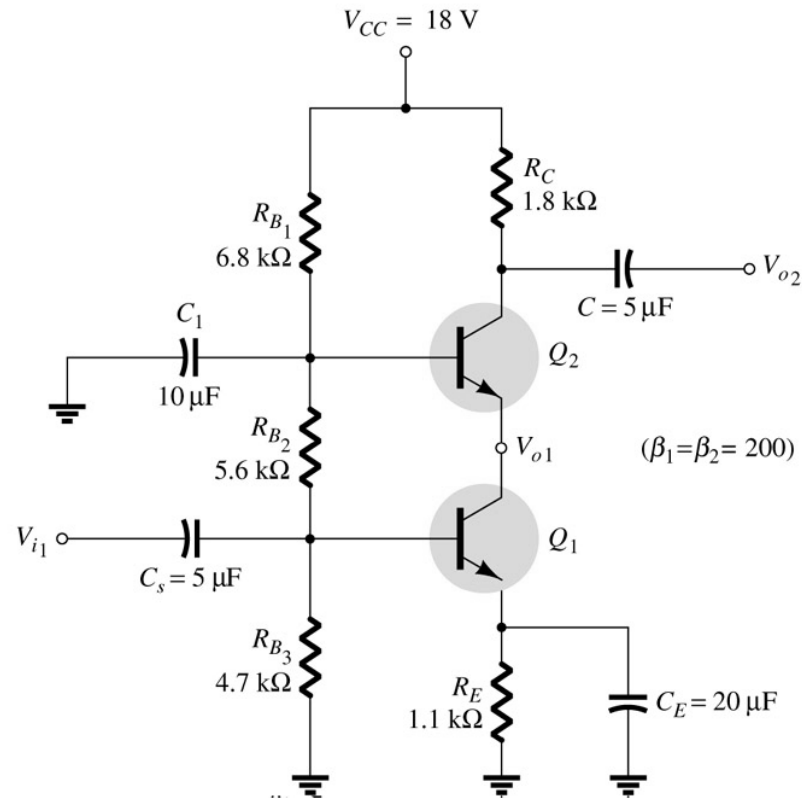


This is a CE – CB combination.


This arrangement provides high input impedance but a low voltage gain.

The low voltage gain reduces the Miller Input Capacitance therefore this combination works well in high frequency applications.

A more elaborate version of cascode amplifier

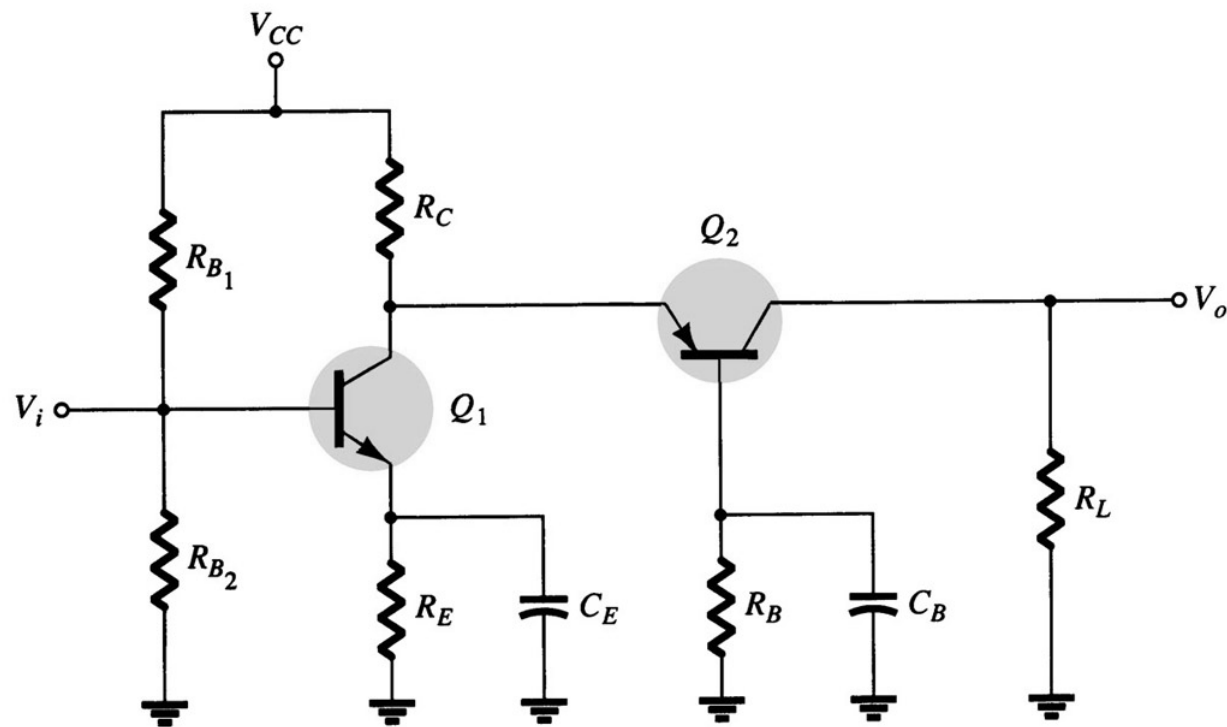

**Ex5:**

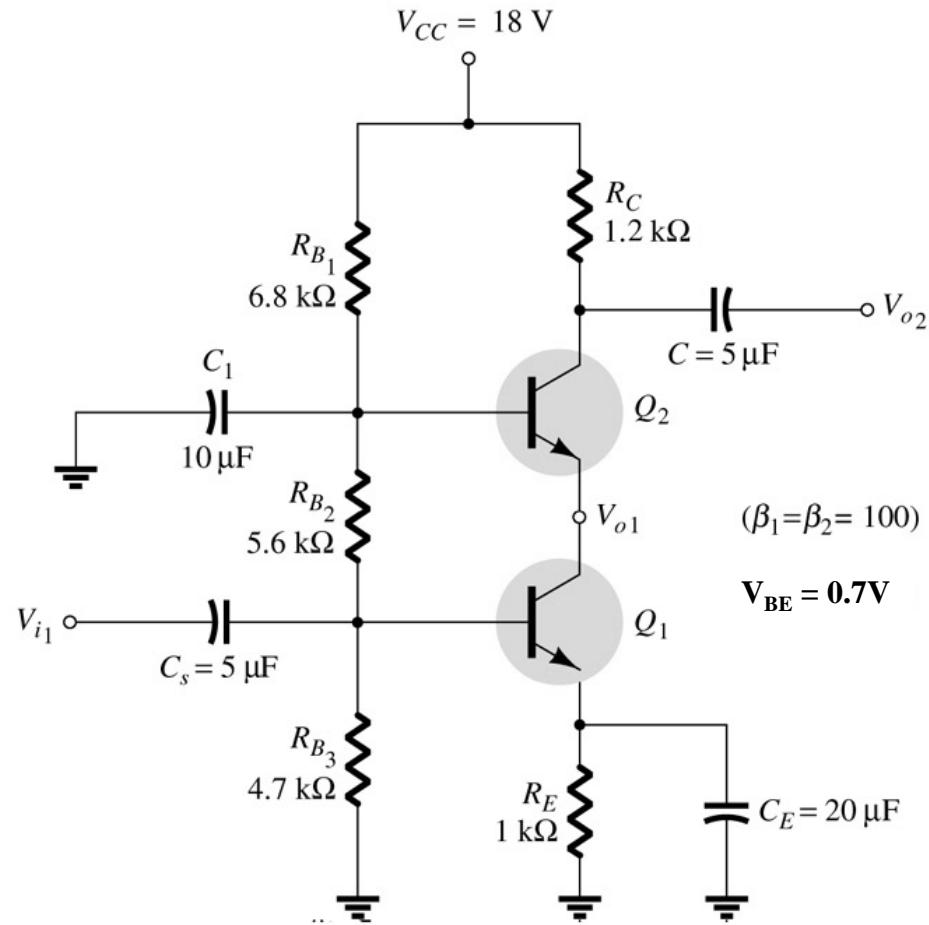


Consider the cascode amplifier above

- Find the voltage gain  $\mathbf{A_v} = \mathbf{v_o}/\mathbf{v_i}$
- Find the input resistance  $\mathbf{R_i}$
- Find the output resistance  $\mathbf{R_o}$




# Darlington Connection

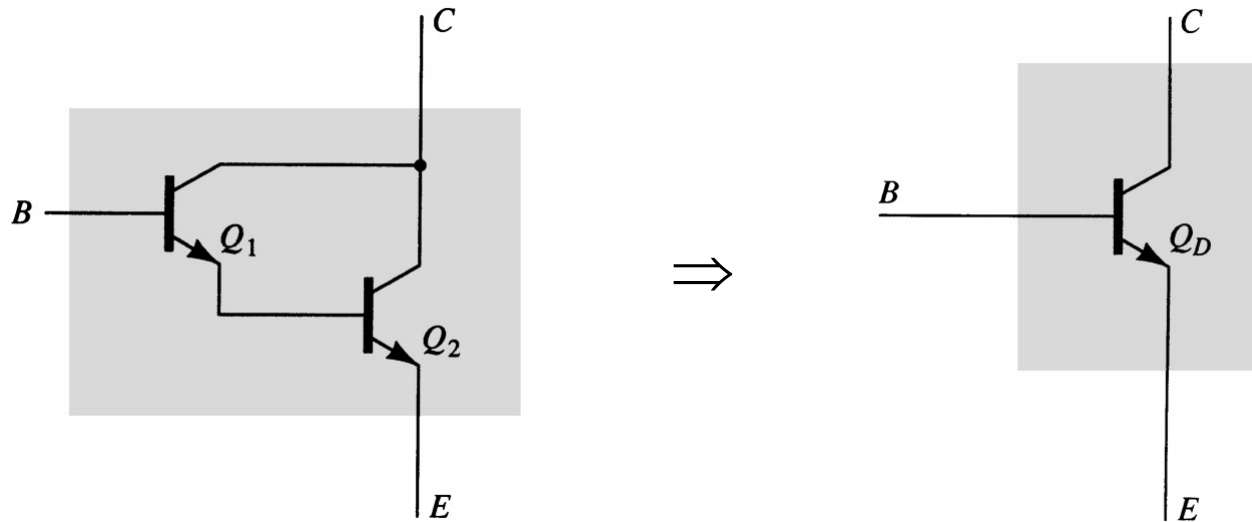

This combination provides large current gain, typically a few thousand.

It has a voltage gain of near 1, a low output impedance and a high input impedance.

## Feedback Pair

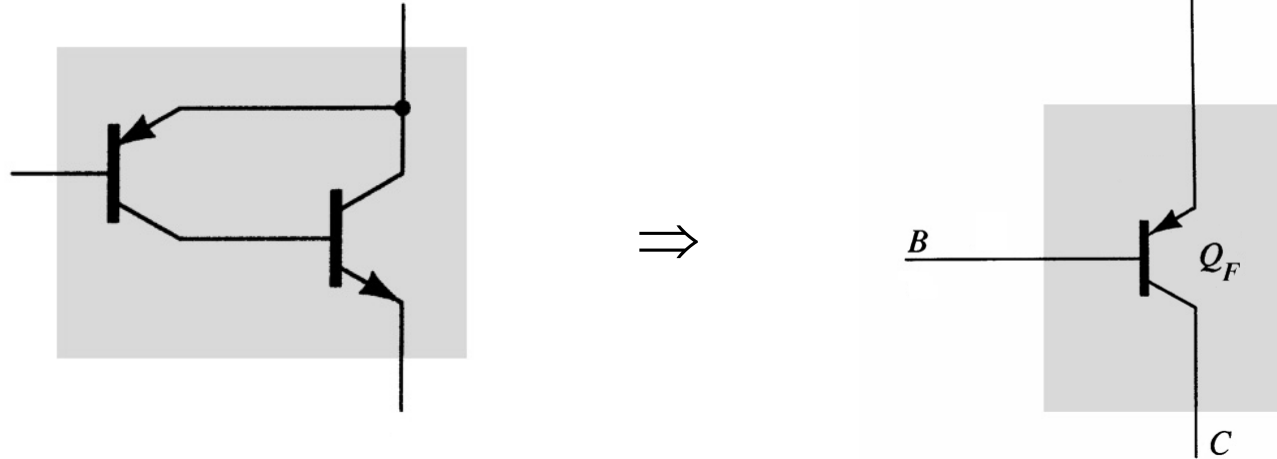

This is a two-transistor circuit that operates like a Darlington pair.

It has similar characteristics: high current gain, voltage gain of near 1, low output impedance and high input impedance.

Note: it is *not the Darlington* configuration:

Darlington: 2 npn BJTs

Feedback Pair: pnp driving an npn BJT