
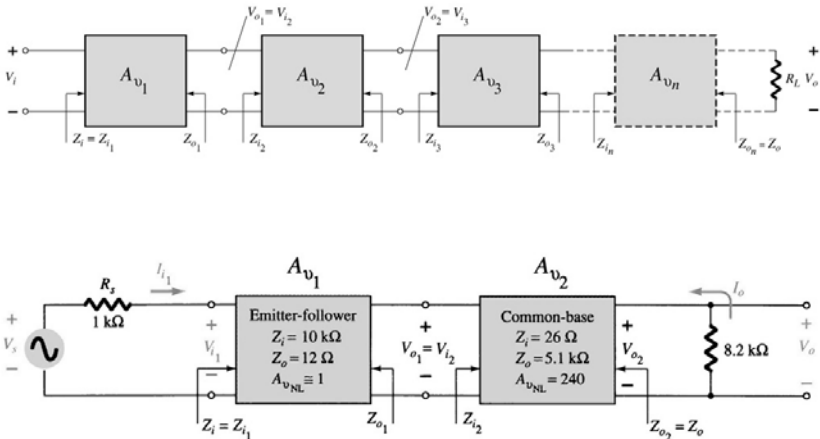



Multistage Amplifiers

Cascade Connection

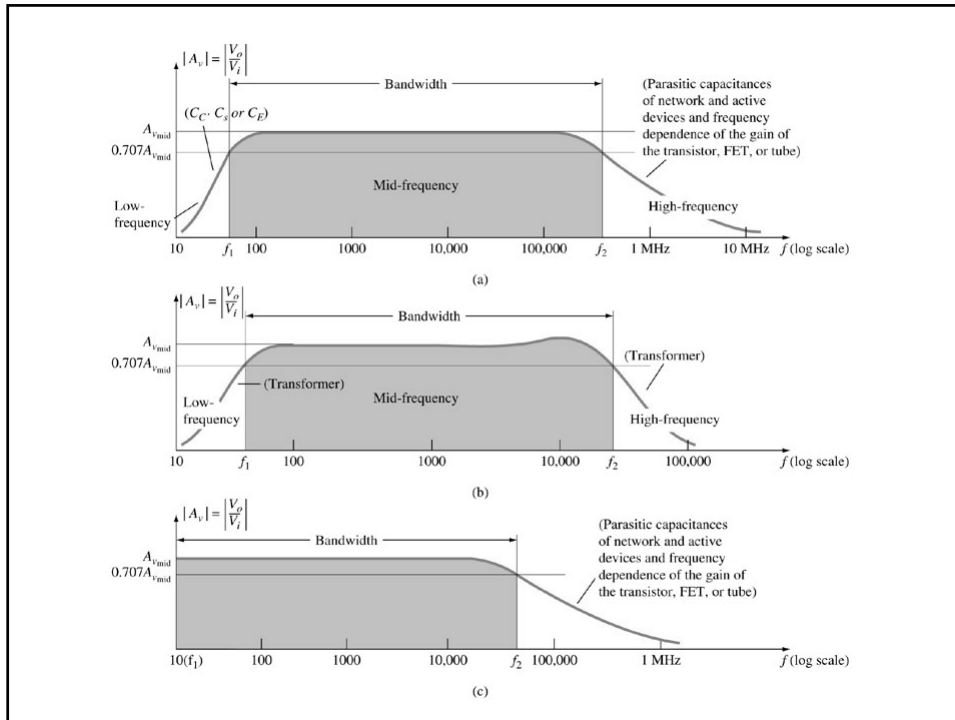



AC Coupled Multistage Amplifiers

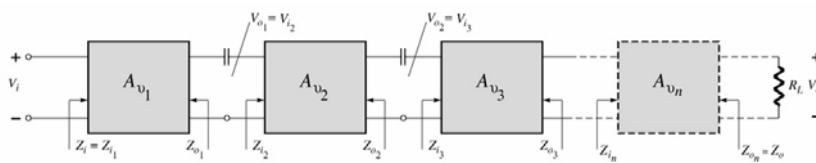

The output of one amplifier is the input to the next amplifier.

Note the DC bias circuits **are isolated** from each other by the coupling capacitors.

The DC calculations **are independent** of the cascading.


The AC calculations for gain and impedance are interdependent.

The overall gain:

$$A_v = A_{v1} \times \frac{Z_{i2}}{Z_{o1} + Z_{i2}} \times A_{v2} \times \dots \times \frac{Z_{ik}}{Z_{o_{k-1}} + Z_{ik}} \times A_{vk} \times \dots \times \frac{Z_{in}}{Z_{o_{n-1}} + Z_{in}} \times A_{vn}$$

with $Z_i = Z_{i1}$ and $Z_o = Z_{on}$

AC Coupled Multistage Amplifiers

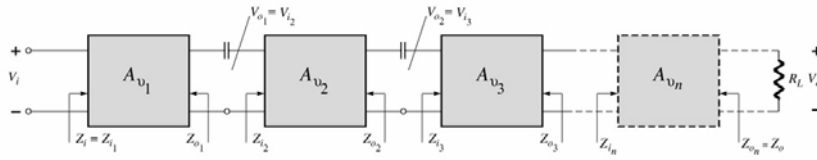


We can also express the overall gain as follows

$$A_v = A_{v_1}^* \times A_{v_2}^* \times \dots \times A_{v_k}^* \dots \times A_{v_n}$$

where

$$A_{v_k}^* = A_{v_k} \times \frac{Z_{i_{k+1}}}{Z_{o_k} + Z_{i_{k+1}}}$$

FET Cascade Amplifier

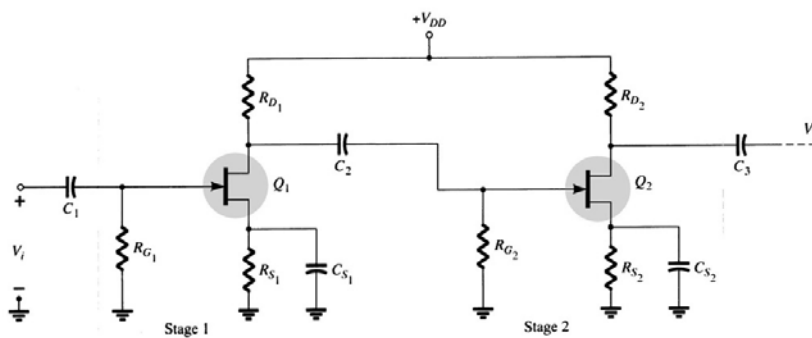


Voltage Gain: $A_v = A_{v_2} A_{v_1}^* = (-g_{m_2} R_{D_2}) [-g_{m_1} (R_{D_1} \parallel R_{G_2})]$

Input Impedance: $Z_i = R_{G_1}$

Output Impedance: $Z_o = R_{D_2}$

BJT Cascade Amplifier

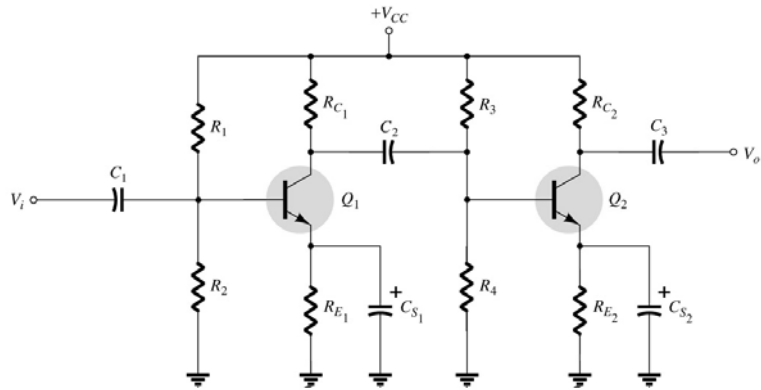

Voltage Gain: $A_v = A_{v_2} A_{v_1}^* = \left(-\frac{h_{fe_2} R_{C_2}}{h_{ie_2}} \right) \left(-\frac{h_{fe_1} [R_{C_1} \parallel (R_3 \parallel R_4 \parallel h_{ie_2})]}{h_{ie_1}} \right)$

Input Impedance: $Z_i = R_1 \parallel R_2 \parallel h_{ie_1}$


Output Impedance: $Z_o = R_{C_2} \parallel \frac{1}{h_{oe_2}}$

Combination of FET and BJT Cascade

A FET-BJT cascade is calculated in a similar fashion as a FET-FET or a BJT-BJT cascade.


This combination provides a high gain from the BJT with the high input impedance from the FET.

Ex1:

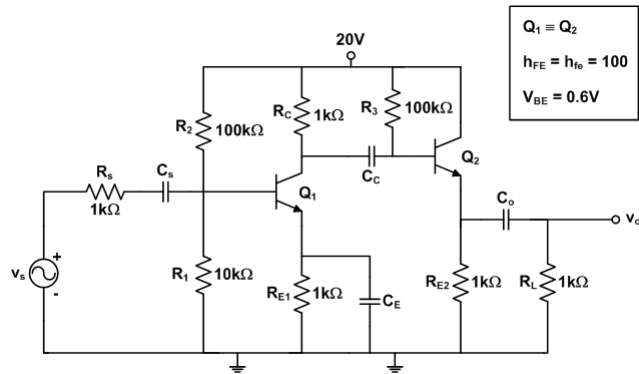

- a) Draw AC and DC load lines for both transistors.
- b) Calculate the overall voltage gain $A_v = v_o / v_s$.
- c) Find $v_{s(\max)}$ which produces maximum undistorted output voltage.

DC Coupled Multistage Amplifiers

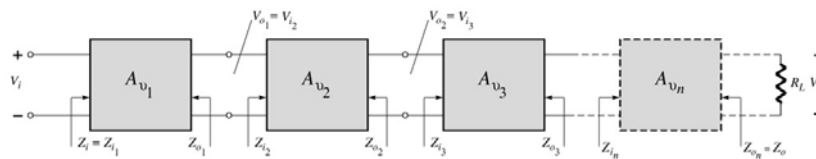

The output of one amplifier is the input to the next amplifier.

Note the DC bias circuits **are not isolated** from each other
 The DC calculations **are not independent** of the cascading.


Used either to amplify very low frequency signals or to amplify DC signals

The overall gain:

$$A_v = A_{v_1} \times \frac{Z_{i_2}}{Z_{o_1} + Z_{i_2}} \times A_{v_2} \times \dots \times \frac{Z_{i_k}}{Z_{o_{k-1}} + Z_{i_k}} \times A_{v_k} \dots \times \frac{Z_{i_n}}{Z_{o_{n-1}} + Z_{i_n}} \times A_{v_n}$$


with $Z_i = Z_{i_1}$ and $Z_o = Z_{o_n}$

Ex2:

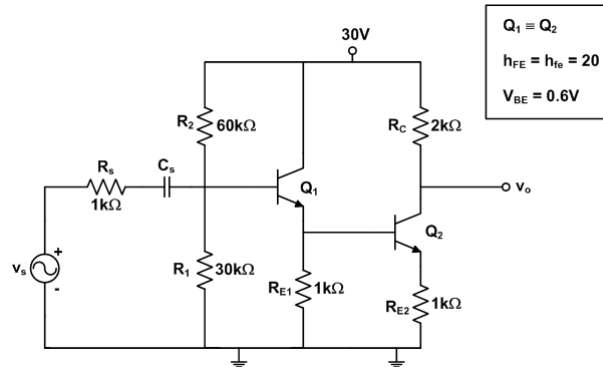


- Draw AC and DC load lines for both transistors.
- Calculate the overall voltage gain $A_v = v_o / v_s$.
- Find $v_{s(\max)}$ which produces maximum undistorted output voltage.

Ex3:

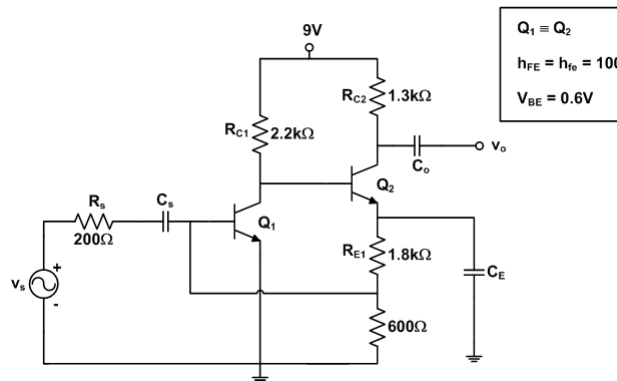


- Draw AC and DC load lines for both transistors.
- Calculate the overall voltage gain $A_v = v_o / v_s$.
- Find $v_{s(\max)}$ which produces maximum undistorted output voltage.

Ex4:

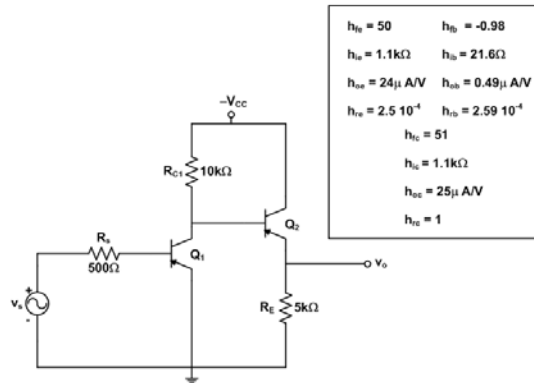


- b) Calculate the overall voltage gain $A_V = v_o / v_s$.
 c) Find R_o .

Cascode Connection

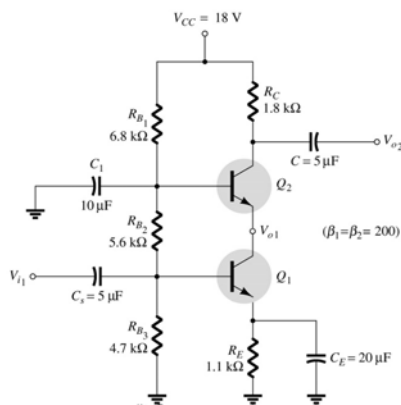


This is a CE – CB combination.
 This arrangement provides high input impedance but a low voltage gain.
 The low voltage gain reduces the Miller Input Capacitance therefore this combination works well in high frequency applications.

A more elaborate version of cascode amplifier

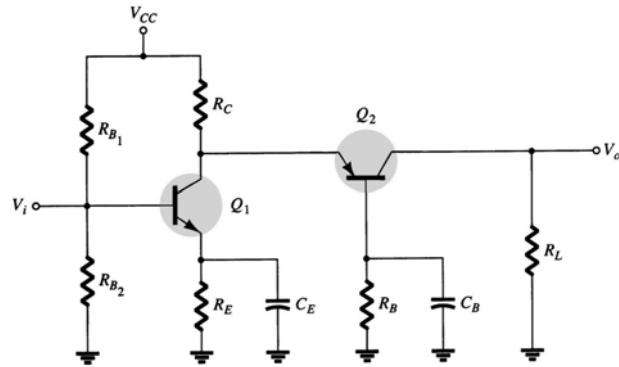


Ex5:

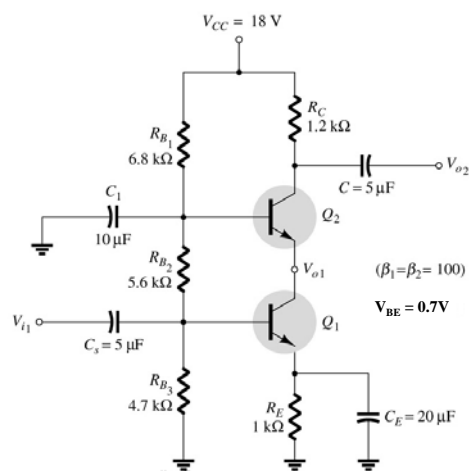

Consider the cascode amplifier above

- Find the voltage gain $A_v = v_o/v_i$
- Find the input resistance R_i
- Find the output resistance R_o


Darlington Connection

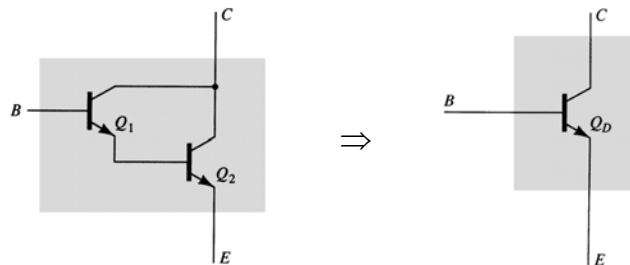

This combination provides large current gain, typically a few thousand.

It has a voltage gain of near 1, a low output impedance and a high input impedance.

Feedback Pair

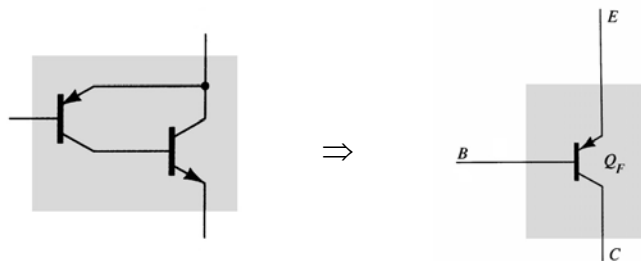

This is a two-transistor circuit that operates like a Darlington pair.

It has similar characteristics: high current gain, voltage gain of near 1, low output impedance and high input impedance.

Note: it is *not the Darlington* configuration:

Darlington: 2 npn BJTs

Feedback Pair: pnp driving an npn BJT