

15.10 COMPUTER ANALYSIS

Program 15.1—Series-Fed Class A Amplifier

Using Design Center, the circuit of a series-fed class A amplifier is drawn as shown in Fig. 15.28. Figure 15.29 shows some of the analysis output. Edit the transistor model for values of only $\beta F = 90$ and $I_S = 2E-15$. This keeps the transistor model more ideal so that PSpice calculations better match those below. The dc bias of the collector voltage is shown to be

$$V_c(\text{dc}) = 12.47 \text{ V}$$

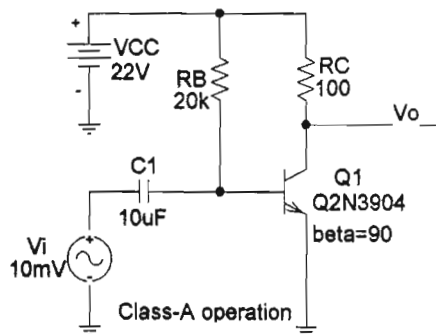


Figure 15.28 Series-fed class A amplifier.

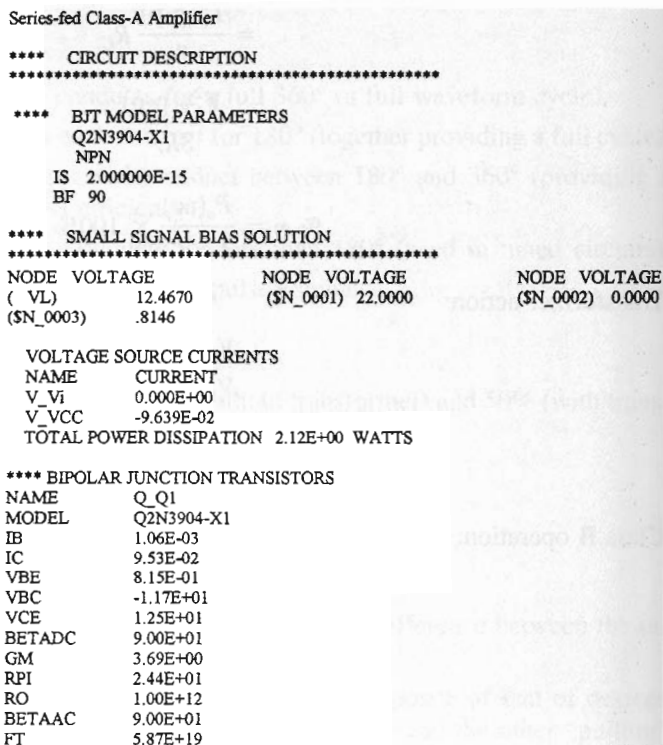


Figure 15.29 Analysis output for the circuit of Fig. 15.28.

With transistor beta set to 90, the ac gain is calculated as follows:

$$I_E = I_c = 95 \text{ mA (from analysis output of PSpice)}$$

$$r_e = 26 \text{ mV} / 95 \text{ mA} = 0.27 \Omega$$

For a gain of

$$A_v = -R_c / r_e = -100 / 0.27 = -370$$

The output voltage is then

$$V_o = A_v V_i = (-370) \cdot 10 \text{ mV} = -3.7 \text{ V(peak)}$$

The output waveform obtained using **probe** is shown in Fig. 15.30.

For a peak-to-peak output of

$$V_o(\text{p-p}) = 15.6 \text{ V} - 8.75 \text{ V} = 6.85 \text{ V}$$

the peak output is

$$V_o(\text{p}) = 6.85 \text{ V} / 2 = 3.4 \text{ V}$$

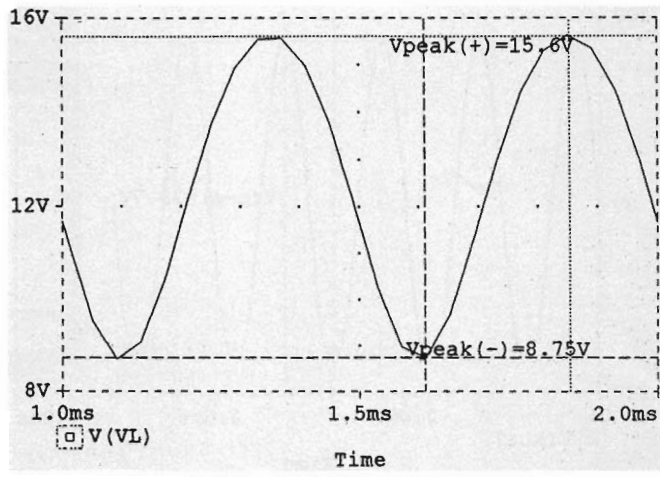


Figure 15.30 Probe output for the circuit of Fig. 15.28.

which compares well with that calculated above. From the circuit output analysis, the input power is

$$P_i = V_{CC}I_C = (22 \text{ V}) \cdot (95 \text{ mA}) = 2.09 \text{ W}$$

From the probe ac data, the output power is

$$P_o(ac) = V_o(p-p)^2/[8 \cdot R_L] = (6.85)^2/[8 \cdot 100] = 58 \text{ mW}$$

The efficiency is then

$$\% \eta = P_o/P_i \cdot 100\% = (58 \text{ mW}/2.09 \text{ W}) \cdot 100\% = 2.8\%$$

A larger input signal would increase the ac power delivered to the load and increase the efficiency (the maximum being 25%).

Program 15.2—Quasi-Complementary Push-Pull Amplifier

Figure 15.31 shows a quasi-complementary push-pull class B power amplifier. For the input of $V_i = 20 \text{ V}(p)$, the output waveform obtained using **probe** is shown in Fig. 15.32.

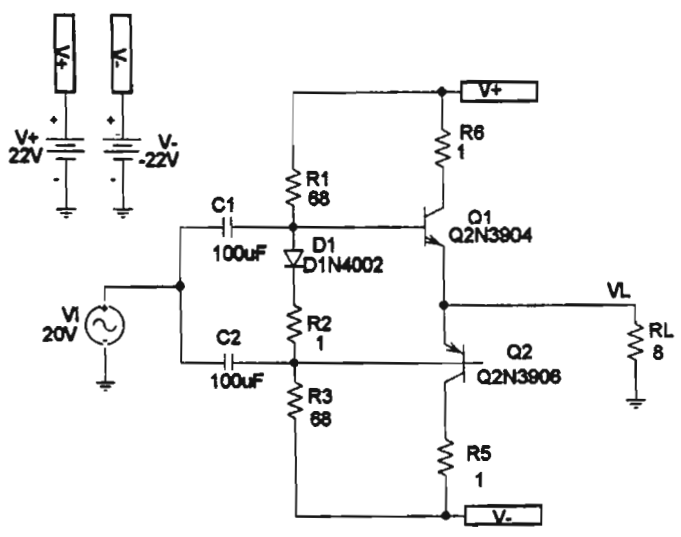


Figure 15.31 Quasi-complementary class B power amplifier.

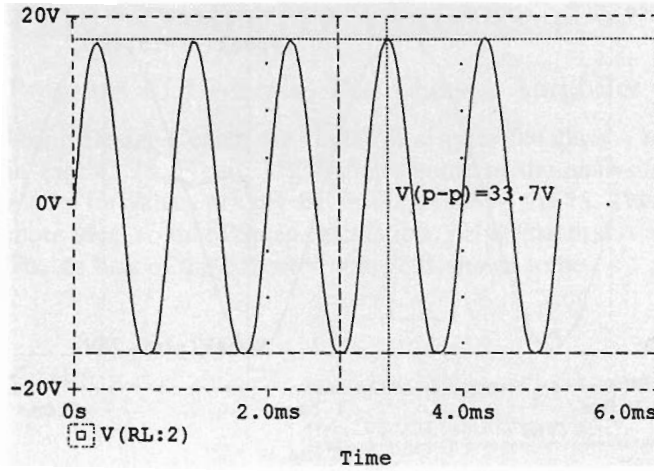


Figure 15.32 Probe output of the circuit in Fig. 15.31.

The resulting ac output voltage is seen to be

$$V_o(p-p) = 33.7 \text{ V}$$

so that

$$P_o = V_o^2(p-p)/(8 \cdot R_L) = (33.7 \text{ V})^2/(8 \cdot 8 \Omega) = 17.7 \text{ W}$$

The input power for that amplitude signal is

$$\begin{aligned} P_i &= V_{CC}I_{dc} = V_{CC}[(2/\pi)(V_o(p-p)/2)/R_L] \\ &= (22 \text{ V}) \cdot [(2/\pi)(33.7 \text{ V}/2)/8] = 29.5 \text{ W} \end{aligned}$$

The circuit efficiency is then

$$\% \eta = P_o/P_i \cdot 100\% = (17.7 \text{ W}/29.5 \text{ W}) \cdot 100\% = 60\%$$

Program 15.3—Op-Amp Push-Pull Amplifier

Figure 15.33 shows an op-amp push-pull amplifier providing ac output to an 8-Ω load. As shown, the op-amp provides a gain of

$$A_v = -R_F/R_1 = -47 \text{ k}\Omega/18 \text{ k}\Omega = -2.6$$

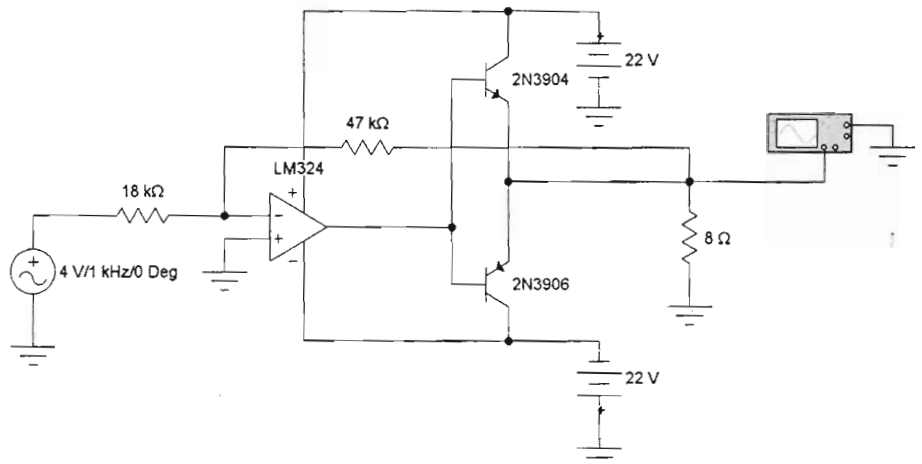


Figure 15.33 Op-amp class B amplifier.

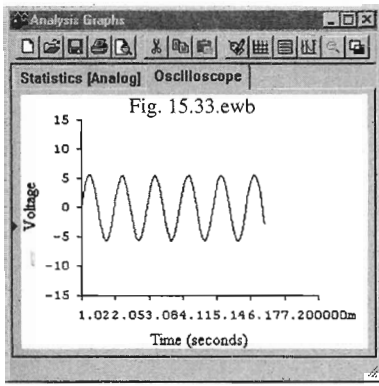


Figure 15.34 Probe output for the circuit of Fig. 15.33.

For the input, $V_i = 1 \text{ V}$, the output is

$$V_o(p) = A_v V_i = -2.6 \cdot (1 \text{ V}) = -2.6 \text{ V}$$

Figure 15.34 shows the oscilloscope display of the output voltage.

The output power, input power, and circuit efficiency are then calculated to be

$$P_o = V_o^2(p-p)/(8 \cdot R_L) = (20.4 \text{ V})^2/(8 \cdot 8 \Omega) = 6.5 \text{ W}$$

The input power for that amplitude signal is

$$\begin{aligned} P_i &= V_{CC} I_{dc} = V_{CC} [(2/\pi)(V_o(p-p)/2)/R_L] \\ &= (12 \text{ V}) \cdot [(2/\pi) \cdot (20.4 \text{ V}/2)/8] = 9.7 \text{ W} \end{aligned}$$

The circuit efficiency is then

$$\% \eta = P_o/P_i \cdot 100\% = (6.5 \text{ W}/9.7 \text{ W}) \cdot 100\% = 67\%$$

MATHCAD

The calculations for the class B power amplifier of Example 15.7 and for the class B power amplifier of Example 15.12 are shown below. Using Mathcad, one can enter any desired value of **VCC**, **RL**, and **VL peak**, with all the calculations immediately providing the new results.

Class-B Power Amplifier (Example 15.7)

$$VCC := 30 \quad RL := 16 \quad VL_{peak} := 20$$

$$IL_{peak} := \frac{VL_{peak}}{RL} \quad IL_{peak} = 1.25$$

$$Idc := 2 \cdot \frac{IL_{peak}}{3.14159} \quad Idc = 0.796$$

$$Pidc := VCC \cdot Idc \quad Pidc = 23.873$$

$$Poac := \frac{VL_{peak}^2}{(2 \cdot RL)} \quad Poac = 12.5$$

$$n := \left(\frac{Poac}{Pidc} \right) \cdot 100 \quad n = 52.36$$

Class-B Power Amplifier (Example 15.12)

$$VCC := 25 \quad RL := 4$$

$$\max Pidc := \frac{(2 \cdot VCC^2)}{(3.14159) \cdot RL} \quad \max Pidc = 99.472$$

$$\max Poac := \frac{VCC^2}{(2 \cdot RL)} \quad \max Poac = 78.125$$

$$n := \left(\frac{\max Poac}{\max Pidc} \right) \cdot 100 \quad n = 78.54$$

$$P2Q := \max Pidc - \max Poac \quad P2Q = 21.347$$

The harmonic distortion calculations of Examples 15.13 and 15.14 are shown for a select set of values for **A1** through **A4**.