


MOS Logic

MOS Logic

- NMOS gates
 - Fabrication
 - Modes of operation
- NMOS Inverters and Analysis
 - General NMOS Inverter
 - Resistor Loaded NMOS Inverter
 - E-MOSFET loaded NMOS Inverter
 - D-MOSFET loaded NMOS Inverter


NMOS (n-channel E-MOSFET) Fabrication Examples

METAL GATE NMOS

 


Cross-section

SILICON GATE NMOS

 


Cross-section

CMOS Fabrication Example

 

Twin-Tub
CMOS

IV Characteristics

 

SATURATION

$$I_D(\text{SAT}) = \frac{k}{2} (V_{GS} - V_T)^2$$

LINEAR


$$I_D(\text{LIN}) = k \left[(V_{GS} - V_T)V_{DS} - \frac{V_{DS}^2}{2} \right]$$

Device transconductance parameter =


$$k = k' \left(\frac{W}{L} \right)$$

Process transconductance parameter


NMOS modes of operation

 


(a) Cutoff mode

 

(b) Linear mode



 


(c) Saturation mode

 


(d) body-bias effect on threshold voltage

Load capacitance

   

Power dissipation

 

(a) Static power dissipation

$$P_{DD} = V_{DD} (I_{DD(OH)} + I_{DD(OL)}) / 2$$

$$\cong V_{DD} I_{DD(OL)} / 2$$

$$P_{TOTAL} = P_{DD} + P_D$$

(b) Transient power dissipation

$$P_D = C_L f V_{DD}^2$$

f : frequency at which the gate is switched

Resistor Loaded NMOS

Resistor Loaded NMOS Inverter



 
 


TABLE 18.1 States of N_O for the Resistor Loaded NMOS Inverter



Critical Point	State of N_O
V_{OH}	Cutoff
V_{IL}	Saturation
V_{IH}	Linear
V_{OL}	Linear
V_M	Saturation

 

Propagation Delay

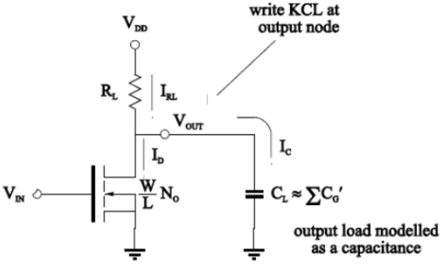

Fall time

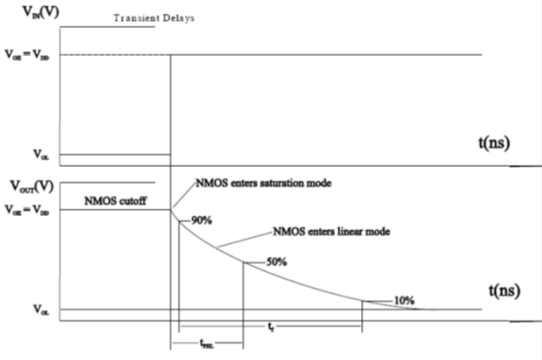 

D-MOSFET Loaded NMOS

D-MOSFET Loaded NMOS Inverter


 
 



TABLE 21.1 States of Transistors for Enhancement-Depletion Loaded NMOS Inverter

Critical Point	Output N_O	Load N_L
V_{OH}	Cutoff	Linear
V_{IL}	Saturation	Linear
V_M	Saturation	Saturation
V_{IH}	Linear	Saturation
V_{OL}	Linear	Saturation

 


NMOS Gates


Symbol Shorthands

 

NOR Gate

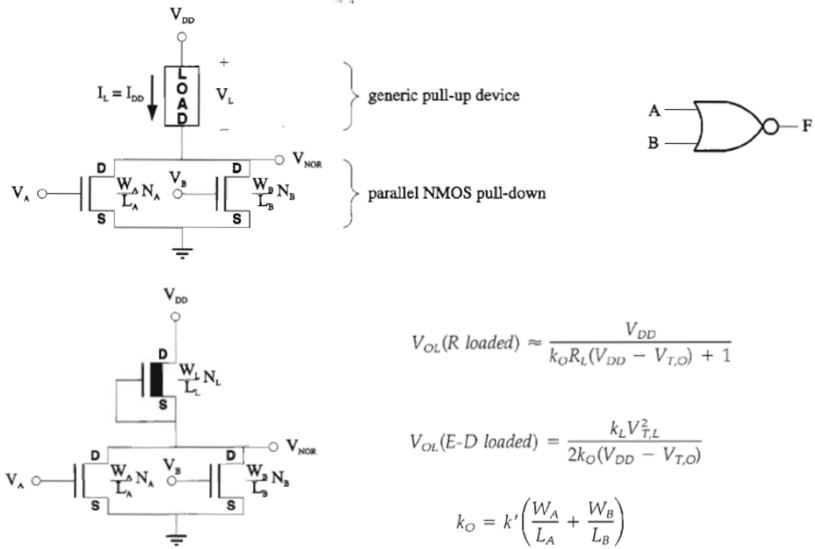


NOR Gates

 


$$V_{OL}(E-D \text{ loaded}) = \frac{k_L V_{T,L}^2}{2k_O (V_{DD} - V_{T,O})}$$

$$V_{OL}(\text{two NOR inputs high}) < V_{OL}(\text{inverter})$$


NAND Gate

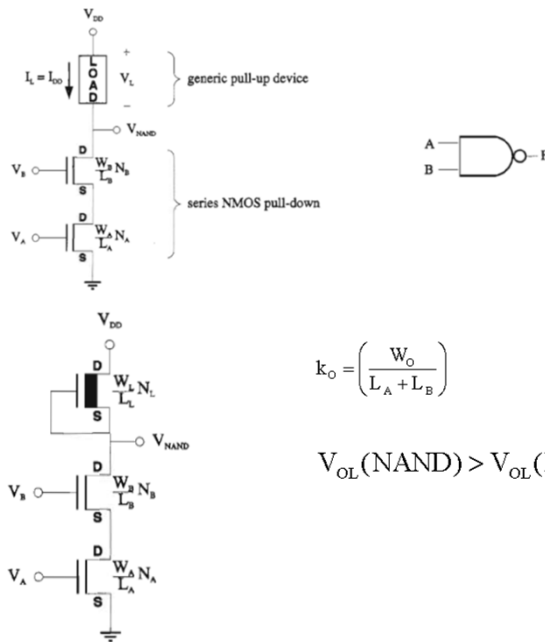


OR Gates

 


AOI (AND-OR-INVERT) Gates

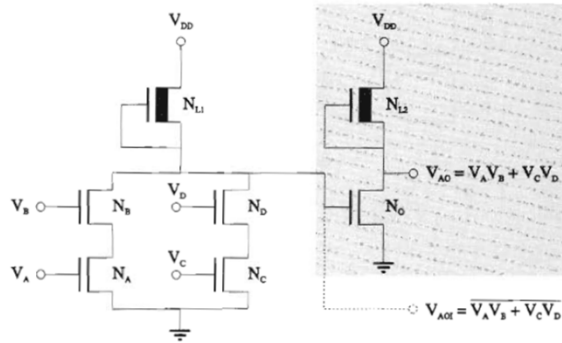


(a)

 


Examples

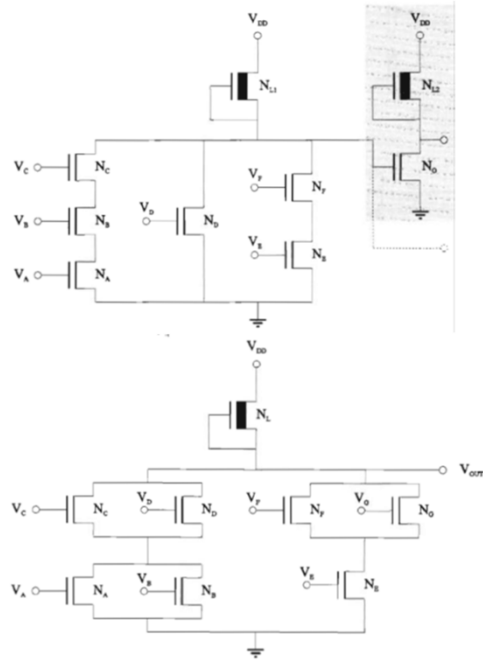



XOR/XNOR Gates

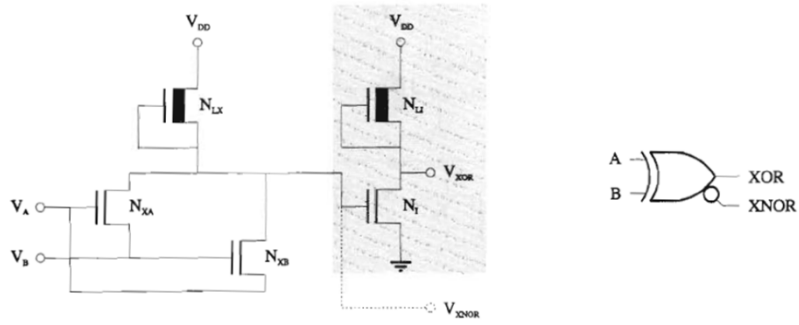

Hysteresis


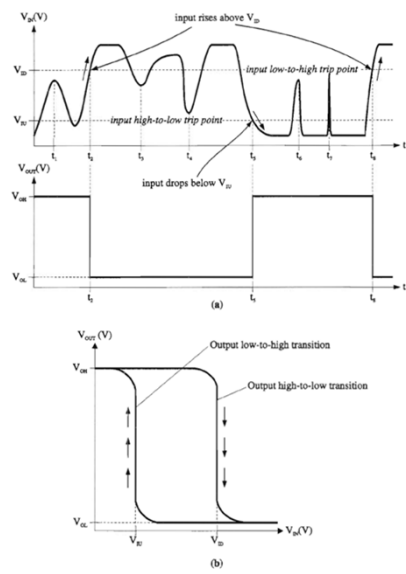


Schmitt Trigger

 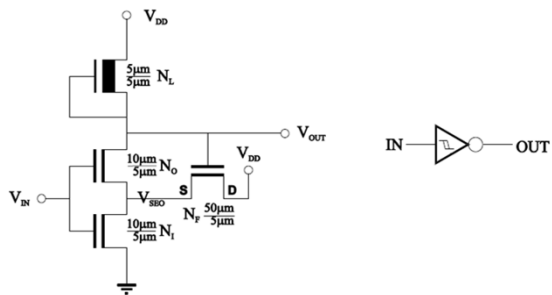


Transmission Gate

transmission gate NMOS device

  


Transmission Gate Array

 


CMOS Logic

CMOS Inverter

 


Critical Point	NMOS N_O	PMOS P_O
V_{OH}	Cutoff	Linear
V_{IL}	Saturation	Linear
V_M	Saturation	Saturation
V_{IH}	Linear	Saturation
V_{OL}	Linear	Cutoff

CMOS Inverter

 

Critical Point	NMOS N_O	PMOS P_O
V_{OH}	Cutoff	Linear
V_{IL}	Saturation	Linear
V_M	Saturation	Saturation
V_{IH}	Linear	Saturation
V_{OL}	Linear	Cutoff

 

Symmetric CMOS Inverter

 


FIGURE 23.5 Symmetric CMOS Inverter with $W_P/L_P = 2.5 W_N/L_N$

Capacitance Effect on Transition - 1

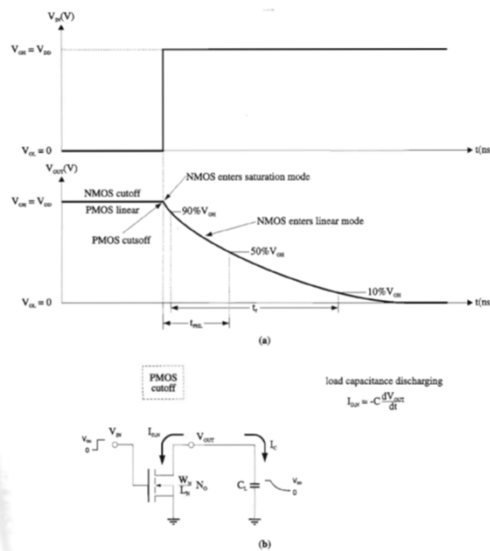


FIGURE 23.10 CMOS Inverter Output High-to-low Transition: (a) Step-up input and output response curves, (b) Load capacitance discharges through active NMOS transistor

Capacitance Effect on Transition - 2

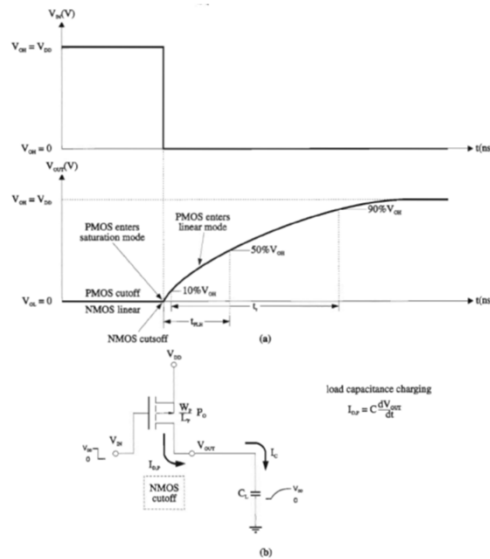


FIGURE 23.11 CMOS Inverter Output Low-to-high Transition: (a) Step-down input and output response curves, (b) Load capacitance charges through PMOS transistor

Electrostatic Discharge (ESD) Protection

 


FIGURE 23.20 Diode Input Protection Circuitry for Metal-gate CMOS


 


FIGURE 23.21 Diode Input Protection Circuitry for Silicon Gate CMOS: (a) Circuitry, (b) D_L is laid out as a base-collector connected BJT diode

CMOS NAND Gate

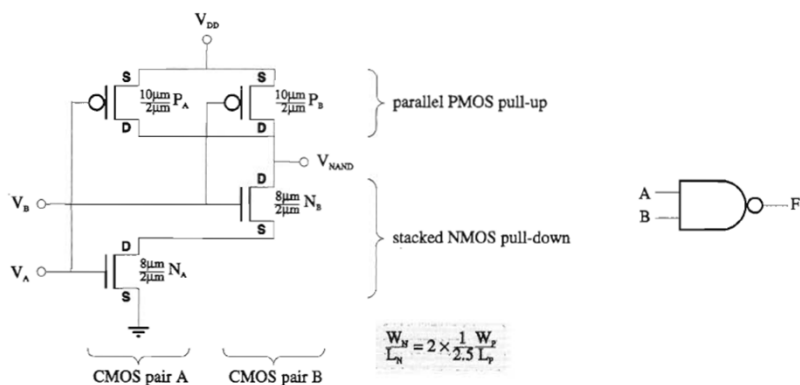


V_A	V_B	N_A	N_B	P_A	P_B	Pull-Up Path(s)	Pull-Down Path	V_{OUT}
low	low	off	off	on	on	P_A, P_B^*	none	high
low	high	off	on	on	off	P_A	none	high
high	low	on	off	off	on	P_B	none	high
high	high	on	on	off	off	none	N_A and N_B^{**}	low


*For V_A and V_B low, two output pull-up paths to V_{DD} are present through P_A and P_B

**For V_A and V_B high, a single output pull-down path to ground through N_A and N_B is present

CMOS NAND Gates

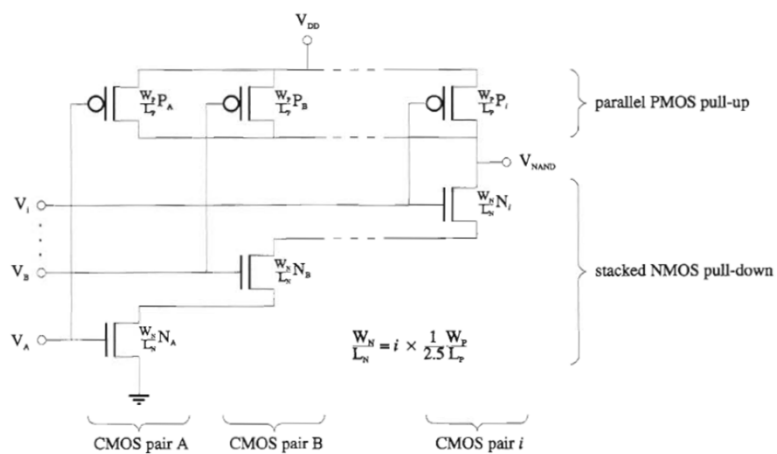

CMOS NOR Gate

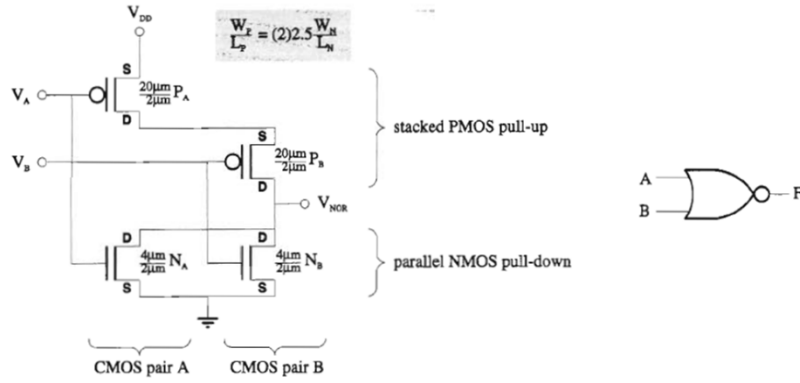


V_A	V_B	N_A	N_B	P_A	P_B	Pull-Up Path	Pull-Down Path(s)	V_{OUT}
low	low	off	off	on	on	P_A and P_B *	none	high
low	high	off	on	on	off	none	N_B	low
high	low	on	off	off	on	none	N_A	low
high	high	on	on	off	off	none	N_A, N_B **	low


*For V_A and V_B low a single output pull-up path to V_{DD} through P_A and P_B is present

**For V_A and V_B high two output pull-down paths to ground are present through N_A and N_B

CMOS NOR Gates

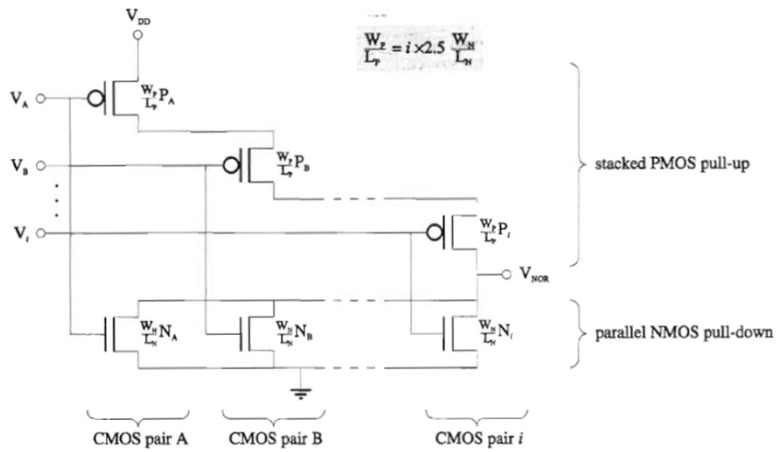

CMOS AND/NAND Gate

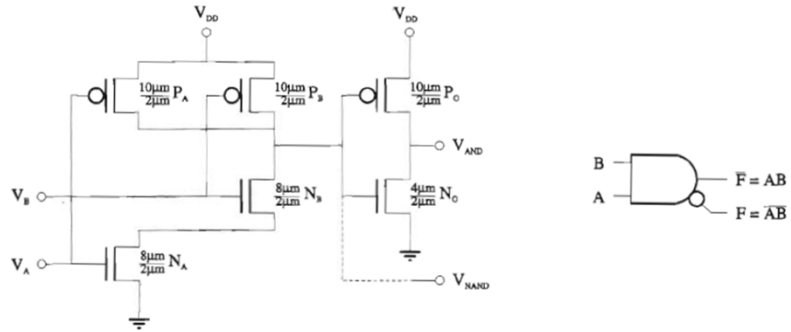

CMOS OR/NOR Gate



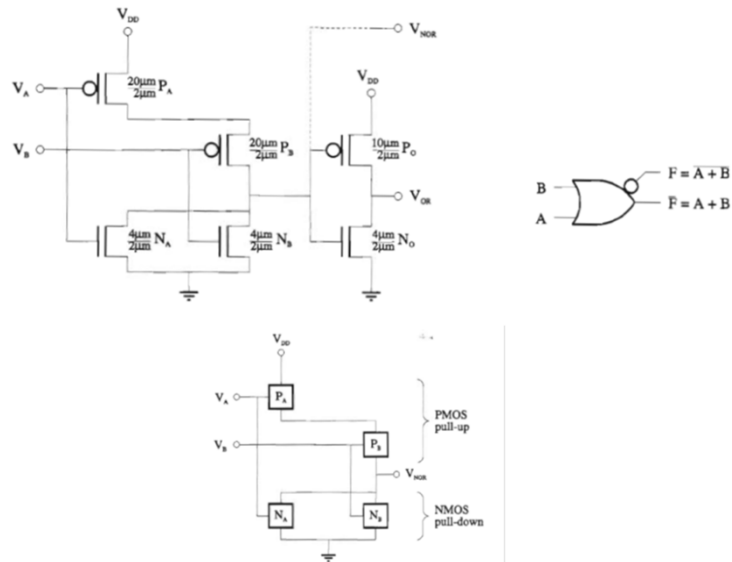


FIGURE 24.15 Block Diagram Representing Transistor Configuration of Two-input CMOS NOR Gate


CMOS AOI Gates

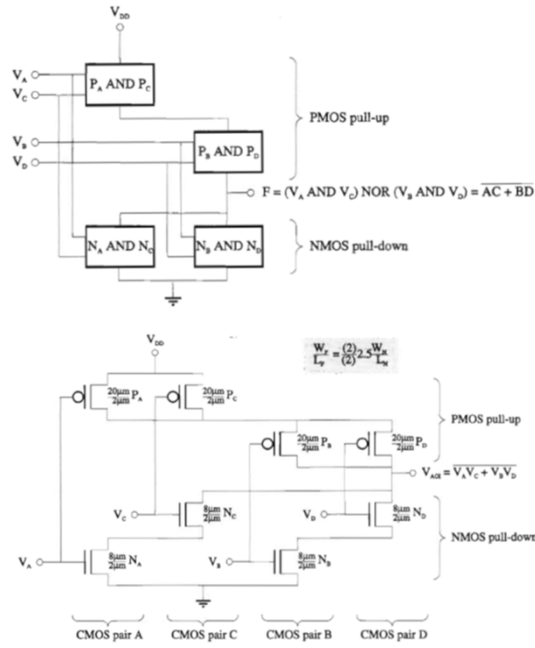


CMOS AOI Gates

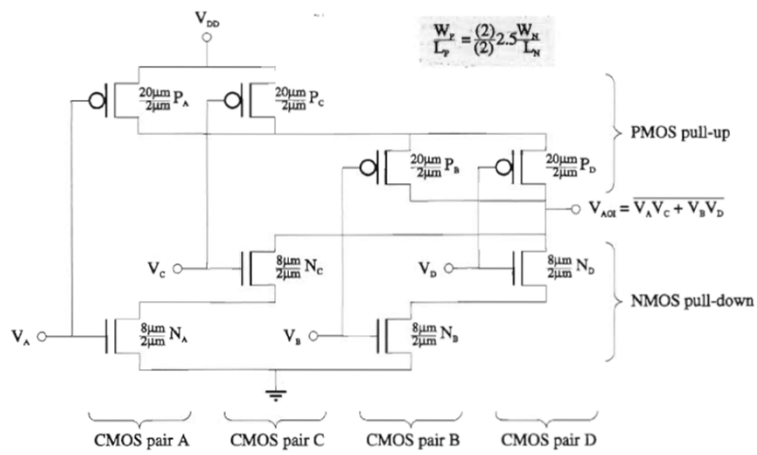


(a)

 



CMOS AND-OR Gate

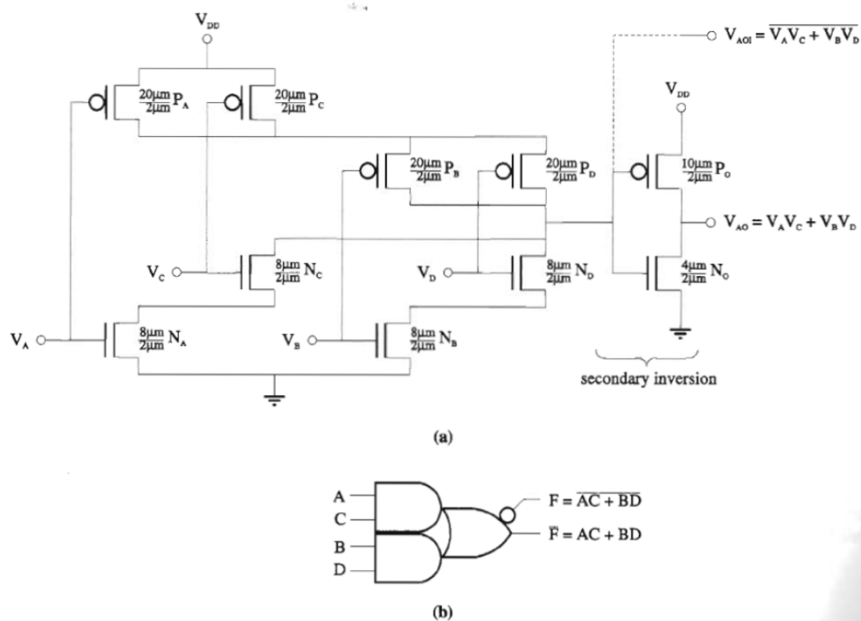

CMOS OAI Gates

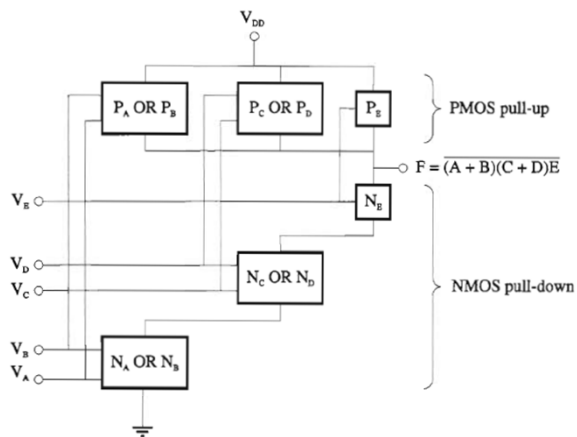

CMOS AOI Gates

 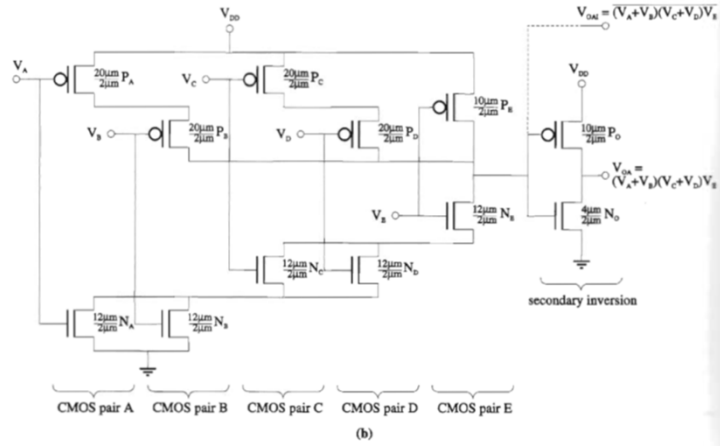

Example

